

➤ *Linearity and Output Resistance:*

- *While supplying/sinking current to/from load,  $Q_1/Q_2$  operate in CC mode*  
$$\Rightarrow A_v = R_L / (R_L + r_{Ei}) \quad (i = 1, 2) \quad (r_{Ei} = V_T / I_{ci})$$
- Thus, if  $R_L \gg r_{Ei}$ , then  $A_v \rightarrow 1$ , and *very high linearity in the VTC can be achieved*
- However,  $r_{Ei}$  *is not constant* - rather *it changes with the load current*
- Thus,  $A_v$  *can depart significantly from unity*, when the *load current is very small* (*large  $r_{Ei}$* )
- Referring to the *VTC*, the *slope of the characteristic near  $\pm V_\gamma$*  will be *significantly less than unity*

- However, *as  $V_o \uparrow$ , load current  $\uparrow$ ,  $r_{Ei} \downarrow$* , and the *VTC starts to attain its maximum slope of unity*
- Thus, *for major part*, the *VTC is highly linear* and *produces an almost distortionless output*
- *Output Resistance:*
  - *Open  $R_L$  and look back from the output*
  - $R_o = r_{Ei}$  (*by inspection*), since *bases of  $Q_1$ - $Q_2$*  can be considered to be at *ac ground*
  - $R_o$  *is variable*, but *for major part, extremely small*
- Generally, the *linearity and output resistance* are *calculated* at the *region of maximum slope* of the *VTC*

➤ *Summary:*

- *Quite small standby power*
- *Large current driving capability*
- *Almost linear VTC*
- *Very low distortion at the output*
- $A_v \sim 1$
- *No phase shift between input and output*
- *Very low output resistance*


*Thus, this stage is a superb one and is highly popular!*

- ***MOS Implementation:***

- *Biased using dual symmetric power supplies  $V_{DD}/V_{SS}$*

- *$M_1$ - $M_2$  in push-pull configuration*

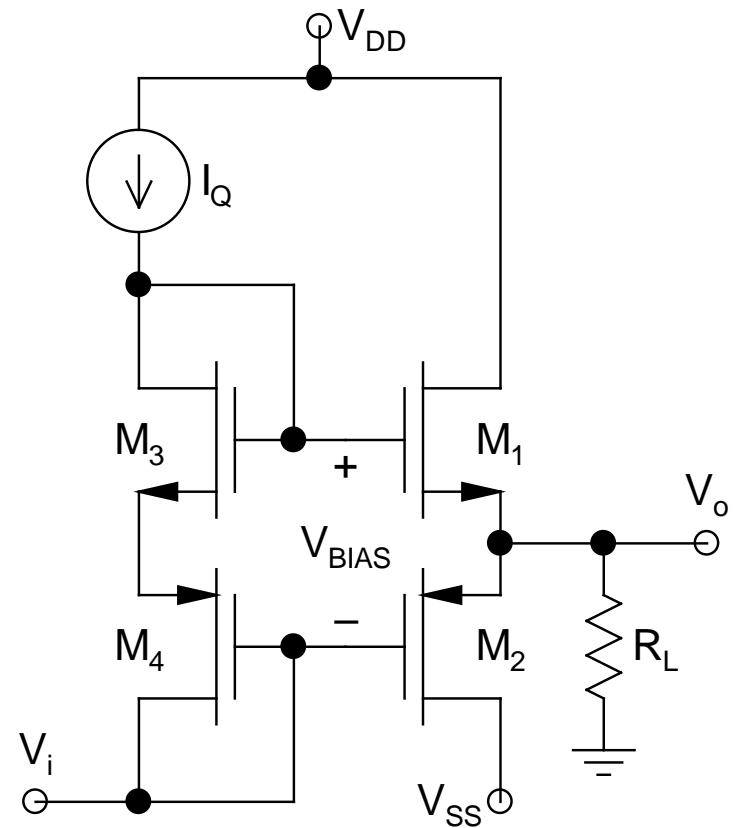- *$M_1$  supplying current to load ( $R_L$ ) during the positive half cycle*
- *$M_2$  pulling current away from load during the negative half cycle*



**Circuit Schematic**

- $M_1$ - $M_2$  *prebiased* by the *series combination* of  $M_3$ - $M_4$  (*both diode-connected*) *biased with  $I_Q$*
- *Develops  $V_{BIAS}$  across the gates of  $M_3$ - $M_4$* , which is *same as that between the gates of  $M_1$ - $M_2$*
- *$V_{BIAS}$  chosen to be slightly less than  $(V_{TN} + |V_{TP}|)$*
- *Crossover Distortion eliminated completely*, at the cost of *introducing standby power* into the system
- *Rest of the operation of the circuit exactly similar to that of a BJT Class AB Push-Pull Output Stage*

- *All transistors suffer from body effect problem*  
⇒ *More distortion at the output*
- *The linearity of the VTC is not that good*
- *Low current drive capability*
- *Biasing itself becomes tricky*, due to the *body effect of  $M_3$ - $M_4$*
- The *output resistance not that low*, since *MOSFETs have lower  $g_m$  than BJTs*
- Overall, the stage *suffers from quite a few problems* and is *not used much*
- We will explore this through an assignment


- **Overload Protection:**

- *Protects the output stage from accidental short-circuits*

- *Needs 4 more components:*

- **2 BJTs** ( $Q_5, Q_6$ )
- **2 Resistors** ( $R_1, R_2$ )

$$R_1, R_2 \sim 25\text{-}50 \, \Omega$$

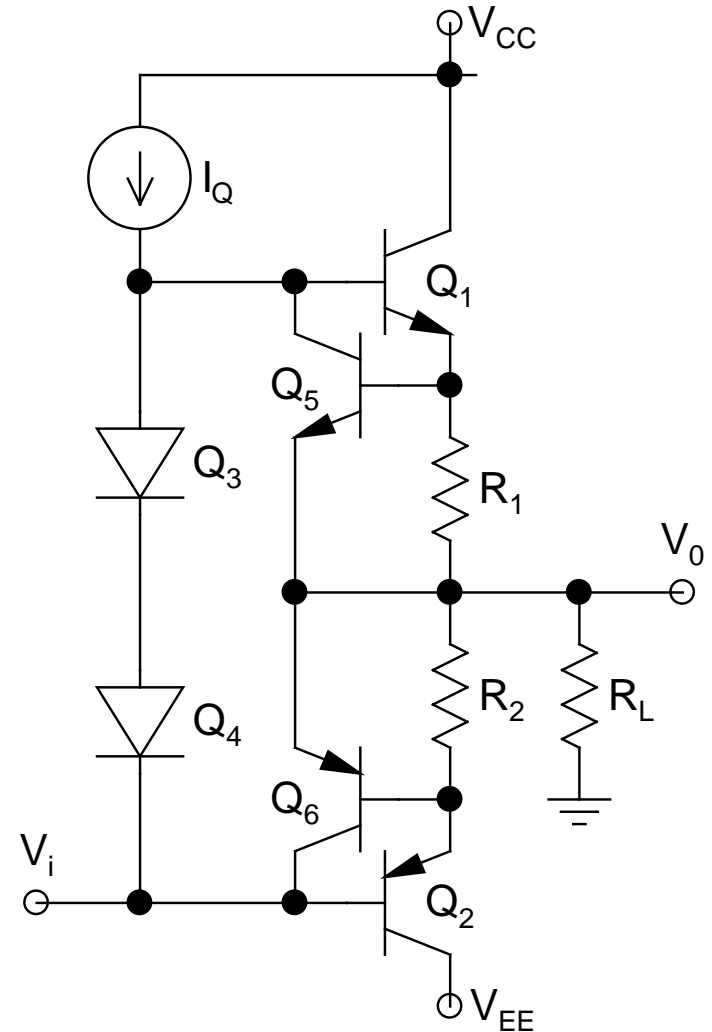

## Circuit Schematic

➤ During *normal operation*, these *extra circuits* play absolutely *no role*, and come *into picture* only under *accidental short-circuit* of the *output terminal to ground*

➤ *Numerical Example:*

- Assume  $V_i$  at its *positive peak*, the *maximum drive current* to the base of  $Q_1 = 1 \text{ mA}$ , and  $\beta_1 = 100$
- Now output gets *accidentally shorted to ground* ( $V_o = 0$ )  
 $\Rightarrow I_{c1} = 100 \text{ mA}$  and  $V_{ce1} = 5 \text{ V}$   
 $\Rightarrow P_1 = 500 \text{ mW}$
- o This may be *way above* the *maximum power rating* of the transistor ( $\sim 100\text{-}150 \text{ mW}$ ) and the transistor would *burn out*  $\Rightarrow$  *potentially dangerous situation!*



## ➤ *Principle of Operation of the Protection Circuit:*


- Assume *positive*  $V_i$  with  $Q_1$  *supplying current to load*
- $Q_2$  *is off during this time*
- As  $R_L \downarrow$ ,  $I_{c1} \uparrow$  (since  $I_{c1} = V_o/R_L$ )  
 $\Rightarrow V_{be5} (= I_{c1}R_1)$  *also*  $\uparrow$
- As  $V_{be5} \rightarrow V_\gamma$  of  $Q_5$ , it starts to *turn on*  
 $\Rightarrow$  A *part of base drive current* of  $Q_1$  starts to get *shunted away* by  $Q_5$ , and *appears at the output* almost *without any gain* ( $1/\alpha_5$ )
- This acts as a *limit of the rate* at which the *output current can increase*, and thus, *protects the circuit*

- Thus, the *current can't increase indefinitely*
- Assume  $R_1 = 30\ \Omega$  and  $V_\gamma = 0.6\text{ V}$   
 $\Rightarrow$  As soon as  $I_{c1}$  reaches about 20 mA,  $Q_5$  cuts in, shunts current away from the base of  $Q_1$ , and protects the circuit
- Due to the exponential dependence of this shunted current on  $V_{be5}$ , the maximum output current will saturate near around 20 mA itself
- Thus, under this case, if the output is accidentally shorted to ground, then  $P_1(\text{max})$  will be around 100 mW, which is well within limit, and protection will be achieved

- Similarly, for the *negative half cycle*, this job of *protection will be achieved by the  $Q_6$ - $R_2$  combination*
- The *drop across  $R_2$*  will depend on the *amount of current* being *sunk by  $Q_2$*
- Once this drop *reaches the cut-in voltage* of  $Q_6$ , it will *turn on*, and *bypass the drive current of  $Q_2$* , thus *protecting the circuit*
- This *protection circuit* is *widely used* due to its *efficacy*, and the *most popular analog building block*, the *op-amp*, *uses this protection scheme*
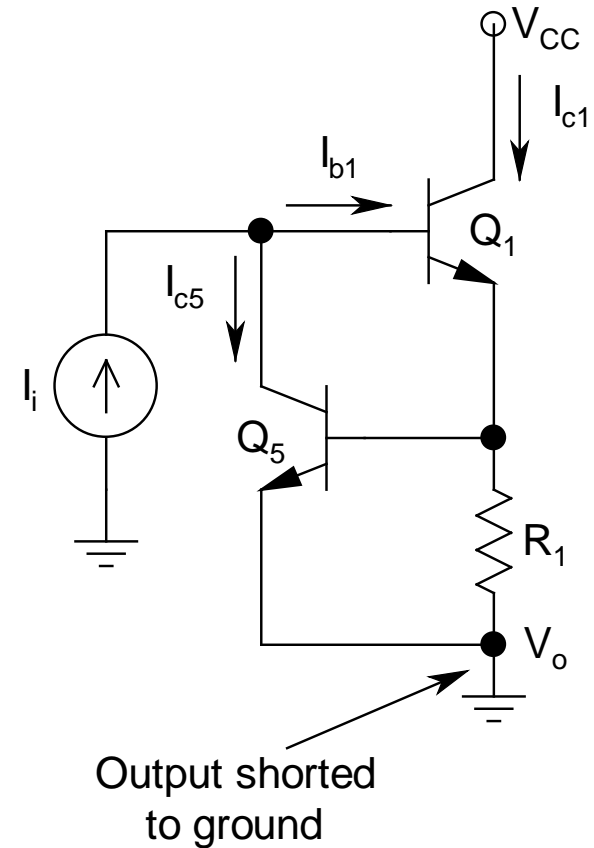
## ➤ *Quantitative Estimate of the Protection Mechanism:*


- Assume  $V_i$  *positive* and *supplying drive current*  $I_i$  to  $Q_1$
- Output shorted to ground*  
 $\Rightarrow V_o = 0$
- $I_i = I_{b1} + I_{c5}$   
 $I_{c5} = I_{S5} \exp(V_{be5}/V_T)$
- $V_{be5} = I_{c1} R_1$  (*assuming*  $\alpha_1 = 1$  and *neglecting*  $I_{b5}$ )



 **Protection Scheme**

- For *small values* of  $I_{c1}$ ,  $V_{be5}$  will be *small*, and  $I_{c5}$  will be *negligible*
- Also,  $I_{c1} = \beta_1 I_{b1} = \beta_1 (I_i - I_{c5})$   
 $\Rightarrow \beta_1 I_i = I_{c1} + \beta_1 I_{S5} \exp(I_{c1} R_1 / V_T)$
- This is the *final protection expression*
- For *small*  $I_{c1}$ , the *second term* on the *RHS* will be *negligible* as compared to the *first term*  
 $\Rightarrow I_{c1}$  would follow  $I_i$  linearly with proportionality constant  $\beta_1$
- As  $I_{c1} \uparrow$ , the *second term* on the RHS *increases at a much more rapid rate* than the *first term*

- Once it starts to become *comparable* to the first term, a *very little change* in  $I_{c1}$  can *counter a large change* in  $I_i$   
 $\Rightarrow I_{c1}$  gets clamped to almost a constant value of  $I_{c1,max}$
- Note that the *protection equation* is *transcendental*  
 $\Rightarrow$  Needs numerical or iterative solution



## Protection Characteristic

# FREQUENCY RESPONSE




- So far, considered *midband analysis*, where *all capacitive effects were neglected*
  - *Voltage/current gain was independent of frequency*
- In *practical amplifier circuits*, however, the *gain would depend on frequency*
- *Characterized by:*
  - *Lower Cutoff Frequency* ( $f_L$ )
    - *Contributed by external capacitors* ( $C_E$ ,  $C_B$ ,  $C_C$ )

➤ *Upper Cutoff Frequency* ( $f_H$ )

- *Contributed by device capacitances* (for BJTs:  $C_\pi$ ,  $C_\mu$ ; *for MOSFETs*:  $C_{gs}$ ,  $C_{gd}$ ,  $C_{sb}$ ,  $C_{db}$ )

 - These capacitors create *charge storage effects*, and *introduce time constants* into the circuit
- *Discrete circuits show both  $f_L$  and  $f_H$*
- *IC stages show only  $f_H$* , since most of them are *direct coupled* without the need for any *external capacitors*



$f_L$ : Lower Cutoff Frequency

$f_H$ : Upper Cutoff Frequency

$$\text{Bandwidth} = f_H - f_L$$

- *Exact analysis extremely complicated*
  - Most often, results in *very complicated expressions*, *completely hiding the physical feel of the phenomenon*
  - *Makes debugging extremely difficult*
    - For example, a circuit having *4 capacitors*, will have a *fourth-order transfer function*, which needs to be *solved* to get all the *poles and zeros* of the system
  - However, there are *techniques*, which make these *analyses* extremely *trivial*
    - *Not accurate*, but *extremely simple*, and makes *debugging easy*

- *Techniques:*
  - *Infinite-Value Time Constant (IVTC) Method*
    - *Used for obtaining  $f_L$*
  - *Zero-Value Time Constant (ZVTC) Method*
    - *Used for obtaining  $f_H$*
- These techniques are *extremely easy to apply*, and the results are *quite close to actuals*
- However, there is *one limitation* of these techniques

- They give information only regarding the *Dominant Pole* (DP) of the circuit
- *Completely hides information* about *other poles and zeros* of the circuit [known as *Non-Dominant Poles* (NDP) or *Zeros* (NDZ)]
- Anyway, information about *NDP and NDZ* are *not* that *critically important* from *practical point of view*