 


- ***NMOS Voltage Reference:***
  - *Highly popular due to its simplicity and effectiveness*
  - *Can generate  $n$  voltage references from  $(n + 1)$  MOSFETs*
  - *All MOSFETs diode-connected*  
 $\Rightarrow$  *Always saturated*
  - *No resistors needed*
  - *All bodies connected to ground*



- *Only for  $M_1$* ,  $V_{TN1} = V_{TN0}$
- *All other MOSFETs will have body effect*,  
e.g.,  $V_{TN2} = V_{TN0} + \gamma \left( \sqrt{2\phi_F + V_{01}} - \sqrt{2\phi_F} \right)$
- Generally, *all  $\lambda$ s also same*, but *aspect ratios are different*
- $V_{01}, V_{02}, \dots, V_{0n}$  are the *needed reference taps*
- $V_{GS1} = V_{DS1} = V_{01}$ ,  $V_{GS2} = V_{DS2} = V_{02} - V_{01}$ ,  
 $V_{GS3} = V_{DS3} = V_{03} - V_{02}, \dots$
- $V_{SB1} = 0$ ,  $V_{SB2} = V_{01}$ ,  $V_{SB3} = V_{02}, \dots$
- *Same DC current  $I_{REF}$  flows through all MOSFETs*

- Assuming that *all MOSFETs* have *same*  $\lambda$  and *same*  $k'_N$ :

$$\begin{aligned} I_{\text{REF}} &= \frac{k'_N}{2} \left( \frac{W}{L} \right)_1 (V_{01} - V_{\text{TN1}})^2 (1 + \lambda V_{01}) \\ &= \frac{k'_N}{2} \left( \frac{W}{L} \right)_2 (V_{02} - V_{01} - V_{\text{TN2}})^2 [1 + \lambda (V_{02} - V_{01})] \end{aligned}$$

...

- *First  $I_{\text{REF}}$  needs to be found by ensuring that the circuit dissipates least DC power*
- *Then, all  $(W/L)$ s can be calculated*

- *Choice depends on several design paradigms*
- $P_D(\text{circuit}) = V_{DD} \times I_{REF}$   
      $\Rightarrow$  *For minimum  $P_D$ ,  $I_{REF}$  should be minimum*
- *Need to pick up a reference MOSFET to start the design process*
- *Area of a MOSFET*  $= W \times L$
- *For minimum area,  $W = L = MFS$* 
  - ***MFS**: Minimum Feature Size (that is allowed by the technology)*
- Pick the *reference MOSFET* by choosing its  $(W/L) = 1$ , and having the *least*  $V_{GT}^2 (1 + \lambda V_{DS})$

- *This will yield minimum  $P_D$*
- *Once the reference MOSFET is chosen,  $I_{REF}$  becomes known, and  $(W/L)$ s of all other MOSFETs can be calculated*
- *Total area taken up by the circuit:*


$$\sum_n (W \times L)_n$$
- *Care: No dimension can be  $< MFS$*
- *Then what to do if  $(W/L) < 1$ ?*

# AMPLIFIERS

# Outline

- *Amplification* of *ac signals* (*voltage*, *current*)
- *Discrete* and *IC*
- *Single-Stage* and *Multi-Stage*
- *Modular approach*
- Interested in:
  - *Voltage/Current Gain* ( $A_v/A_i$ )
  - *Input/Output Resistance* ( $R_i/R_o$ )

# Midband Analysis

 

$f_L$ : Lower Cutoff Frequency

$f_H$ : Upper Cutoff Frequency

$$\text{Bandwidth} = f_H - f_L$$



# Single-Stage Topologies

- **BJT:**
  - **Common-Emitter** (CE)
    - *i/p to B, o/p from C, E common to both i/p and o/p*
  - **Common-Base** (CB)
    - *i/p to E, o/p from C, B common to both i/p and o/p*
  - **Common-Collector** (CC)
    - *i/p to B, o/p from E, C common to both i/p and o/p*
  - **Common-Emitter (Degeneration)** [CE(D)]
    - *Same as CE, but now with an emitter resistance attached*

- **MOSFET:**

- **Common-Source (CS)**

- *i/p to G, o/p from D, S common to both i/p and o/p*

- **Common-Gate (CG)**

- *i/p to S, o/p from D, G common to both i/p and o/p*

- **Common-Drain (CD)**

- *i/p to G, o/p from S, D common to both i/p and o/p*

- **Common-Source (Degeneration) [CS(D)]**

- *Same as CS, but now with a source resistance attached*

- For *MOSFETs*, an *additional topology* possible: *i/p to Body*, *o/p from S/D*
  - Known as *body-driven* or *bulk-driven* stage
- Each of the *topologies* has *specific characteristics* in terms of *voltage/current gain* and *input/output resistance*
- Each of these will be treated as a *module*, and will do a *complete analysis* for each of these stages

# Multi-Stage Topologies

- Also known as *Compound Connections*
- *Combination of 2 or more stages*
  - *A module by itself*
- *Some widely used topologies:*
  - *Darlington*
  - *Cascode*
  - *Differential Amplifier/Differential Pair*  
(*DA/DP*)

# Basic Structure

- Consists of a *driver* and a *load*
- *Driver*: Universally *active devices*, e.g., *BJTs* or *MOSFETs*
- *Load*: Can either be *resistors* (*passive*) or *transistors* (*active*)
- Generally, *discrete stages* have *passive loads*, while *IC stages* have *active loads*

# Resistance Transformation (Only for BJTs)

- *A very useful technique*


- For *equivalence*:

$$I_b R_2 = I_e R_1$$

$$\Rightarrow R_2 = (\beta + 1)R_1$$


$$\text{or } R_1 = R_2/(\beta + 1)$$

- *Apply it freely!*

 


# Single-Stage Amplifiers

- **Common-Emitter (CE):**

 

ac Schematic

 

ac Low-Frequency Equivalent

➤ ***Biasing circuit not shown***