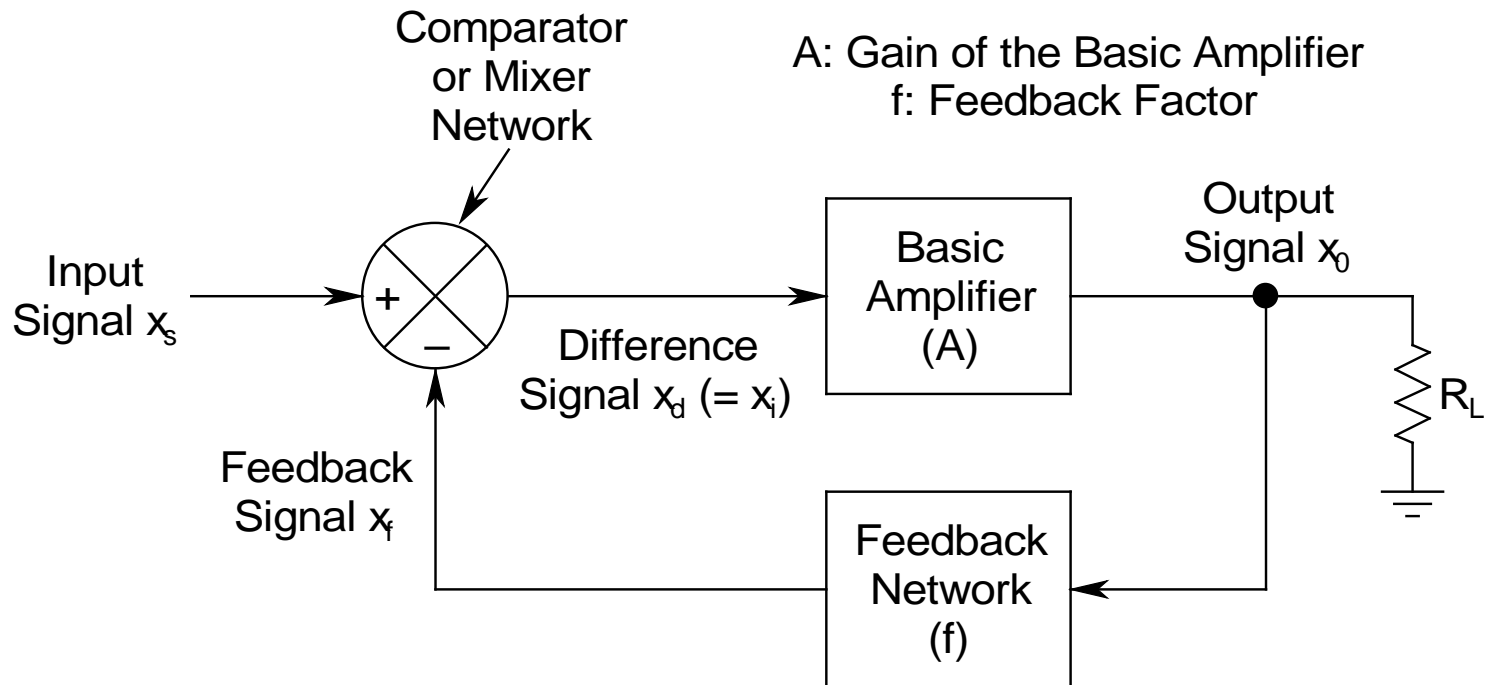


# FEEDBACK, STABILITY, & COMPENSATION

- *Properties of Negative Feedback:*
  - *Reduction in gain*
    - ⇒ *Improvement in bandwidth*  
(*Due to constant GBP*)
  - *Tailoring of input and output resistances*
  - *Desensitization of gain*
    - *Gain becomes almost independent of the properties of the active device*
  - *Minimization of frequency and phase distortion*

- *Reduction in nonlinear distortion*
  - *By suppression of harmonics present in the output*
- *Reduction of noise*
- *If not properly designed, can have problem of stability*
- *Properties of Positive Feedback:*
  - *Inherently unstable*
    - *Due to its regenerative nature*
    - *This property can be effectively utilized in the design of oscillators, which do not need any input*

- Mathematical Foundation of Negative Feedback:***



**Block Schematic of a Negative Feedback System**

➤ **3 Main Blocks:**

- **The Basic Amplifier** (**Gain  $A$**  )
- **The Feedback Network** (**Feedback Factor  $f$**  )
- **The Mixer** (**note the negative sign**)

➤ **Defining Relations:**

- **Input Signal**  $x_s$
- **Output Signal**  $x_o = Ax_i$
- **Feedback Signal**  $x_f = fx_o$
- **Difference Signal**  $x_d = x_i = x_s - x_f$

➤ **Gain with feedback:**  $A_f = x_o/x_s$

➤ Thus:

$$\begin{aligned} A_f &= \frac{X_0}{X_s} = \frac{X_0}{X_i} \frac{X_i}{X_s} = A \frac{X_s - X_f}{X_s} = A \left( 1 - \frac{X_f}{X_s} \right) \\ &= A \left( 1 - \frac{X_f}{X_0} \frac{X_0}{X_s} \right) = A (1 - fA_f) \end{aligned}$$

➤ Gives the *fundamental expression* for *negative feedback*:

$$A_f = \frac{A}{1 + fA}$$

- *Some Definitions:*

- *Loop Gain* (L) = fA

- *Return Difference* (D) = 1 + L

- *Amount of Feedback* (N) =  $20 \log_{10} D$  (dB)

- *Positive Feedback:*

- *Output fed back to the input through the mixer, but now with a positive sign*

- ⇒ *Feedback signal gets added to the input signal*

➤ *Under this condition:*

$$A_f(j\omega) = \frac{A(j\omega)}{1 - f(j\omega)A(j\omega)} = \frac{A(j\omega)}{1 - L(j\omega)}$$

➤ This is a *general expression*, taking both A and f as *frequency dependent*

➤ Note: As  $L \rightarrow 1$ ,  $A_f \rightarrow \infty$

- *Implies that output is possible even without any input*
- This is the *basic principle of oscillation*



- *Conditions for Oscillation:*

*Barkhausen's Criteria:*

- *L becoming unity implies that the signal has completely regenerated itself while traversing once through the loop*
  - ⇒ *There is no need for any input any more, since the loop has become self-sustained!*
- *Since A and f are frequency dependent, hence, there may exist a frequency  $\omega_0$ , at which:*

$$L(j\omega_0) = f(j\omega_0)A(j\omega_0) = 1$$

- Since  $\omega_0$  is a *particular frequency*, for which *this condition holds*, hence, the output will be a *pure sinusoid* of *this frequency*
- Similar to *picking out*  $f_0$  only from a *Fourier Spectrum*
  - This phenomenon is known as *Sinusoidal Oscillation*
- German physicist *Heinrich Georg Barkhausen* summed this up by *two conditions*, came to be known as the *Barkhausen's Criteria*:
1.  $|L(j\omega_0)| = 1$  and
  2.  $\angle L(j\omega_0) = 0^\circ$

➤ ***Barkhausen's Criteria in words:***

*For a feedback system to oscillate, the magnitude of the loop gain must at least be unity, and the total phase shift around the loop should be  $0^\circ$  or  $360^\circ$*

➤ *If these criteria are satisfied exactly, then the oscillations would go on forever, and can be stopped only by shutting the power off for the system*

➤ However, for *practical circuits*, the *exact conditions for oscillations* are *very difficult to achieve*

- If  $|L|$  becomes *slightly less than 1*, but  $\angle L$  is *exactly  $0^\circ$* , then with *each pass around the loop*, the *amplitude of oscillation* would keep on *going down*, and eventually, it will *die down* on its own
  - Thus, *under this condition*, *sustained sinusoidal oscillation won't be achieved*
- On the other hand, if  $|L|$  becomes *slightly larger than unity*, but  $\angle L$  is *exactly  $0^\circ$* , then with *each pass around the loop*, the *amplitude* of the signal will *keep on growing*
  - Will eventually *get limited* by the *nonlinearities* present in the circuit

# Stability

- *2 Types of Systems:*
  - *Stable*
  - *Unstable*
- *Stable System:*
  - *Any transient disturbance would result in a response that will die down with time*
  - *The system will be able to get rid of the disturbance on its own*

- *Unstable System:*

- *Any transient disturbance would result in a response that will persist or even blow up with time*
  - *Eventually gets limited by the nonlinearities of the system*
- *Positive feedback systems are inherently unstable*
  - *They are designed as such, e.g., oscillators*
- *Negative feedback systems are inherently stable*

- *However, there may be situations when they may become unstable and break out into spontaneous oscillations*
- *Potentially dangerous situation*, and the *system should be protected against it*
- *How does a negative feedback system become unstable?*
  - Write the *loop gain* expression in *polar form*:
$$L(j\omega) = f(j\omega)A(j\omega) = |f(j\omega)A(j\omega)|\exp[j\phi(\omega)]$$
$$\phi(\omega): \text{Frequency dependent phase of the system}$$

- Consider a *particular frequency*  $\omega_x$ , at which  $\phi(\omega_x) = 180^\circ$
- At  $\omega_x$ , L would be a *real number* with *negative sign*
  - $\Rightarrow$  *The feedback turns positive at this frequency*
- *3 conditions may arise at  $\omega_x$ :*
  - $|L| < 1$ :
    - ❖  $A_f(j\omega_x) > A(j\omega_x)$ , but the *system will be stable*
  - $|L| = 1$ :
    - ❖  $A_f(j\omega_x) \rightarrow \infty$ , and *output will appear without any input*  
 $\Rightarrow$  *Oscillator*



- $|L| > 1$ :
  - ❖  $A_f(j\omega_x) < A(j\omega_x)$ , but the *output will oscillate with gradually increasing amplitude*, and will *eventually get limited by the nonlinearities present in the system*
- Thus, for a *negative feedback system* to turn into a *positive feedback one*, the *loop gain* ( $L = fA$ ) being *equal to or less than  $-1$*  is a *sufficient and necessary condition*
- *For this to happen*, the *magnitude of the loop gain* ( $L$ ) *should be equal to or greater than unity*, and the *total phase around the loop should be  $180^\circ$*