

- **Double Cascode:**

- *Can be implemented in both BJT & MOS*

- *In npn Double Cascode, another pair Q_5 - Q_6 stacked upon Q_3 - Q_4*

- *Find $V_{0,min}$ and R_0*

- *In NMOS Double Cascode, another pair M_5 - M_6 stacked upon M_3 - M_4*

- *Find $V_{0,min}$*


- $R_0 \approx g_{m6}r_{o6}R_0$ ($R_0 \approx g_{m4}r_{o2}r_{o4}$)

- *Hence, show that double cascode in BJT offers absolutely no advantage in terms of R_0*

- *Low Value Current Source:*
 - *Current thrust: Low-power circuits*
⇒ *Increase in battery life*
 - *If bias current can be reduced from mA to μA , for the same power supply voltage, power drawn reduces by three orders of magnitude!*
 - *Normal CMs can also produce bias current in μA range, however, the required resistance will be huge ⇒ uneconomical for ICs*
 - *Most common: Widlar Current Source*
 - *After its inventor Bob Widlar (father of op-amp)*

- **Widlar Current Source:**

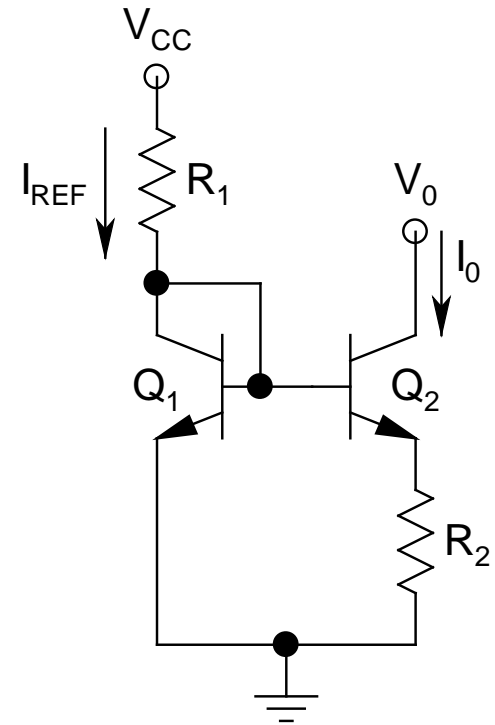- *Q_1 - Q_2 matched pair*
- $I_{REF} = (V_{CC} - V_{BE1})/R_1$
- If $I_0 = I_{REF}$, then $V_{BE1} = V_{BE2}$
 - *No drop across R_2 !*
$$\Rightarrow I_0 \neq I_{REF}$$
- *Actually, the difference between V_{BE1} and V_{BE2} drops across R_2*



- *KVL around Q_1 - Q_2 BE loop:*

$$V_{BE1} = V_{BE2} + I_0 R_2$$

$$\Rightarrow I_0 = \frac{V_{BE1} - V_{BE2}}{R_2} = \frac{V_T}{R_2} \ln \left(\frac{I_{REF}}{I_0} \right)$$

(since $I_{S1} = I_{S2}$)

- *Transcendental equation in I_0*
- *If I_0 is known, finding R_2 is absolutely easy!*
- On the other hand, *if R_2 is given, to find I_0 , need to iterate, but the solution will converge rapidly (Why?)*

- *The \ln function compresses a large difference between I_{REF} and I_0 into a small range*
 - For $I_{REF} \sim \text{mA}$, $I_0 \sim \mu\text{A}$, with $R_1 \sim \text{few k}\Omega\text{s}$ and $R_2 \sim \text{few 10s of k}\Omega$
 \Rightarrow *Significant flexibility!*
- $V_{0,\min} = V_{CE2}(\text{SS}) + I_0 R_2$
 \sim *0.3-0.4 V for practical values of I_0 and R_2*
- *R_0 can be obtained by sheer inspection of the circuit by noting that the base of Q_2 is approximately at ac ground*
- Also, $r_{\pi 2} \gg R_2$ (*Why?*)

➤ Thus,

$$R_0 \approx r_{02}(1 + g_{m2}R_2)$$

➤ **Note:** *To approximate this as $g_{m2}r_{02}R_2$, first make sure that $g_{m2}R_2 \gg 1$ (may not be!)*

➤ **Actual expression:**

$$R_0 \approx r_{02}(1 + g_{m2}R_{\text{eff}}) \text{ with } R_{\text{eff}} = R_2 || r_{\pi 2}$$

➤ *During further simplification, always check the validity of your assumption/approximation*

▪ *Otherwise it may lead to large errors!*

➤ *Counterpart of this circuit in MOS technology does not exist (Why?)*


DC Voltage References

- *Along with current sources/sinks, also need stable and precise DC voltage references*
- *Provides DC bias voltages at specific points of the circuit*
- *Should be independent of power supply and temperature*
- *Can range from -ve to +ve power supplies*
- *On-Chip: Generated within the chip itself*


- *In ICs, diodes are not fabricated as such*
 - *BJTs are used as diodes by shorting their Base and Collector terminals*
- *Various Voltage References:*
 - *Single Diode Reference*
 - *Multiple Diode Reference*
 - *V_{BE} (or V_D) Multiplier*
 - *Saturated Transistor*
 - *NMOS Voltage Reference*

- ***Single Diode Reference:***

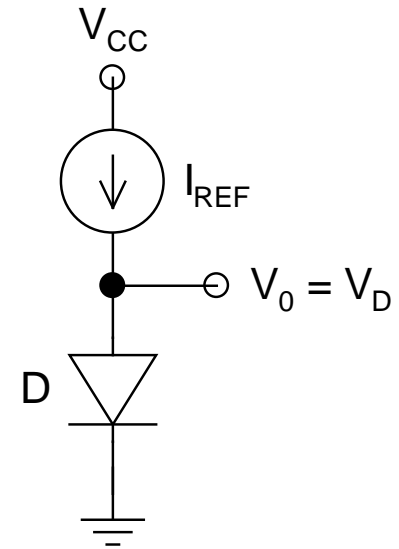- I_{REF} : ***DC Bias Current***
- ***Creates a voltage drop of V_D (or V_{BE}) across the diode of $\sim 0.7\text{ V}$***
- ***Known as V_{BE} (or V_D) Reference***
- ***Precision quite poor***
- ***Thermal tracking poor***




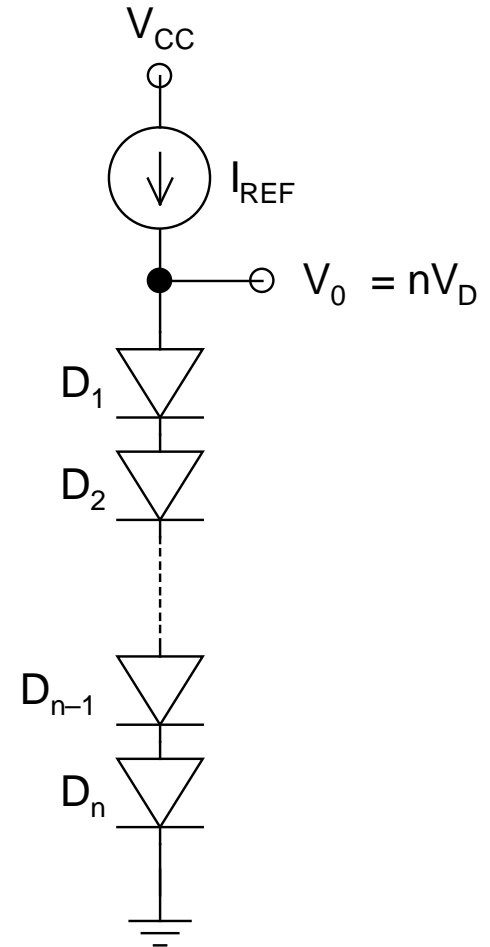- **Multiple Diode Reference:**
 - **Putting multiple diodes in series**
 - **DC bias current I_{REF} pushed through them**
 - **Each diode creates a drop of V_D across it**
 - **Has same problems as Single Diode Reference**
 - **Note: n can only be an integer**



- **V_{BE} (or V_D) Multiplier Circuit:**

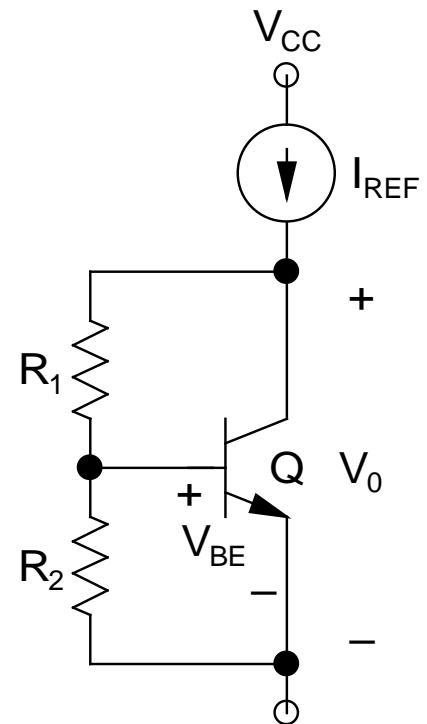- *Previous two circuits provide $V_0 = nV_D$, with n being an integer ≥ 1*
- *For any arbitrary value of n (≥ 1), this circuit becomes useful*
- *Immensely popular because of its simplicity and effectiveness*
- *Biased by a DC current source I_{REF}*



➤ *Neglecting base current:*

$$V_{BE} = \frac{R_2}{R_1 + R_2} V_0$$

$$\Rightarrow V_0 = \left(1 + \frac{R_1}{R_2}\right) V_{BE}$$

$\Rightarrow V_{BE}$ *Multiplier* with *multiplication factor* $(1 + R_1/R_2)$

➤ *Any arbitrary ratio of R_1 and R_2 can be used, but the multiplication factor is always ≥ 1*

- *Least possible $V_0 = V_{BE}$ [$R_1 = 0$ (short-circuit) and $R_2 \rightarrow \infty$ (open-circuit)]*
 \Rightarrow *Diode-Connected BJT*
- *The term $(1 + R_1/R_2)$ has excellent thermal tracking, since the TC_F of R_1 and R_2 cancel each other, but the TC_F of V_{BE} remains*
- *So far, we have got voltage references having $V_0 \geq V_{BE}$*
- *How to have a voltage reference having $V_0 < V_{BE}$?*

- ***Saturated Transistor:***

- ***Neglecting base current:***

$$V_0 = V_{BE} - I_{REF}R$$

- ***Note: V_0 is actually V_{CE} ,***

which is $< V_{BE}$

$\Rightarrow Q$ saturated

***\Rightarrow Analysis highly approximate,
since base current can't be
neglected in saturation***

- ***Typical range of $V_0 \sim 0.2-0.7$ V***

