

High-Frequency Response


- Will consider *3 methods*:
 - *Exact Analysis*:
 - The *most accurate* and the *most rigorous*
 - *Gives information about all poles and zeros of the system*
 - *Miller Effect Approximation*:
 - *One level of approximation*
 - *Gives information about the Dominant Pole (DP) and one Non-Dominant Pole (NDP)*

➤ *Zero-Value Time Constant (ZVTC)*


Technique:

- *The easiest one*
- *Information regarding only the DP*
- *Suppresses information about all other poles and zeros of the system*
- *Reasonable accuracy*
- *Underestimates f_H slightly (better than overestimating and not achieving it!)*
- *Based on heuristic*
- *Similar to the IVTC technique, based on an algorithm*

- *Exact Analysis of a CE Stage:*

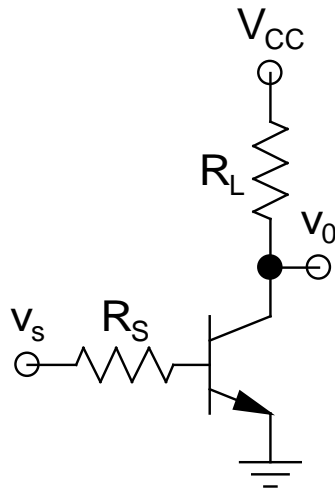

ac Schematic

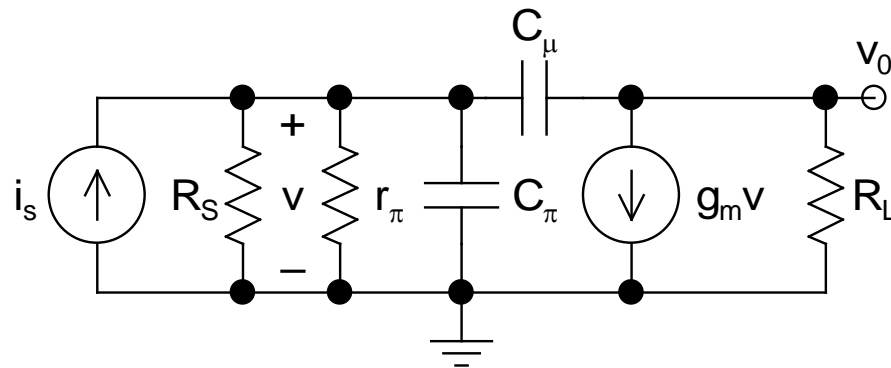

High-Frequency Equivalent

- *Biasing circuits omitted for simplicity*
- *Converted input v_s to its Norton equivalent*

➤ ***KCL at input node*** (using ***Laplace operator*** $s = j\omega$ and $R = R_S || r_\pi$):

$$\begin{aligned} i_s &= v/R + sC_\pi v + sC_\mu(v - v_0) \\ &= [1/R + s(C_\pi + C_\mu)]v - sC_\mu v_0 \end{aligned}$$

➤ ***KCL at output node***:

$$sC_\mu(v_0 - v) + g_m v + v_0/R_L = 0$$

$$\Rightarrow v = -\frac{1/R_L + sC_\mu}{g_m - sC_\mu} v_0$$

$$\Rightarrow \frac{v_0}{i_s}(s) = -\frac{R_L R (g_m - sC_\mu)}{1 + s(R_L C_\mu + R C_\mu + R C_\pi + g_m R_L R C_\mu) + s^2 R_L R C_\pi C_\mu}$$

➤ Thus, the *voltage gain*:

$$A_v(s) = \frac{V_o}{V_s} = -\frac{g_m R_L R}{R_S} \frac{(1 - sC_\mu / g_m)}{1 + sa + s^2 R_L R C_\pi C_\mu} \quad (1)$$

$$a = R_L C_\mu + R(C_\pi + C_\mu) + g_m R_L R C_\mu$$

➤ Hence, the circuit has *one zero* and *two poles*

$$\Rightarrow A_v(s) = A_{v0} \frac{(1 - s/z_1)}{(1 - s/p_1)(1 - s/p_2)} \quad (2)$$

$$\begin{aligned} A_{v0} &= \textit{midband gain} = -g_m R_L R / R_S \\ &= -g_m R_L r_\pi / (r_\pi + R_S) \end{aligned}$$

- $z_1 (= g_m/C_\mu)$: *positive real zero*
- The *frequency* corresponding to z_1 occurs at $z_1/(2\pi)$, which is *extremely high*, and generally, is *not of much consequence*
- *Computation of the two poles p_1 and p_2 is slightly more tricky*
- From Eqs.(1) and (2), it is obvious that *both p_1 and p_2 are real and negative*

- To find these, *write the denominator* of Eq.(1) as:

$$\begin{aligned} D(s) &= (1 - s/p_1)(1 - s/p_2) \\ &= 1 - s(1/p_1 + 1/p_2) + s^2/(p_1 p_2) \end{aligned} \quad (3)$$

- *Matching coefficients* with Eq.(2), we can get p_1 and p_2 , however, the *resulting algebra* will become *extremely tedious*
- Hence, we invoke the *Dominant Pole Approximation* (DPA)


➤ **DPA:**

- The *smallest pole* [*Dominant Pole* (DP)] is *at least 10 times away from its nearest pole*
- This is an *excellent approximation for practical analog circuits*

➤ *Apply this approximation* and *assume p_1 to be the DP* and *at least 10 times away from p_2* [*Non-Dominant Pole* (NDP)]

➤ The *pole frequencies* are $|p_1|/(2\pi)$ and $|p_2|/(2\pi)$

➤ *Note:* $|p_1|/(2\pi)$ is the *Upper Cutoff Frequency* (f_H)

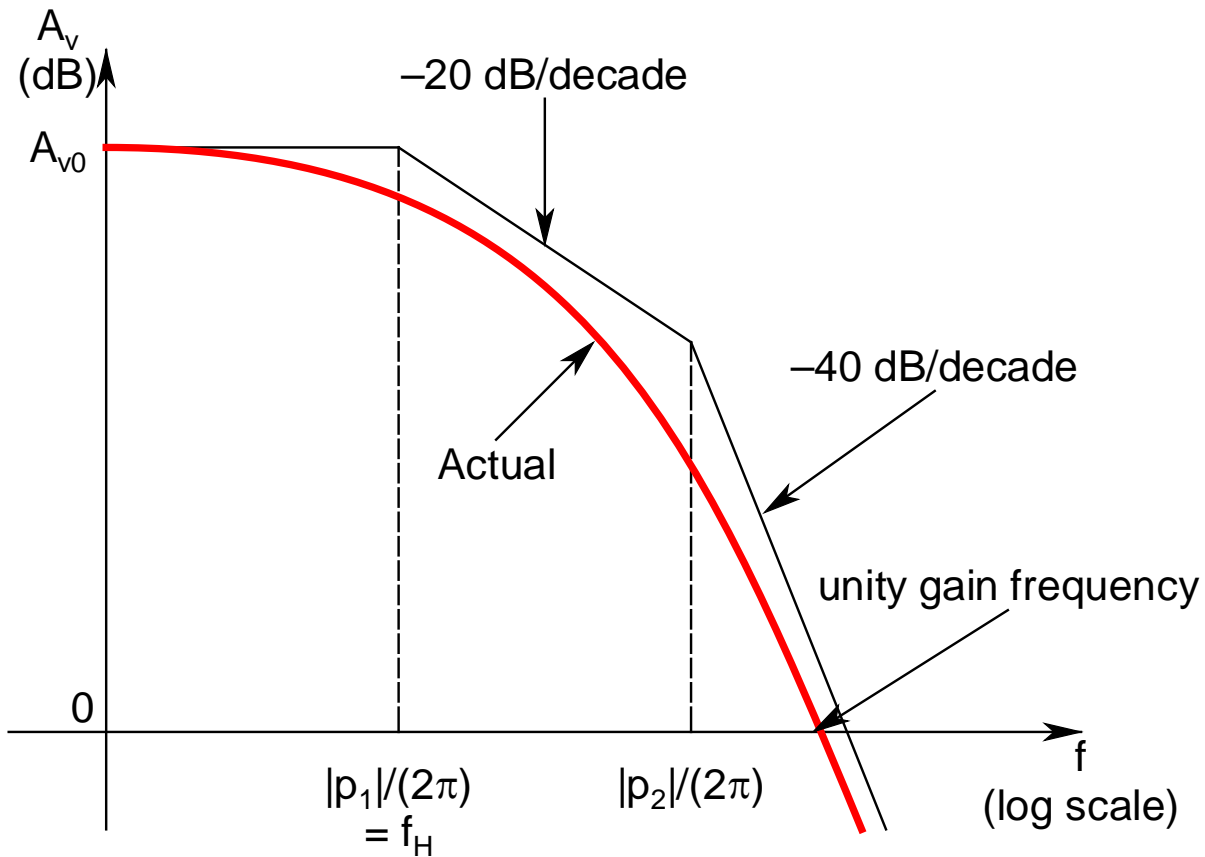

Bode Plot of the Frequency Response of a 2-Pole System

- *2-pole system*
- *For frequencies till the first pole p_1 , gain remains constant at its midband value of $20\log_{10}A_{v0}$*
- *Beyond this*, the *gain rolls off at -20 dB/decade till the second pole p_2 is encountered*
- *After this*, the *gain rolls off at -40 dB/decade*, and *eventually crosses zero* (at *unity gain frequency*)
- *Beyond this*, the circuit actually *attenuates the input signal instead of amplifying it* (gain magnitude drops below unity)

- *It's assumed that z_1 is $\gg |p_2|$*
- *Task remains to find p_1 and p_2*
- *Under DPA*, Eq.(2) can be simplified as:

$$D(s) \approx 1 - s/p_1 + s^2/p_1p_2 \quad (4)$$
- *Comparing* Eq.(4) with the *denominator* of Eq.(1):


$$p_1 = -\frac{1}{(R_S \parallel r_\pi)C_\pi + [(R_S \parallel r_\pi) + R_L + g_m(R_S \parallel r_\pi)R_L]C_\mu}$$

$$p_2 = -\left(\frac{1}{R_L C_\mu} + \frac{1}{(R_S \parallel r_\pi)C_\pi} + \frac{1}{R_L C_\pi} + \frac{g_m}{C_\pi} \right)$$


- In general, $|p_2| \gg |p_1|$
- **Ex.**: $I_C = 1 \text{ mA}$, $\beta = 200$, $R_S = 1 \text{ k}\Omega$, $R_L = 2 \text{ k}\Omega$, $C_\pi = 10 \text{ pF}$, $C_\mu = 0.5 \text{ pF}$
 $\Rightarrow DPF = 3.8 \text{ MHz}$, $NDPF = 798.8 \text{ MHz}$, $ZF = 12.3 \text{ GHz}$, and $f_H = DPF = 3.8 \text{ MHz}$
- **Note**: Even for a *simple CE circuit*, the *analysis is so cumbersome*, and the *results are so complicated*
- *Definitely not acceptable for routine application, particularly for circuits having more than one active device*

- *Miller Effect Approximation:*

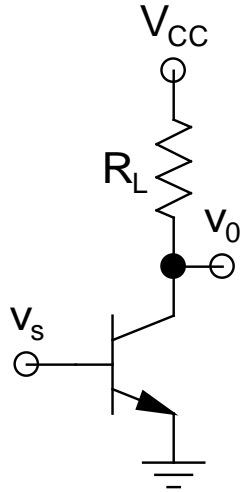- *Technique by which an input-output coupled circuit can be decoupled by removing the coupling element*
- This *removal* is done by *splitting* it into *two components* - putting *one in the input circuit*, and the *other in the output circuit*
- We take the *same example* as the *CE circuit* discussed earlier, but now *without R_S*



ac Schematic

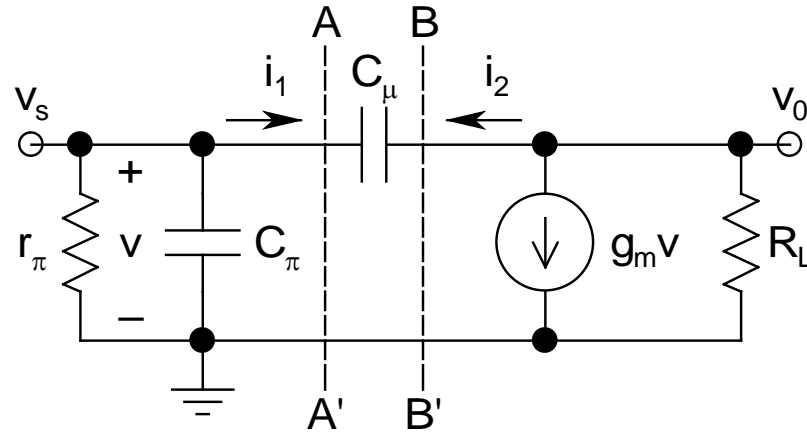

High-Frequency Equivalent

- Identify C_μ as the input-output coupling element
- After **application** of the **technique**, this **coupling element** will be **removed** by **splitting** it into **two parts** - **one at input**, **other at output**

➤ These *two parts* can be found by *evaluating* the *impedances* looking into the *planes* AA' and BB'

➤ *KCL at output node:*

$$g_m v + v_0/R_L + sC_\mu(v_0 - v) = 0$$

➤ Noting that $v = v_s$, the *voltage gain*:

$$A_v(s) = -g_m R_L (1 - sC_\mu/g_m) / (1 + sR_L C_\mu)$$

⇒ *Midband or low-frequency gain*:

$$A_v(0) = -g_m R_L$$

This result can also be written from inspection

➤ *Current entering plane AA' :*

$$i_1 = sC_\mu(v - v_0) = sC_\mu[1 - A_v(s)]v$$

➤ Hence, the *admittance* looking into the *plane* AA' :

$$y|_{AA'} = i_1/v = sC_\mu[1 - A_v(s)]$$

➤ This *admittance* is *capacitive* in nature, and is known as the *Miller Capacitance* C_M :

$$C_M = C_\mu[1 - A_v(s)]$$

➤ Now, since $A_v(s)$ is a function of frequency, so *would* $C_M \Rightarrow$ *Problem!*

- Here, we invoke the *Miller Effect Approximation* (MEA)
 - $A_v(s)$ is replaced by $A_v(0)$, i.e., by its *midband value*, which is a *constant*
 - Thus, C_M becomes a constant with a value of

$$C_M = [1 - A_v(0)]C_\mu = (1 + g_m R_L)C_\mu$$
- Thus, $C_M \gg C_\mu$, since, in general, $g_m R_L \gg 1$
- This effect is known as the *Miller Effect Multiplication*
- *Care: The gain that multiplies C_μ is across its two ends*

- Similarly, *current entering plane BB'*:

$$i_2 = sC_\mu(v_0 - v) = sC_\mu[1 - 1/A_v(s)]v_0$$

- Hence, the *admittance* looking into the *plane BB'*:

$$y'|_{BB'} = i_2/v_0 = sC_\mu[1 - 1/A_v(s)]$$

- Again *replacing* $A_v(s)$ by $A_v(0)$, we get:

$$C'_M = [1 - 1/A_v(0)]C_\mu = [1 + 1/(g_m R_L)]C_\mu$$

- In general, $g_m R_L \gg 1 \Rightarrow C'_M \simeq C_\mu$