
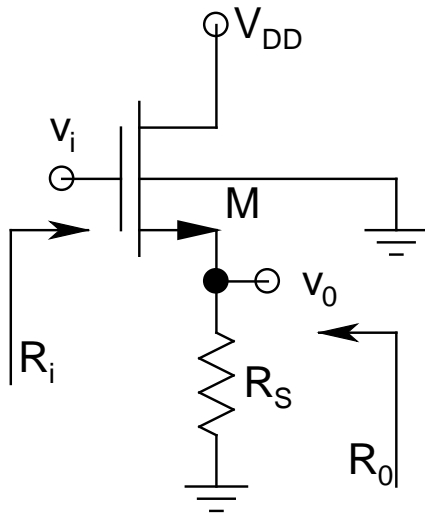


- **Common-Drain (CD):**

➤ Also known as *Source Follower*

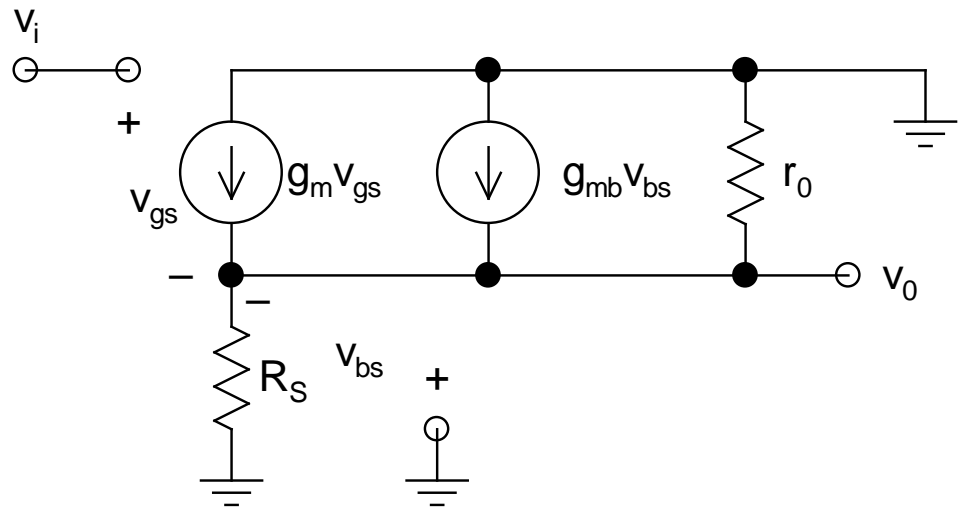

ac Schematic



ac Low-Frequency Equivalent

➤ *Biasing circuit not shown*

- **Note:** *Body terminal at ground*, but *source is at a floating potential (it's the output terminal)*
⇒ *Body effect will be very much present for M*
⇒ *Can be avoided by putting M in its separate island* (to be discussed later)

➤ **Voltage Gain:**

- *KCL at output node:*

$$g_m v_{gs} + g_{mb} v_{bs} = v_o / (R_S \parallel r_o)$$

with $v_{gs} = v_i - v_o$, and $v_{bs} = -v_o$

$$\Rightarrow A_v = \frac{v_o}{v_i} = \frac{g_m (R_S \parallel r_o)}{1 + (g_m + g_{mb})(R_S \parallel r_o)}$$

➤ *Simplification:*

- In general, $r_0 \gg R_S$:

$$\Rightarrow A_v \simeq \frac{g_m R_S}{1 + (g_m + g_{mb}) R_S}$$

- If *body effect is neglected*:

$$\Rightarrow A_v \simeq \frac{g_m R_S}{1 + g_m R_S} = \frac{R_S}{1/g_m + R_S}$$

Note the remarkable similarity with CC stage

- If $(g_m + g_{mb}) R_S \gg 1$:

$$\Rightarrow A_v \simeq \frac{g_m}{g_m + g_{mb}} = \frac{1}{1 + \chi}$$

■ **Note:**

$$\chi = \frac{\gamma}{2\sqrt{2\phi_F + V_{SB}}}$$

with $V_{SB} = -V_0$ (*DC level of v_0*)

- *Typical values of $\chi \sim 0.1-0.5$*
- Thus, *A_v can depart significantly from its ideal value of unity*
- *No phase shift between input and output*

➤ *Input Resistance: $R_i \rightarrow \infty$*

➤ *Output Resistance: By inspection:*

$$R_0 = (g_m + g_{mb} + g_0 + g_S)^{-1} \quad (g_0 = 1/r_0, g_S = 1/R_S)$$

- **Common-Emitter (Degeneration) [CE(D)]:**

➤ Let's attempt to analyze this circuit by *inspection*

➤ $v_0 = -i_c R_C$


$v_i = i_e (r_E + R_E)$

$\Rightarrow A_v = v_0/v_i$
 $\approx -R_C/(r_E + R_E)$

Piece of cake?

➤ $A_i = i_c/i_b = \beta$

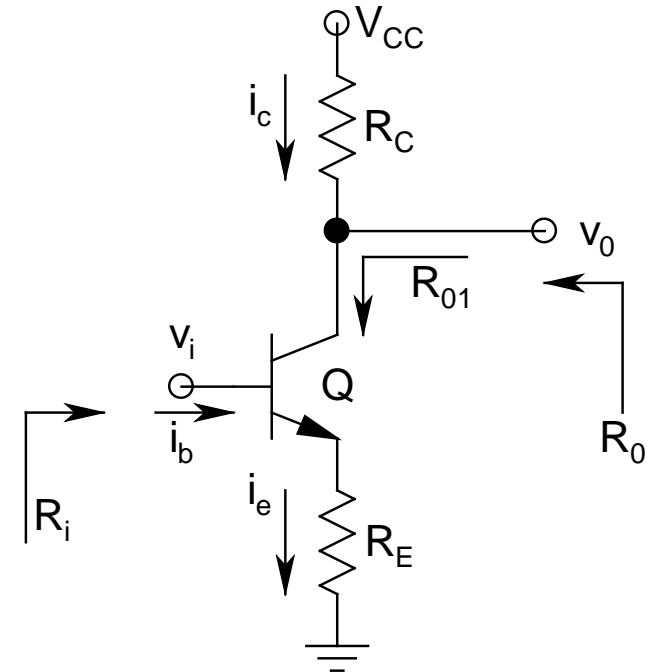➤ $R_i = r_\pi + (\beta + 1)R_E = (\beta + 1)(r_E + R_E)$



➤ $R_0 = R_{01} \parallel R_C$

Can you identify R_{01} by *inspection*?

$$R_{01} = r_0 [1 + g_m (r_\pi \parallel R_E)]$$

Generally, $R_{01} \gg R_C$

$$\Rightarrow R_0 \approx R_C$$

➤ *Probe A_v further:*

$$A_v = -R_C / (r_E + R_E) \approx -g_m R_C / (1 + g_m R_E)$$


For *CE stage*, $A_v = -g_m R_C$

For this stage, A_v is *lower* by a *factor* $(1 + g_m R_E) \Rightarrow$ *Gain Degeneration*


- $(1 + g_m R_E)$ is known as the *Degeneration Factor*
- R_i can also be written as:
$$R_i \approx r_\pi + \beta R_E = r_\pi (1 + g_m R_E)$$
Thus, $R_i \uparrow$ by the *Degeneration Factor* as compared to the *CE stage*
- *Interesting to note that the loss in gain is returned by this circuit to its R_i by the same factor!*

- *Why do we sacrifice gain?*
 - Later on, we will see that this *sacrifice in gain* leads to a *commensurate increase in the bandwidth* of the circuit
- *For a given bias point*, the *gain-bandwidth product (GBP) of a circuit remains constant* (will be explored later)
- This is one of the *famous paradoxes* of analog circuits:
 - *To increase gain, sacrifice bandwidth, and vice versa*

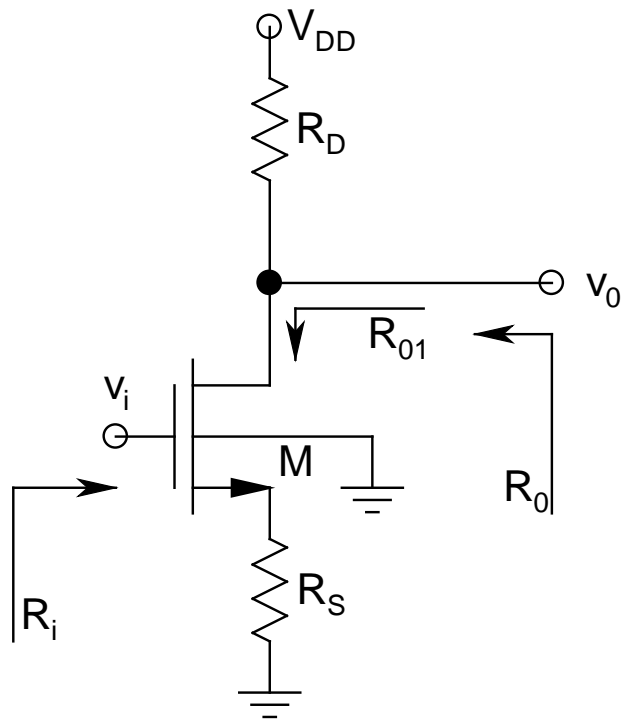- **Common-Source (Degeneration) [CS(D)]:**



ac Schematic

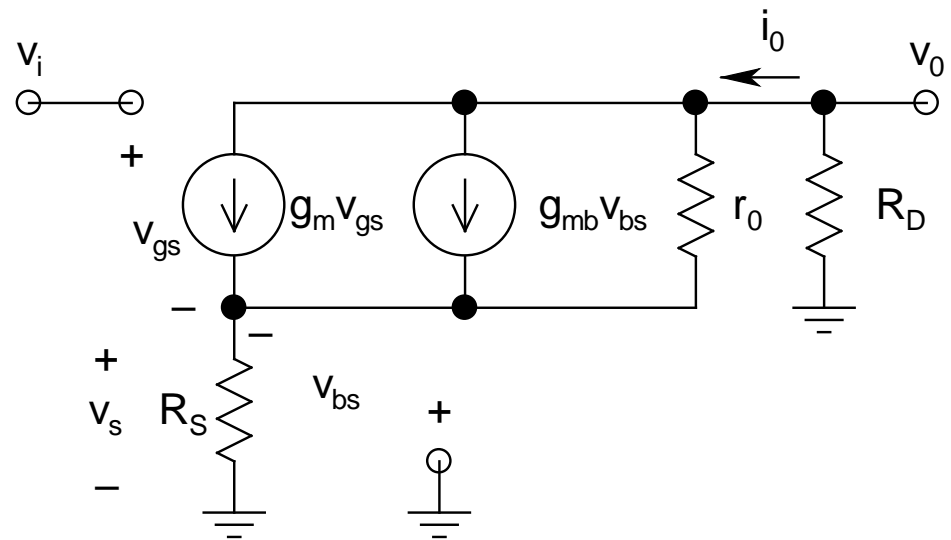

ac Low-Frequency Equivalent

➤ *Defining Relations:*

$$v_0 = -i_0 R_D$$

$$i_0 = g_m v_{gs} + g_{mb} v_{bs} + (v_0 - v_s)/r_0$$

$$v_s = i_0 R_S$$

$$v_{gs} = v_i - v_s$$

$$v_{bs} = -v_s$$

$$\Rightarrow A_v = \frac{v_0}{v_i} = -\frac{g_m R_D}{1 + (g_m + g_{mb}) R_S + (R_S + R_D)/r_0}$$

➤ Pretty *complicated* expression, however,
simplifications can be made

- Generally, $(R_S + R_D)/r_0$ can be *neglected*:

$$\Rightarrow A_v = \frac{v_o}{v_i} \simeq -\frac{g_m R_D}{1 + (g_m + g_{mb}) R_S}$$

- *Neglect body effect*:

$$\Rightarrow A_v \simeq -\frac{g_m R_D}{1 + g_m R_S} = -\frac{R_D}{1/g_m + R_S}$$


- Again, *remarkable similarity with CE(D) stage*

- *Golden Observation*:


- *MOS stages, in absence of body effect, is absolutely similar to BJT stages, with r_E replaced by $1/g_m$*

- Note that here the *Degeneracy Factor* is $(1 + g_m R_S)$
- $R_i \rightarrow \infty$
- $R_0 = R_{01} || R_D$
 $R_{01} = r_0 [1 + (g_m + g_{mb}) R_S]$ (*Show!*)
- Again *gain is sacrificed* in order to *improve the bandwidth* by the *same amount*
- The complexity of analysis of this circuit is slightly more than the others encountered so far

- **Common-Base (CB):**

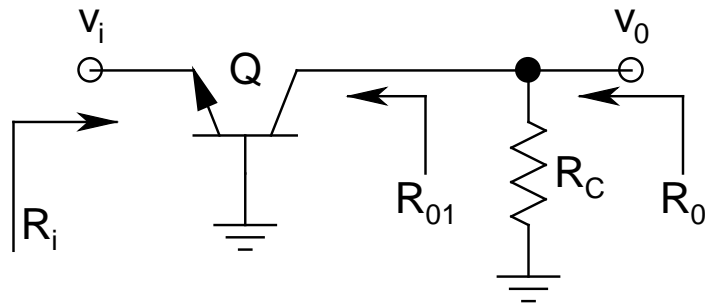

ac Schematic

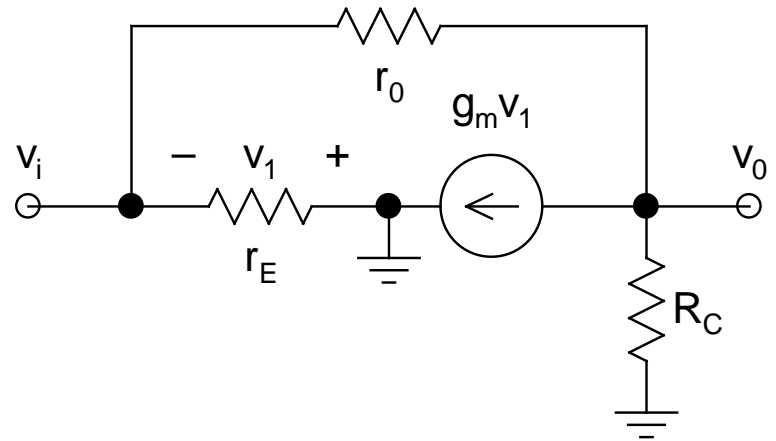

ac Low-Frequency Equivalent

- Note that the **alternate hybrid- π model** appropriate for **CB circuit** has been used
- **r_0 appears between input and output**

- For now, *neglect r_o*
- Noting that $v_1 = -v_i$:

$$A_v = \frac{v_o}{v_i} = \frac{-g_m v_1 R_C}{v_i} = +g_m R_C \simeq \frac{R_C}{r_E}$$

- Note that the *expression* for A_v is *identical* to that for the *CE stage*, *without the negative sign in front*
- For this circuit, *input and output are in phase*
- $A_i = i_c/i_e = \alpha$
- $R_i = r_E$

➤ $R_0 = R_{01} || R_C$

$R_{01} \rightarrow \infty$ (Why?)

$\Rightarrow R_0 = R_C$

➤ *Ex.: Find A_v and R_i with r_o included*

➤ *With r_o included*, the circuit shows *two different values* of R_{01} :

- *When excited by a voltage source*, $R_{01} = r_o$
- *When excited by a current source*, $R_{01} = \beta r_o$ (*Show*)
[*Hint: For this derivation, need to use $g_m r_E = \alpha$*]
- *Thus, possibility of huge R_0 under the second case, but R_C ruins it!*