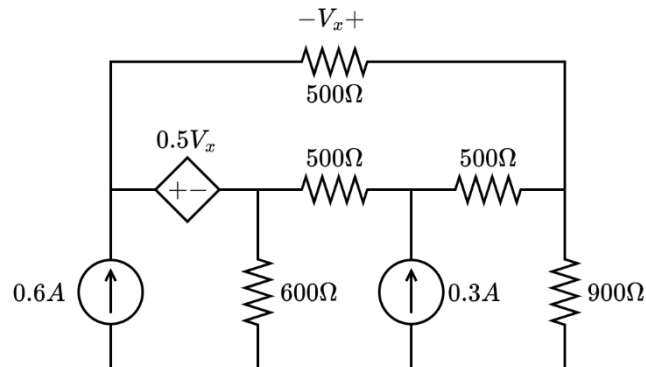


ESO203 Tutorial 2 SOLUTIONS

Q. 1: Find the value of V_x in the following figure.



Solution:

Let us consider 4 meshes with mesh current I_1, I_2, I_3, I_4 .

Mesh 2 and mesh 3 have a current source in common. So, they will form a supermesh.

Now, from mesh 1, we get

$$I_1 = 0.6 \text{ A} \quad \dots (i)$$

Also,

$$I_2 - I_3 = -0.3 \text{ A} \quad \dots (ii)$$

From supermesh,

$$600(I_2 - I_1) + 500(I_2 - I_4) + 500(I_3 - I_4) + 900I_3 = 0$$

$$-600I_1 + 1100I_2 + 1400I_3 - 1000I_4 = 0 \quad \dots (iii)$$

From mesh 4,

$$-0.5V_x + 500I_4 + 500(I_4 - I_3) + 500(I_4 - I_2) = 0$$

$$-0.5V_x - 500I_2 - 500I_3 + 1500I_4 = 0 \quad \dots (iv)$$

Also,

$$V_x = -500I_4 \quad \dots (v)$$

Putting equation (i), (ii), (v) in equation (iii), (iv), we get


$$2500I_3 - 1000I_4 = 690 \quad \dots (vi)$$

$$-1000I_3 + 1750I_4 = -150 \quad \dots (vii)$$

From equation (vi) and (vii), we get


$$I_3 = 0.3133 \text{ A}, \quad I_4 = 0.0933 \text{ A}$$

So,

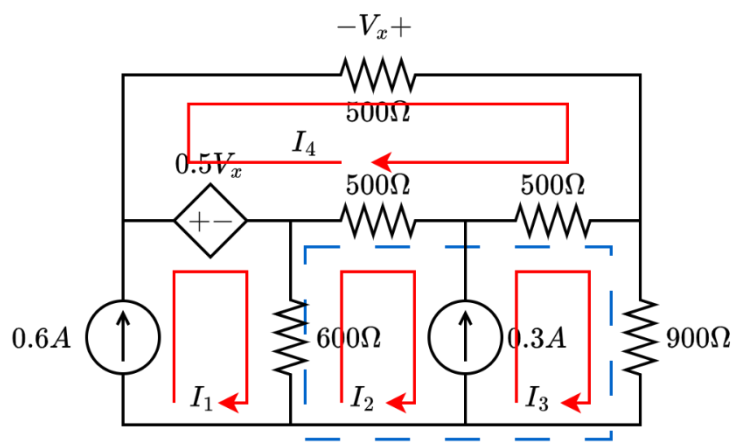

$$V_x = -46.65V$$

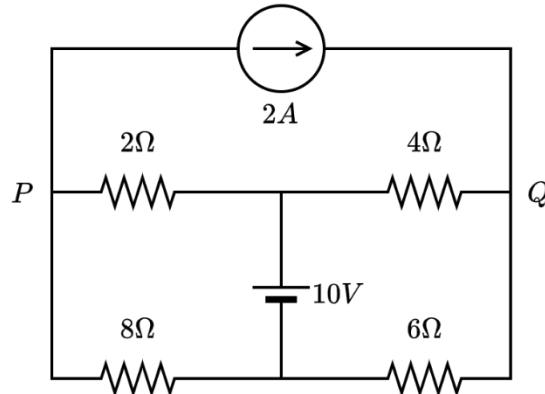Q. 2: Determine the potential difference between P and Q.



Solution:

Let a reference node. Consider the reference node at the ground.

Using nodal analysis at node P,

$$\frac{V_P - 0}{8} + \frac{V_P - 10}{2} + 2 = 0$$

$$V_P = 4.8V$$


Using nodal analysis at node Q,

$$\frac{V_Q - 0}{6} + \frac{V_Q - 10}{4} = 2$$


$$V_Q = 10.8V$$

So, the potential difference between P and Q is


$$V_{PQ} = -6V$$

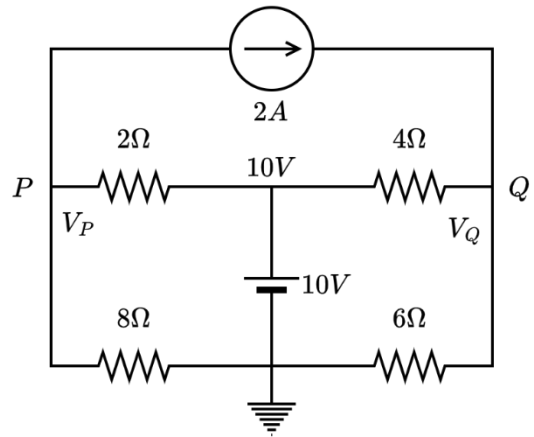

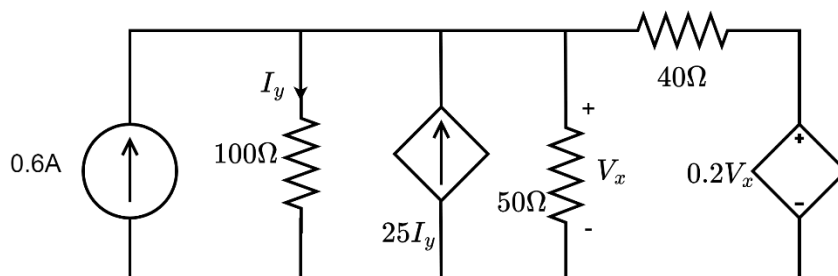Q. 3: For the circuit of the given figure, find the voltage V_x using the nodal analysis.



Solution:

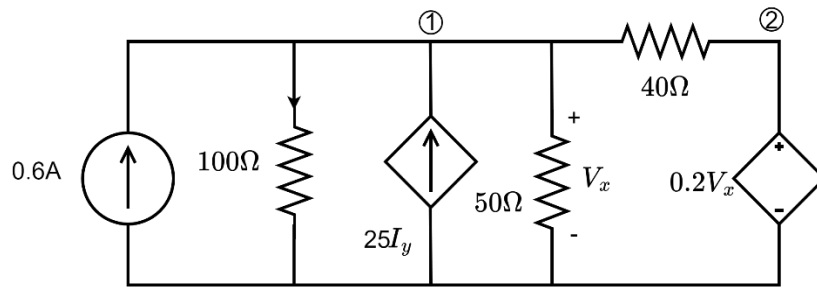

By applying KCL at node (1)

$$-0.6 + I_y + \frac{V_x}{50} - 25I_y + \frac{V_1 - V_2}{40} = 0 \quad \dots \dots \dots (1)$$

By KCL at node (2),

$$V_2 = 0.2V_x \quad \dots \dots \dots (2)$$


And other constraint equations,

$$I_y = \frac{V_x}{100} \text{ and } V_1 = V_x$$

Putting value of I_y , V_1 , and V_2 in terms of V_x in the equation (1),

$$\begin{aligned} -0.6 + \frac{V_x}{100} + \frac{V_x}{50} - 25 \frac{V_x}{100} + \frac{(V_x - 0.2V_x)}{40} &= 0 \\ \Rightarrow -120 + 2V_x + 4V_x - 50V_x + 5V_x - 5 \times 0.2V_x &= 0 \\ \Rightarrow V_x = \frac{120}{-40} &= -3V \end{aligned}$$

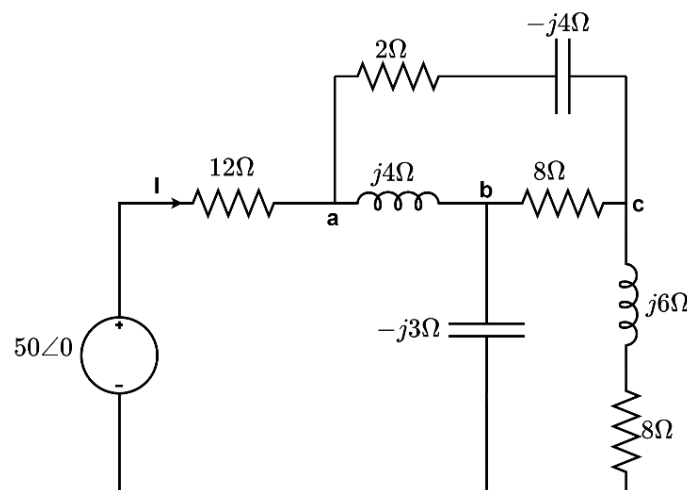Q. 4: Find the current I in the given circuit.



Solution:

The delta network connected to nodes a, b, and c can be converted to the Y network of the given figure. We obtain the Y impedances as:

$$Z_{an} = \frac{j4(2 - j4)}{j4 + 2 - j4 + 8} = \frac{4(4 + j2)}{10} = (1.6 + j0.8)\Omega$$

$$Z_{bn} = \frac{j4(8)}{10} = j3.2\Omega$$


$$Z_{cn} = \frac{8(2-j4)}{10} = (1.6-j3.2)$$

The total impedance at the source terminal is


$$\begin{aligned} Z &= 12 + Z_{an} + (Z_{bn} - j3) \parallel (Z_{cn} + j6 + 8) \\ &= 12 + 1.6 + j0.8 + (j0.2) \parallel (9.6 + j2.8) \\ &= 13.64 \angle 4.204^\circ \Omega \end{aligned}$$

The current is

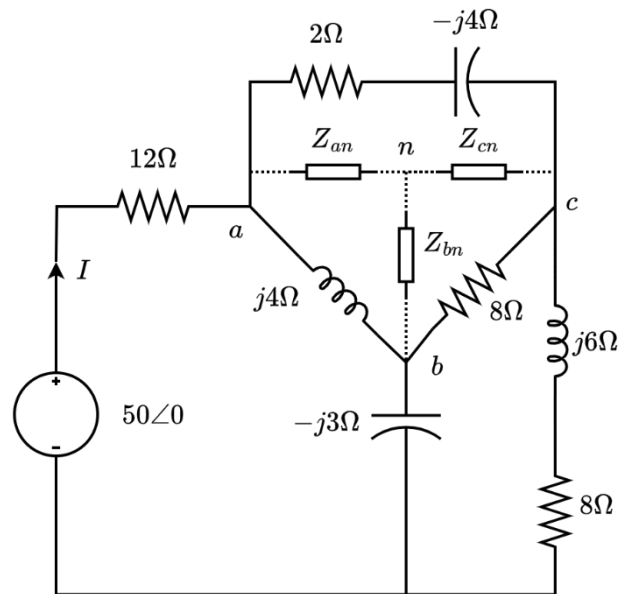
$$I = \frac{V}{Z} = \frac{50 \angle 0^\circ}{13.64 \angle 4.204^\circ} = 3.666 \angle -4.204^\circ \text{ A}$$



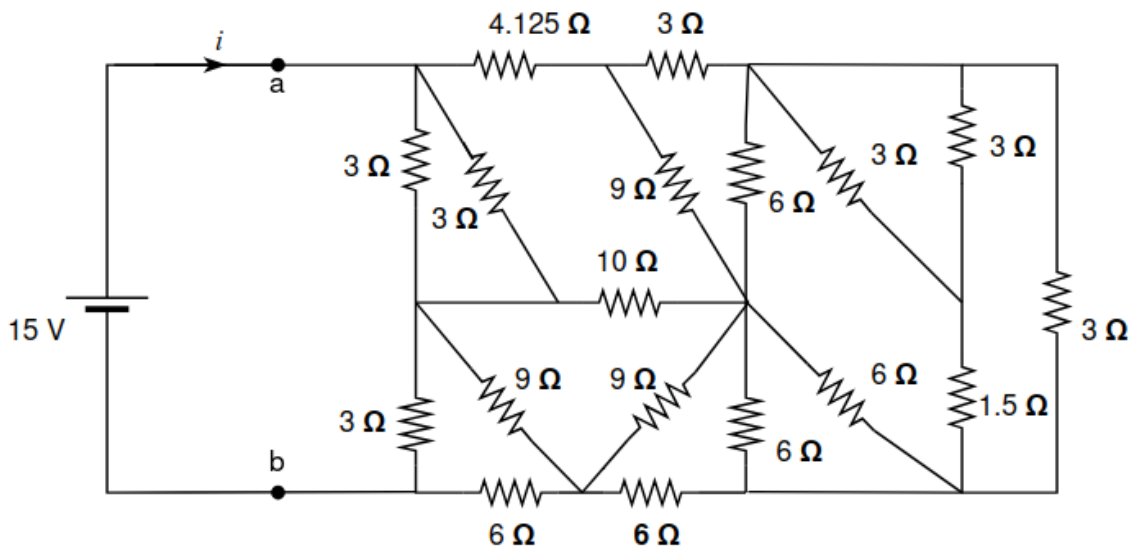Q. 5: Obtain the equivalent resistance R_{ab} for the circuit shown in the figure and find the current " i ".




Solution:

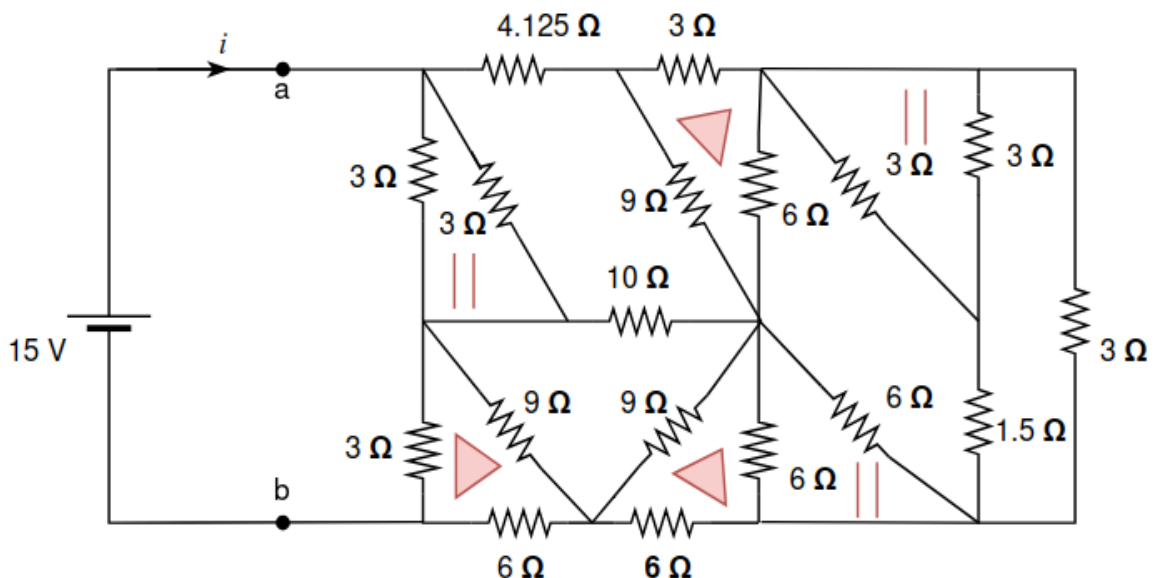


Using star-delta conversion, the above deltas shown in the figure is converted into stars,

Now,

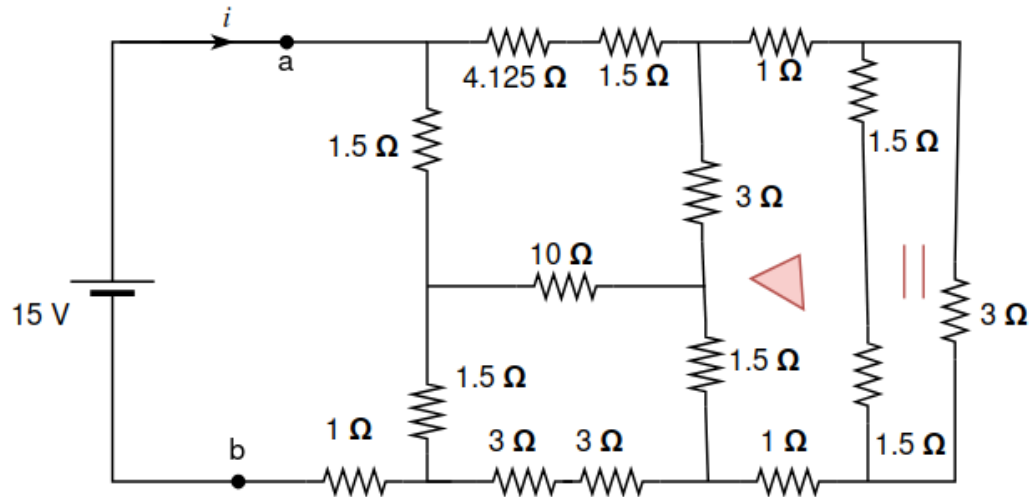

Further simplification,

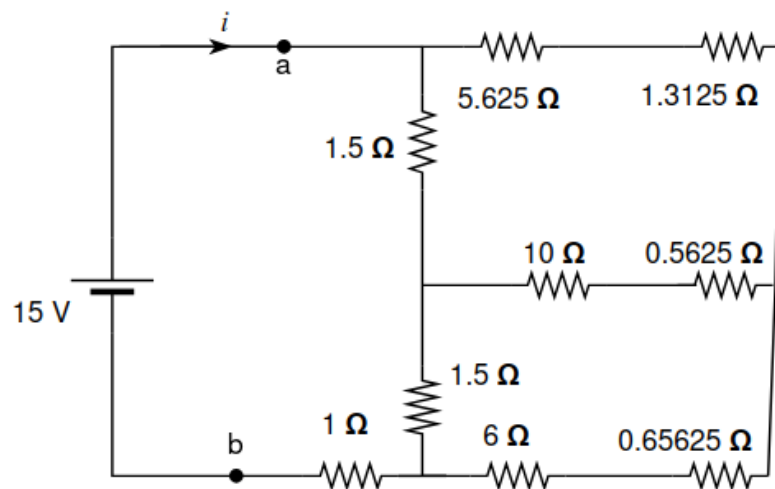

Taking approximation value to deduce the circuit ($6.65625\Omega \approx 6.9375\Omega$), and applying wheatstone bridge.

The 10Ω and 0.5625Ω can be removed.

Now 3Ω and 14Ω is parallel.


We can calculate the equivalent resistance between a and b by

$$R_{ab} = \frac{14 \times 3}{17} + 1\Omega, \quad R_{ab} = 3.47\Omega$$

and

$$i = \frac{15}{3.47}A, \quad i = 4.32A$$

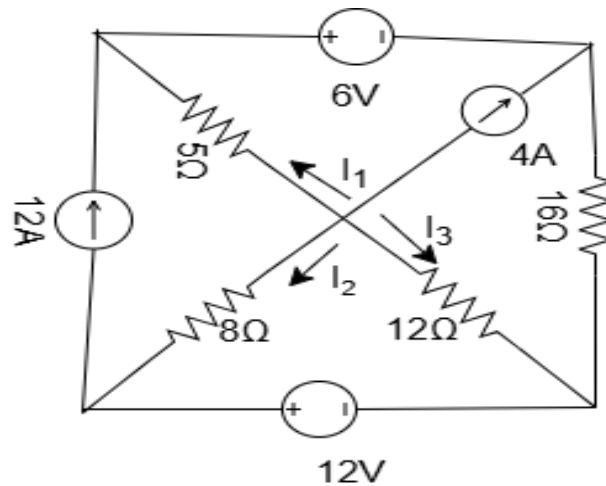Q. 6: In the given circuit, find the current I_1 , I_2 , and I_3 using nodal and mesh analysis.



Solution:

Using KCL, the current in 6V battery is $12 + I_1$.

Similarly, current in 16Ω resistance is $16 + I_1$.

Apply KCL at the central node,

$$I_1 + I_2 + I_3 + 4 = 0 \quad \dots (i)$$

Apply KVL in Bottom mesh L1,

$$8 * I_2 - 12 * I_3 + 12 = 0 \quad \dots (ii)$$

Apply KVL in Right top supermesh L2:

$$-12 * I_3 + 5 * I_1 + 6 + 16 * (16 + I_1) = 0$$


$$12 * I_3 - 21 * I_1 - 262 = 0 \quad \dots (iii)$$

By solving above equation, we get:


$$I_1 = -10.62A$$

$$I_2 = 3.372A$$

$$I_3 = 3.248A$$

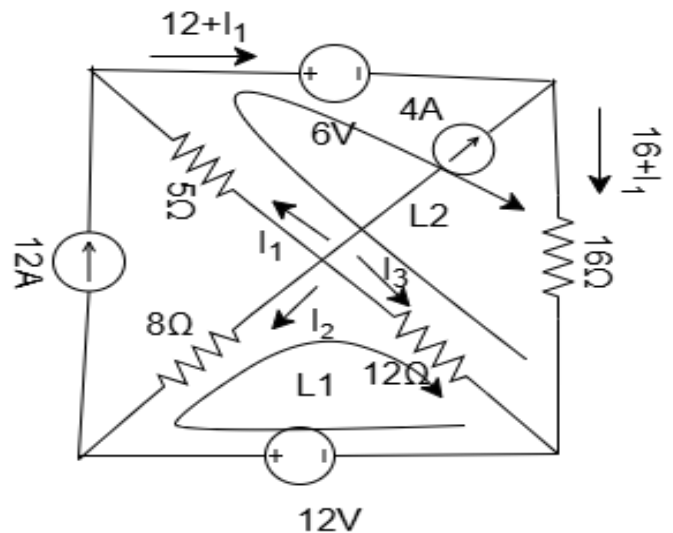

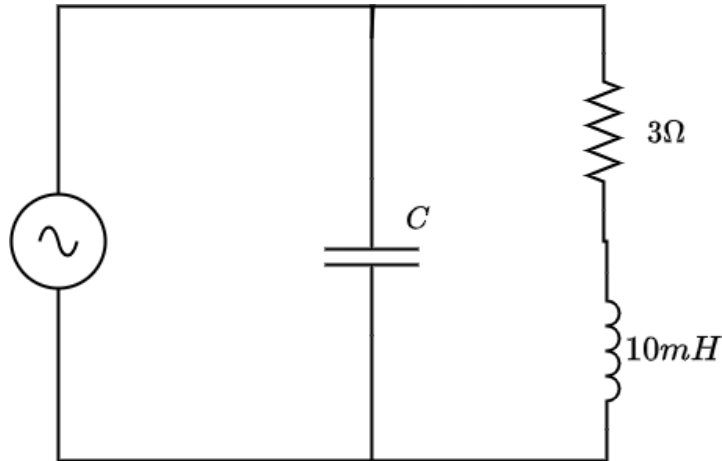Q. 7: A source $\omega = 314 \text{ rad/sec}$ is connected to a load Z_L as shown in the figure. Find the value of the capacitance for the load Z_L to be completely resistive. Z_L is the impedance seen from the source.



Solution:

The equivalent impedance Z_L can be calculated by parallel combination of capacitance and series R-L.

$$Z_L = \left(-\frac{j}{\omega C} \right) \parallel (3 + j\omega L)$$

$$Z_L = \frac{(3 + j\omega L) \left(-\frac{j}{\omega C} \right)}{3 + j\omega L - \left(\frac{j}{\omega C} \right)}$$

$$Z_L = \frac{\left(3 - j \left(\omega L - \left(\frac{1}{\omega C} \right) \right) \right) * \left(\left(\frac{L}{C} \right) - \left(\frac{j3}{\omega C} \right) \right)}{9 + \left(\omega L - \left(\frac{1}{\omega C} \right) \right)^2}$$

$$Z_L = \frac{3 \left(\frac{L}{C} \right) - \left(\omega L - \left(\frac{1}{\omega C} \right) \right) \left(\frac{3}{\omega C} \right) - j \left(\omega L - \left(\frac{1}{\omega C} \right) \right) \left(\frac{L}{C} \right) - j \left(\frac{9}{\omega C} \right)}{9 + \left(\omega L - \left(\frac{1}{\omega C} \right) \right)^2}$$

Z_L is purely resistive if imaginary part of Z_L is zero.

Equate the imaginary part to 0

$$- \left(\omega L - \left(\frac{1}{\omega C} \right) \right) \left(\frac{L}{C} \right) - \left(\frac{9}{\omega C} \right) = 0$$

$$\frac{L}{\omega C^2} = \frac{\omega L^2}{C} + \left(\frac{9}{\omega C} \right)$$

$$L = \omega^2 L^2 C + 9C \Rightarrow C = \frac{L}{\omega^2 L^2 + 9}$$

$$C = 53 \mu F$$