

## Lecture-4

On

# INTRODUCTION TO ELECTRICAL ENGINEERING (ESO203)

- Series and Parallel resistor, capacitor and inductor.
- Voltage division rule.
- Current division rule.
- Mesh analysis.
- Nodal analysis.


## Kirchhoff's Law (cont...)

- Kirchhoff's second law is based on the principle of conservation of energy.
- This law is known as Kirchhoff's voltage law and states that the algebraic sum of all the voltages around a closed loop is zero.

$$\sum_{m=1}^M v_m = 0$$

- Here,  $M$  is the number of voltages in the loop and  $v_m$  is the  $m^{\text{th}}$  voltage.
- Following the above convention and applying KVL in the loop in the figure,

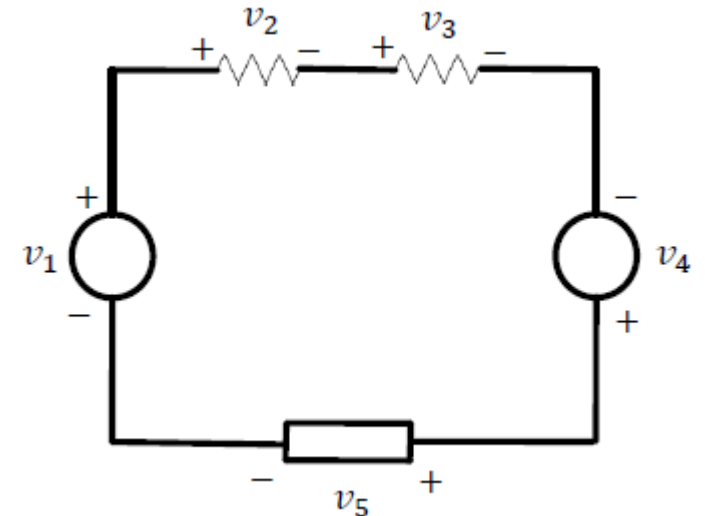
$$\begin{aligned} -v_1 + v_2 + v_3 - v_4 + v_5 &= 0 \\ \Rightarrow v_1 + v_4 &= v_2 + v_3 + v_5 \end{aligned}$$



- This implies that the sum of voltage drops is equal to the sum of voltage rises.
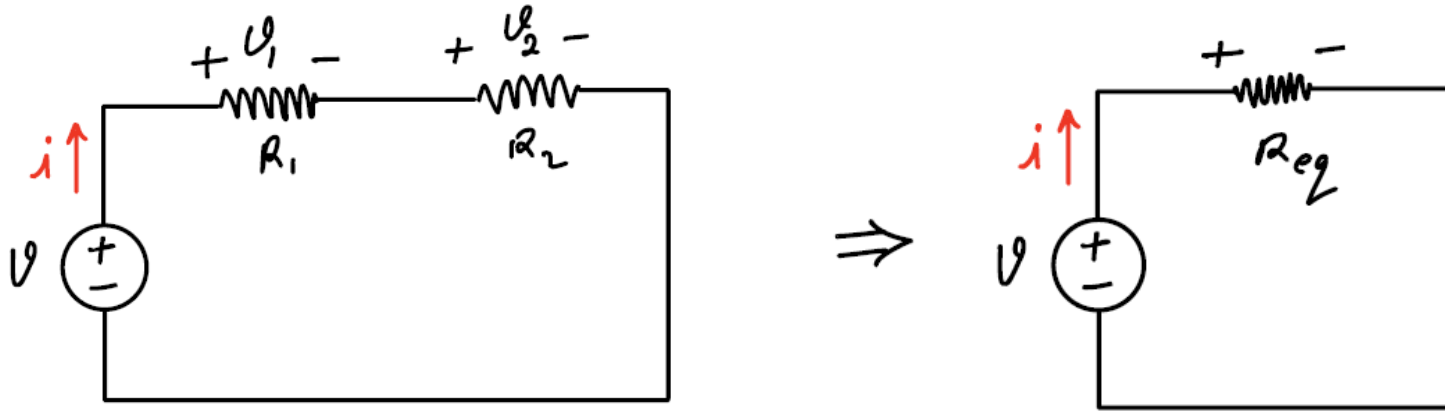
## Series Resistors and Voltage Division

- Consider the circuit below, where two resistors are connected in series as the same current flows through both of them.




- Applying Ohm's law to each resistor, we have  $v_1 = iR_1$  and  $v_2 = iR_2$ .
- Applying KVL to the loop we get,  $v = v_1 + v_2 = i(R_1 + R_2) = iR_{eq}$ .

## Series Resistors and Voltage Division (cont...)

- The equivalent resistance of the circuit is therefore,

$$R_{eq} = R_1 + R_2$$

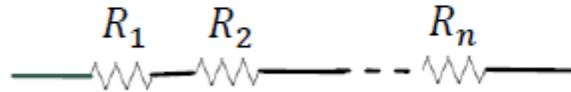- The same can be extended for multiple resistors.
- The equivalent resistance of any number of resistors connected in series is the sum of the individual resistances.



$$R_{eq} = R_1 + R_2 + \cdots + R_n = \sum_{i=1}^n R_i$$


- The voltage is divided among the resistors in direct proportion to their resistances.
- The voltage across resistor  $n$ ,  $v_n$  is given by

$$v_n = \frac{R_n}{R_1 + R_2 + \cdots + R_n} v$$
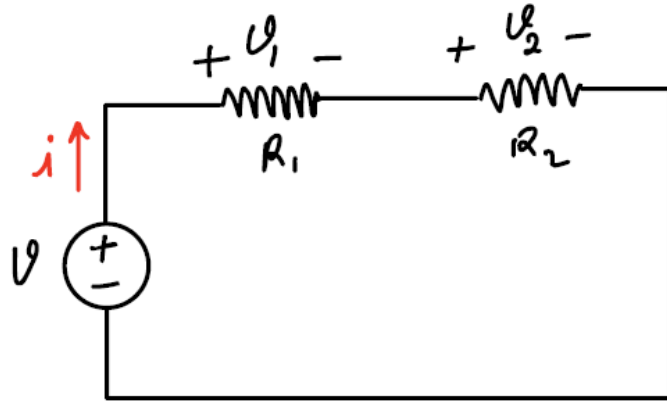
## Series Resistors and Voltage Division (cont...)


- The voltage across resistor  $n$ ,  $v_n$  is given by

$$v_n = \frac{R_n}{R_1 + R_2 + \cdots + R_n} v$$


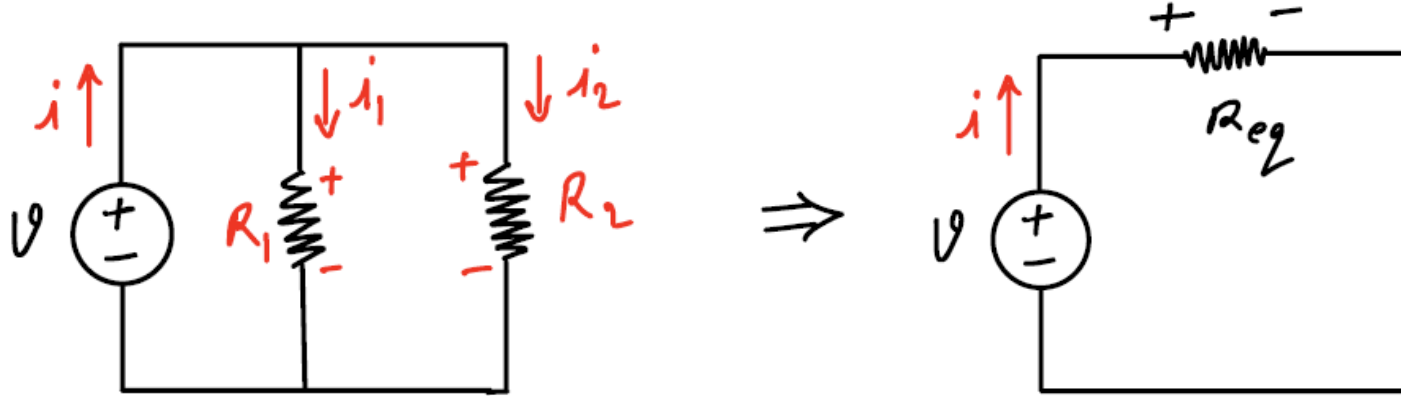
## Parallel Resistors and Current Division

- Consider the circuit below, where two resistors are connected in parallel as they have the same voltage across them.



- Applying Ohm's law to each resistor, we have  $v = i_1 R_1 = i_2 R_2$ .
- Applying KCL at the node we get,

$$i = i_1 + i_2 = \frac{v}{R_1} + \frac{v}{R_2} = v \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{v}{R_{eq}}$$


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

## Parallel Resistors and Current Division (cont...)

- The equivalent resistance of the circuit is therefore,

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

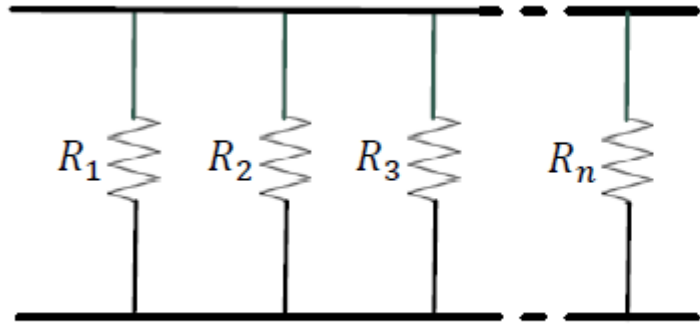- The equivalent resistance of any number of resistors connected in parallel is the reciprocal of the sum of the reciprocal of the individual resistances.




$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \cdots + \frac{1}{R_n} = \sum_{i=1}^n \frac{1}{R_i}$$

- For the circuit given in the previous slide the total current,  $i$  is shared by the resistors in inverse proportion to their resistances. The currents through the resistors are expressed as,

$$i_1 = \frac{iR_2}{R_1 + R_2} \text{ \& } i_2 = \frac{iR_1}{R_1 + R_2}$$
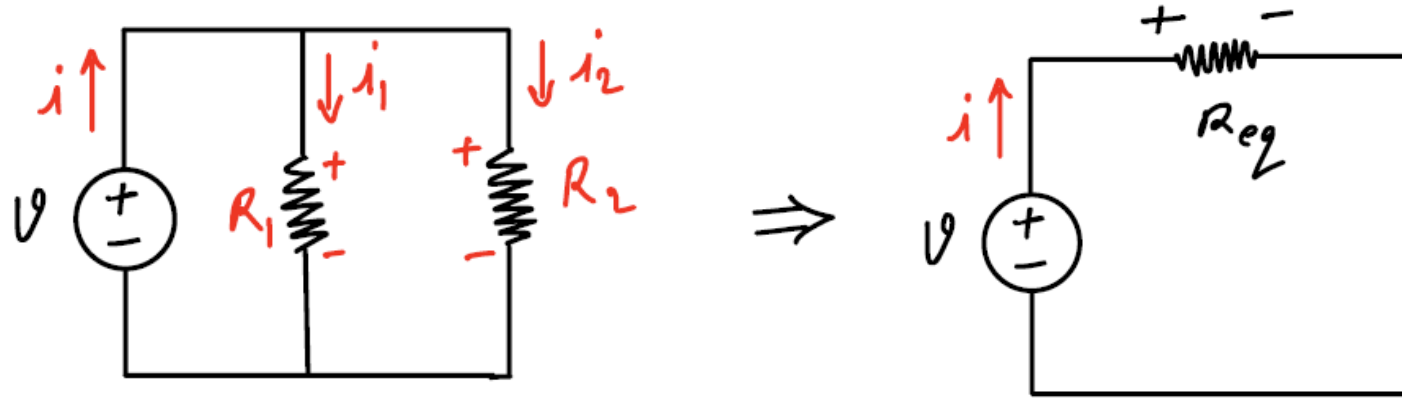
## Parallel Resistors and Current Division (cont...)


- For the circuit given in the previous slide the total current,  $i$  is shared by the resistors in inverse proportion to their resistances. The currents through the resistors are expressed as,




$$i_1 = \frac{iR_2}{R_1 + R_2} \text{ \& } i_2 = \frac{iR_1}{R_1 + R_2}$$




## EXAMPLE

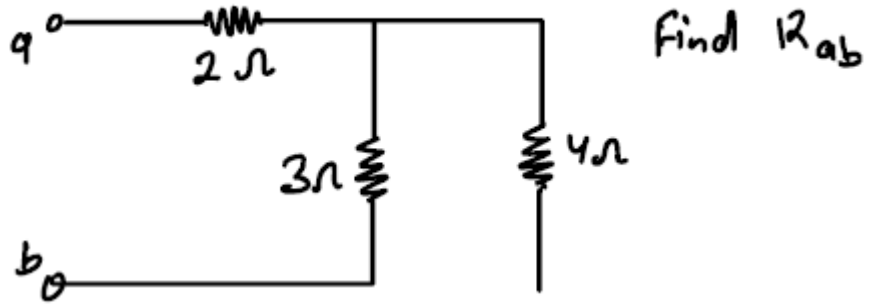

$$R_{ab} = 5\Omega$$

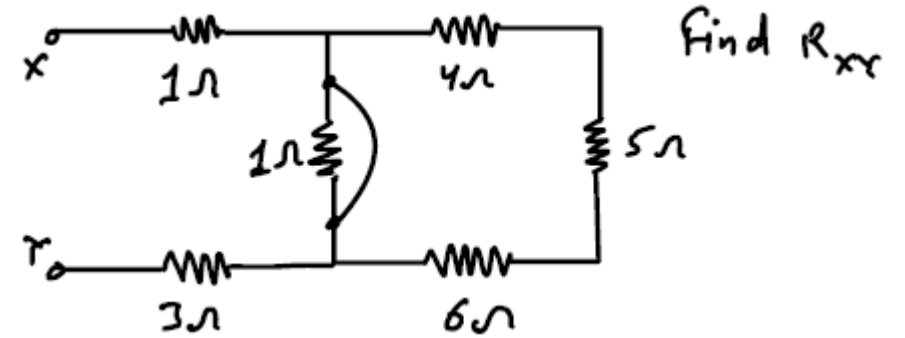

$$R_{xy} = 4\Omega$$

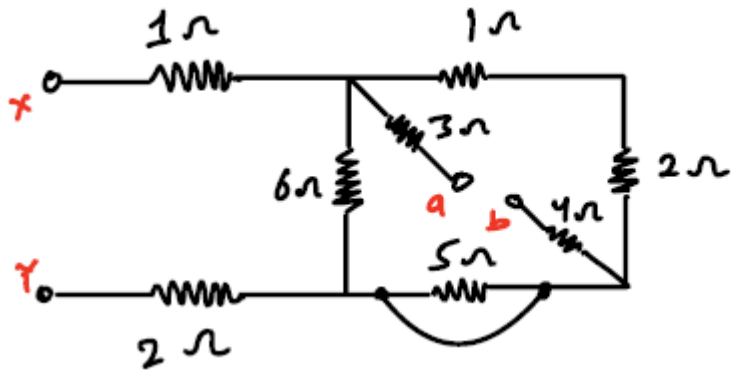

$$R_{xy} = 5\Omega$$

$$R_{ab} = 9\Omega$$

## EXAMPLE (cont...)

- Find  $i_2$  and  $v_2$  in the circuit shown in the figure? Also, calculate the power dissipated in the  $3\Omega$  resistor?

**SOLUTION:** The equivalent resistance for the circuit is


$$R_{eq} = 4 + (6 || 3) = 4 + \frac{6 \times 3}{6 + 3} = 6 \Omega$$

The current  $i$  is equal to,

$$i = \frac{v}{R_{eq}} = \frac{12}{6} = 2 \text{ A}$$

Apply current division rule:
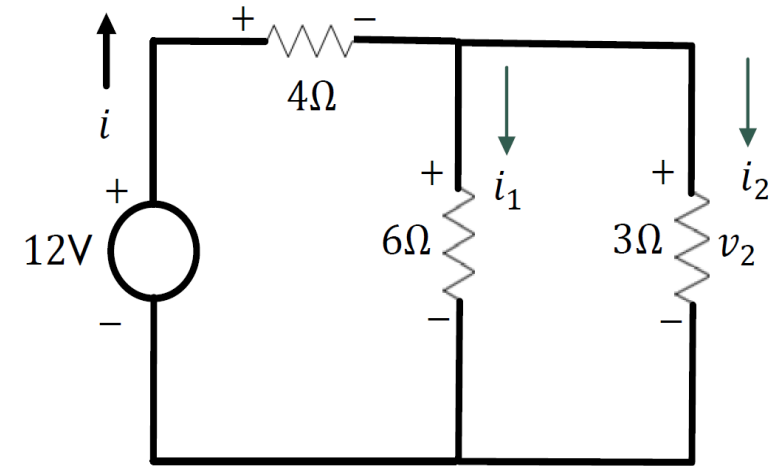
$$i_2 = \frac{i \times 6\Omega}{6\Omega + 3\Omega} = \frac{2 \times 6}{9} = \frac{4}{3} \text{ A}$$



### EXAMPLE (cont...)


$$i_2 = \frac{i \times 6\Omega}{6\Omega + 3\Omega} = \frac{2 \times 6}{9} = \frac{4}{3} \text{ A}$$

Voltage  $v_2$  is calculated as:

$$v_2 = i_2 * 3\Omega = 4\text{V}$$


The power dissipated is given by,
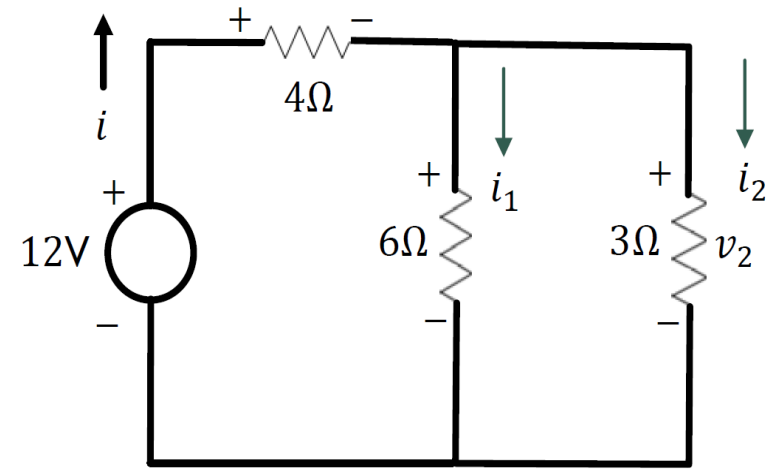
$$P = v_2 i_2 = 4 * \left(\frac{4}{3}\right) = 5.33\text{W}$$


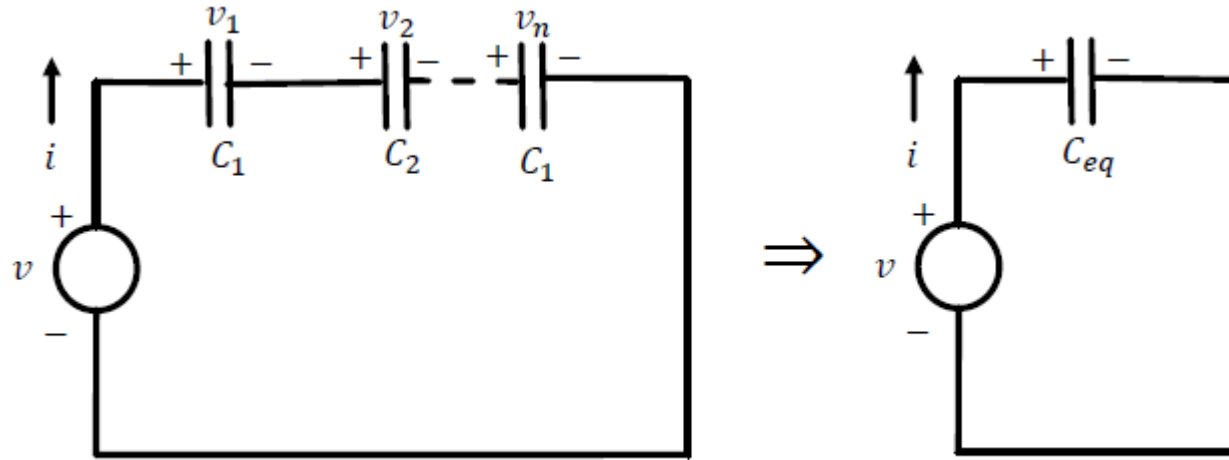
## Series Capacitors

- Consider the circuit below, where  $n$  capacitors are connected in series and its corresponding equivalent circuit



- The capacitors have the same current flowing through them.
- Applying KVL in the loop we get,  $v = v_1 + v_2 + \dots + v_n$ .

## Series Capacitors (cont..)

- But we know that  $v_{k(t)} = \frac{1}{c_k} \int_0^t i dt + v_{k(t_0)}$ . Therefore,

$$\begin{aligned} v &= \frac{1}{C_1} \int_{t_0}^t i dt + v_1(t_0) + \frac{1}{C_2} \int_{t_0}^t i dt + v_2(t_0) + \cdots + \frac{1}{C_n} \int_{t_0}^t i dt + v_n(t_0) \\ &= \left( \frac{1}{C_1} + \frac{1}{C_2} + \cdots + \frac{1}{C_n} \right) \int_{t_0}^t i dt + v_1(t_0) + v_2(t_0) + \cdots + v_n(t_0) = \frac{1}{C_{eq}} \int_{t_0}^t i dt + v(t_0) \end{aligned}$$


Therefore

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \cdots + \frac{1}{C_n} = \sum_{i=1}^n \frac{1}{C_i}$$

- The equivalent capacitance of **n** series-connected capacitors is the reciprocal of the sum of the reciprocal of the individual capacitances.
- We observe that capacitors in series combine in the same manner as resistors in parallel.
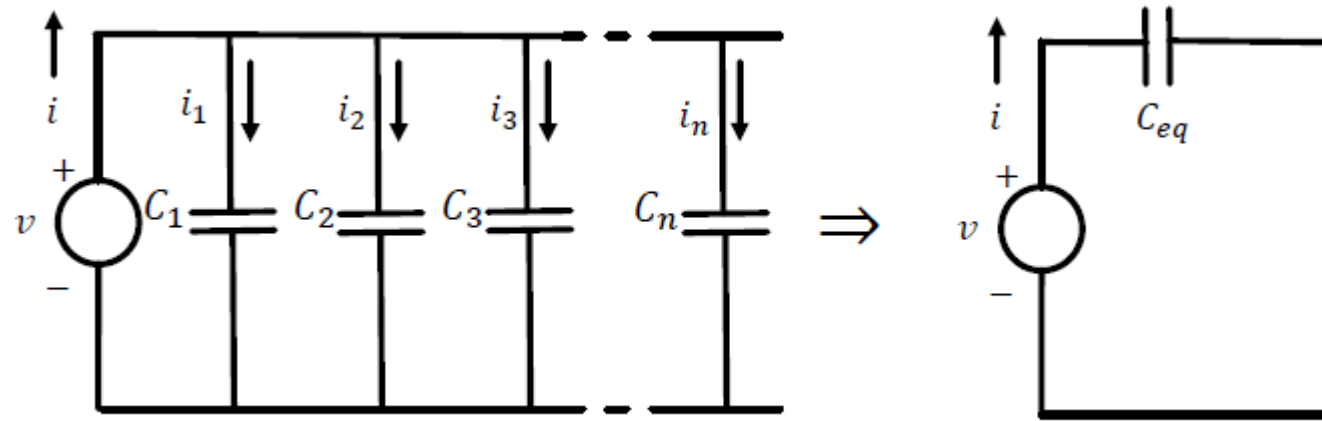
## Parallel Capacitors

- Consider the circuit below, where  $n$  capacitors are connected in parallel.



- The capacitors have the same voltage across them
- Applying KCL at the node we get,  $i = i_1 + i_2 \dots + i_n$ .

## Parallel Capacitors (cont...)

But we know that  $i_k = c_k \frac{dv}{dt}$ . Therefore,

$$\begin{aligned} i &= C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + \cdots + C_n \frac{dv}{dt} \\ &= \sum_{i=1}^n C_i \frac{dv}{dt} = C_{eq} \frac{dv}{dt} \end{aligned}$$


Therefore,

$$C_{eq} = C_1 + C_2 + \cdots + C_n = \sum_{i=1}^n C_i$$

- The equivalent capacitance of  $n$  parallel-connected capacitors is the sum of the individual capacitances.
- We observe that capacitors in parallel combine in the same manner as resistors in series.
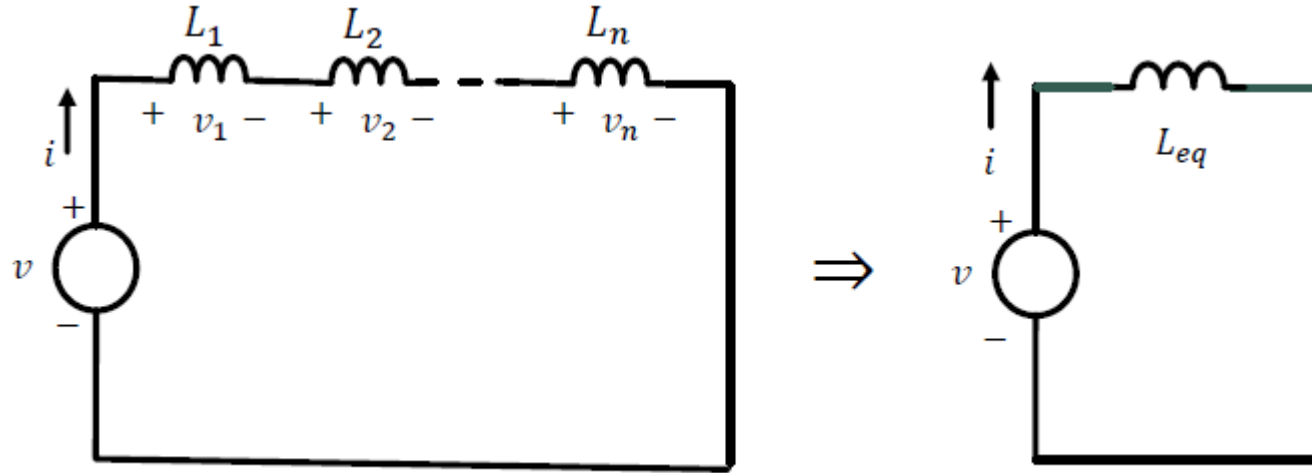
## Series Inductors

- Consider the circuit below, where  $n$  inductors are connected in series and its corresponding equivalent circuit



- The inductors have the same current flowing through them.
- Applying KVL in the loop we get,  $v = v_1 + v_2 + \cdots + v_n$ .



## Series Inductors (cont...)

- But we know that  $v_k = l_k \frac{di}{dt}$ . Therefore,

$$\begin{aligned} v &= L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + \cdots + L_n \frac{di}{dt} \\ &= \sum_{i=1}^n L_i \frac{di}{dt} = L_{eq} \frac{di}{dt} \end{aligned}$$


- Therefore,

$$L_{eq} = L_1 + L_2 + \cdots + L_n = \sum_{i=1}^n L_i$$

- The equivalent inductance of n series-connected inductors is the sum of the individual inductances.
- We observe that inductors in series combine in the same manner as resistors in series.
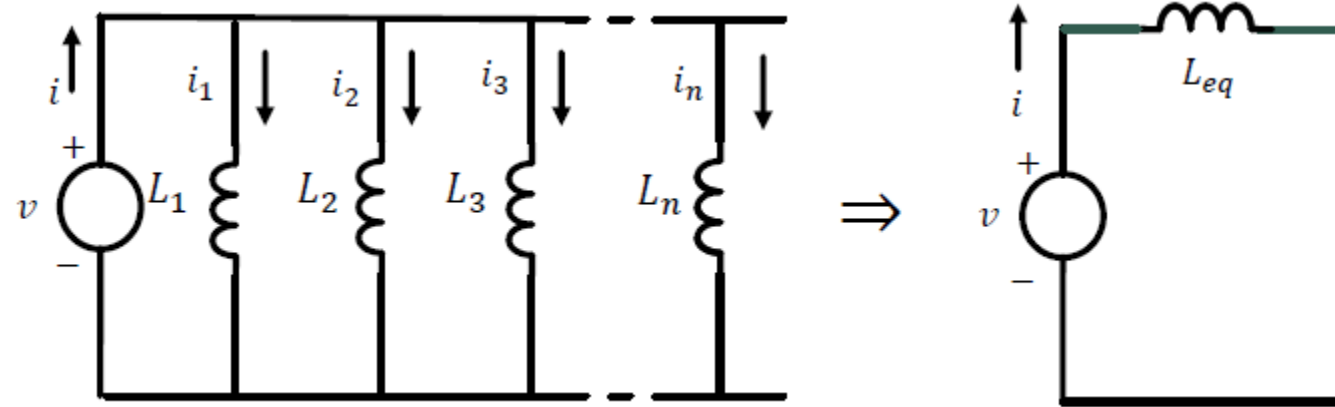
## Parallel Inductors

- Consider the circuit below, where  $n$  inductors are connected in parallel –



- The inductors have the same voltage across them.
- Applying KCL at the node we get,  $i = i_1 + i_2 + \dots + i_n$ .

## Parallel Inductors (cont...)

- But we know that  $i_k = \frac{1}{L_k} \int_{t_0}^t v dt + i_k(t_0)$  . Therefore,


$$\begin{aligned} i &= \frac{1}{L_1} \int_{t_0}^t v dt + i_1(t_0) + \frac{1}{L_2} \int_{t_0}^t v dt + i_2(t_0) + \cdots + \frac{1}{L_n} \int_{t_0}^t v dt + i_n(t_0) \\ &= \left( \frac{1}{L_1} + \frac{1}{L_2} + \cdots + \frac{1}{L_n} \right) \int_{t_0}^t v dt + i_1(t_0) + i_2(t_0) + \cdots + i_n(t_0) = \frac{1}{L_{eq}} \int_{t_0}^t v dt + i(t_0) \end{aligned}$$

- Therefore,


$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \cdots + \frac{1}{L_n} = \sum_{i=1}^n \frac{1}{L_i}$$

- The equivalent inductance of n parallel-connected inductors is the reciprocal of the sum of the reciprocal of the individual inductances.
- We observe that inductors in parallel combine in the same manner as resistors in parallel.


## EXAMPLE

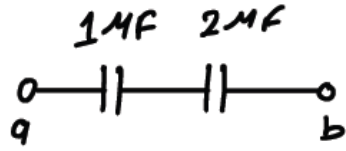

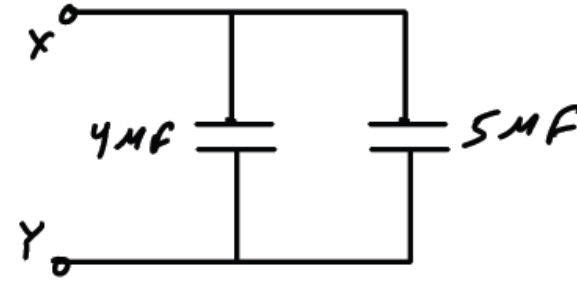
$$\frac{1}{C_{ab}} = \frac{1}{1 \times 10^{-6}} + \frac{1}{2 \times 10^{-6}}$$


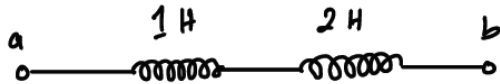
$$C_{ab} = 4 \times 10^{-6} + 5 \times 10^{-6}$$



$$L_{ab} = 1 + 2$$

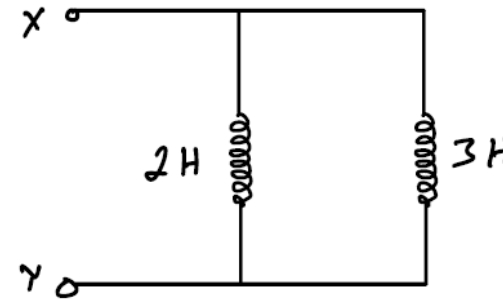


$$\frac{1}{L_{ab}} = \frac{1}{2} + \frac{1}{3}$$

## Methods of Analysis

- Mesh Analysis = KVL + OHM's.
- Nodal Analysis = KCL + OHM's.

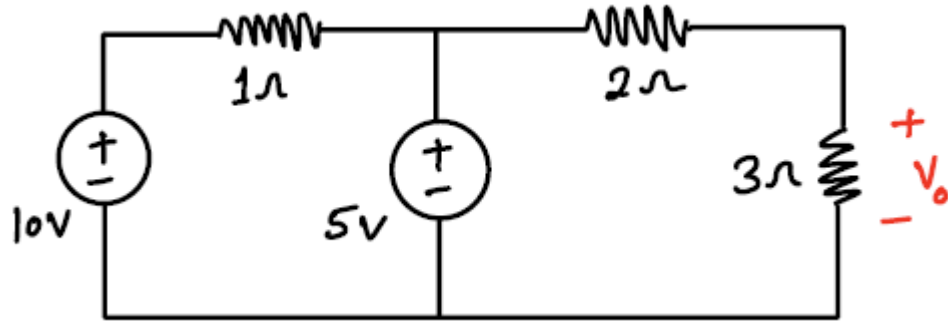Q1: Using mesh analysis find the value of  $v_o$ ?



Mesh-1:

$$-10 + i_1 + 5 = 0$$

$$i_1 = 5 \text{ A}$$

Mesh-2:

$$-5 + 2i_2 + 3i_2 = 0$$


$$i_2 = 1 \text{ A}$$

$$v_o = 3i_2 = 3 \times 1 = 3 \text{ V}$$

## Methods of Analysis (cont...)

- Mesh Analysis = KVL + OHM's.
- Nodal Analysis = KCL + OHM's.

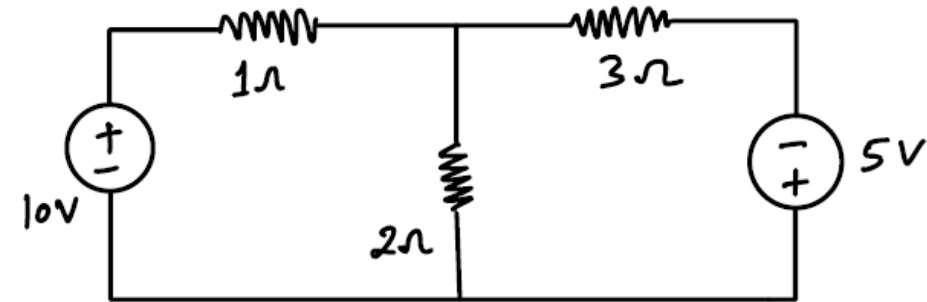Q1: Using mesh analysis find the value of  $v_o$ ?



Mesh-1:

$$-10 + i_1 + 2(i_1 - i_2) = 0$$

$$3i_1 - 2i_2 = 10$$



Mesh-2:

$$2(i_2 - i_1) + 3i_2 - 5 = 0$$

$$-2i_1 + 5i_2 = 5$$
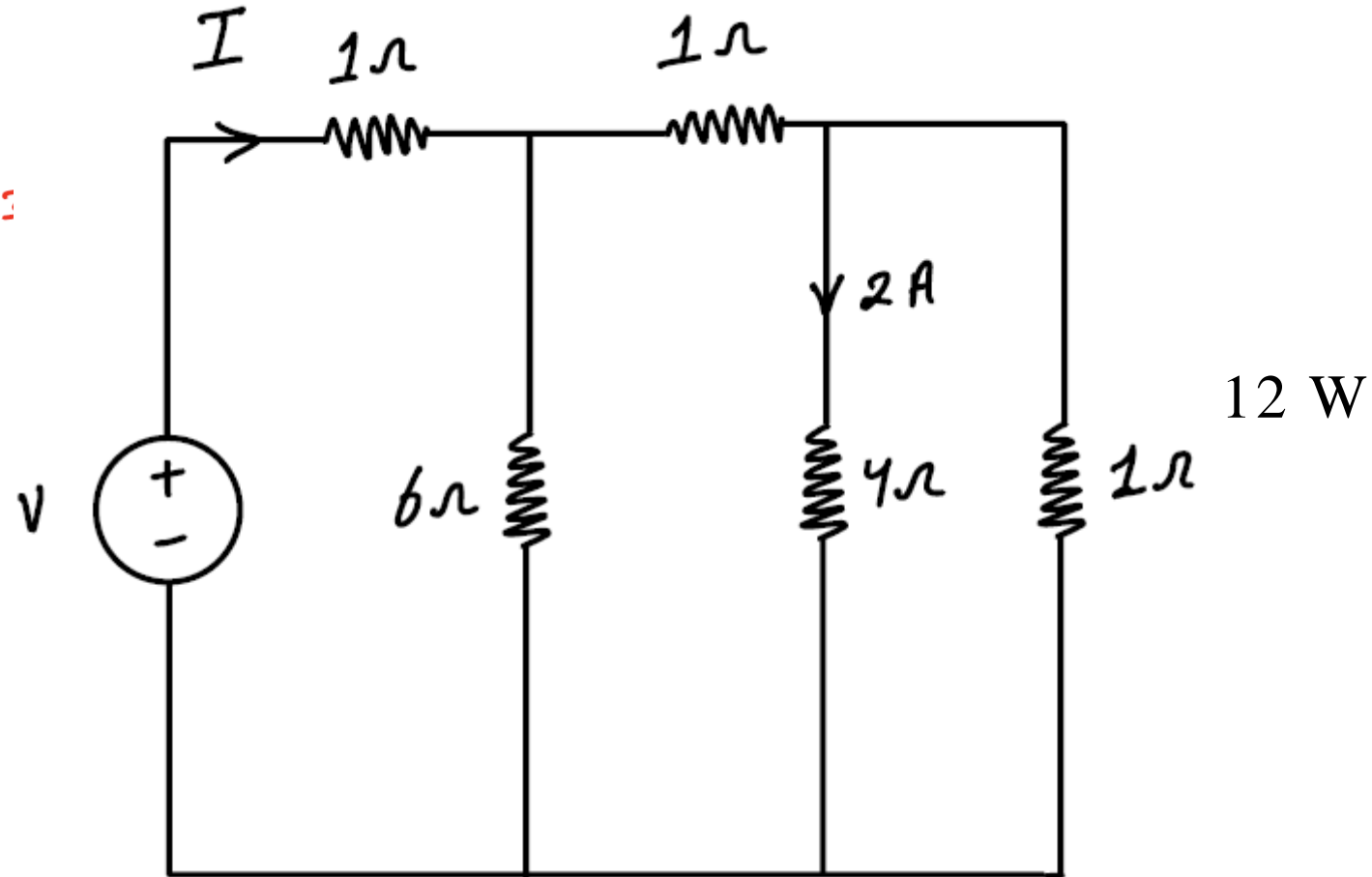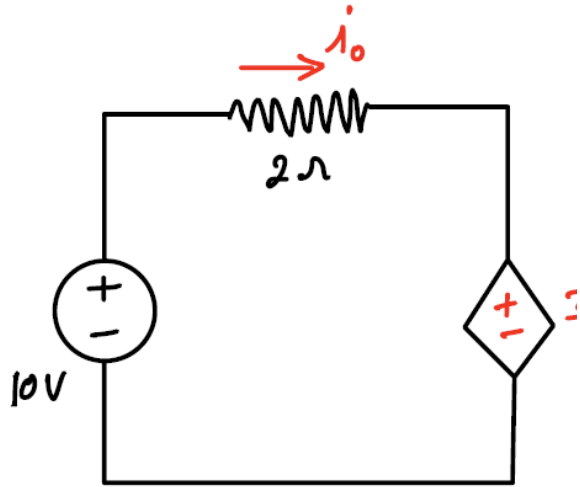
## EXAMPLE

- Find power delivered by dependent source?



## EXAMPLE

- Find the value of  $V$  and  $I$ , if current through  $4\Omega$  resistor is  $2A$ .

