


➤ $I_{S1}-I_{S2}$ typically 10 times or more than $I_{S3}-I_{S4}$


⇒ $I_{standby} \geq 10I_Q$

⇒ Adds to the power
overhead of the circuit

➤ Another option of
prebias circuit:

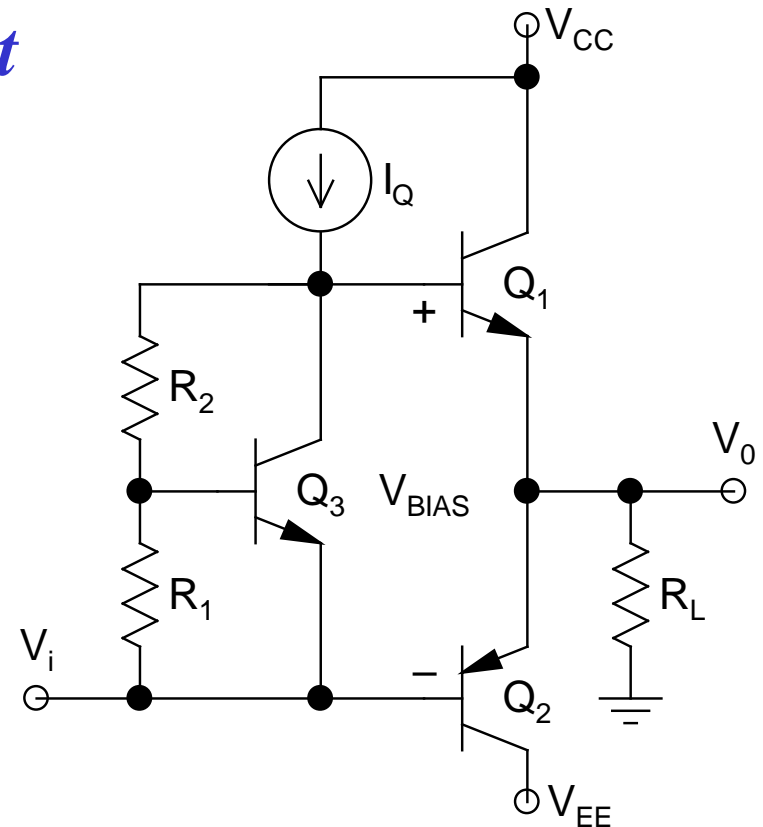- V_{BE} -Multiplier
- $V_{BIAS} = V_{BE3}(1 + R_2/R_1)$
- Values of R_1 and R_2
chosen to give
 $V_{BIAS} = 2V_\gamma$



 

The Voltage Transfer Characteristic (VTC)


- *The VTC does not pass through origin*
- *Intercepts* (known as *input-output offset*):
 - $V_i = 0, V_o = V_{BE3} + V_{BE4} - V_{BE1}$
 - $V_o = 0, V_i = -V_{EB2}$
- *For $V_i > -V_{EB2}$, $V_{be1} \uparrow$ and $V_{eb2} \downarrow$, with their sum remaining constant at V_{BIAS}*
 - \Rightarrow *Q_1 starts to conduct and supply current to the load (R_L), while Q_2 starts to go deeper into cutoff*
 - \Rightarrow *V_o starts to follow V_i with a slope ~ 1 (CC stage)*

- *V_o can rise all the way up to $[V_{CC} - V_{CE1}(HS)]$, provided that V_i can drive it that far*
- Similarly, *for $V_i < -V_{EB2}$, $V_{eb2} \uparrow$ and $V_{be1} \downarrow$, with their sum again remaining constant at V_{BIAS}*
 - \Rightarrow *Q_2 starts to conduct and pull current away from the load (R_L), while Q_1 starts to go deeper into cutoff*
 - \Rightarrow *V_o again starts to follow V_i with a slope ~ 1 , and can go down all the way to $[V_{EE} + V_{EC2}(HS)]$*

➤ *Power Output and Efficiency:*

- Refer to the figure in the next slide
 - ❖ *The constant offset of $|V_{EB2}|$ is neglected*
- *Both transistors are not ON over the entire cycle*
 - ❖ *Q_1 takes care of the positive half cycle*
 - ❖ *Q_2 takes care of the negative half cycle*
- V_{oM} : *Maximum value of V_o*
 - ❖ *Maximum possible swing between $[V_{CC} - V_{CE1}(HS)]$ and $[V_{EE} + V_{EC2}(HS)]$*
- I_{oM} : *Maximum value of load current* ($= V_{oM}/R_L$)
- *Average rms power P_L delivered to load:*
 
$$P_L = \frac{V_{oM}}{\sqrt{2}} \times \frac{I_{oM}}{\sqrt{2}} = \frac{V_{oM}^2}{2R_L}$$



- Now, we need to calculate the *power supplied to the stage by the power supplies*
- The *average current I_{supply} drawn by Q_1 from V_{CC} (happens only during the positive half cycle)*:

$$I_{supply} = \frac{1}{T} \int_0^T I_{c1}(t) dt = \frac{1}{2\pi} \int_0^\pi I_{oM} \sin \theta d\theta = \frac{I_{oM}}{\pi} = \frac{V_{oM}}{\pi R_L}$$

- *The same current will also be pushed by Q_2 to V_{EE} ($= -V_{CC}$) during the negative half cycle*
- *Thus, over a complete cycle, the average supply power P_{supply} drawn from the power supplies:*

$$P_{supply} = 2V_{CC} I_{supply} = 2V_{CC} V_{oM} / (\pi R_L)$$

- Thus, the *power conversion efficiency* (η):

$$\eta = \frac{P_L}{P_{\text{supply}}} = \frac{V_{oM}^2 / (2R_L)}{2V_{CC} V_{oM} / (\pi R_L)} = \frac{\pi V_{oM}}{4V_{CC}}$$

- η directly proportional to V_{oM} , and independent of R_L

\Rightarrow *Significant advantage*

- Also, $V_{oM}(\text{max}) \approx V_{CC}$

$\Rightarrow \eta_{\text{max}} = \pi/4 = 0.785$ (or 78.5%)


- *This value may not be attainable in practice*

❖ For $V_{oM} = -V_{CC}$, V_i has to be less than $-V_{CC}$, which *may not be practically achievable*

❖ This analysis *neglects the standby power* (quite small *though*) \Rightarrow *Inclusion of this term will reduce η_{max}*

➤ *Transistor Ratings:*

- Specified by *two parameters*:
 - ❖ *Breakdown Voltage*
 - ❖ *Maximum Power Rating*
- *Breakdown Voltage*:
 - ❖ *Maximum positive/negative V_{CE} that can be applied to an npn/pnp BJT*
 - Known as the *Collector-to-Emitter Breakdown Voltage with Base Open* (BV_{CE0})
 - ❖ *Focus on Q_1 (Q_2 will be similar)*
 - ❖ Refer to the diagram in the next slide (*Output characteristic of Q_1 along with the load line*)
 - ❖ In the analysis, the *offset in the VTC*, the *small standby current*, and $V_{CE1}(HS)$ are *neglected*

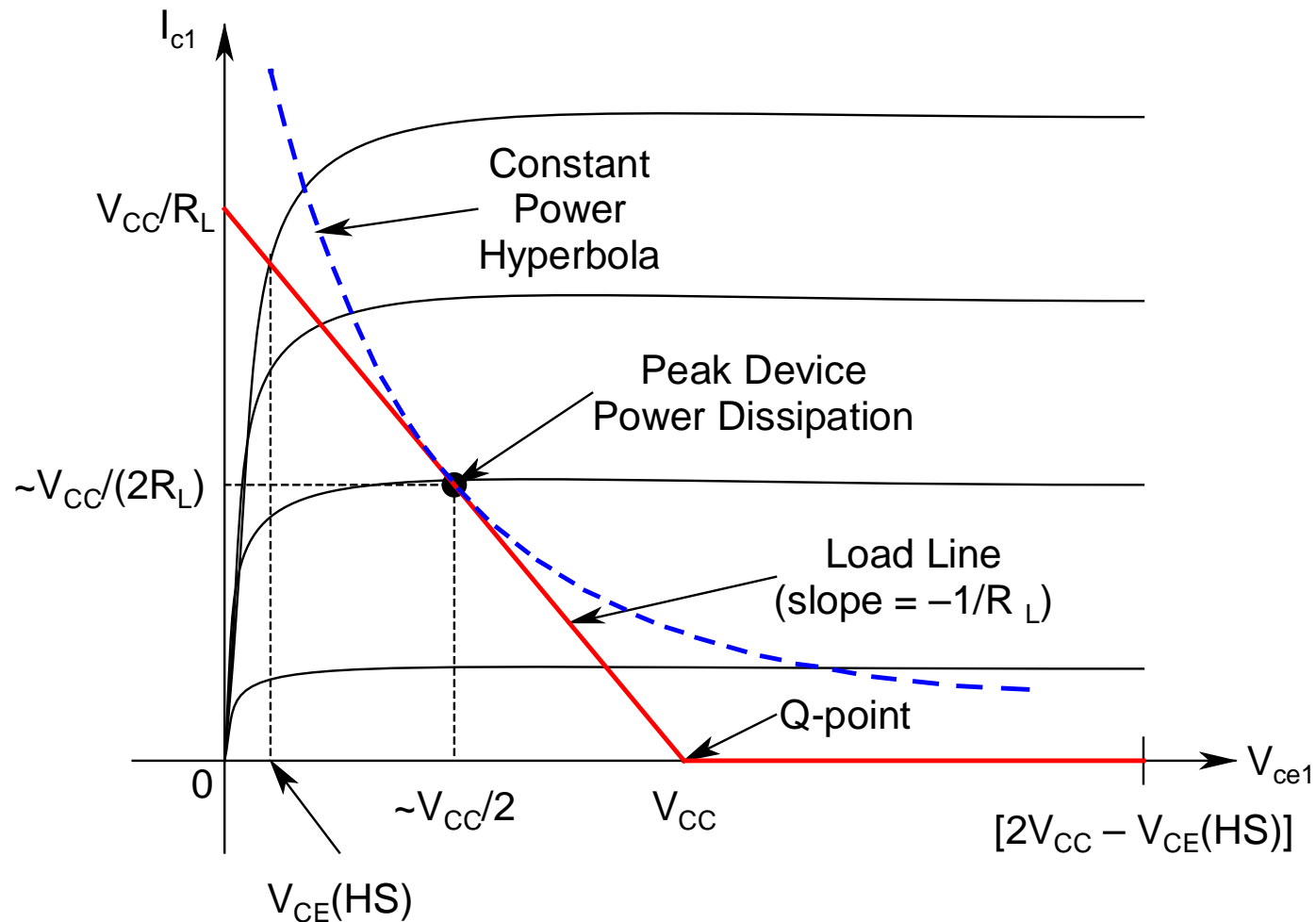

The Output Characteristics of Q_1 along with the Load Line

- ❖ *At Q-point: $V_o = 0 \Rightarrow V_{ce1} = V_{CC}$*
- ❖ *During positive half cycle:*
 - $V_o(max) \approx V_{CC} \Rightarrow V_{ce1} \approx 0$
 - $\Rightarrow V_{ce1}$ *ranges between 0 and V_{CC} during the positive half cycle*
- ❖ The *slope of the load line* in this part of the characteristic = $-1/R_L$
- ❖ *For negative half cycle, Q_1 cuts off (Q_2 conducts during this period)*
 - $\Rightarrow I_{c1} = 0$ *for V_o ranging between 0 and $-V_{CC}$*
 - $\Rightarrow V_{ce1}(max) = 2V_{CC}$
 - $\Rightarrow BV_{CE0} = 4V_{CC}$ [using a *Safety Factor* (or *Factor of Safety*) of 2] (*same for Q_2*)

■ **Maximum Power Rating:**

❖ *Same for both Q_1 and Q_2*

❖ *Average power P_L delivered by Q_1 to R_L during the positive half cycle = area covered under the load line*

$$\Rightarrow P_L = \frac{1}{2} \times V_{CC} \times \frac{V_{CC}}{R_L} = \frac{V_{CC}^2}{2R_L}$$

❖ Refer to the *constant power hyperbola* ($V_{ce1} \times I_{c1}$) shown in the figure

❖ *Maximum power dissipation of Q_1 happens when this hyperbola becomes tangent to the load line, which is right at the middle of the load line*

❖ *Proof:*

Constant power hyperbola (P_1):

$$P_1 = V_{ce1} \times I_{c1} = (V_{CC} - I_{c1} R_L) \times I_{c1} = V_{CC} I_{c1} - I_{c1}^2 R_L$$

Plug $dP_1/dI_{c1} = 0$ to get $I_{c1} = V_{CC}/(2R_L)$

This is the *mid-point of the load line*, with *coordinates* $[V_{CC}/2, V_{CC}/(2R_L)]$

$$\Rightarrow P_{\max} = \frac{V_{CC}^2}{2R_L} \text{ (using a Safety Factor of 2)}$$

❖ There is also *idling power*:

$$P_{\text{idling}} = 2V_{CC}I_{\text{standby}} + (V_{CC} - V_I)I_Q$$


❖ In general, $P_{\max} \gg P_{\text{idling}}$

❖ Refer to the figure in the next slide

o V_{ce1} *oscillates between 0 and $2V_{CC}$*

o I_{c1} *appears only during the positive half cycle, with peak value of V_{CC}/R_L (when $V_{ce1} = 0$)*

 o $P_1 (= V_{ce1} \times I_{c1})$ *oscillates* between 0 and $V_{CC}^2/(4R_L)$ at *twice the frequency* only during the *positive half cycle*



❖ *Two Special Cases:*

- $R_L \rightarrow \infty$ (*open-circuit*):

Load line becomes horizontal with $I_{c1} = 0$

$\Rightarrow P_1 = 0 \Rightarrow$ *no issue*

- $R_L = 0$ (*short-circuit*):

Load line becomes vertical with $I_{c1} \rightarrow \infty$

Potentially dangerous situation

Resulting power dissipation and consequent heat generation can completely damage the device

❖ *In actual situation, I_{c1} won't reach infinite value due to:*

- *Limited current driving capability of the driver stage*
- *Fall of β at high current levels due to High-Level Injection or Kirk Effect*

❖ These two are *in-built self-protection mechanisms*

❖ Nevertheless, *practical output stages need short-circuit protection*

➤ *Linearity and Output Resistance:*

- *While supplying/sinking current to/from load, Q_1/Q_2 operate in CC mode*
$$\Rightarrow A_v = R_L / (R_L + r_{Ei}) \quad (i = 1, 2) \quad (r_{Ei} = V_T / I_{ci})$$
- Thus, if $R_L \gg r_{Ei}$, then $A_v \rightarrow 1$, and *very high linearity in the VTC can be achieved*
- However, r_{Ei} *is not constant* - rather *it changes with the load current*
- Thus, A_v *can depart significantly from unity*, when the *load current is very small* (*large r_{Ei}*)
- Referring to the *VTC*, the *slope of the characteristic near $\pm V_\gamma$* will be *significantly less than unity*