

Lecture-17

On


INTRODUCTION TO ELECTRICAL ENGINEERING (ESO203)

- Circuit Analysis using Laplace Transform.
- Transfer Function.
- Network Stability.

Circuit Analysis using Laplace Transform (Cont...)

□ Example:

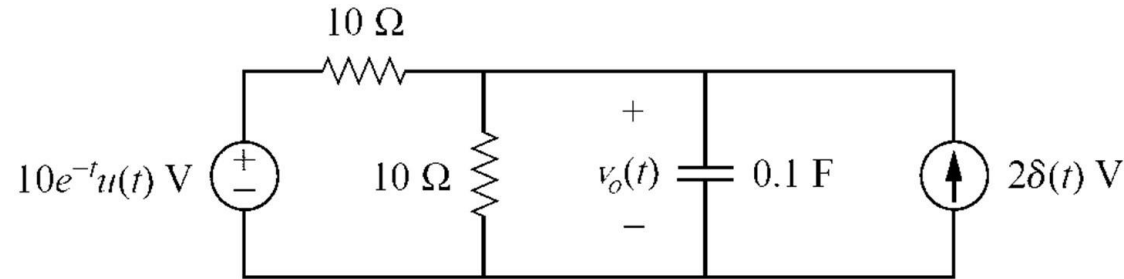
Find $v_o(t)$ in the circuit. Assume $v_o(0) = 5 \text{ V}$



Solution:


We transform the circuit to the s domain as shown in the Figure in next slide. The initial condition is included in the form of the current source

$$Cv_0(0) = 0.1(5) = 0.5 \text{ A}$$

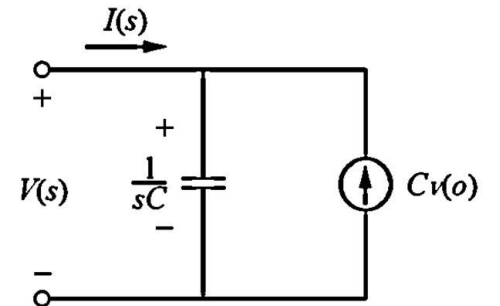

Circuit Analysis using Laplace Transform (Cont...)

Solution:

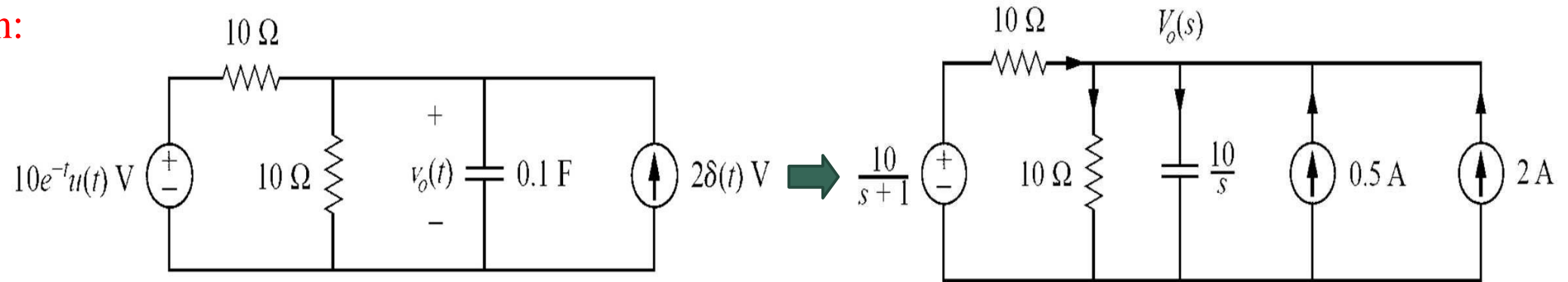

Apply nodal analysis. At the top node,

$$\frac{10/(s+1) - V_o}{10} + 2 + 0.5 = \frac{V_o}{10} + \frac{V_o}{10/s}$$

Multiplying through by 10,

$$\frac{10}{s+1} + 25 = V_o(s+2) \quad \text{or}$$

$$V_o = \frac{25s + 35}{(s+1)(s+2)} = \frac{A}{s+1} + \frac{B}{s+2}$$

Circuit Analysis using Laplace Transform (Cont...)

Solution:


On solving, we get $A = 10, B = 15$

Thus,

$$V_0(s) = \frac{10}{s+1} + \frac{15}{s+2}$$

Taking the inverse Laplace transform, we obtain

$$v_0(t) = (10e^{-t} + 15e^{-2t})u(t)$$

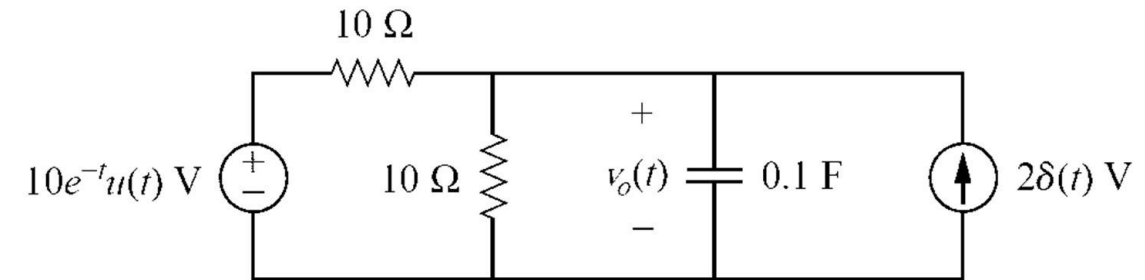

Transfer Function

- The *transfer function* is a key concept in signal processing because it indicates how a signal is processed as it passes through a network.
- It is a fitting tool for finding the network response, determining (or designing for) network stability, and network synthesis.
- The transfer function of a network describes how the output behaves in respect to the input.
- It specifies the transfer from the input to the output in the s domain, assuming no initial energy.

Transfer Function (Cont...)

The **transfer function** $H(s)$ is the ratio of the output response $Y(s)$ to the input excitation $X(s)$, assuming all initial conditions are zero. Thus,

$$H(s) = \frac{Y(s)}{X(s)}$$

- The transfer function depends on what we define as input and output.
- Since the input and output can be either current or voltage at any place in the circuit, there are four possible transfer functions:

$$H(S) = \text{Voltage Gain} = \frac{V_o(s)}{V_i(s)}$$

$$H(S) = \text{Current Gain} = \frac{I_o(s)}{I_i(s)}$$

$$H(s) = \text{Impedance} = \frac{V(s)}{I(s)}$$

$$H(s) = \text{Admittance} = \frac{I(s)}{V(s)}$$

Transfer Function (Cont...)

- A circuit can have many transfer functions.
- Note that $H(s)$ is dimensionless for first two transfer functions.
- In the transfer function equations, we assume that $X(s)$ and $Y(s)$ are known.
- Sometimes we know only $X(s)$ and $H(s)$.
- In that case $Y(s)$ can be found as:- $Y(s) = H(s)X(s)$.

Transfer Function (Cont...)

- We take inverse Laplace transform of $Y(s)$ to get the $y(t)$
- As a special case, *when* $x(t) = \delta(t)$, then $X(s) = 1$
- In that case, $Y(s) = H(s)$, and hence, $y(t) = h(t)$
- Therefore,

$$h(t) = \mathcal{L}^{-1}[H(s)],$$

represents unit impulse response of the circuit.

Transfer Function (Cont...)

The set of transfer functions shown in previous slide can be found in two ways.

- One way is to assume any convenient input $X(s)$, use any circuit analysis technique (such as current or voltage division, nodal or mesh analysis) to find the output $Y(s)$, and then obtain the ratio of the two.
- The other approach is to apply the *ladder method*, which involves walking through the circuit.
- By this approach, we assume that the output is 1 V , or 1 A as appropriate, and use the basic laws of Ohm and Kirchhoff (KCL only) to obtain the input.
- The transfer function becomes unity divided by the input.

Transfer Function (Cont...)

- This approach may be more convenient to use when the circuit has many loops or nodes and applying nodal or mesh analysis becomes cumbersome.
- In the first method, assume an input and find the output; in the second method, assume the output and find the input.
- In both methods, calculate $H(s)$ as the ratio of output to input transforms. The two methods rely on the linearity property.

Transfer Function (Cont...)

□ Example:

The output of a linear system is $\mathbf{y(t) = 10e^{-t} \cos 4t u(t)}$ when the input is $\mathbf{x(t) = e^{-t} u(t)}$. Find the transfer function of the system and its impulse response.

Solution:

$$y(t) = 10e^{-t} \cos 4t u(t) \quad \text{and} \quad x(t) = e^{-t} u(t), \quad \text{then --}$$

$$X(s) = \frac{1}{s+1} \quad \text{and} \quad Y(s) = \frac{10(s+1)}{(s+1)^2 + 4^2}$$

$$\text{Hence, } H(s) = \frac{Y(s)}{X(s)} = \frac{10(s+1)^2}{(s+1)^2 + 1} = \frac{10(s^2 + 2s + 1)}{s^2 + 2s + 17}$$

Transfer Function (Cont...)

□ Solution:

To find $h(t)$ we write $H(s)$ as –


$$H(S) = 10 - 40 \frac{4}{(s + 1)^2 + 4^2}$$

$$\text{So,} \quad h(t) = 10\delta(t) - 40e^{-t} \sin 4t u(t)$$

Transfer Function (Cont...)

□ Example:

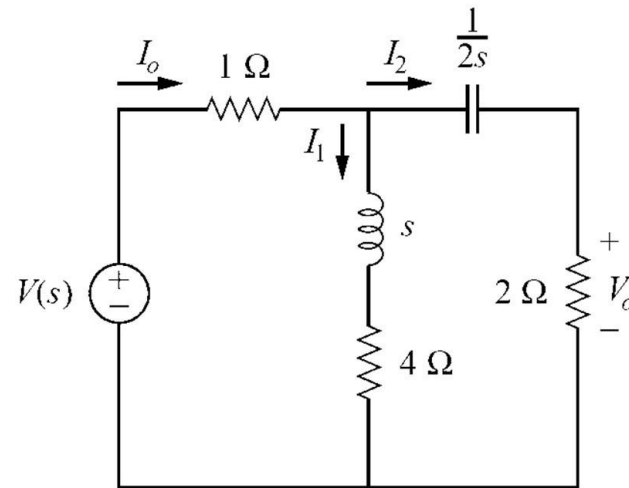Determine the transfer function $H(S) = V_o(s)/I_o(s)$ of the circuit



Transfer Function (Cont...)


□ Solution:

METHOD 1: By Current Division

$$I_2 = \frac{(s + 4)I_0}{s + 4 + 2 + 1/2s}$$

But, $V_0 = 2I_2 = \frac{2(s + 4)I_0}{s + 6 + 1/2s}$

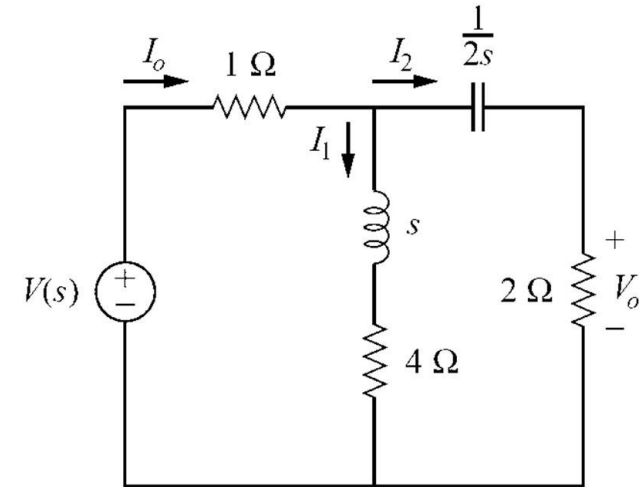Hence, $H(s) = \frac{V_0(s)}{I_0(s)} = \frac{4s(s + 4)}{2s^2 + 12s + 1}$



Transfer Function (Cont...)

□ Solution:

Method 2: We can apply the ladder method. We let $V_o = 1\text{ V}$.

By Ohm's law, $I_2 = V_o/2 = 1/2\text{ A}$. The voltage across the $(2 + 1/2s)$ impedance is

$$V_1 = I_2 \left(2 + \frac{1}{2s} \right) = 1 + \frac{1}{4s} = \frac{4s + 1}{4s}$$

This is the same as the voltage across the $(s + 4)$ impedance. Hence,

$$I_1 = \frac{V_1}{s + 4} = \frac{4s + 1}{4s(s + 4)}$$


Applying KCL at the top node yields

$$I_0 = I_1 + I_2 = \frac{4s+1}{4s(s+4)} + \frac{1}{2} = \frac{2s^2+12s+1}{4s(s+4)}$$

Hence

$$H(s) = \frac{V_o}{I_0} = \frac{4s(s + 4)}{2s^2 + 12s + 1}$$

As before.

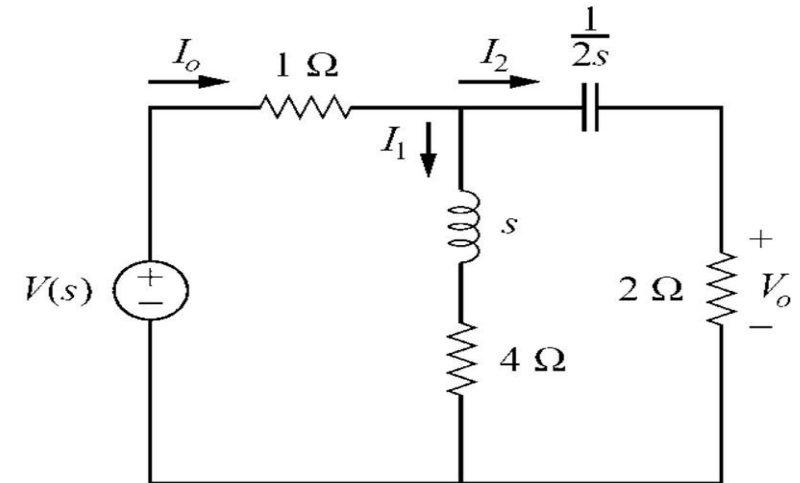

Network Stability

A circuit is *stable* if its impulse response $h(t)$ is bounded (i.e., $h(t)$ converges to a finite value) as $t \rightarrow \infty$; it is *unstable* if $h(t)$ grows without bound as $t \rightarrow \infty$. In mathematical terms, a circuit is stable when

$$\lim_{t \rightarrow \infty} |h(t)| = \text{finite}$$

Since the transfer function $H(s)$ is the Laplace transform of the impulse response $h(t)$,


$H(s)$ must meet certain requirements in order for above Equation to hold. As we know that

$H(s)$ may be written as:-

$$H(s) = \frac{N(s)}{D(s)}$$

Network Stability (Cont...)

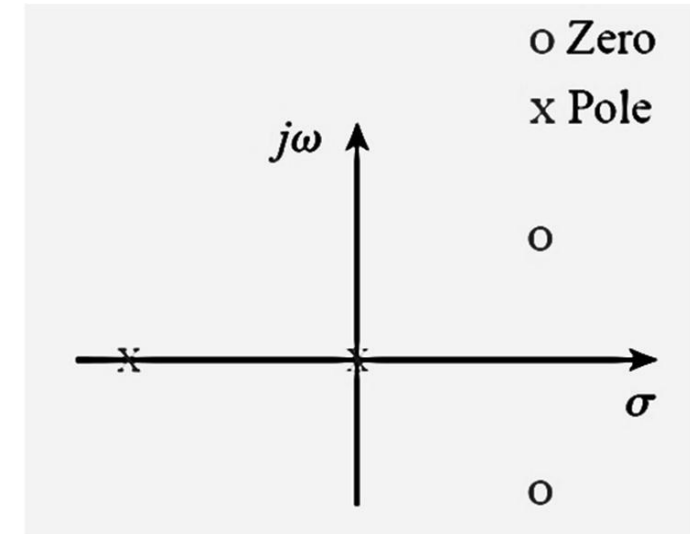- where the roots of $N(s) = 0$ are called the *zeros* of $H(s)$ because they make $H(s) = 0$,
- while the roots of $D(s) = 0$ are called the *poles* of $H(s)$ since they cause $H(s) \rightarrow \infty$.
- The *zeros* and *poles* of $H(s)$ are often located in the s plane as shown in Figure.



$H(s)$ can also be written in terms of its poles as

$$H(s) = \frac{N(s)}{D(s)} = \frac{N(s)}{(s + p_1)(s + p_2) \dots (s + p_n)}$$

Network Stability (Cont...)

$H(s)$ must meet two requirements for the circuit to be stable.


1. **The degree of $N(s)$ must be less than the degree of $D(s)$; otherwise,** long division would produce

$$H(s) = k_n s^n + k_{n-1} s^{n-1} + \dots + k_1 s + k_0 + \frac{R(s)}{D(s)}$$

where $R(s)$ is remainder of the long division. The degree of $R(s)$ is less than the degree of $D(s)$.

The inverse of $H(s)$ in this case does not meet the stability condition .

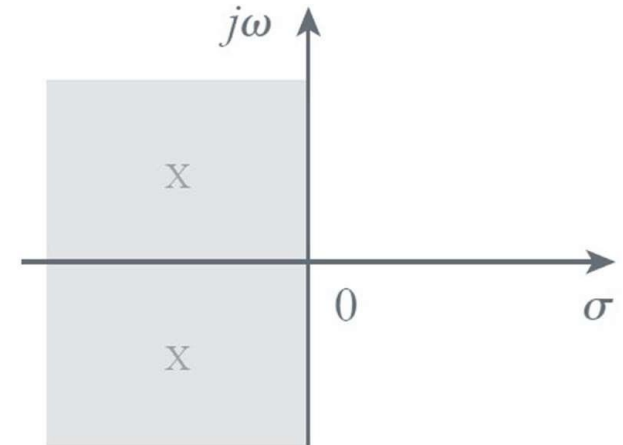2. **All the poles of $H(s)$ (i.e., all the roots of $D(s) = 0$) must have negative real parts, i.e. all the poles must lie in the left half of the s plane, as shown in Figure.**



Network Stability (Cont...)

The inverse of $H(s)$ is given as :

$$h(t) = k_1 e^{-p_1 t} + k_2 e^{-p_2 t} + \dots \dots \dots + k_n e^{-p_n t}$$


It is observed from this equation that

- each pole $-p_i$ must be positive (i.e., pole $s = -p_i$ in the left-half plane) in order for $e^{-p_i t}$ to decrease with increasing t .
- An unstable circuit never reaches steady state because the transient response does not decay to zero.
- Consequently, steady-state analysis is only applicable to stable circuits.

Network Stability (Cont...)

- A circuit made up of passive elements (R , L , and C) and *independent sources* cannot be unstable, because that would imply that some branch currents or voltages would grow indefinitely with sources set to zero.
- Passive elements cannot generate such indefinite growth. Passive circuits either are stable or have poles with zero real parts.
- To verify the above aspect, consider the series RLC circuit in Figure. The transfer function is given by
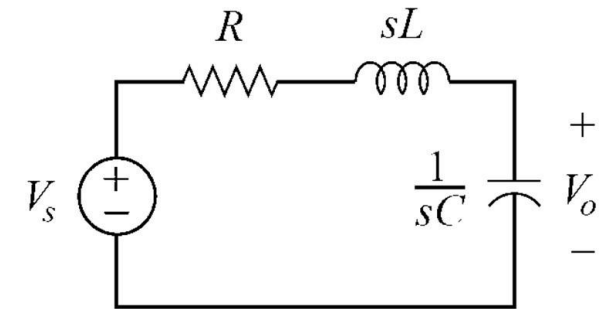
$$H(s) = \frac{V_o}{V_s} = \frac{1/sC}{R + sL + 1/sC} = \frac{1/LC}{s^2 + \frac{sR}{L} + 1/LC}$$



Network Stability (Cont...)

Here, $D(s) = s^2 + \frac{sR}{L} + 1/LC = 0$ is the same as the characteristic equation obtained for the series *RLC* circuit. The circuit has poles at

$$p_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

where

$$\alpha = \frac{R}{2L}, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

For *R*, *L*, *C* > 0, the two poles always lie in the left half of the *s* plane, implying that the circuit is always stable.

However, when *R* = 0, $\alpha = 0$ and the circuit becomes oscillatory. Although ideally this is possible, it does not really happen practically, because *R* is never zero.

Network Stability (Cont...)

- Active circuits or passive circuits with controlled sources can supply energy, and they can be unstable.
- An oscillator is an example of a circuit designed to be unstable. An oscillator is designed such that its transfer function is of the form


$$H(s) = \frac{N(s)}{s^2 + \omega_0^2} = \frac{N(s)}{(s + j\omega_0)(s - j\omega_0)}$$

So that its output is sinusoidal.

Network Stability (Cont...)

□ Example:

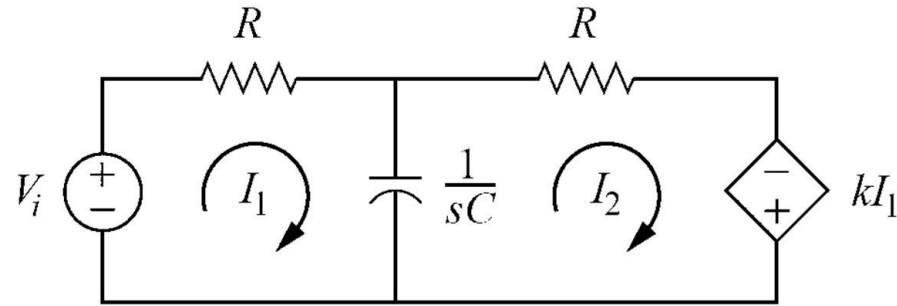Determine the values of k for which the circuit in *Figure* is stable.



Network Stability (Cont...)

□ Solution:

Applying mesh analysis to the first-order circuit in *Figure* gives


Mesh-1:

$$V_i = \left(R + \frac{1}{sC} \right) I_1 - \frac{I_2}{sC}$$

Mesh-2:

$$0 = -kI_1 + \left(R + \frac{1}{sC} \right) I_2 - \frac{I_1}{sC}$$
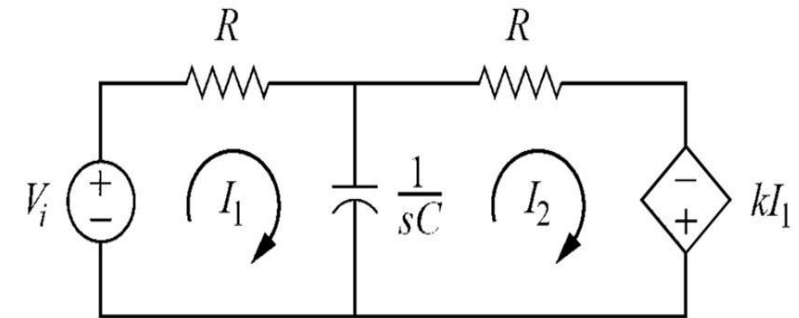
$$0 = -\left(k + \frac{1}{sC} \right) I_1 - \left(R + \frac{1}{sC} \right) I_2$$



or

Network Stability (Cont...)

Writing *Eqs.* in matrix form as

$$\begin{bmatrix} V_i \\ 0 \end{bmatrix} = \begin{bmatrix} \left(R + \frac{1}{sC}\right) & -\frac{1}{sC} \\ \left(k + \frac{1}{sC}\right) & \left(R + \frac{1}{sC}\right) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

The determinant is

$$\Delta = \left(R + \frac{1}{sC}\right)^2 - \frac{k}{sC} - \frac{1}{s^2 C^2} = \frac{sR^2 C + 2R - k}{sC}$$

The characteristic equation ($\Delta = 0$) gives the single pole as

$$p = \frac{k - 2R}{R^2 C}$$

which is negative when $k < 2R$. Thus, we conclude the circuit is stable when $k < 2R$ and unstable for $k > 2R$.

Network Synthesis

- Network synthesis is the process of obtaining an appropriate network for a given transfer function.
- Network synthesis is easier to carry out in the s domain than in the time domain.

In network analysis, we find the transfer function of a given network. While in network synthesis, we reverse the approach: i.e. we are required to find a suitable network for a given transfer function


- In synthesis, there may be many different answers or possibly no answers, because there may be many circuits that can be used to represent the same transfer function.
- While in network analysis, there is only one answer.

❑ **Example:** Given the transfer function

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{10}{s^2 + 3s + 10}$$

Realize the function using the circuit shown in Figure.

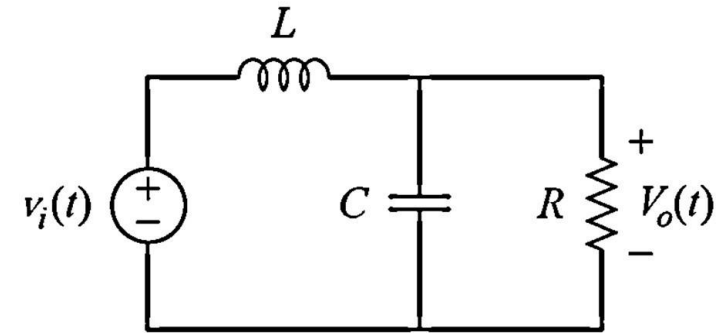- (a) Select **$R = 5\Omega$** , and find **L** and **C** .
- (b) Select **$R = 1\Omega$** , and find **L** and **C** .



❑ **Solution:**

The **s -domain** equivalent of the circuit shown in figure is shown in next slide.

Network Synthesis (Cont...)

□ Solution:



The parallel combination of R and C gives

$$R \parallel \frac{1}{sC} = \frac{R/sC}{R + \frac{1}{sC}} = \frac{R}{1 + sRC}$$

Using the voltage division principle,

$$V_o = \frac{R/(1 + sRC)}{sL + R/(1 + sRC)} V_i$$
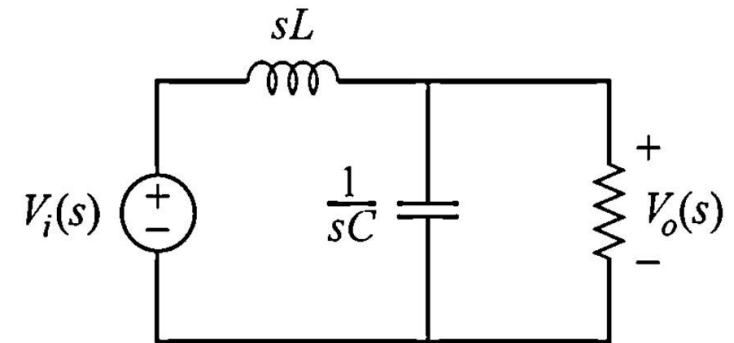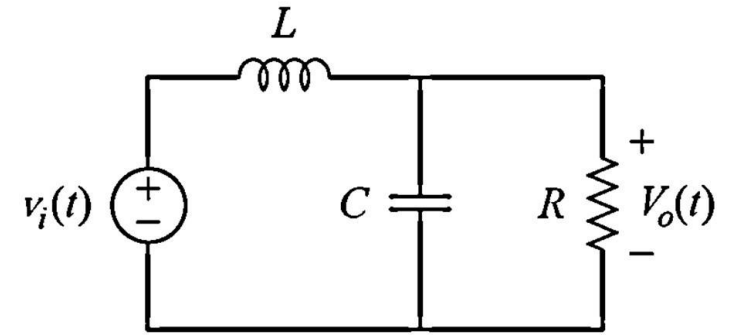
$$\frac{V_o}{V_i} = \frac{R}{s^2 RLC + sL + R} = \frac{1/LC}{s^2 + \frac{s}{RC} + 1/LC}$$



□ Solution:

$$\frac{V_o}{V_i} = \frac{R}{s^2 RLC + sL + R} = \frac{1/LC}{s^2 + \frac{s}{RC} + 1/LC}$$

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{\mathbf{10}}{s^2 + \mathbf{3}s + \mathbf{10}}$$

Comparing this with the given transfer function $H(s)$ reveals that

$$\frac{1}{LC} = 10, \qquad \frac{1}{RC} = 3$$

There are several values of R , L , and C that satisfy these requirements. So, specifying one element value, can help in determining others.

(a) If we select $R = 5\Omega$, then

$$C = \frac{1}{3R} = 66.67 \text{ mF},$$

$$L = \frac{1}{10C} = 1.5 \text{ H}$$

□ Solution:

(b) If we select $R = 1\Omega$, then

$$C = \frac{1}{3R} = 0.333 F,$$

$$L = \frac{1}{10C} = 0.3 H$$

Making $R = 1\Omega$ can be regarded as *normalizing* the design.

Impedance Parameters



□ Introduction

- A pair of terminals through which a current may enter or leave a network is known as a port.
- A port is an access to the network and consists of a pair of terminals; the current entering one terminal leaves through the other terminal so that the net current entering the port equals zero.
- Two-terminal devices or elements (such as resistors, capacitors, and inductors) result in one-port networks.
- Most of the circuits we have dealt with so far are two-terminal or one-port circuits.
- In general, a network may have n ports.
- In this module, the discussion is mainly focused on two-port networks.

Impedance Parameters (Cont...)



□ Introduction

- A two-port network is an electrical network with two separate ports for input and output.
- Thus, a two-port network has two terminal pairs acting as access points unlike the one port network.
- As shown in the figure below, the current entering one terminal of a pair leaves the other terminal in the pair.
- To characterize a two-port network, it is required that we relate the terminal quantities V_1 , V_2 , I_1 , and I_2 , out of which two are independent.
- The various terms that relate these voltages and currents are called parameters.

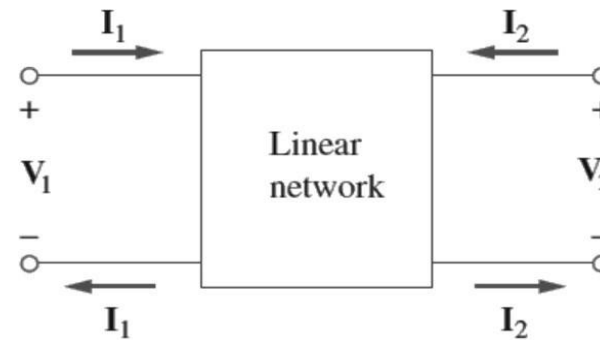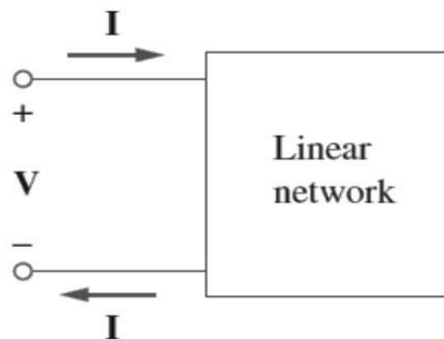

Impedance Parameters (Cont...)

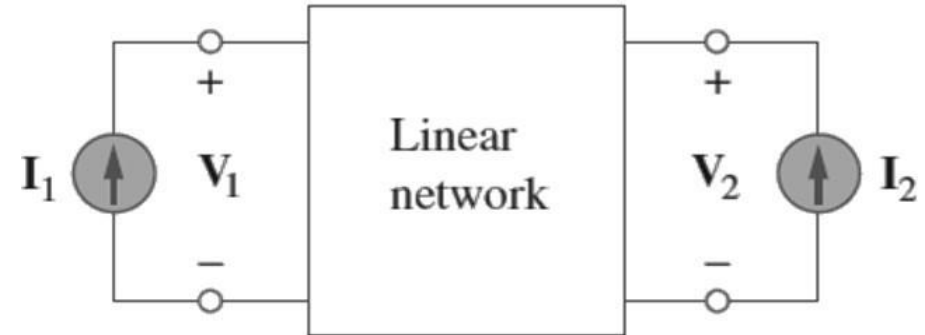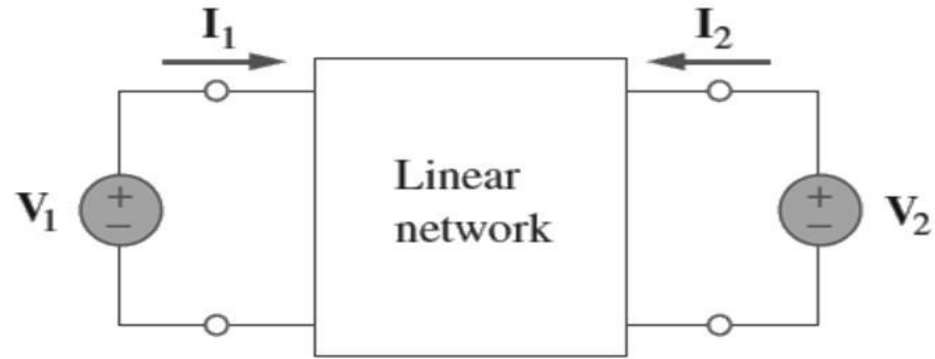- A two-port network may be voltage driven or current driven as illustrated in the figure below.
- To determine the impedance parameters the terminal voltages are expressed in terms of the terminal currents.



Impedance Parameters (Cont...)


- The relation between the terminal voltage and the terminal current can be established using the following equations:

$$\mathbf{V}_1 = \mathbf{z}_{11}\mathbf{I}_1 + \mathbf{z}_{12}\mathbf{I}_2$$

$$\mathbf{V}_2 = \mathbf{z}_{21}\mathbf{I}_1 + \mathbf{z}_{22}\mathbf{I}_2$$

- This can alternatively be expressed in matrix form as,
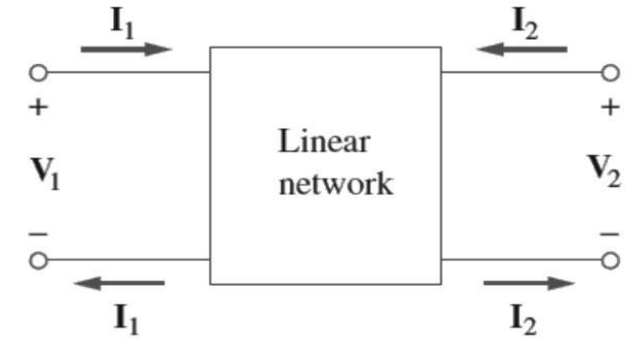
$$\begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = \begin{bmatrix} \mathbf{z}_{11} & \mathbf{z}_{12} \\ \mathbf{z}_{21} & \mathbf{z}_{22} \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = [\mathbf{z}] \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix}$$



- Here the **z** terms are known as the impedance parameters or the **z** parameters.
- Impedance parameters are expressed in ohms.

Impedance Parameters (Cont...)

- The values of the parameters can be evaluated by setting $\mathbf{I}_1 = \mathbf{0}$ (input port open-circuited) or $\mathbf{I}_2 = \mathbf{0}$ (output port open-circuited).
- Since the \mathbf{z} parameters are obtained by open-circuiting the input or output port, they are also called the open-circuit impedance parameters.
- The individual parameters are evaluated as follows:

$$\mathbf{V}_1 = \mathbf{z}_{11}\mathbf{I}_1 + \mathbf{z}_{12}\mathbf{I}_2$$

$$\mathbf{V}_2 = \mathbf{z}_{21}\mathbf{I}_1 + \mathbf{z}_{22}\mathbf{I}_2$$

- If $\mathbf{I}_2 = \mathbf{0}$, then

$$\mathbf{z}_{11} = \frac{\mathbf{V}_1}{\mathbf{I}_1}, \mathbf{z}_{21} = \frac{\mathbf{V}_2}{\mathbf{I}_1}$$

- If $\mathbf{I}_1 = \mathbf{0}$, then

$$\mathbf{z}_{12} = \frac{\mathbf{V}_1}{\mathbf{I}_2}, \mathbf{z}_{22} = \frac{\mathbf{V}_2}{\mathbf{I}_2}$$

Impedance Parameters (Cont...)

- Specifically,

- \mathbf{z}_{11} = Open-circuit input impedance
- \mathbf{z}_{12} = Open-circuit transfer impedance from port 1 to port 2
- \mathbf{z}_{21} = Open-circuit transfer impedance from port 2 to port 1
- \mathbf{z}_{22} = Open-circuit output impedance
- The values of \mathbf{z}_{11} and \mathbf{z}_{21} can be obtained by connecting a voltage \mathbf{V}_1 (or current \mathbf{I}_1) to port 1 with port 2 open-circuited ($\mathbf{I}_2 = 0$).
- \mathbf{I}_1 , \mathbf{V}_1 and \mathbf{V}_2 are then obtained which can be used to evaluate $\mathbf{z}_{11} = \frac{\mathbf{V}_1}{\mathbf{I}_1}$ and $\mathbf{z}_{21} = \frac{\mathbf{V}_2}{\mathbf{I}_1}$
- Similarly, the values of \mathbf{z}_{12} and \mathbf{z}_{22} can be obtained by connecting a voltage \mathbf{V}_2 (or current \mathbf{I}_2) to port 2 with port 1 open-circuited ($\mathbf{I}_1 = 0$).
- \mathbf{I}_2 , \mathbf{V}_2 and \mathbf{V}_1 are then obtained which can be used to evaluate $\mathbf{z}_{12} = \frac{\mathbf{V}_1}{\mathbf{I}_2}$ and $\mathbf{z}_{22} = \frac{\mathbf{V}_2}{\mathbf{I}_2}$

Impedance Parameters (Cont...)

- The above procedure can be easily understood using the following Figure.

