

**Department of Electrical Engineering  
Indian Institute of Technology, Kanpur**

**EE 210**


**Assignment #1**

**Assigned: 10.1.25**


For all problems in this course, assume  $T = 300$  K (with  $V_T = 26$  mV), unless otherwise stated.

1. A pn junction diode has reverse saturation current  $I_0 = 10$  pA. Determine the magnitude of the diode current (along with its direction) when it is under: i) forward bias of: a) 50 mV, and b) 500 mV; and ii) reverse bias of: a) 50 mV, and b) 500 mV.

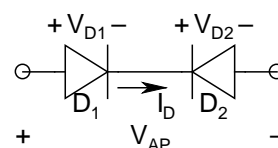2. Two diodes  $D_1$  and  $D_2$  are connected back to back with an applied bias of  $V_{AP}$  ( $= 5$  V), as shown in the figure. Calculate the current  $I_D$  and the diode drops  $V_{D1}$  and  $V_{D2}$ . Data:  $I_0(D_1) = 1$  pA, and  $I_0(D_2) = 1$  nA.



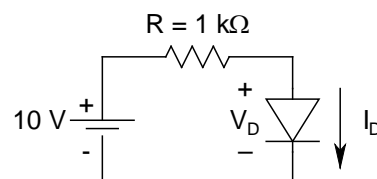3. A simple diode circuit is shown alongside. Perform a self-consistent analysis to find the diode current  $I_D$  and the diode voltage  $V_D$ . Take  $I_0 = 10$  pA.



4. The measured junction capacitance  $C_{dep}$  (in  $\mu$ F) as a function of the applied voltage  $V_D$  (in volts) of an abrupt Si pn junction (area  $= 10$  mm<sup>2</sup>) is given by  $1/C_{dep}^2 = [2.5 \times 10^5 \times (4 - 6.25V_D)]$ . Determine the built-in voltage and the depletion region width at zero bias.
5. Consider Prob.3. Assuming that the junction is linearly graded, determine the small-signal parameters of the diode, and draw its small-signal equivalent circuit. Data:  $V_0 = 0.8$  V,  $C_{dep0} = 1$  pF, and  $\tau = 1$   $\mu$ sec.