 


## Basic Three-Stage Architecture of an Op-Amp



Symbol

MacroModel

- **2 Input Terminals:**
  - $V_1$  (*non-inverting* [+])
  - $V_2$  (*inverting* [-])
- **1 Output Terminal:**  $V_0$
- $V_1$ ,  $V_2$ , and  $V_0$  can be *simply DC*, or *simply ac*, or a *combination of both*
- $I_1$ ,  $I_2$ : *Input currents flowing into the + and – terminals respectively*
- **Dual symmetric power supplies** ( $V_{S+}$  and  $V_{S-}$ )

- Refer to the *MacroModel*:

- $R_i$ : *Input Resistance*

- *Very high (ideally infinite)*

- $R_o$ : *Output Resistance*

- *Very small (ideally zero)*

- $A_{vOL}$ : *Open-Loop Gain*

- *Very large (ideally infinite)*

- *Input-Output Relation*:


$$V_o = A_{vOL}(V_1 - V_2)$$

- $V_1$ ,  $V_2$ , and  $V_0$  are measured *w.r.t. ground*, but  $V_i$  is a *floating signal* (*difference* between  $V_1$  and  $V_2$ )
- The *controlled source* in the *MacroModel* is *VCVS* (*Voltage Amplifier*)
- For  $V_1 > (<) V_2$ ,  $V_0$  is *positive* (*negative*)
- *Typical values for 741 op-amp*:
  - $A_{vOL} \sim 10^5$  (*100 dB*),  $R_i > 1\text{ M}\Omega$ ,  $R_o < 100\ \Omega$ ,  
CMRR  $\sim 80\text{-}100\text{ dB}$ ,  $V_{S+}$  and  $V_{S-}$ :  $\pm 3\text{ V to } \pm 15\text{ V}$

- *Uncompensated bandwidth* typically *larger than 1 MHz*
- Such a *large gain* and *high bandwidth* system will be prone to *oscillations* (*instability*)
- Need adequate *compensation*
  - *Compensated bandwidth* drops to about *5-10 Hz*
- *History of 741 Op-Amp:*
  - In *1965*, *Bob Widlar* (remember *Widlar current source*?) of *Fairchild Semiconductors* (now defunct) first came up with the design of a *monolithic* (*single substrate IC*) *op-amp*

- Named it  $\mu\text{A } 709$  ( $\mu\text{A}$  was the *trademark* of *Fairchild Semiconductors*)
- Almost immediately thereafter, *a number of improvements* were made on the *original architecture*, and  $\mu\text{A } 741$  evolved
- It became so *popular* that *the term 741* became a *legend*
- *All subsequent op-amp designs continued to be called 741!*
- *Initial design* of course was based on *bipolar technology*, since at that time, *MOSFETs were not even there!*

- In *late 70s*, *JFET version* of op-amps came into existence, followed by the *MOSFET version* in the *80s*
- The *design pedagogy* of the *original version* is a *real beauty*
- So many *brilliant innovations* were *incorporated* in the *design*, that it is a *learner's paradise*!
- The *detailed analysis* of the *bipolar version* of the *741 op-amp* is given in my book
- Go through it and enjoy! :)

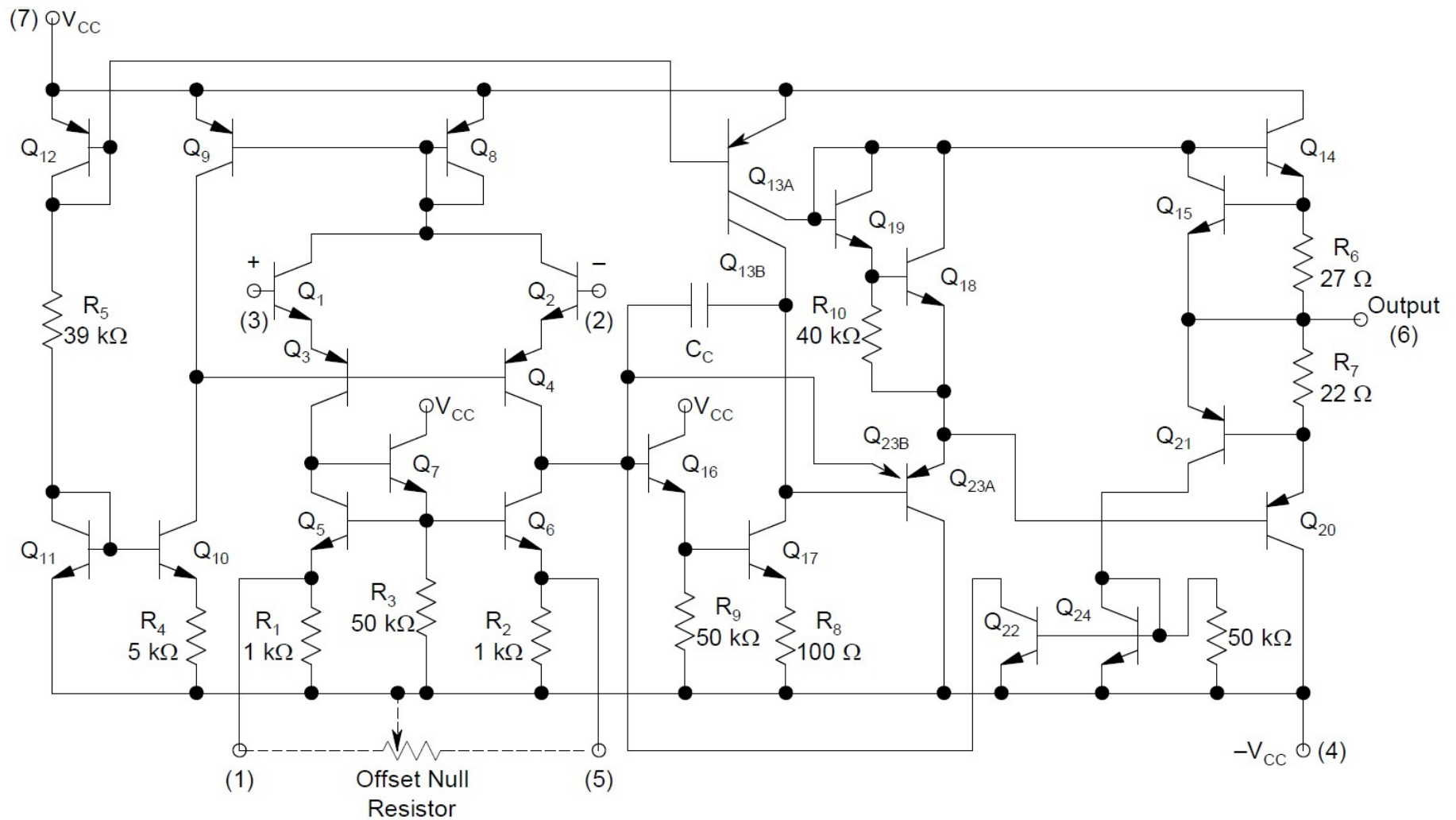

The schematic of the 741 bipolar op-amp (the pin numbers of the 741 chip is shown in parantheses).




Transistor(s)	Magnitude ( $\mu\text{A}$ )
$I_{C1}, I_{C2}, I_{C3}, I_{C4}, I_{C5}, I_{C6}$	9.5
$I_{C7}$	12.1
$I_{C8}, I_{C9}, I_{C10}$	19
$I_{C11}, I_{C12}$	733.3
$I_{C13A}, I_{C23A}$	183.3
$I_{C13B}, I_{C17}$	550
$I_{C14}, I_{C20}$	216
$I_{C16}$	17.9
$I_{C18}$	165.7
$I_{C19}$	17.6

## The DC Bias Currents of Different Transistors


- The *DC power dissipation* of the circuit:

$$\begin{aligned} P_{DC} &= V_{CC} \times (I_{C12} + I_{C9} + I_{C8} + I_{C13A} + I_{C13B} + \\ &\quad I_{C14} + I_{C7} + I_{C16}) + \\ &\quad |-V_{CC}| \times (I_{C11} + I_{C10} + I_{C5} + I_{C7} + I_{C6} + \\ &\quad I_{R9} + I_{C17} + I_{C23A} + I_{C20}) \\ &= 52.3 \text{ mW} \end{aligned}$$

 
- Note that the *reference branch* consumes the *highest DC power*, followed by the *Darlington branch*
- On the other hand, the *least DC power* is consumed by the *DA branch*



**2-Port Equivalent of the Input Stage**

 


**2-Port Equivalent of the Gain Stage**

 

**2-Port Equivalent of the Output Stage**  
(Driving a load of  $5 \text{ k}\Omega$ )
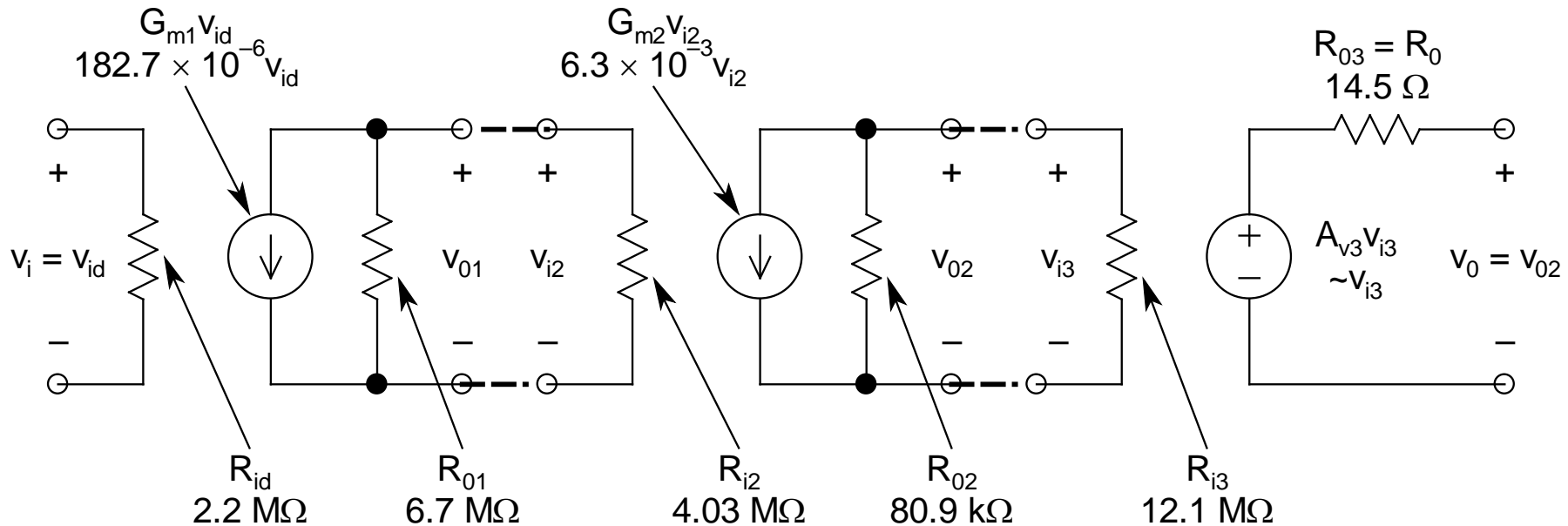
## ➤ *Overall Performance:*

- Just *cascade* the *2-port equivalents* of the *three stages*



## Complete 2-Port Representation of 741 Op-Amp

- *Voltage gain of the input stage:*

$$A_{v1} = v_{01}/v_{id} = -G_{m1}(R_{01}||R_{i2}) = -459.7$$

- *Voltage gain of the gain stage:*

$$A_{v2} = v_{02}/v_{01} = -G_{m2}(R_{02}||R_{i3}) = -506.3$$

- *Voltage gain of the output stage:*

$$A_{v3} \sim 1$$

- Thus, the *overall voltage gain* of *741 op-amp*:

$$\begin{aligned} A_{VOL} &= v_0/v_{id} = (v_0/v_{i3}) \times (v_{i3}/v_{i2}) \times (v_{i2}/v_{id}) \\ &= 2.33 \times 10^5 \text{ (107.3 dB)} \end{aligned}$$

*Note:*  $v_{i3} = v_{02}$ , and  $v_{i2} = v_{01}$

- This is an *excellent value*, in spite of the *significant loading effect* of the *gain stage* on the *input stage*

## ➤ *Observations:*

- $A_{vOL}$  is actually the *differential-mode gain* ( $A_{dm}$ )
- It is *positive*
  - ❖ *Positive*  $v_{id}$  produces *positive*  $v_o$
  - ❖ *Bases* of  $Q_1$  and  $Q_2$  are termed as *non-inverting* (+) and *inverting* (−) terminals respectively
- *Input and output resistances* are  $2.2\text{ M}\Omega$  and  $14.5\text{ }\Omega$  respectively, both of which are *excellent values*
- The *exact value* of  $A_{cm}$  is *a bit difficult to evaluate*, but it's quite small
- Has *extremely high CMRR*, typically more than 80 dB