

## Lecture-11

On

# INTRODUCTION TO ELECTRICAL ENGINEERING (ESO203)

- Thevenin's Theorem.
- Norton's Theorem.
- Maximum Power Transfer.

▪ **Quiz-1:**


- **Date:** 5<sup>th</sup> Feb 2025 (Wednesday).
- **Time:** 5:00 pm to 6:00 pm.
- **Venue:** Tutorial block (T101 to T106).
- **Syllabus:** till 4<sup>th</sup> Feb 2025.

## Thevenin's Theorem (Cont...)

- To find out  $R_{TH}$  we need to consider two cases.
- **Case 1:**
  - ❖ If the network has no dependent sources, we turn off all the independent sources.
  - ❖  $R_{TH}$  is the input resistance of the network looking between terminals **a** and **b**, as shown in the previous figure.
- **Case 2:**
  - ❖ If the network has dependent sources, we turn off only all independent sources.
  - ❖ The dependent sources cannot be turned off as they are controlled by circuit variables.
  - ❖ We apply a voltage  $v_0$  at terminals **a-b** and determine the current  $i_0$ .

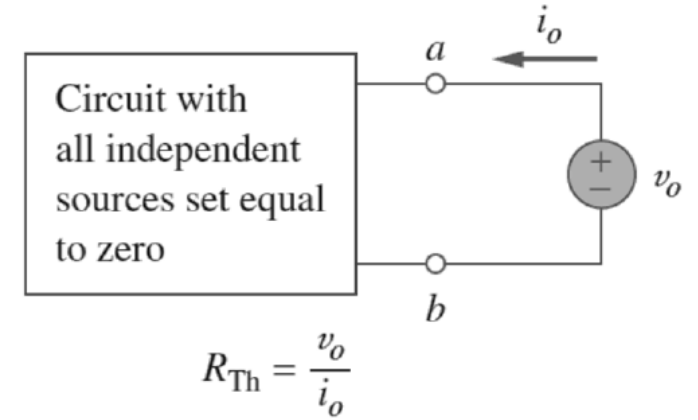
## Thevenin's Theorem (Cont...)

- Then,  $R_{TH}$  is given by  $\rightarrow R_{TH} = v_o / i_o$



- Alternatively,  $R_{TH}$  can be evaluated by inserting a current source as shown in the figure below.

- Again,  $R_{TH}$  is  $v_o / i_o$ .

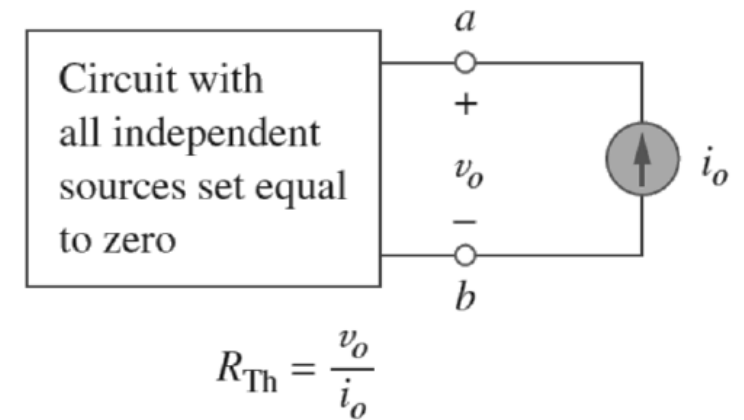


## Thevenin's Theorem (Cont...)

- Both approaches will give the same result.
- In either approach the value of  $v_o$  and  $i_o$  may be assumed to be equal to any value.
- It often occurs that  $R_{TH}$  takes a negative value. This implies that the circuit is delivering power.
- Negative value of  $R_{TH}$  is also possible in the circuit with dependent sources.
- Thevenin's theorem is very important in the circuit analysis because helps in simplifying the circuit.
- A large circuit may be replaced by a **single independent voltage source** and a **single resistor**. This replacement technique is a powerful tool in circuit design.

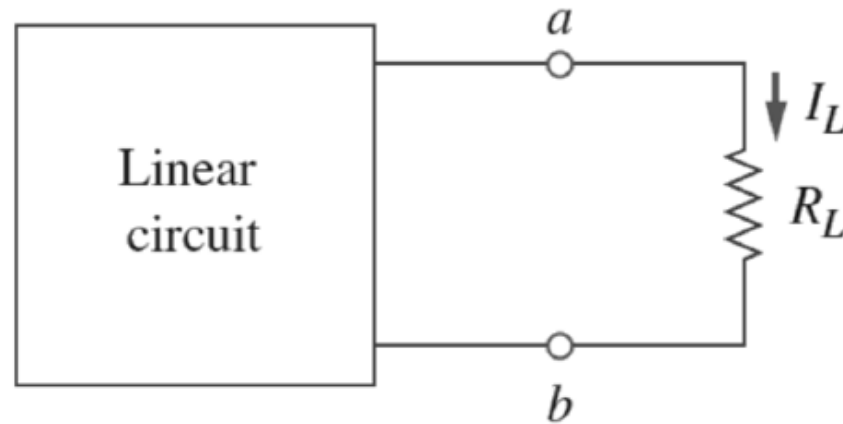
## Thevenin's Theorem (Cont...)

- As mentioned earlier, a linear circuit with a variable load can be replaced by the Thevenin equivalent, exclusive of the load.
- The equivalent network behaves the same way externally as the original circuit.
- Let us consider a linear circuit terminated by a load  $R_L$ .


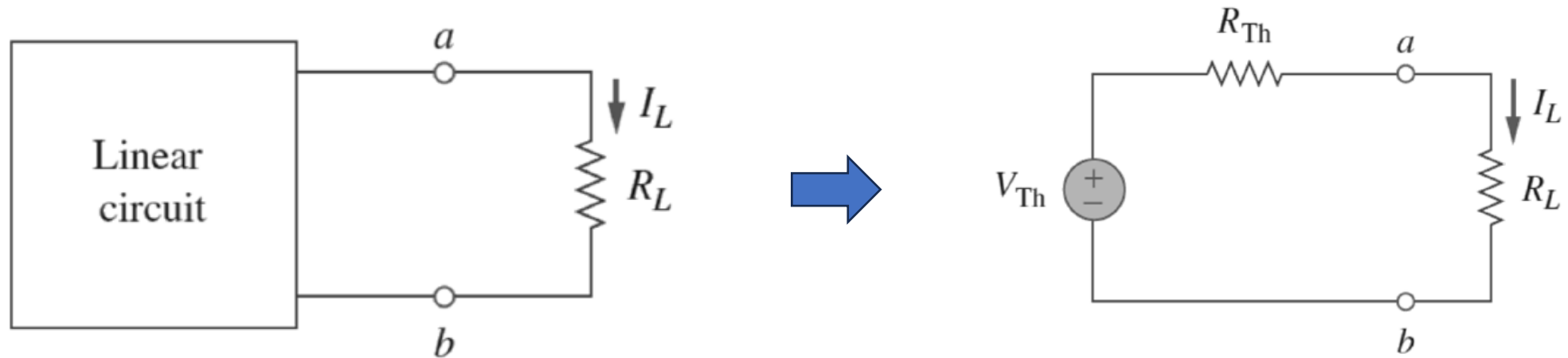
## Thevenin's Theorem (Cont...)

- The current  $I_L$  through the load and the voltage  $V_L$  across the load are easily determined once the Thevenin equivalent of the circuit are determined.
- The circuit can then be transformed as shown below.




- From the above figure we obtain,

$$I_L = V_{Th} / (R_{Th} + R_L)$$

$$V_L = I_L R_L = V_{Th} R_L / (R_{Th} + R_L)$$
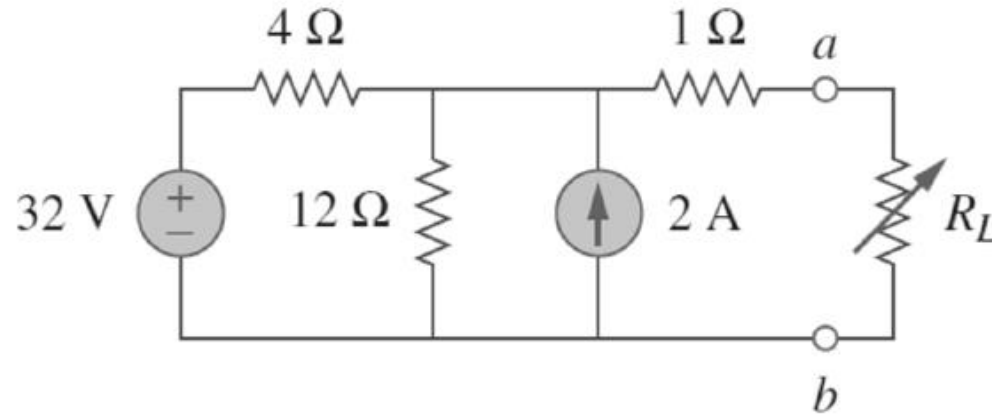
### □ Example:

For the below circuit find the Thevenin equivalent to the left of terminals a-b? Also, find current through load when  $R_{Th} = 6$  and  $36\Omega$ .



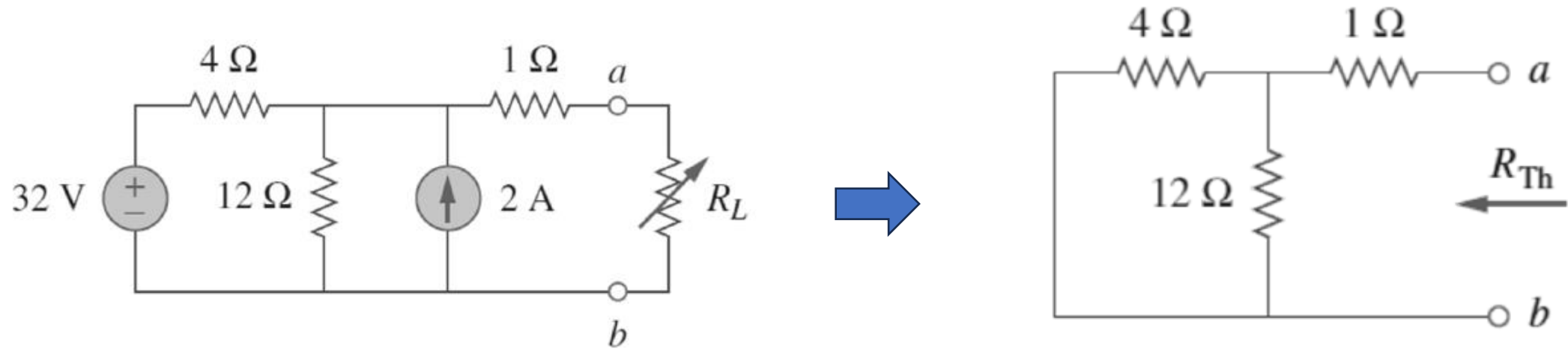
### Solution:

We find the Thevenin resistance by turning off the 32V source (replacing it with a short circuit) and the 2A current source (replacing it with an open circuit).



The circuit then becomes as shown in the figure below.




From the above figure  $R_{Th}$  can be evaluated as,

$$R_{Th} = 4 || 12 + 1 = \frac{4 * 12}{4 + 12} + 1 = 4 \Omega$$

The next step is to find  $V_{Th}$ .

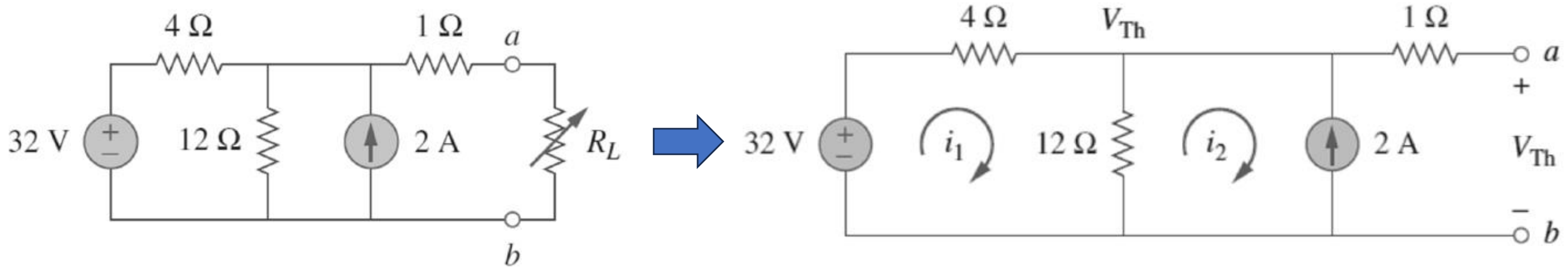To find  $V_{Th}$  we consider the circuit given below.




Applying mesh analysis to the two loops,

$$\begin{aligned} -32 + 4i_1 + 12(i_1 - i_2) &= 0 \\ i_2 &= -2A \end{aligned}$$

Solving for  $i_1$ , we get  $i_1 = 0.5A$ . Thus,

$$V_{Th} = 12(i_1 - i_2) = 12(0.5 + 2) = 30V$$

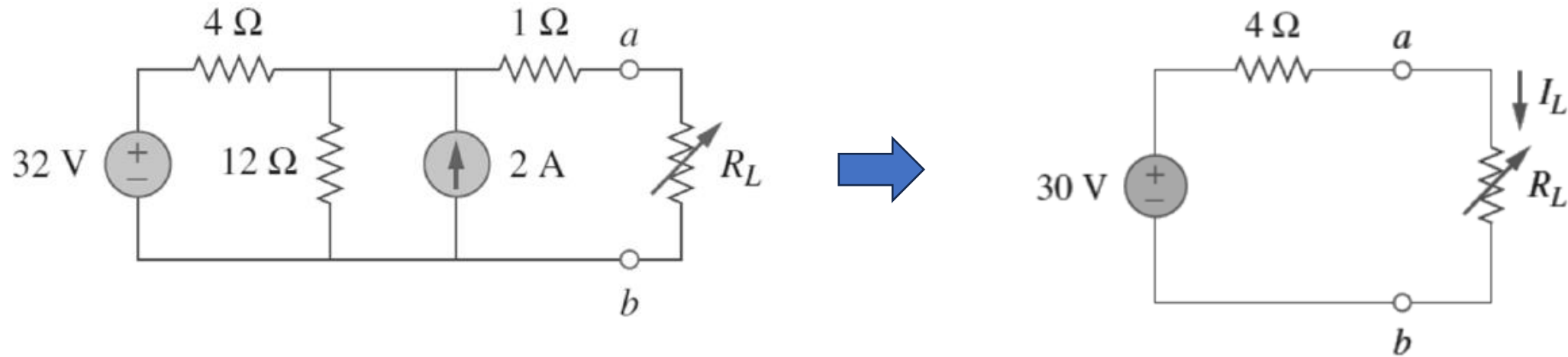The Thevenin equivalent circuit is as shown in the below figure.




The current through  $R_L$  is,

$$\text{When } R_L = 6\Omega, I_L = \frac{30}{10} = 3A.$$

$$\text{When } R_L = 16\Omega, I_L = \frac{30}{20} = 1.5A.$$


□ Example:

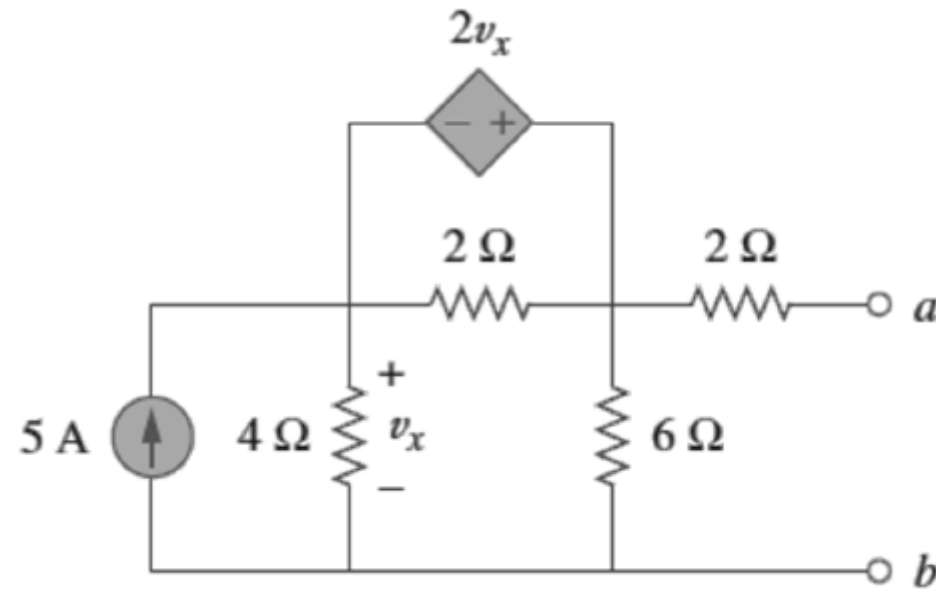For the below circuit find the Thevenin equivalent to the left of terminals a-b?



**Solution:** The circuit contains dependent source, unlike the circuit given in the previous example.

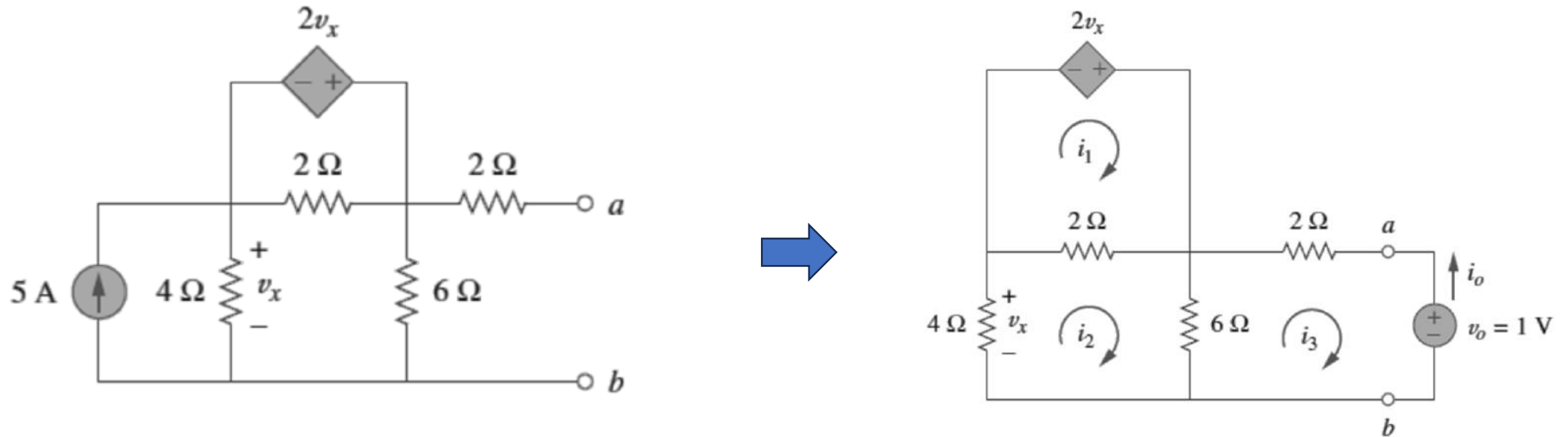To find  $R_{Th}$  we set the independent source to zero but leave the dependent source alone. As there is a dependent source, we excite the network with a source voltage  $v_o$  connected to the terminals as shown in the circuit below.



We may set  $v_o = 1\text{ V}$  to ease the calculation, since the circuit is linear.

- The next step is to find the current  $i_o$  through the terminals and then evaluate  $R_{Th} = \frac{i_o}{1}$ .
- Alternatively, insert a 1 A current source, find the corresponding voltage  $v_o$  and obtain  $R_{Th} = \frac{v_o}{1}$ .
- Applying mesh analysis to loop 1 of the circuit results in.

$$-2v_x + 2(i_1 - i_2) = 0 \Rightarrow v_x = i_1 - i_2$$


- But  $-4 i_2 = v_x = i_1 - i_2$ , hence

$$i_1 = -3i_2$$

- Applying KVL to loops 2 and 3 gives,

$$4i_2 + 2(i_1 - i_2) + 6(i_2 - i_3) = 0$$

$$6(i_3 - i_2) + 2i_3 + 1 = 0$$

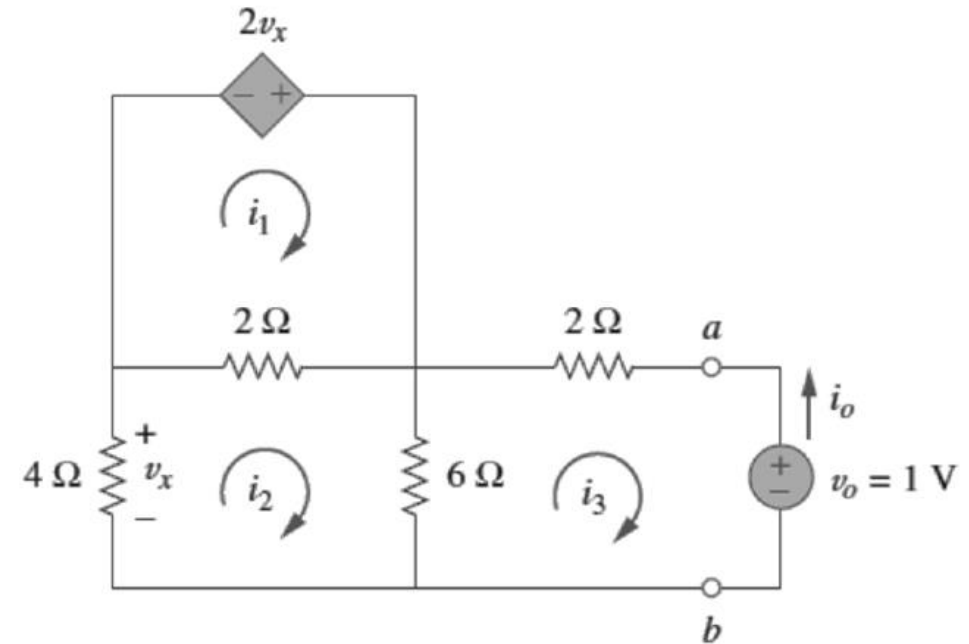


- Solving the above equations we get,

$$i_3 = -\frac{1}{6}A$$

- But  $i_0 = -i_3 = 1/6$  A. Hence,

$$R_{Th} = \frac{1V}{i_0} = 6\Omega$$

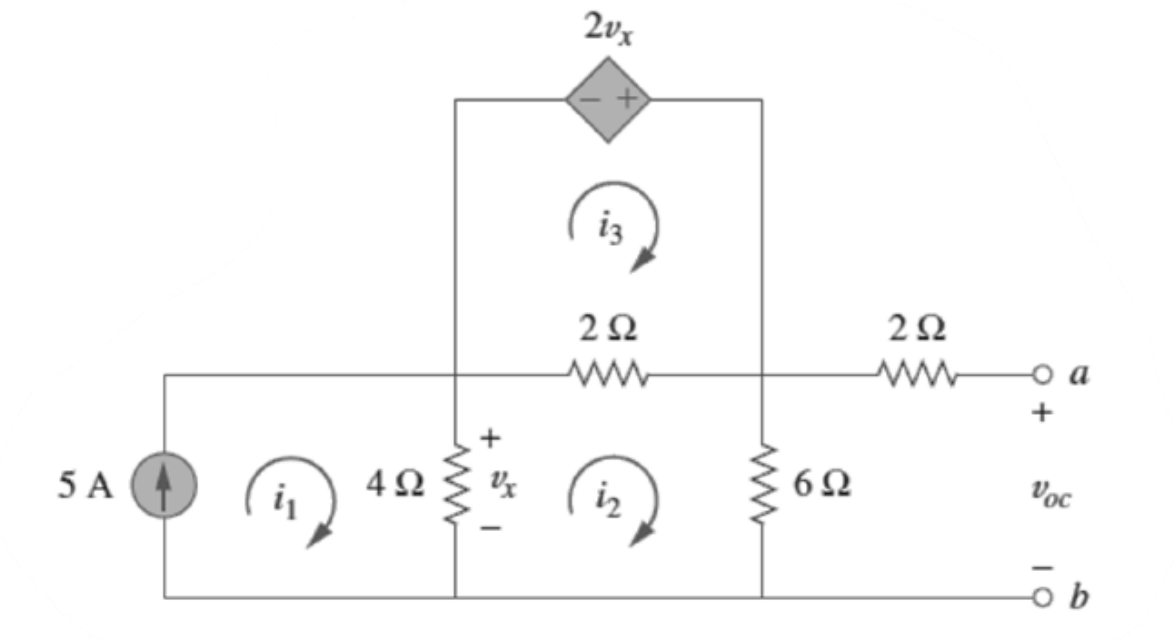- To determine  $V_{Th}$ , we find  $v_{oc}$  in the circuit shown below.



- Applying mesh analysis we obtain,

$$i_1 = 5$$





$$-2v_x + 2(i_3 - i_2) = 0 \Rightarrow v_x = i_3 - i_2$$

$$4(i_2 - i_1) + 2(i_2 - i_3) + 6i_2 = 0 \Rightarrow 12i_2 - 4i_1 - 2i_3 = 0$$

- But  $4(i_1 - i_2) = v_x$ .
- Solving these equations leads to  $i_2 = 10/3$ .
- Hence,

$$V_{Th} = v_{oc} = 6i_2 = 20V$$

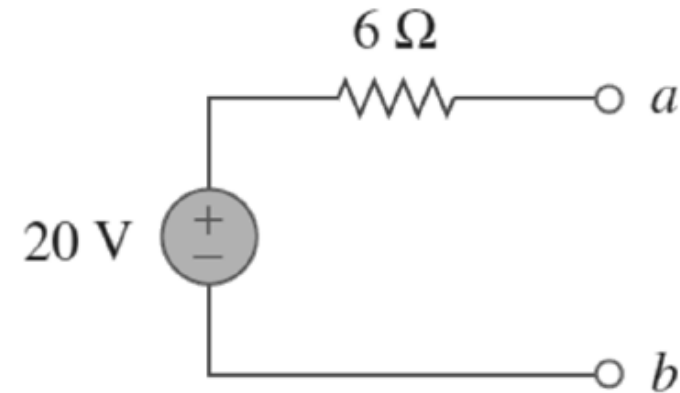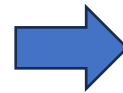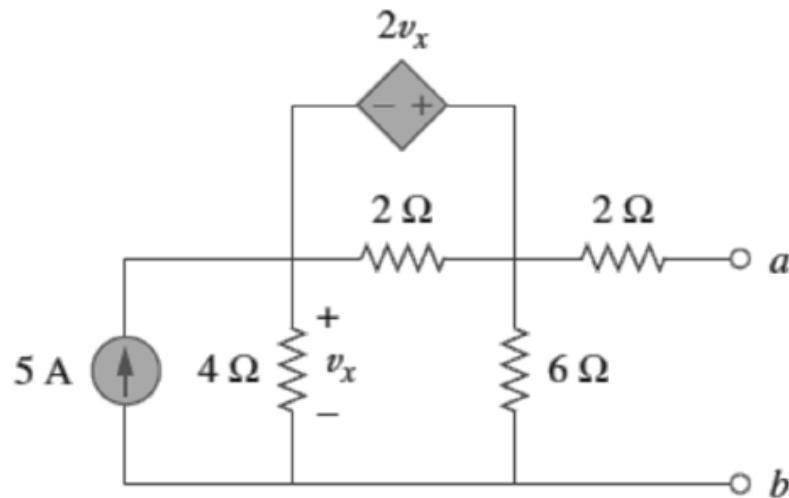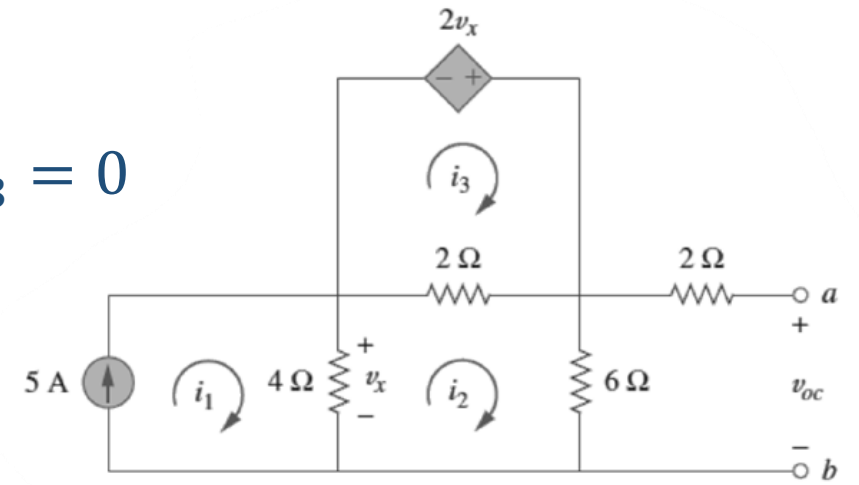- The Thevenin equivalent is as shown in the adjacent figure.






## Norton's Theorem

- In 1926, about 43 years after Thevenin published his theorem, E. L. Norton, an American engineer at Bell Telephone Laboratories, proposed a similar theorem, called Norton's theorem.
- Norton's theorem states that a linear two-terminal circuit can be replaced by an equivalent circuit consisting of a current source  $I_N$  in parallel with a resistor  $R_N$ , where  $I_N$  is the short-circuit current through the terminals and  $R_N$  is the input or equivalent resistance at the terminals when the independent sources are turned off.

## Norton's Theorem (Cont...)

- Similar to the Thevenin's theorem, our major concern here is to find out the values of  $I_N$  and  $R_N$ .
- We find  $R_N$  the same way we found  $R_{Th}$ .
- In fact, from what we know from source transformation, the Thevenin and Norton resistances are the same, i.e.,

$$R_N = R_{Th}$$

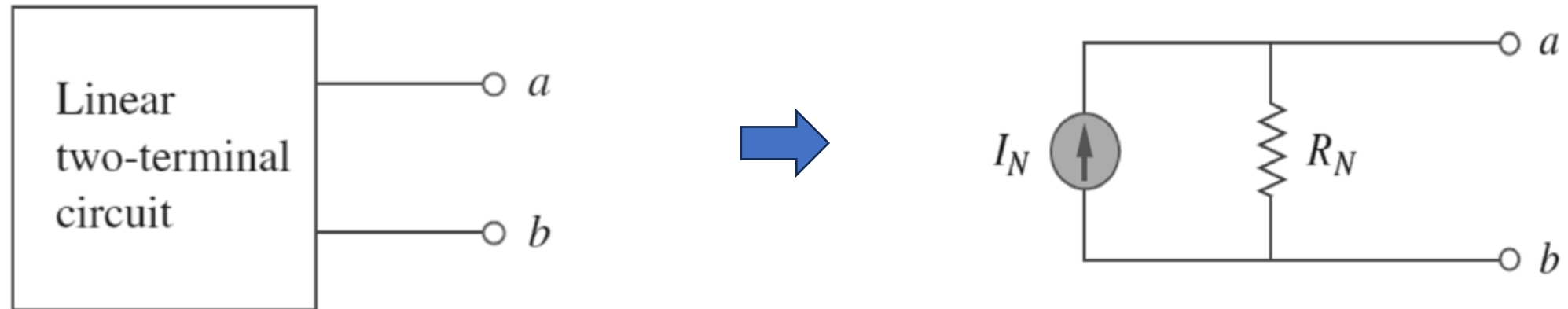


## Norton's Theorem (Cont...)

- To find the Norton's equivalent current  $I_N$  we find the short circuit current flowing from terminal **a** to **b** in both the circuits shown in the previous figure.
- It is evident from the figure that the short circuit is equal to  $I_N$ .
- This must be same short circuit current from terminal **a** to **b** in the figure on the left in previous slide, since both circuits are equivalent.
- Thus,

$$I_N = i_{sc}$$

as shown in the below figure.

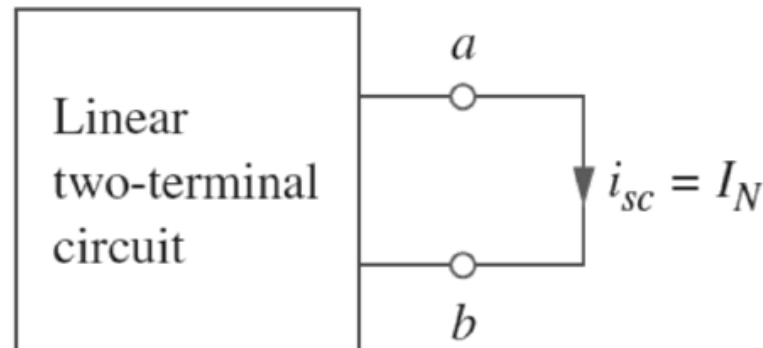

## Norton's Theorem (Cont...)

- Dependent and independent sources are treated the same way as in Thevenin's theorem.

### □ Case 1:

- If the network has no dependent sources, we turn off all the independent sources.
- $R_N$  is the input resistance of the network looking between terminals **a** and **b**, as shown in the previous figure.

### □ Case 2:

- If the network has dependent sources, we turn off all the independent sources only, leaving dependent sources connected to the circuit.
- As with the Thevenin's theorem, the dependent sources cannot be turned off as they are controlled by circuit variables.
- We apply a voltage  $v_o$  at terminals **a-b** and determine the current  $i_o$ .
- $R_N$  is found the same way as  $R_{Th}$ .

## Norton's Theorem (Cont...)

- The close relationship between Thevenin circuit and Norton circuit is obvious.
- $R_{Th} = R_N$  and  $I_N = V_{Th} / R_{Th}$ .
- This is essentially a source transformation.
- For this reason, the source transformation is often called Thevenin-Norton transformation.
- According to the above relation,  $V_{Th}$ ,  $I_N$ , and  $R_{Th}$  are related. Therefore, to determine the Thevenin or Norton equivalent circuit, we find them as follows -
  - The open circuit voltage  $v_{oc}$  across the terminals  $a$  and  $b$
  - The short circuit current  $i_{sc}$  at the terminals  $a$  and  $b$
  - The equivalent or the input resistance  $R_{in}$  at terminals  $a$  and  $b$  when all independent sources are turned off.

## Norton's Theorem (Cont...)

- We can calculate any two of the three, using the method that takes the least effort, and use them to get the third parameter value using Ohm's law.
- Therefore,

$$V_{Th} = v_{oc}$$

$$I_N = i_{sc}$$


$$R_{Th} = \frac{v_{oc}}{i_{sc}} = R_N$$

**The open and short circuit tests are sufficient to determine any Thevenin or Norton equivalent, of a circuit which contains at least one independent source.**
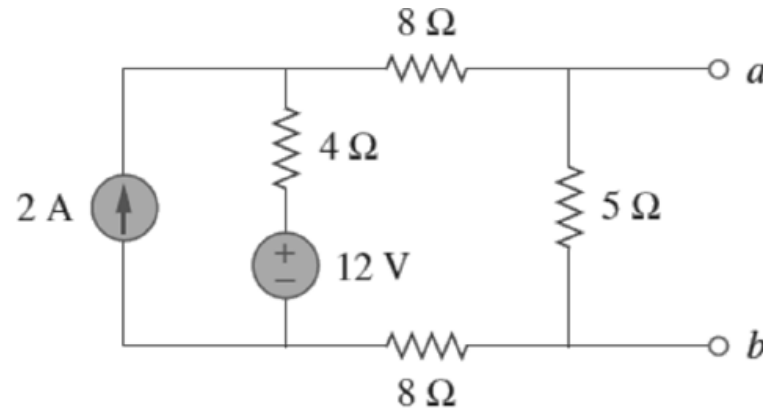
## Norton's Theorem (Cont...)


□ Example:

Find the Norton equivalent for the circuit given in the below figure?



**Solution:** We find the value of Norton resistance the same way we found it for Thevenin equivalent circuit.

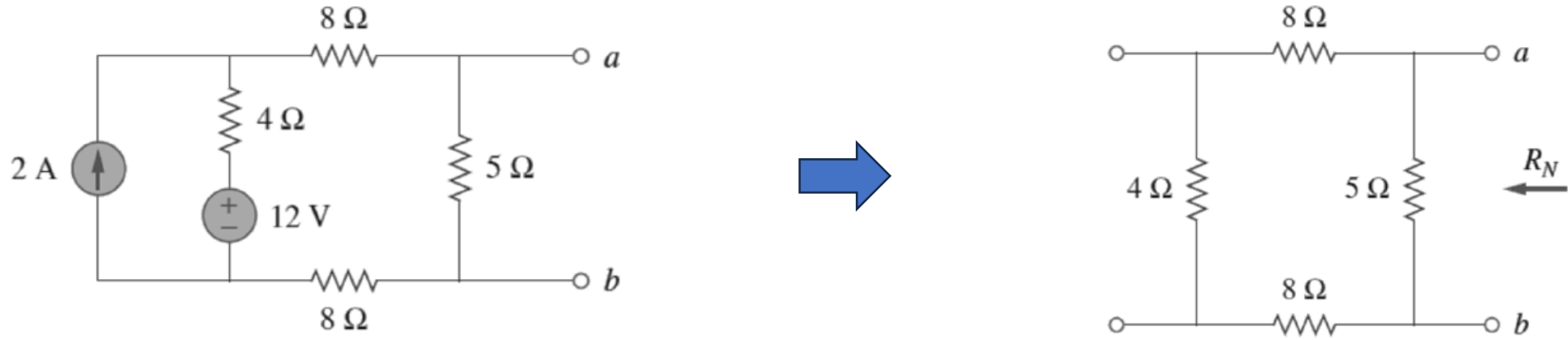Set the independent sources to zero, to obtain the following circuit,




$$R_N = 5 \parallel (8 + 4 + 8) = 5 \parallel 20$$

$$= \frac{20 * 5}{25} = 4\ \Omega$$



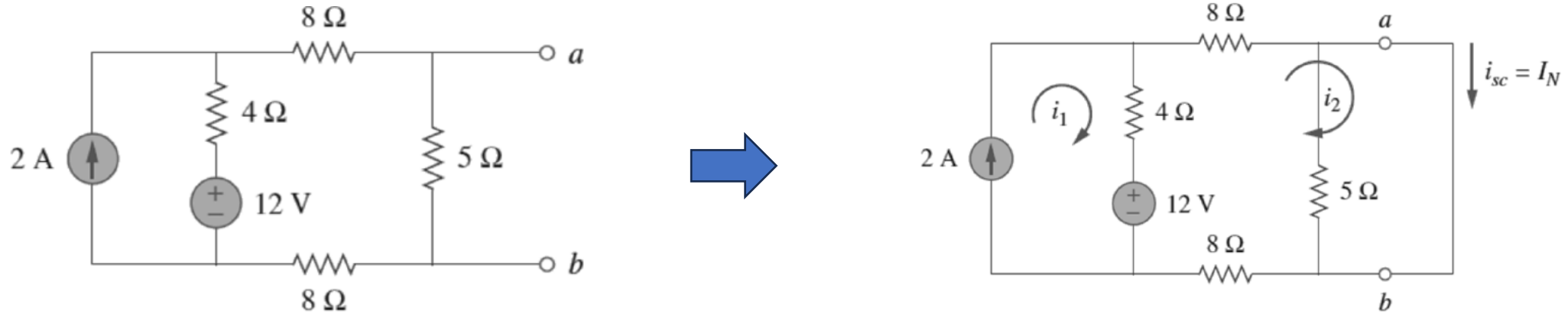- To find  $I_N$  we short the terminals a and b.



- We ignore the  $5\ \Omega$  resistor as it is short circuited.

- Applying mesh analysis we get,

$$i_1 = 2A$$





$$20i_2 - 4i_1 - 12 = 0$$

- From these equations we obtain,


$$i_2 = i_{sc} = I_N = 1A$$

- The Norton circuit can also be obtained as,

$$I_N = \frac{V_{Th}}{R_{Th}}$$

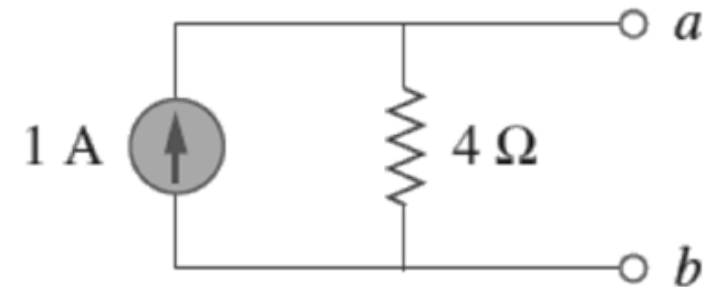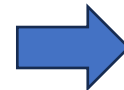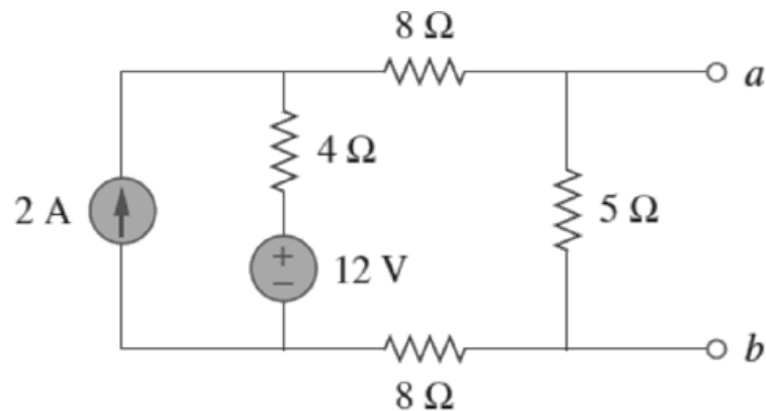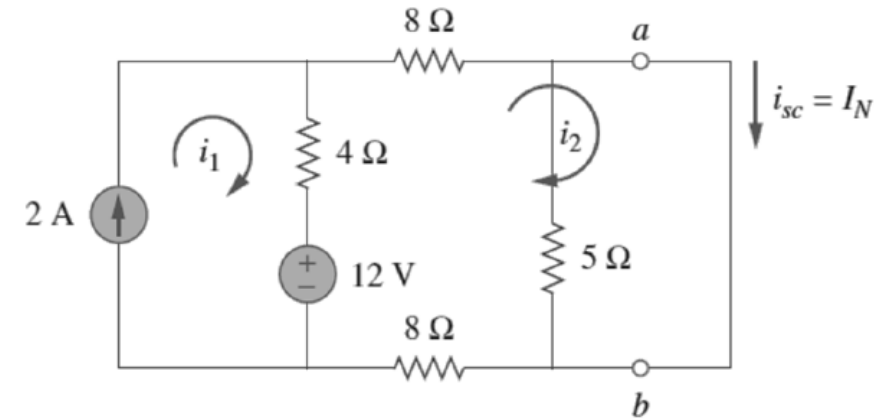

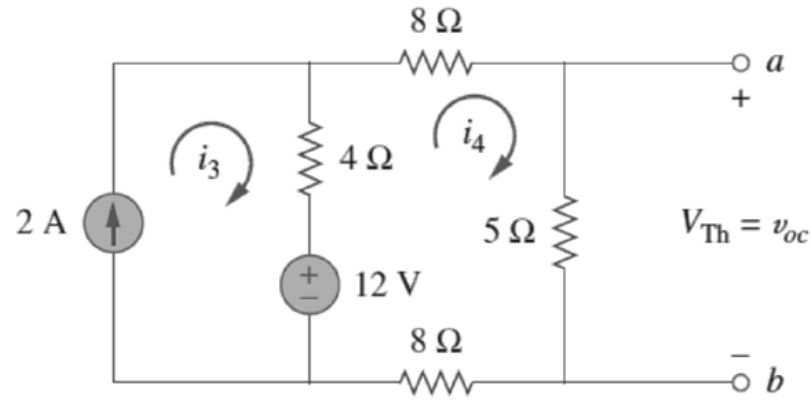- We obtain  $V_{Th}$  as the open circuit voltage across terminals **a** and **b** in the figure given below:



- Using mesh analysis, we obtain,

$$i_3 = 2A$$

$$25i_4 - 4i_3 - 12 = 0 \Rightarrow i_4 = 0.8A$$

- And,


$$v_{oc} = V_{Th} = 5i_4 = 4V$$

- Hence,

$$I_N = \frac{V_{Th}}{R_{Th}} = \frac{4}{4} = 1A$$


as obtained previously.

Therefore, the Norton's equivalent is -

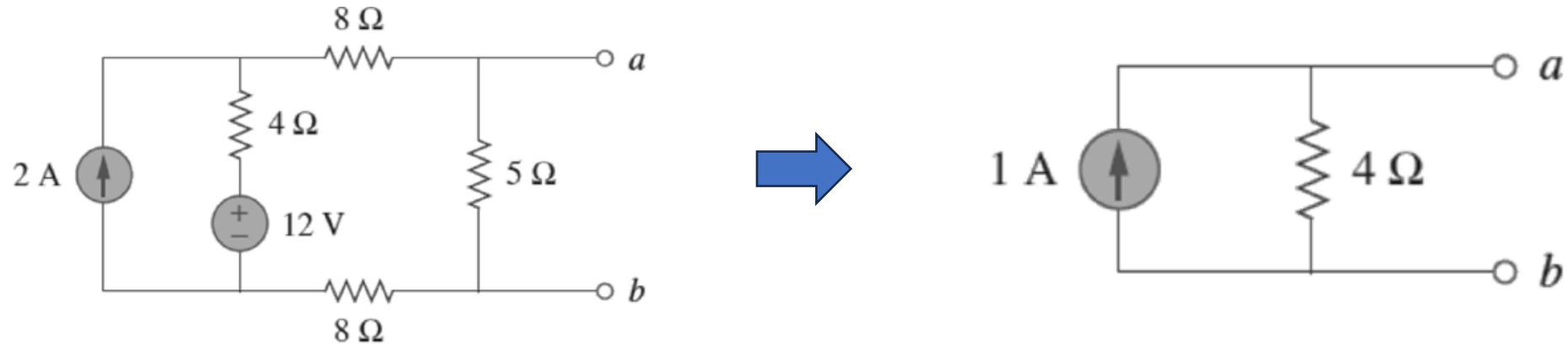


□ Example:

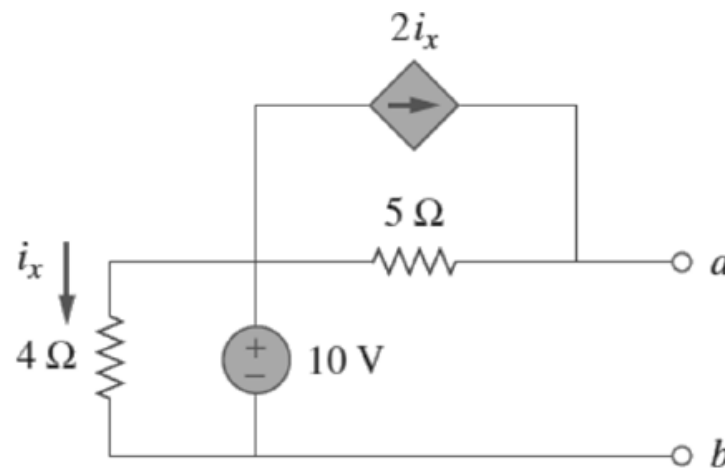Find the Norton equivalent for the circuit given in the below figure?



**Solution:** Unlike the previous circuit this circuit has a dependent source. To find the Norton resistance we set the independent source equal to zero but leave the dependent source as it is.

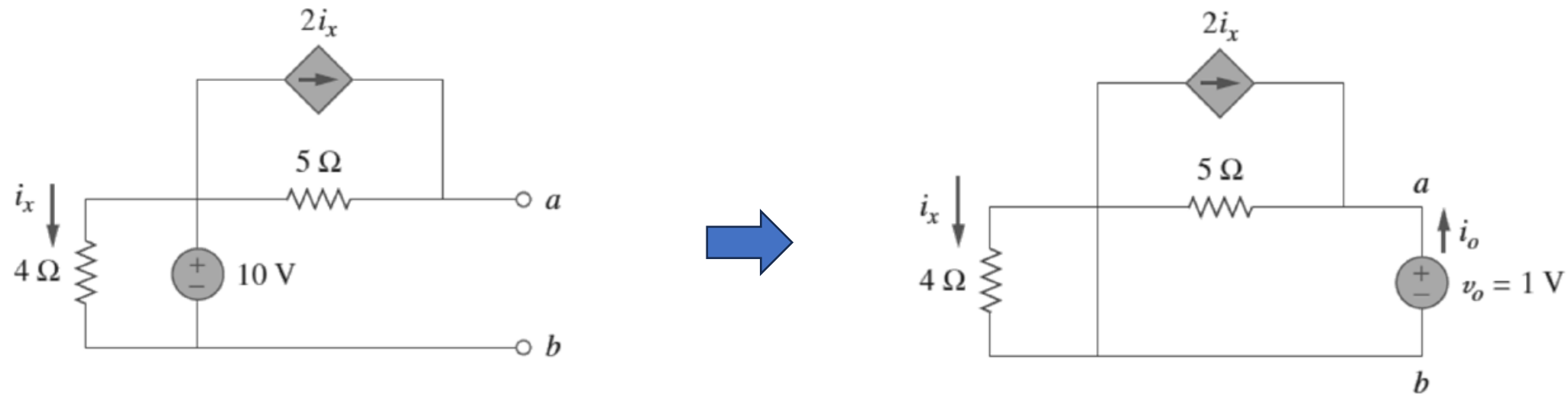- A voltage source  $v_o = 1\text{ V}$  (or of any value) is connected across the terminals as shown in the below figure,



- We ignore the  $4\Omega$  resistor as it is short circuited.
- Also, due to the short circuit the  $5\Omega$  resistor, the voltage source, and the dependent current source are in parallel.

Hence,


$$i_x = 0$$

At node **a**,


$$i_0 = \frac{1V}{5\Omega} = 0.2A$$


And,
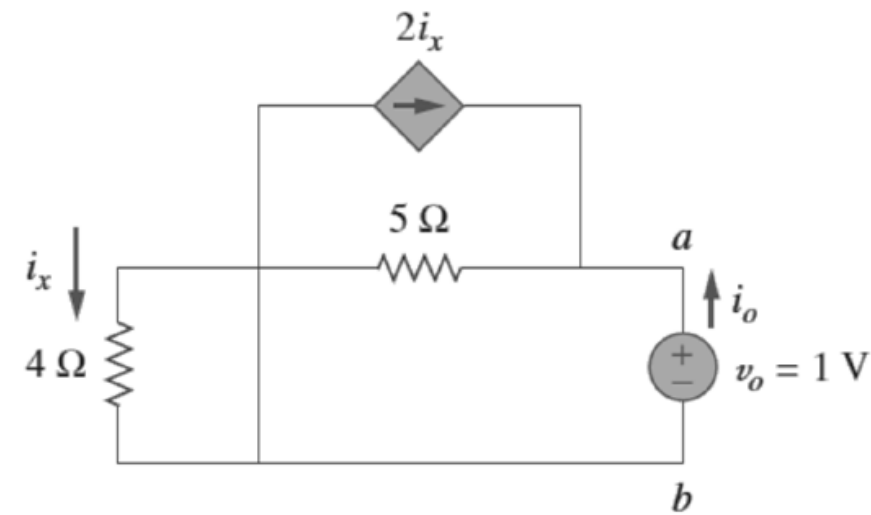
$$R_N = \frac{v_0}{i_0} = \frac{1}{0.2} = 5\Omega$$



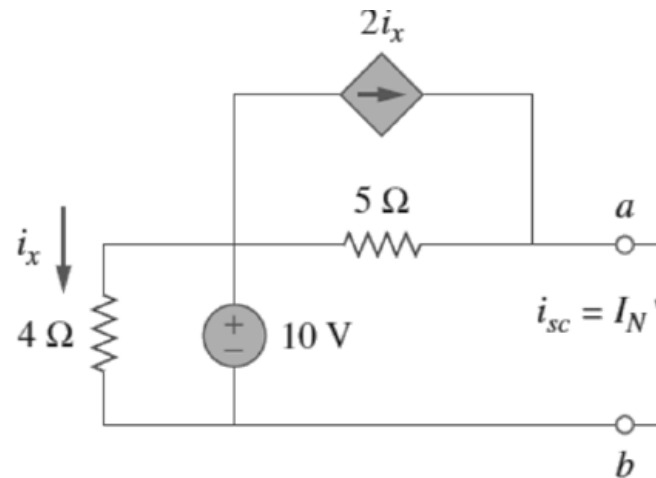- To find  $I_N$ , we short circuit the terminals **a** and **b** and find the current  $i_{sc}$  as indicated in the figure given below:



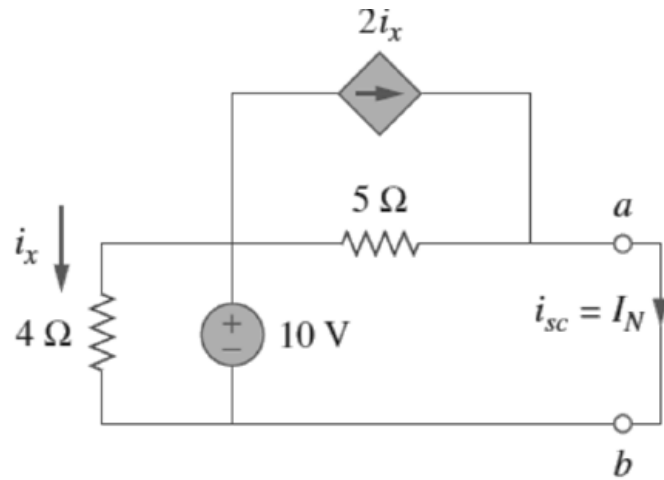




- Note from this figure that the  $4\Omega$  resistor, the  $10\text{V}$  voltage source, the  $5\Omega$  resistor, and the dependent current source are all in parallel.
- Hence,

$$i_x = \frac{10}{4} = 2.5\text{A}$$

- At node **a** KCL gives,
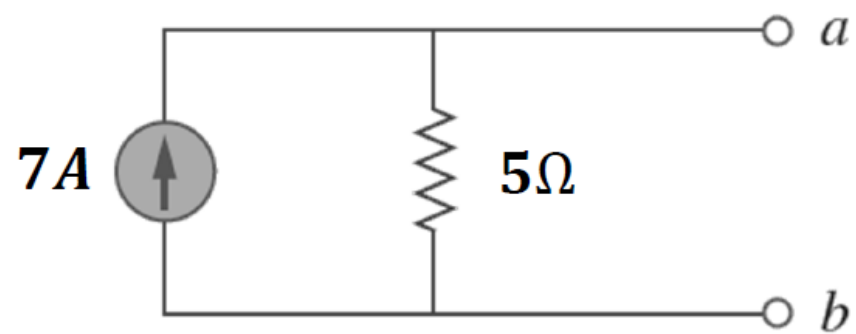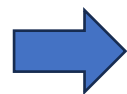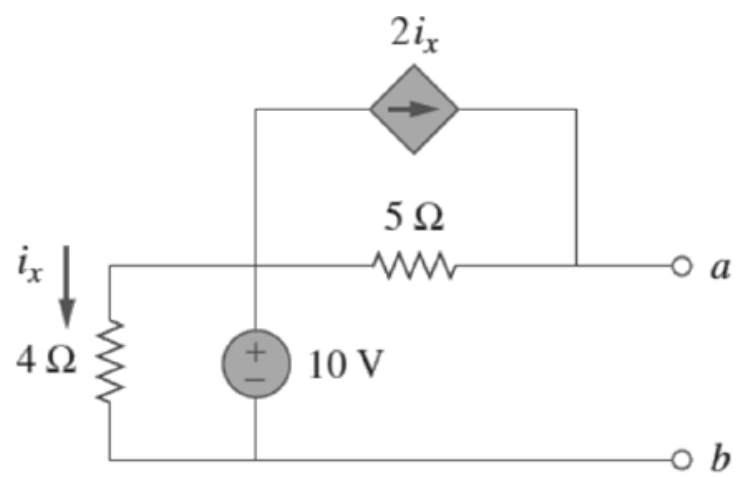
$$i_{sc} = \frac{10}{5} + 2i_x = 2 + 2(2.5) = 7\text{A}$$






## Maximum Power Transfer

- In many practical situations, a circuit is designed to provide power to a load.
- There are applications in areas such as communications where it is desirable to maximize the power delivered to a load.
- We need to address the problem of delivering the maximum power to a load when internal losses are known for given system.
- It should be noted that this will result in significant internal losses greater than or equal to the power delivered to the load.
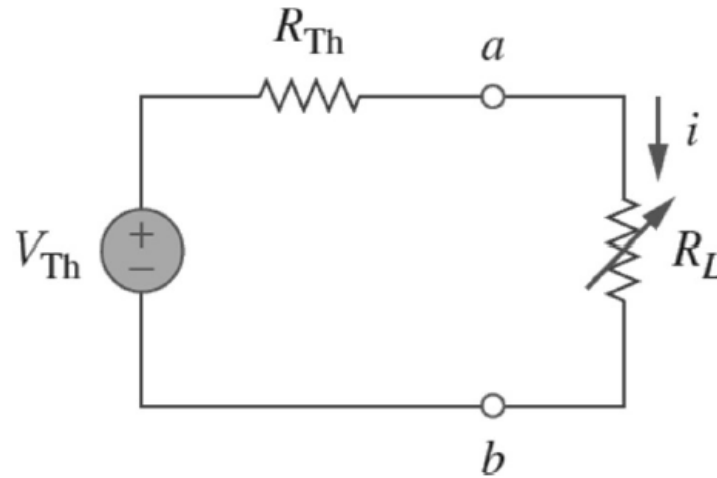
## Maximum Power Transfer (cont...)


- The Thevenin equivalent is useful in finding the maximum power a linear circuit can deliver to a load.
- We assume that we can adjust the load resistance  $R_L$ .
- Let the entire circuit is replaced by its Thevenin equivalent except for the load, as shown in the figure below.



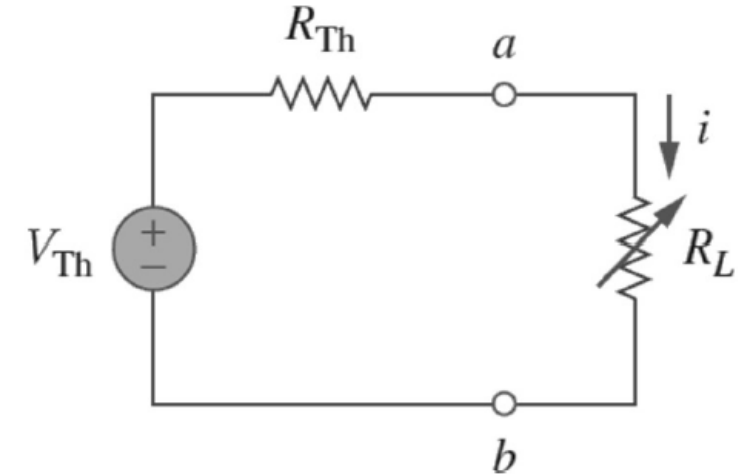
## Maximum Power Transfer (Cont...)

- The power delivered to the load in this scenario is

$$p = i^2 R_L = \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$



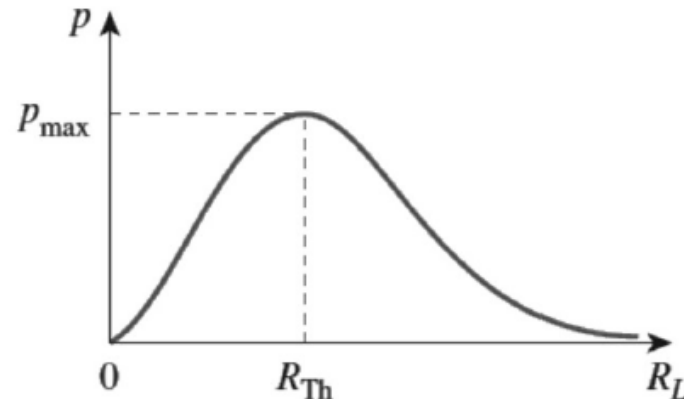- For any given circuit the values of  $R_{Th}$  and  $V_{Th}$  are fixed.
- By varying the load resistance  $R_L$ , the power delivered to the load varies as shown in the figure below.



## Maximum Power Transfer (Cont...)

- We notice that the power delivered is small for small and large values of  $R_L$  but is maximum for some value of  $R_L$  in between 0 and  $\infty$ .
- We will show that maximum power occurs when the value of  $R_L = R_{Th}$ .
- This is known as the maximum power transfer theorem.
- Maximum power is transferred to the load when the load resistance equals the Thevenin's resistance as seen from the load.
- To prove maximum power transfer theorem, we differentiate  $p$ , as given in the following equation, with respect to  $R_L$  and set the result to 0.

$$p = i^2 R_L = \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$

## Maximum Power Transfer (Cont...)

$$p = i^2 R_L = \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$

- Differentiating

$$\begin{aligned} \frac{dp}{dR_L} &= \frac{V_{Th}^2 [(R_{Th} + R_L) - 2R_L]}{(R_{Th} + R_L)^3} \\ &= \frac{V_{Th}^2 [(R_{Th} + R_L) - 2R_L]}{(R_{Th} + R_L)^3} = 0 \end{aligned}$$

- Equating the numerator to 0

$$(R_{Th} + R_L) - 2R_L = 0 = R_{Th} - R_L$$

- Therefore,

$$R_{Th} = R_L$$

