

## Lecture-8

On

# INTRODUCTION TO ELECTRICAL ENGINEERING (ESO203)

- Impedance and Admittance.
- Effective or RMS Voltage, Current and power.

## Average Power (Cont...)

- Next, we consider two special cases.
- When  $\theta_v = \theta_i$ , we know that the voltage and the current are in phase.
- This is a purely resistive circuit, and the average power is given by,

$$P = \frac{1}{2} V_m I_m = \frac{1}{2} I_m^2 R$$

- This shows that a purely resistive load absorbs power at all times.
- When  $\theta_v - \theta_i = \pm 90^\circ$ , the circuit is a purely reactive circuit, and the average power is.

$$P = \frac{1}{2} V_m I_m \cos 90 = 0$$

- Thus, a purely reactive circuit absorbs no average power.

□ Example:

Find the instantaneous and average power absorbed by a passive linear circuit if it is excited by a source  $v(t) = 120 \cos(377t + 45^\circ)$  V and current in the circuit is  $i(t) = 10 \cos(377t - 10^\circ)$  A?

**Solution:** The instantaneous power is given by,

$$\begin{aligned} p(t) &= vi = 1200 \cos(377t + 45^\circ) \cos(377t - 10^\circ) \\ &= 600 \cos[(754t + 35^\circ) + \cos 55^\circ] \end{aligned}$$

The average power can be evaluated using:

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{1}{2} * 120 * 10 * \cos(45 - (-10)) = 344.2 \text{ W}$$

This is same as the constant part of  $p(t)$  above.

## Impedance and Admittance

- The voltage-current relation for the circuit elements is given by,

$$V = RI, \quad V = j\omega LI, \quad V = \frac{I}{j\omega C}$$

- The above equations can be rewritten in the terms of the ratio of phasor voltage to the phasor current as,

$$\frac{V}{I} = R, \quad \frac{V}{I} = j\omega L, \quad \frac{V}{I} = \frac{1}{j\omega C}$$

- From the above equations we obtain Ohm's law in phasor notation for any element as,

$$\frac{V}{I} = Z \quad \text{or} \quad V = ZI$$

- Here, **Z** is a frequency dependent quantity known as the impedance.

## Impedance and Admittance (cont...)

- The impedance  $\mathbf{Z}$  of a circuit is the ratio of the phasor voltage  $\mathbf{V}$  to the phasor current  $\mathbf{I}$ , measured in ohms ( $\Omega$ ).
- The impedance represents the opposition that the circuit exhibits to the flow of sinusoidal current.
- Although the impedance is the ratio of two phasors, it is not a phasor, because it does not correspond to a sinusoidally varying quantity.
- As a complex quantity, the impedance can be expressed in rectangular form as,

$$\mathbf{Z} = R + jX$$

- Here,  $R$ , the real part of  $\mathbf{Z}$ , is the resistance and  $X$ , the imaginary part of  $\mathbf{Z}$ , is the reactance.
- We say that the impedance is inductive when  $X$  is positive and the impedance is capacitive when  $X$  is negative.

## Impedance and Admittance (cont...)

- Thus, impedance  $\mathbf{Z} = R + jX$  is said to be inductive or lagging since current lags the voltage.
- Similarly, the impedance  $\mathbf{Z} = R - jX$  is said to be capacitive or leading since current leads the voltage.
- As a complex quantity, the impedance can be expressed in polar form as,  $\mathbf{Z} = |\mathbf{Z}| \angle \theta$ .
- Therefore, impedance can be expressed as,

$$\mathbf{Z} = R + jX = |\mathbf{Z}| \angle \theta$$

$$|\mathbf{Z}| = \sqrt{R^2 + X^2}$$

$$R = |\mathbf{Z}| \cos \theta$$

$$\theta = \tan^{-1} \left( \frac{X}{R} \right)$$

$$X = |\mathbf{Z}| \sin \theta$$

## Impedance and Admittance (cont...)

- It is sometimes convenient to use reciprocal of the impedance in calculations.
- This quantity is known as the admittance and is measured in siemens (S).
- It is expressed mathematically as,

$$Y = \frac{1}{Z} = \frac{I}{V} = G + jB$$

- Here,  $G$ , the real part of  $Y$ , is the conductance and  $B$ , the imaginary part of  $Y$ , is called the susceptance.






$$G + jB = \frac{1}{R + jX} = \frac{R - jX}{R^2 + X^2}$$

- Therefore,

$$G = \frac{R}{R^2 + X^2}, B = -\frac{X}{R^2 + X^2}$$

## Impedance and Admittance (cont...)

□ Find  $Z_{ab}$ ?

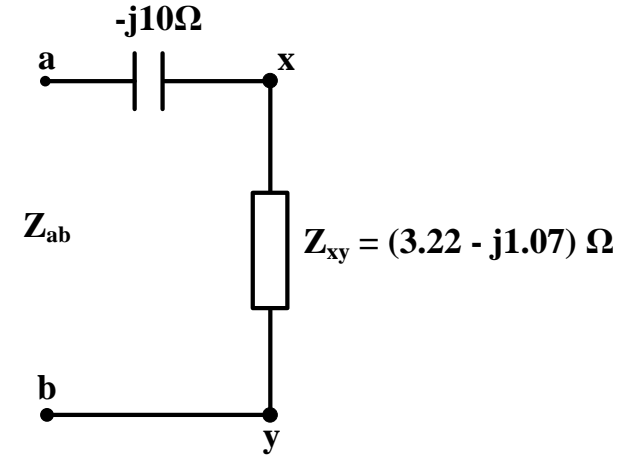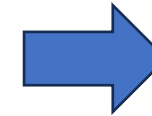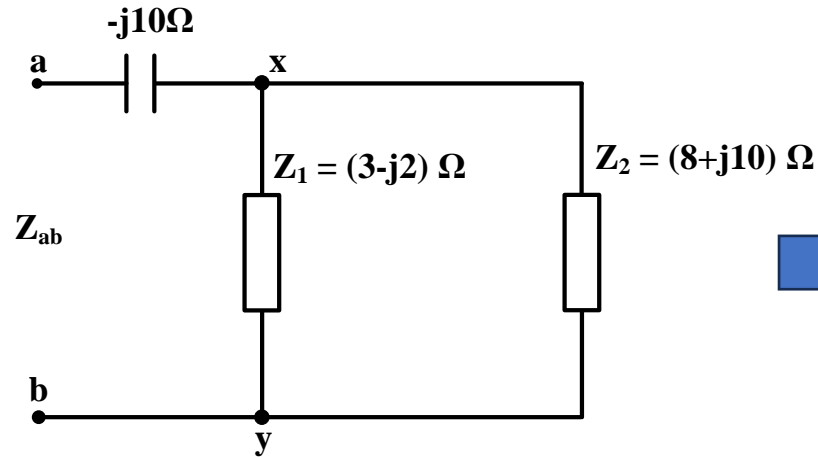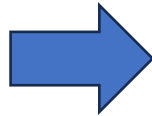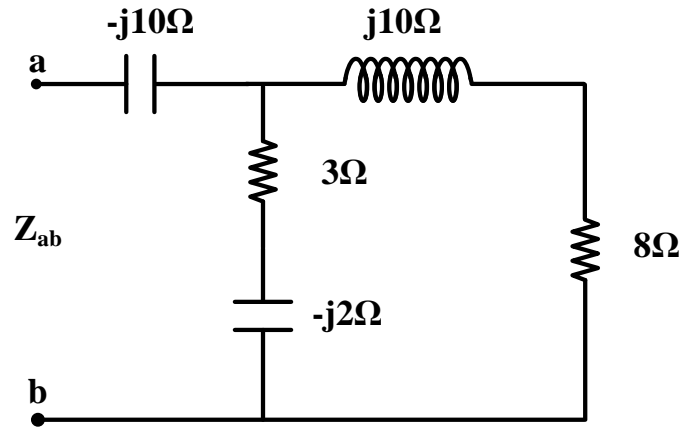



$$Z_{xy} = \frac{(3 - j2) \times (8 + j10)}{(3 - j2) + (8 + j10)} = 3.22 - j1.07$$

$$Z_{ab} = -j10 + 3.22 - j1.07 = 3.22 - j11.07$$


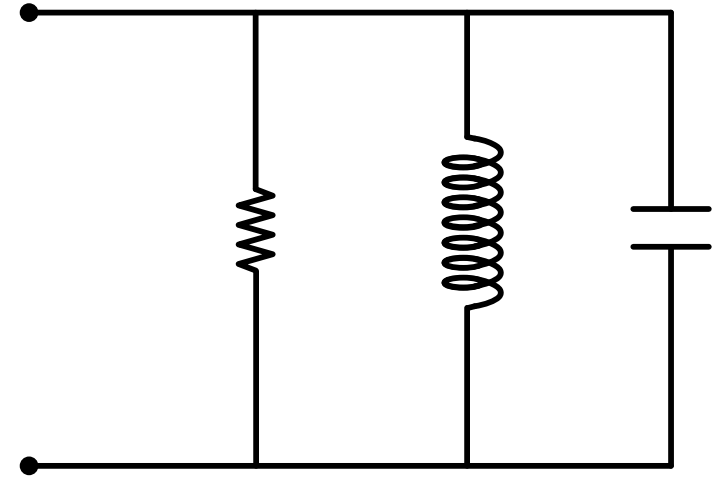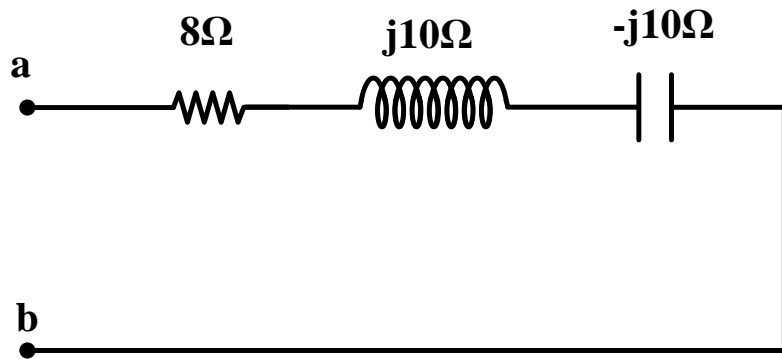
## Impedance and Admittance (cont...)

□ Draw the phasor diagram for the circuits shown below:



## Effective or RMS Voltage and Current

- The idea of effective value arises from the need to measure the effectiveness of a sinusoidal voltage or current source in delivering power to a resistive load.
- The effective value of a periodic current is the equivalent **DC** current that delivers the same average power to the resistor as the periodic current does.
- The average power absorbed by a resistor in an **AC** circuit is given by,

$$P = \frac{1}{T} \int_0^T p(t) dt$$

$$P = \frac{1}{T} \int_0^T i^2 R dt$$

## Effective or RMS Voltage and Current (cont...)

- The average power absorbed by a resistor in **DC** circuit is given by,

$$P = I_{eff}^2 R$$

- From the above two equations we can observe that,

$$I_{eff} = \sqrt{\frac{1}{T} \int_0^T i^2 dt}$$

$$\therefore P = \frac{1}{T} \int_0^T i^2 R dt$$

- The effective value of voltage can be found out in a similar way as,

$$V_{eff} = \sqrt{\frac{1}{T} \int_0^T v^2 dt}$$

## Effective or RMS Voltage and Current (cont...)

- For the sinusoid  $v(t) = V_m \cos \omega t$ :

$$V_{eff} = \sqrt{\frac{1}{T} \int_0^T V_m^2 \cos^2 \omega t dt} = \sqrt{\frac{V_m^2}{T} \int_0^T \frac{1}{2} (1 + \cos(2\omega t)) dt}$$

## Effective or RMS Voltage and Current (cont...)

- The effective value is the square root of the mean (or average) of the square of the periodic signal. Thus, the effective value is often known as the root-mean-square value, or rms value for short.
- Therefore, for the sinusoid  $v(t) = V_m \cos \omega t$ , the rms value is given by,

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V_m^2 \cos^2 \omega t dt} = \sqrt{\frac{V_m^2}{T} \int_0^T \frac{1}{2} (1 + \cos(2\omega t)) dt} = \frac{V_m}{\sqrt{2}}$$

- For the sinusoid  $i(t) = I_m \cos \omega t$ ,

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

- Please note that the above relationship holds only for **sinusoidal signals**.

## RMS Power

- We know that the average power absorbed by a circuit under sinusoidal excitation can be expressed as,

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

- This can be alternately written as,

$$P = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos(\theta_v - \theta_i) = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$$

- Similarly, the average power absorbed by a resistor can be written as,


$$P = \frac{1}{2} V_m I_m = \frac{1}{2} I_m^2 R = I_{rms}^2 R = \frac{V_{rms}^2}{R}$$

## RMS Power (Cont...)

- When a sinusoidal voltage or current is specified, it is often in terms of its maximum (or peak) value or its rms value, since its **average value is zero**.
- The power industries specify phasor magnitudes in terms of their **rms values** rather than **peak values**.
- For instance, the **230 V** available at every household is the **rms value** of the voltage from the power company.
- It is convenient in power analysis to express voltage and current in their rms values.
- Also, analog voltmeters and ammeters are designed to read directly the **rms value** of **voltage** and **current**, respectively.

□ Example:

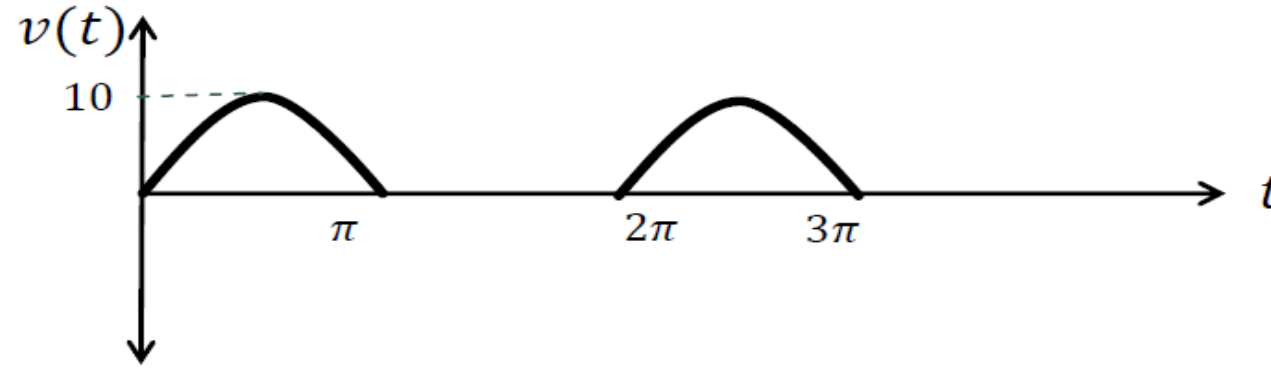Find the rms value of the half wave rectified sine wave  $v(t) = 10\sin t$  shown in the below figure? Also, find the average power dissipated in a  $10\ \Omega$  resistor?



**Solution:** The period of the voltage waveform is  $T = 2\pi$ , and

$$v(t) = \begin{cases} 10\sin t, & 0 < t < \pi \\ 0, & \pi < t < 2\pi \end{cases}$$

The rms value can be evaluated as:

$$V_{rms}^2 = \frac{1}{T} \int_0^T v^2 dt = \frac{1}{2\pi} \left[ \int_0^{\pi} (10\sin t)^2 dt + \int_{\pi}^{2\pi} 0 dt \right]$$



But  $\sin^2 (t) = \frac{1}{2} (1 - \cos 2t)$ . Hence,

$$\begin{aligned} V_{rms}^2 &= \frac{1}{2\pi} \int_0^\pi \frac{100}{2} (1 - \cos 2t) dt = \frac{50}{2\pi} \left( t - \frac{\sin 2t}{2} \right) \Bigg|_0^\pi \\ &= \frac{50}{2\pi} \left( \pi - \frac{1}{2} \sin 2\pi - 0 \right) = 25 \end{aligned}$$

$$V_{rms} = 5V$$

The average power absorbed is given by,

$$P = \frac{V_{rms}^2}{R} = \frac{25}{10} = 2.5W$$

□ Example:

Determine the rms value of the current waveform shown in figure below. If the current is passed through a  $2\ \Omega$  resistor, find the average power absorbed by the resistor?


**Solution:** The period of the waveform is  $T=4$ . Over a period, we can write the current waveform as,

$$i(t) = \begin{cases} 5t, & 0 < t < 2 \\ -10, & 2 < t < 4 \end{cases}$$

The rms value can be evaluated as:

$$\begin{aligned} I_{rms} &= \sqrt{\frac{1}{T} \int_0^T i^2 dt} = \sqrt{\frac{1}{4} \left[ \int_0^2 (5t)^2 dt + \int_2^4 (-10)^2 dt \right]} \\ &= \sqrt{\frac{1}{4} \left[ 25 \frac{t^3}{3} \Big|_0^2 + 100t \Big|_2^4 \right]} = \sqrt{\frac{1}{4} \left( \frac{200}{3} + 200 \right)} = 8.165 A \end{aligned}$$

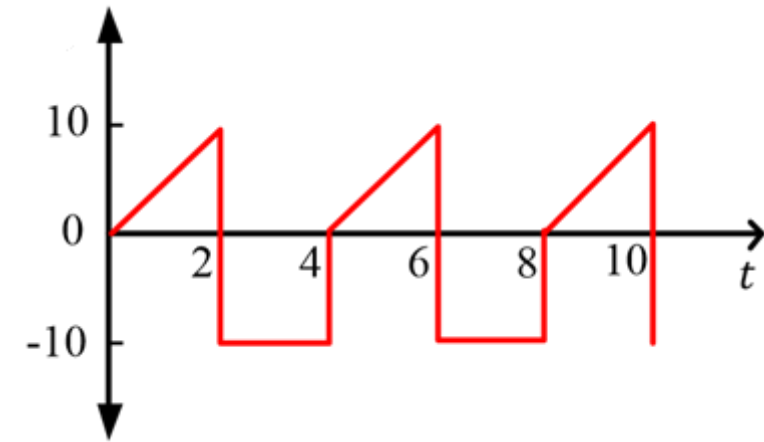The power absorbed by a  $2\ \Omega$  resistor is  $= I_{rms}^2 R = 133.3\text{ W}$



## Apparent Power and Power Factor

- Earlier, we derived that the average power absorbed by a circuit, excited by a sinusoidal signal, is expressed in terms of rms voltage and current as,

$$P = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos(\theta_v - \theta_i) = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$$

- The above equation can be rewritten as,

$$P = V_{rms} I_{rms} \cos(\theta_v - \theta_i) = S \cos(\theta_v - \theta_i)$$

- The quantity  $S$  is known as the apparent power and is defined as the product of rms voltage and current.

## Apparent Power and Power Factor (Cont...)

- The apparent power is so called because it seems apparent that the power should be the voltage-current product, by analogy with **DC** resistive circuits.
- It is measured in volt-amperes or **VA** to distinguish it from the **average or real power**, which is measured in **watts**.
- From the previous expression, it can be observed that the apparent power needs to be multiplied by a **factor** to compute the real or average power.
- This **factor** is known as power factor and is expressed mathematically as,

$$P = V_{rms} I_{rms} \cos(\theta_v - \theta_i) = S \cos(\theta_v - \theta_i)$$

$$Pf = \frac{P}{S} = \cos(\theta_v - \theta_i)$$

## Apparent Power and Power Factor (Cont...)

- The value of **pf** ranges between **zero** and **unity**.
- For a purely resistive load, the voltage and current are in phase, so that  $\theta_v - \theta_i = 0$  and  **$pf = 1$** .
- This implies that the **apparent power** is equal to the **average power**.
- For a purely reactive load,  $\theta_v - \theta_i = 90^\circ$  and  **$pf = 0$** .
- In this case the average power is zero.
- In between these two extreme cases, **pf** is said to be leading or lagging.
- Leading power factor means that current leads voltage, which implies a **capacitive load**.
- Lagging power factor means that current lags voltage, implying an **inductive load**.

$$P = V_{rms} I_{rms} \cos(\theta_v - \theta_i) = S \cos(\theta_v - \theta_i)$$

□ **Example:**

A series connected load draws a current  $i(t)=4 \cos(100\pi t + 10^\circ)\text{A}$  when the applied voltage is  $v(t) = 120 \cos(100\pi t - 20^\circ)\text{V}$ . Find the apparent power and power factor of the load. Determine the element values that form the load.

**Solution:** The apparent power is given by,

$$S = V_{rms} I_{rms} = \frac{120}{\sqrt{2}} * \frac{4}{\sqrt{2}} = 240 \text{VA}$$

The power factor can be evaluated using:

$$pf = \cos(\theta_v - \theta_i) = \cos(-20-10) = 0.866$$

The power factor is leading as the current leads the voltage.

$$v(t) = 120 \cos(100\pi t - 20^\circ) \text{V}$$

$$i(t) = 4 \cos(100\pi t + 10^\circ) \text{A}$$

The load impedance can be calculated as follows.

$$Z = \frac{V}{I} = \frac{120 \angle -20^\circ}{10 \angle 10^\circ} = 30 \angle -30^\circ = 25.98 - j15 \Omega$$

The load impedance  $\mathbf{Z}$  can therefore be modelled using a  $25.98 \Omega$  resistor in series with a capacitor whose impedance  $\mathbf{X}_c = -\frac{1}{\omega C} = -15$ .

Therefore,

$$C = \frac{1}{15\omega} = \frac{1}{15 * 100\pi} = 212.2 \mu\text{F}.$$

