

➤ Thus:

$$V_{id} = \frac{\sqrt{I_{d1}} - \sqrt{I_{d2}}}{\sqrt{\frac{k'_N}{2} \left(\frac{W}{L} \right)}} \quad (1)$$

➤ Also:

$$I_{d1} + I_{d2} = I_{SS} \quad (2)$$

➤ ***Solving Eqs.(1) and (2):***

$$I_{d1} = I_{SS}/2 + \xi \quad \text{and}$$

$$I_{d2} = I_{SS}/2 - \xi$$

$$\xi = \frac{k'_N}{4} \left(\frac{W}{L} \right) V_{id} \sqrt{\frac{4I_{SS}}{k'_N (W/L)} - V_{id}^2}$$

- For $V_{id} = 0$, $\xi = 0$, and $I_{d1} = I_{d2} = I_{SS}/2$
 - *Most preferred DC bias point of the circuit*
- For $V_{id} > 0$, $I_{d1} \uparrow$ and $I_{d2} \downarrow$
- For $V_{id} < 0$, $I_{d1} \downarrow$ and $I_{d2} \uparrow$
- But for both cases, the *sum of I_{d1} and I_{d2} remains constant at I_{SS}*
- *Linear Range* of this circuit is *defined by the values of V_{id} , which turns either M_1 or M_2 off*


- To find the **Linear Range**, use **Eq.(1)** and put either I_{d1} or I_{d2} equal to I_{SS} :

$$\begin{aligned}\Rightarrow V_{id} &= \pm \sqrt{\frac{2I_{SS}}{k'_N (W/L)}} = \pm \sqrt{2} \left(\sqrt{\frac{2I_{d1}}{k'_N (W/L)}} \right) \Big|_{V_{id}=0} \\ &= \pm \sqrt{2} (\Delta V) \Big|_{V_{id}=0}\end{aligned}$$

since for $V_{id} = 0$, $I_{SS} = 2I_{d1} = 2I_{d2}$

ΔV = Gate Overdrive for M_1/M_2 for $V_{id} = 0$

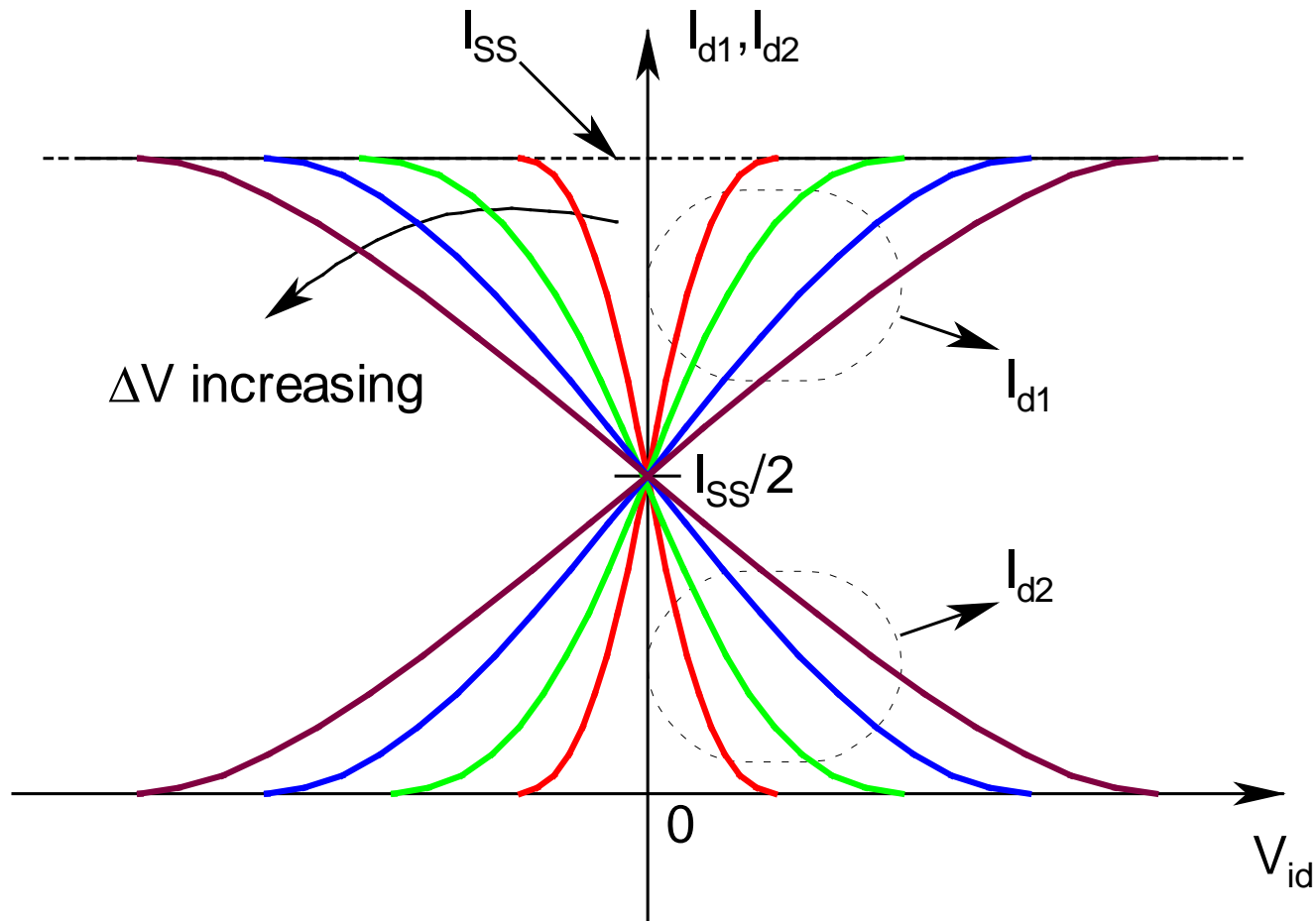- Thus, the Linear Range is a function of I_{SS} and $(W/L) \Rightarrow$ Tremendous flexibility!
- Recall: In **npn DA**, this Linear Range was $\pm 4V_T$, and depended only on temperature



The Current Transfer Characteristics of an NMOS DA

➤ *Differential Current:*

$$\partial I_d = I_{d1} - I_{d2} = 2\xi$$

➤ *Differential-Mode Output Voltage:*

$$\begin{aligned} V_{od} &= V_{o1} - V_{o2} = (V_{DD} - I_{d1}R_D) - (V_{DD} - I_{d2}R_D) \\ &= -(\partial I_d)R_D = -2\xi R_D \end{aligned}$$

➤ *Note:*

- When $V_{id} = 0$, $\xi = 0$, $\partial I_d = 0$, and $V_{od} = 0$
- *This is the perfect DC bias point*
- *No need for interstage coupling capacitor*
- $I_{D1} = I_{D2} = I_{SS}/2$
- $V_{ID} = 0 \Rightarrow$ *Tie both gates to ground and use a negative power supply*

➤ ***ac Analysis:***

- *The procedure adopted for npn DA can be lifted verbatim*

➤ ***Differential-Mode Half-Circuit:***

Calculation of A_{dm} :

- *The common-source node is at ac ground (from symmetry)*


- ***Body is also at ac ground***

$$\Rightarrow v_{bs} = 0 \Rightarrow g_{mb} v_{bs} = 0$$

- ***Simple CS stage:***

$$\Rightarrow A_{dm} = v_{od}/v_{id} = -g_m R_D$$

$$g_m = k_N \Delta V$$

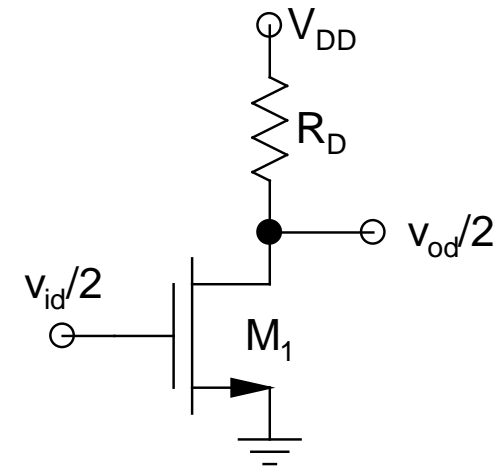

**Differential-Mode
Half-Circuit**

➤ **Common-Mode Half-Circuit:**

Calculation of A_{cm} :

- **$CS(D)$ stage**, but now **with body effect present**

$$\Rightarrow A_{cm} = v_{oc}/v_{ic}$$
$$= -g_m R_D / [1 + (g_m + g_{mb})2R_{SS}]$$


➤ Thus:

$$CMRR = 20\log_{10}(|A_{dm}/A_{cm}|)$$
$$\approx 20\log_{10}[2(g_m + g_{mb})R_{SS}]$$

➤ Again, **R_{SS} plays no role in**

A_{dm} , but **determines A_{cm} and CMRR**

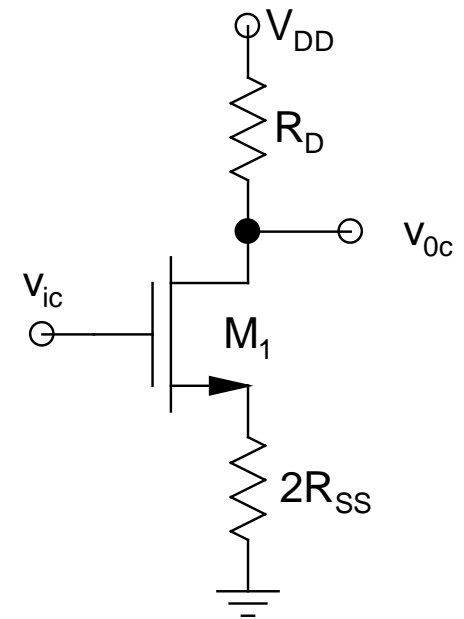\Rightarrow **A high value of R_{SS} highly desirable**



**Common-Mode
Half-Circuit**

- *Actual situation is not so rosy and hunky-dory*
- *The DA can become unbalanced if there is a mismatch between the devices and/or the resistors, and our analysis would fail!*
- Gives rise to *offset voltage* (*for both npn and NMOS DA*) and *offset current* (*only for npn DA*)
- *This mismatch is caused by technology and is totally random*
- *Fortunately, the effect is not that severe, since there are technological innovations to match devices and/or resistors*


Actively Loaded Amplifier Stages

- *Main Goal: To reduce usage of resistors as much as possible and use transistors instead as active load*
- Interesting to note that *transistors offer much higher resistance than physical resistors*, while *occupying much smaller chip area*

- *npn CE Stage With pnp Active Load:*

- Q_1 : *Driver*, Q_2 : *Load*
- Identify Q_2 - Q_3 as a *pnp current mirror*
- Q_2 - Q_3 constitute a *matched pair*
- *Neglecting base currents:*
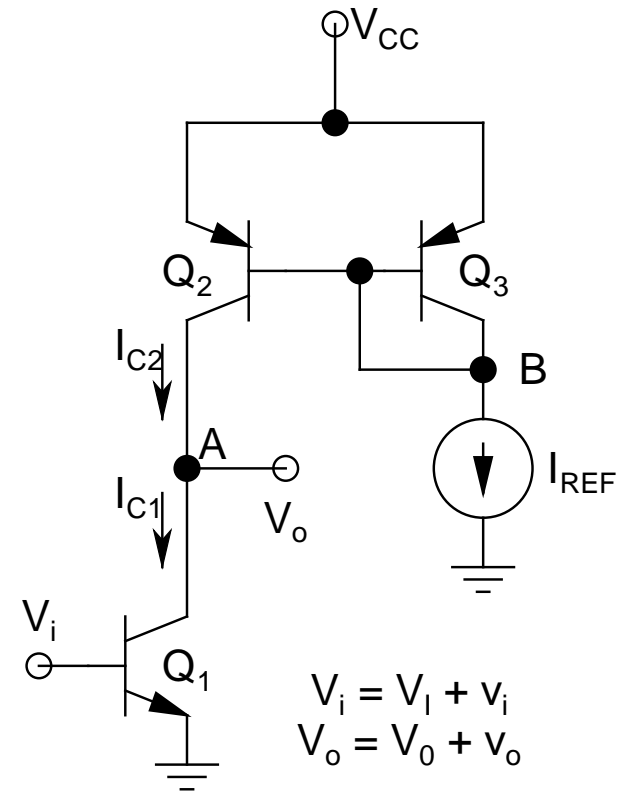
$$I_{C2} = I_{REF}$$
- *Biasing of the circuit is tricky*




Circuit Diagram

- There is a *trivial solution* of $I_{C1} = I_{C2} = 0$, and the *biasing collapses*
- For *proper biasing*, I_{C1} must equal I_{C2} ($= I_{REF}$)
- Thus, V_I should be properly adjusted, such that:


$$V_I = V_T \ln(I_{REF}/I_{S1})$$

- *Such a high precision in V_I may not be practically achievable*
- ⇒ *Use a resistor in series with V_I and self-consistently solve for the bias point*

➤ *ac Analysis:*

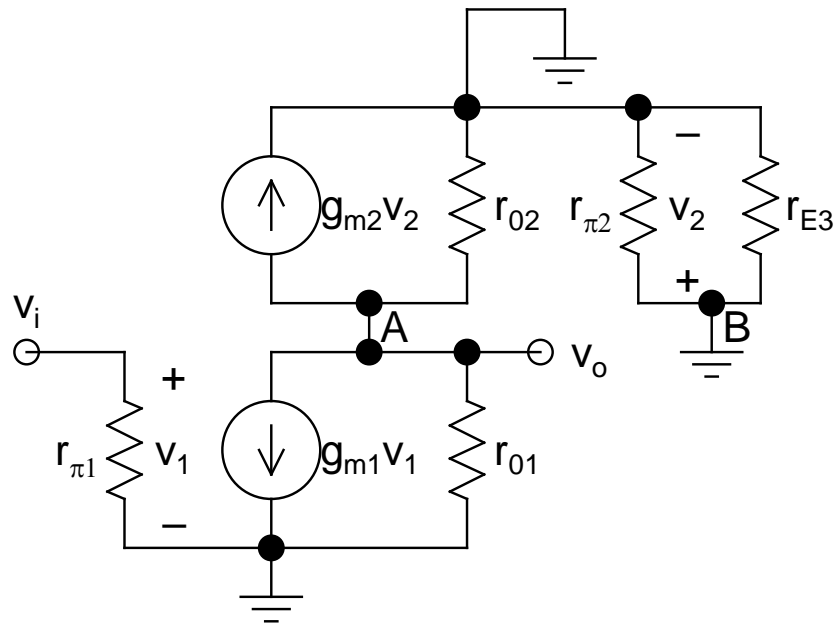

ac Midband Equivalent

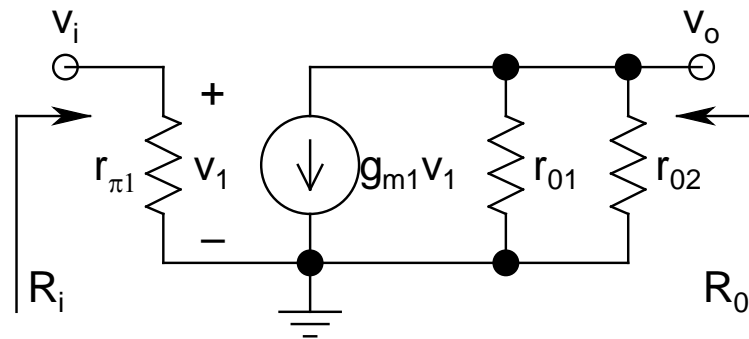

Simplified Equivalent

- First, note that Q_3 is *diode-connected* (*BC short*)
 \Rightarrow The *equivalent* of Q_3 is simply a *resistor* r_{E3}
- *Node B* is a peculiar one, and can be considered *both open and short*!
 - ❖ *Open because the current source I_{REF} is ideal*
 - ❖ *Short because the base of Q_2 - Q_3 is at a fixed DC potential, and thus ac ground*
- In either case, $v_2 = 0 \Rightarrow g_{m2}v_2$ *disappears*!
 \Rightarrow Leads to the *simplified equivalent*
- *By inspection*: $R_i = r_{\pi1}$ and $R_o = r_{o1} || r_{o2}$
- $A_v = v_o/v_i = -g_{m1}R_o = -1/(\eta_n + \eta_p)$
 $\eta_n = V_T/V_{AN}$ and $\eta_p = V_T/V_{AP}$
- *Enormously large gain possible*!