 


Complete I-V Characteristic



Note that the forward and reverse current scales are not same

Reverse Breakdown

- *2 Mechanisms:*

- *Zener*

- *Avalanche*

- *Zener:*


- *For junctions with both sides very heavily doped*

- *Thin depletion region*, through which carriers *tunnel through* (*quantum mechanical process*)

- *Typical $|V_{br}| < 3 V$*

- *Avalanche*:
 - *Classical breakdown process*
 - *At least one side must be lightly doped*
 - *Carrier multiplication* due to *impact ionization*
 - *Typical $|V_{br}| > 5\text{ V}$*
- For diodes having $|V_{br}|$ *in between 3 V and 5 V*, *a combination of these two processes*
- *Breakdowns* are generally *destructive*, unless the *current* is *controlled* by *external means*, e.g., by a *resistor*

Piece-Wise Linear (PWL) Model

 

Note: The forward and reverse current scales are not same

PWL Regions


- $0 \leq V_D \leq V_\gamma$: *Forward Blocking*
 - V_γ : *Cut-in Voltage* (~ 0.6 V for Si diodes)
 - $I_D = 0$
- $V_D \geq V_\gamma$: *Forward Conduction*
 - I_D increases linearly with V_D with an *inverse slope of r_F*
 - r_F : *Diode Forward Resistance* (~ 10 s of Ω)
 $= [dI_D/dV_D]^{-1}$

- Diodes under *forward bias* and for $V_D \geq V_\gamma$, offer *small resistance* (results from the *exponential* I-V characteristic)
- V_D negative and $0 \leq |V_D| \leq |V_{br}|$: *Reverse Blocking*
 - *$I_D = 0$*
- V_D negative and $|V_D| \geq |V_{br}|$: *Reverse Breakdown*
 - *$|I_D|$ increases linearly with $|V_D|$ with an inverse slope of r_Z*

➤ r_Z : **Zener Resistance** ($\sim 50\text{-}200\ \Omega$)
 $= [d|I_D|/d|V_D|]^{-1}$

- Diodes under **reverse bias** and for $|V_D| \geq |V_{br}|$, offer **small resistance**
 \Rightarrow **If current is not controlled by external means, then it may damage the device completely**
- Generally, diodes, unless they are to be operated in **breakdown mode**, e.g., in a **voltage regulator**, have **very high** $|V_{br}|$, typically of the order of **100s of V or more**

PWL Circuit Models

 

Forward Bias : V_D positive: (a) 0th order model,
 (b) 1st order model, (c) 2nd order model,
Reverse Bias : V_D negative: (d) 0th order model,
 Breakdown : (e) 1st order model, (f) 2nd order model
 (g) Corresponding piecewise linear models

0th-Order Model:
Ideal Diode

- Ex.: Find I_D and V_D , using: i) 0th order, ii) 1st order, and 2nd order diode models. [$V_\gamma = 0.6$ V, $r_F = 50$ Ω]

i) **0th order model:** $I_D = 2 / (1 \text{ k}\Omega) = 2 \text{ mA}$

$$V_D = 0 \text{ V}$$


ii) **1st order model:**

$$I_D = (2 - 0.6) / (1 \text{ k}\Omega) = 1.4 \text{ mA and } V_D = 0.6 \text{ V}$$

 iii) **2nd order model:**


$$I_D = (2 - 0.6) / (1 \text{ k}\Omega + 50 \text{ }\Omega) = 1.33 \text{ mA}$$

$$V_D = V_\gamma + I_D r_F = 0.667 \text{ V}$$



Finding the DC Operating Point

 - Known as the ***Q-Point*** (*Quiescent Point*)
- *Defined by (I_D, V_D)*
- *Two solution techniques:*
 - *Graphical Method* (*Using Load Line*)
 - *Iterative Method* (*Self-Consistent*)
- *Graphical Method:*
 - *Use diode I-V relation:* $I_D = I_0 \exp(V_D/V_T)$
 - *Use Load Line equation:* $I_D = (2 - V_D)/(1 \text{ k}\Omega)$
 - *Intersection point is the operating point*



V_{DQ} , I_{DQ} : Quiescent values of V_D , I_D
 $= 0.7$ V, 1.3 mA
 (obtained from iterative method using $I_0 = 3$ fA)

DC Quiescent Power Dissipation
 $= V_{DQ} \times I_{DQ} = 0.9$ mW

Graphical Method

The two *end points* of the *load line*:

1. $V_D = 0$: $I_D = 2/(1 \text{ k}) = 2$ mA
2. $I_D = 0$: $V_D = 2$ V