


**Department of Electrical Engineering  
Indian Institute of Technology, Kanpur**

**EE 210**

**Assignment #2**

**Assigned: 21.1.25**

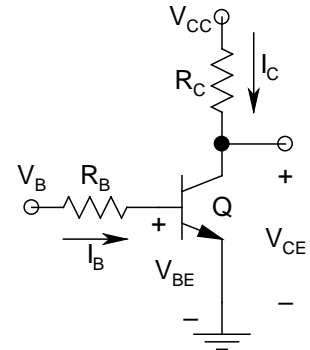1. Consider the BJT circuit shown in the figure. Determine the values of  $R_C$  and  $R_B$  that would make the transistor Q operate at the bias point of  $I_C = 0.5$  mA and  $V_{CE} = 3$  V. Assume  $V_{CC} = V_B = 5$  V, and  $\beta = 100$ . Keeping the value of  $R_B$  unchanged, determine the new value of  $R_C$  that would make the transistor operate at the onset of saturation. Now, assume that this value of  $R_C$  is further doubled. What is the new mode of operation of Q, and what is its degree of saturation (DoS) under this condition?



2. The total emitter-base capacitance  $C_\pi$  for an npn transistor under forward active mode of operation is measured to be 6 pF and 8 pF at dc bias current  $I_C$  of 1 mA and 2 mA respectively. Determine the zero bias emitter-base junction capacitance  $C_{je0}$  (using the thumb rule given in class for forward biased junctions), and the base transit time  $\tau_F$ , assuming that both of these are constants.
3. An integrated-circuit npn transistor has  $\beta_0 = 100$ , and  $r_0 = 50$  k $\Omega$  at  $I_C = 1$  mA. With  $V_{CB}$  held constant at 10 V,  $C_\mu = 0.15$  pF, and  $f_T = 600$  MHz and 1 GHz for  $I_C = 1$  mA and 10 mA respectively. Assume  $V_0 = 0.55$  V for all junctions, and  $C_{je}$  is constant in the forward-bias region. Use  $r_\mu = 5 \beta_0 r_0$ . Form the complete small-signal equivalent circuits for this transistor at  $I_C = 0.1$  mA, 1 mA, and 5 mA, all with  $V_{CB}$  held constant at 2 V.
4. An integrated-circuit npn transistor has the following parameters:  $\tau_F = 0.25$  nsec, small-signal short-circuit common-emitter current gain is 9 with  $I_C = 1$  mA at  $f = 50$  MHz,  $V_A = 40$  V,  $\beta_0 = 100$ , and  $C_\mu = 0.6$  pF at the bias voltage used. Determine all elements in the small-signal equivalent circuit at  $I_C = 2$  mA, assuming that  $V_{CB}$  is held constant (as that for  $I_C = 1$  mA), and  $\tau_F$  remains constant.
5. An npn transistor has the following specifications:  $\beta_0 = 100$ ,  $\tau_F = 26$  psec,  $C_{je} = 5$  pF, and  $C_\mu = 0.5$  pF at a particular bias point with  $I_C = 2$  mA. Determine the three important characteristic frequencies  $f_T$  (unity-gain cutoff frequency),  $f_\beta$  (beta-cutoff frequency), and  $f_\alpha$  (alpha-cutoff frequency) of the transistor at this bias point. Also, estimate  $f_{max}$  (absolute maximum operable frequency) of the transistor.