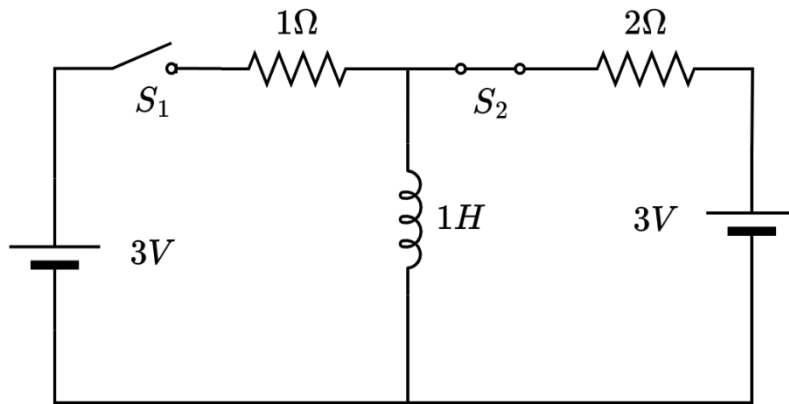


## ESO203 Tutorial 4 Solutions

### Question 1:

In the circuit shown, switch  $S_2$  has been closed for a long time. At time  $t = 0$ ,  $S_1$  is closed. At  $t = 0^+$ , the rate of change of current through the inductor, in amperes per second, is \_\_\_\_\_.




### Solution:

At  $t = 0^-$ ,  $S_1$  is open and  $S_2$  is closed.

Circuit in steady state is

$$i_L(0^-) = \frac{3}{2} = 1.5A$$

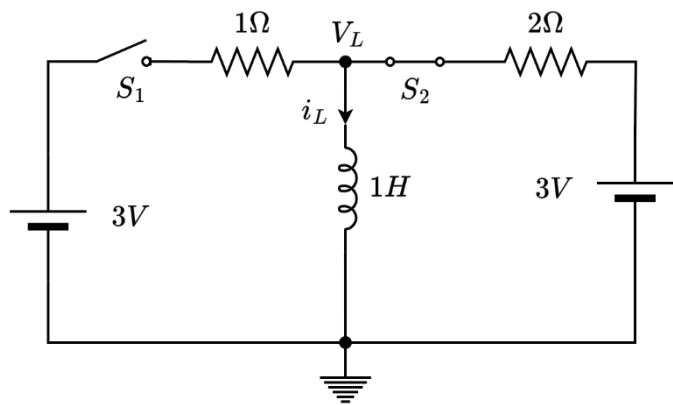


For  $t > 0$ ,  $S_1$  is closed and  $S_2$  is closed.

By KCL,

$$\frac{(V_L - 3)}{1} + \frac{(V_L - 3)}{2} + i_L = 0$$

$$2V_L - 6 + V_L - 3 + 2i_L = 0$$

$$V_L = 3 - \frac{2}{3}i_L$$

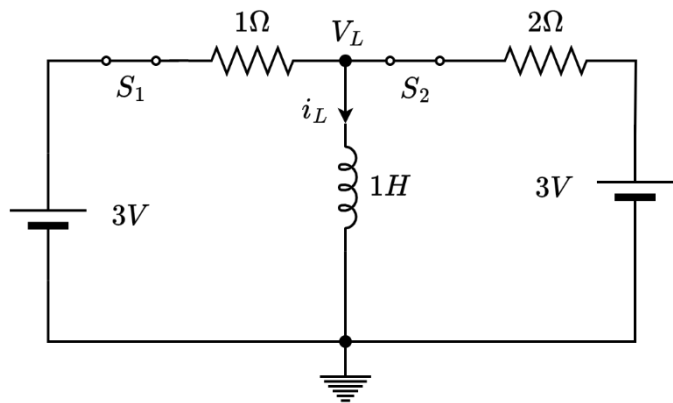

We know that

$$V_L = L \frac{di}{dt}$$


At  $t = 0^+$ ,

$$1 \frac{di}{dt} = 3 - \frac{2}{3}i_L(0^+) = 2 A/s$$

### Question 2:

The switch  $S_1$  has been closed for a long time.

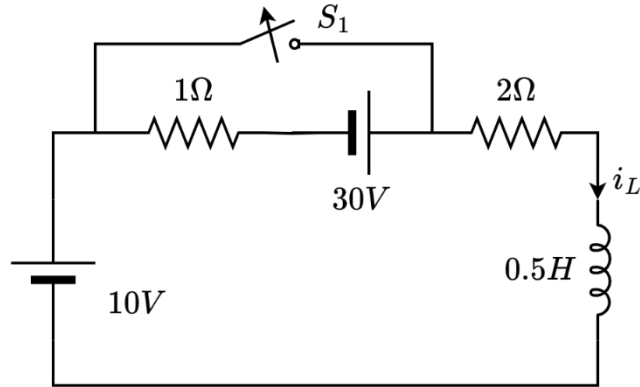- (a) Find  $i_L$  for  $t < 0$ .
- (b) Find  $i_L(t)$  for all  $t$  after the switch opens at  $t = 0$ .




### Solution:

- (a) For  $t < 0$ ,  $S_1$  is closed for long time. Inductor act as short circuit.  
The circuit in steady state is

$$i_L(0^-) = \frac{10}{2} = 5A$$

$$i_L(0^-) = 5u(-t) A$$

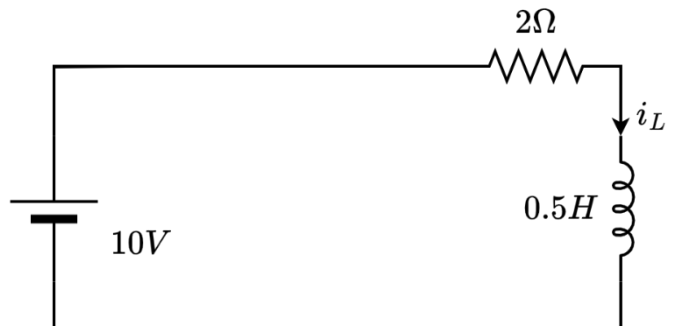


- (b) For  $t > 0$ ,  $S_1$  is open.  
Circuit is shown in figure.

Equivalent resistance is given by

$$R_{eq} = 1 + 2 = 5\Omega$$

The time constant is
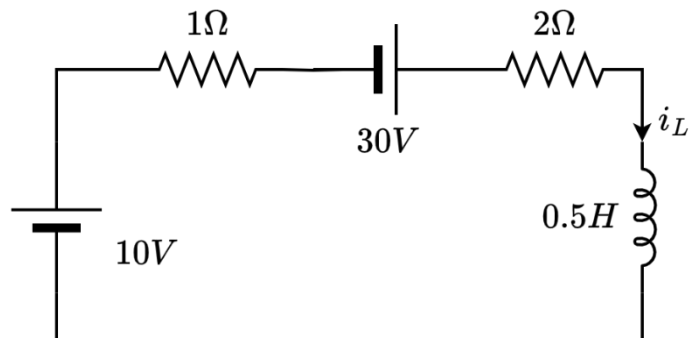
$$\tau = \frac{L}{R_{eq}} = \frac{0.5}{3} = 0.167 \text{ sec}$$



Steady state current is given by

$$i_L(\infty) = \frac{40}{3} = 13.33 A$$


By formula,

$$i_L(t) = i_L(\infty) + [i_L(0^+) - i_L(\infty)]e^{-t/\tau}$$

$$i_L(t) = 13.33 - 8.33e^{-6t}$$


**Question 3:**

In the circuit shown below if the maximum power is transferred to the  $R_L$ , then find  $R_L$ .

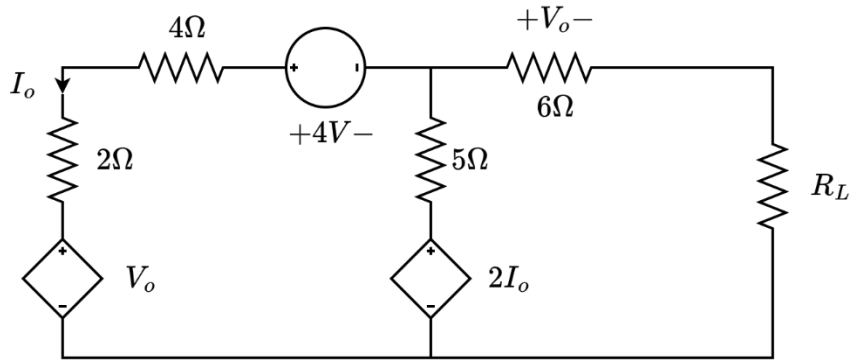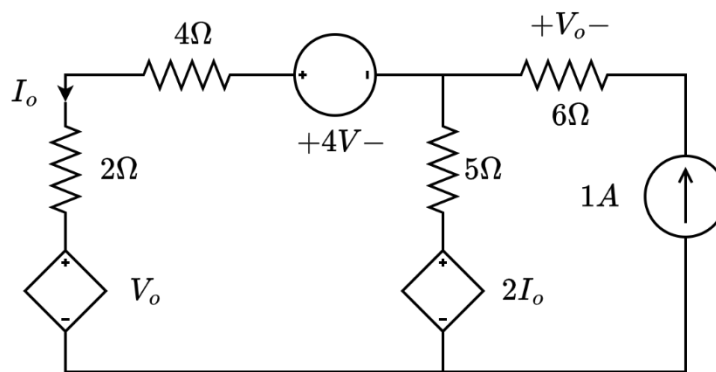**Solution:**

Resistance  $R_L$  is kept open and independent source is kept short.

A 1A current source replaced the  $R_L$ .



$$V_o = -6 \times 1 = -6V$$

Now, by KVL,

$$-2I_o + 5(I_o - 1) + 4I_o + 2I_o + V_o = 0$$

$$-9I_o + 11 = 0$$

$$I_o = \frac{11}{9} A$$

Now, let the voltage across  $R_L$  is  $V_L$ .

By KVL,

$$-V_L - V_o + 5(1 - I_o) + 2I_o = 0$$


$$V_L = 6 + 5 - 3I_o$$

$$V_L = \frac{22}{3} V$$

$$R_L = R_{th} = \frac{V_L}{1} = \frac{22}{3} = 7.33\Omega$$

**Question 4:**

Find the Thevenin's equivalent between terminals a and b of the circuit given in figure.

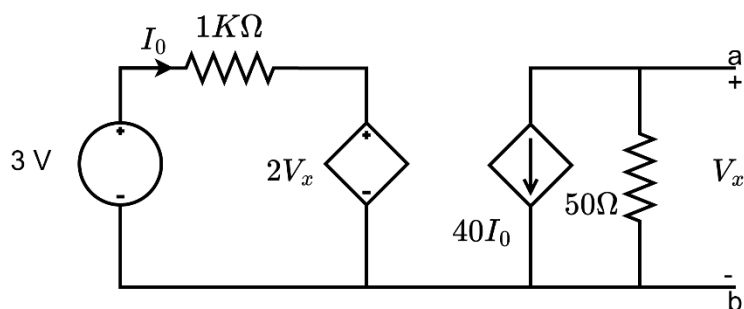**Solution:**

Apply the KVL on the right-hand side of the mesh,

$$V_x = V_{oc} = (-40 \times I_0) \times 50 = -2000I_0 \quad \dots (1)$$


Find out the current  $I_0$  from left-hand side loop,

$$I_0 = \frac{3 - 2V_x}{1000} = \frac{3 - 2V_{oc}}{1000} \quad \dots (2)$$

From equation (1) and (2), we get,


$$V_{oc} = -2000 \left( \frac{3 - 2V_{oc}}{1000} \right) \Rightarrow V_{oc} = 2 \text{ V}$$

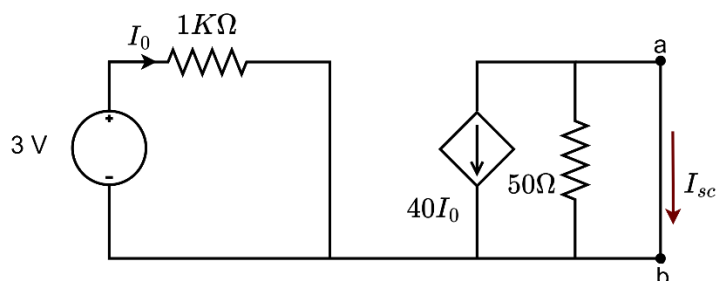To determine the Thevenin's impedance, we short-circuit the terminals a and b.




$$I_{sc} = -40 \times \left( \frac{3}{1000} \right) = -0.12$$

$$R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{0.2}{0.12} = 16.67 \Omega$$

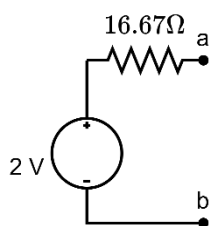

**Question 5:**

Determine the value of  $R_L$  that will draw the maximum power from the circuit. Find the maximum power.

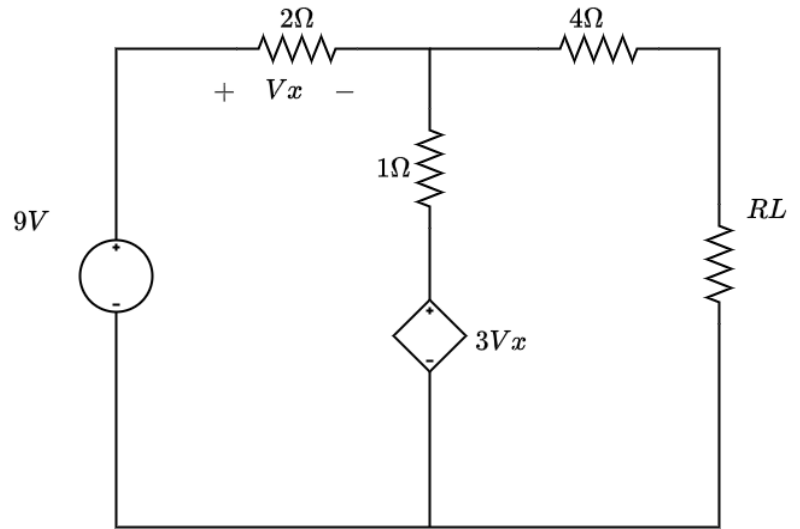**Solution:**

We need to find Thevenin resistance

$R_{th}$

$$R_{th} = \frac{V}{I}$$

Applying nodal analysis we get,

$$\frac{V_1}{2} + (V_1 - 3V_x) + \frac{V_1 - V}{4} = 0$$

$$V_x = -V_1$$

$$\frac{9}{2}V_1 = \frac{V - V_1}{4} = I$$

$$V_1 = \frac{2}{9}I$$

So, putting  $V_1$  in above equation, we get

$$R_{th} = \frac{V}{I} = 4.222\Omega$$

Using nodal analysis to find  $V_{th}$

$$\frac{V_1 - 9}{2} + \frac{V_1 - 3V_x}{1} = 0$$



$$4V_1 = \frac{9 - V_1}{2}$$

$$V_1 = 1V$$

$$V_{th} = V_1 = 1V$$

Maximum power transferred is when

$$R_L = R_{th} = 4.222\Omega$$

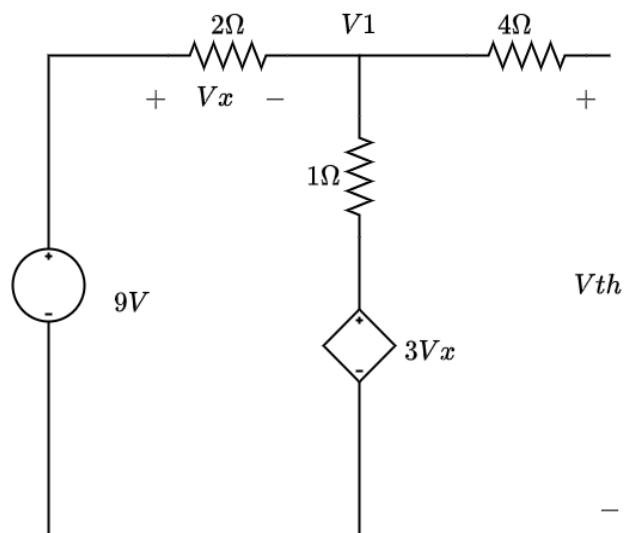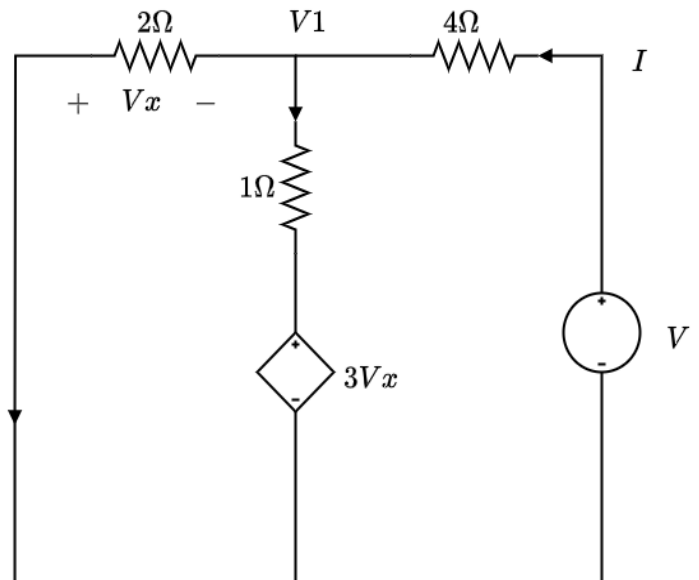


Maximum power transferred

$$P_{max} = \frac{V_{th}^2}{4R_L} = \frac{1^2}{4 * 4.22} = 59.24 \text{ mW}$$
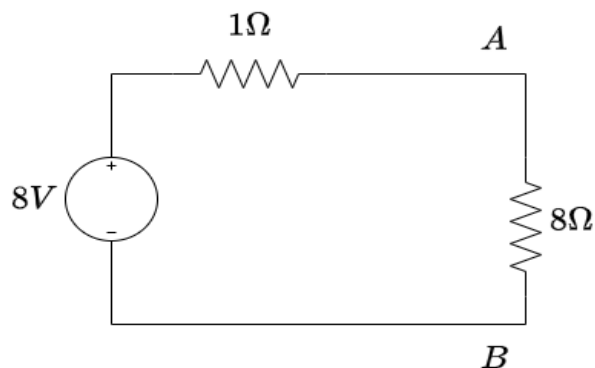
### Question 6:

The value of resistance between terminals A and B is changed to  $6\Omega$ . Find the compensation voltage.



### Solution:

Applying the KVL,

$$-8 + 1i + 8i = 0$$

$$9i = 8$$

$$i = \frac{8}{9} \text{ A}$$

$$\Delta R = 8\Omega - 6\Omega$$

$$\Delta R = 2\Omega$$


Compensation Voltage

$$V_c = -i(\Delta R)$$


$$V_c = -\frac{8}{9} * 2 = 1.77 \text{ V}$$
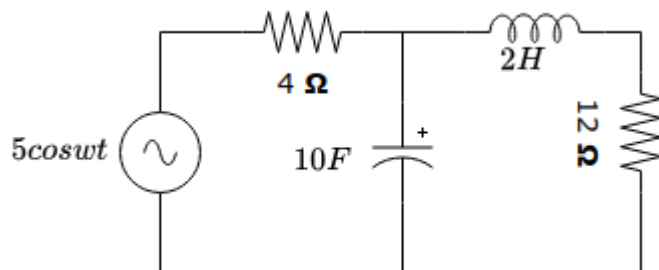
### Question 7:

For the given circuit, construct an exact dual circuit.



**Solution:**

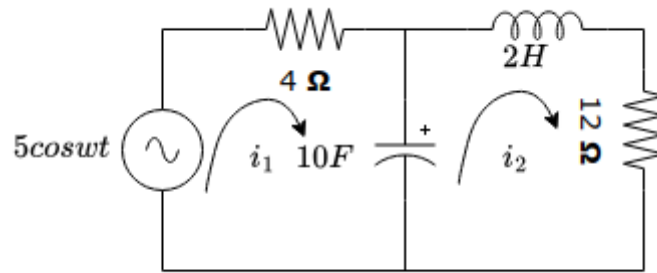

Assuming at  $t = 0$ , no voltage and no current across the capacitor and inductor.

Mesh equations in loop 1 & 2, we have.

$$5\cos(\omega t) - 4i_1 - \frac{1}{10} \int (i_1 - i_2) dt = 0 \quad (1)$$

$$12i_2 + 2 \frac{di_2}{dt} - \frac{1}{10} \int (i_1 - i_2) dt = 0 \quad \dots (2)$$

Represent these equations in nodal equations form.

$$5\cos(\omega t) - 4v_1 - \frac{1}{10} \int (v_1 - v_2) dt = 0 \quad \dots (3)$$

$$12v_2 + 2 \frac{dv_2}{dt} - \frac{1}{10} \int (v_1 - v_2) dt = 0 \quad \dots (4)$$

Now, we can construct dual circuit.

