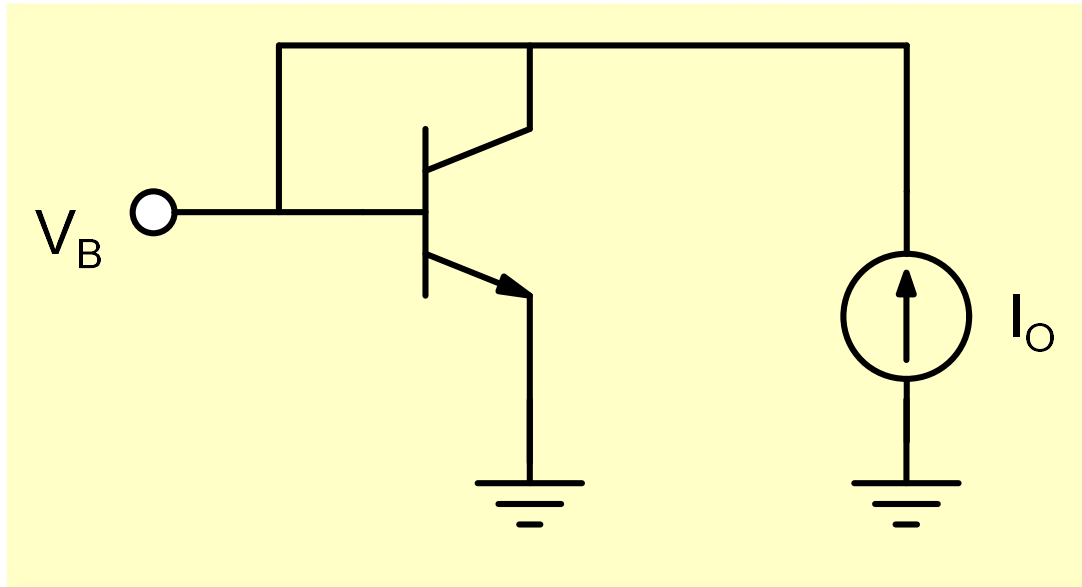


EE381: Exp-2

Design and Implementation of a Temperature Sensor

B. Mazhari
Dept. of EE, IIT Kanpur

Temperature measurement using a diode/BJT




$$I_O \sim I_C = I_S \times \exp\left(\frac{V_B}{V_T}\right)$$

$$V_B = \frac{kT}{q} \times \ln\left(\frac{I_O}{I_S}\right)$$

Basic principle




Complete Circuit

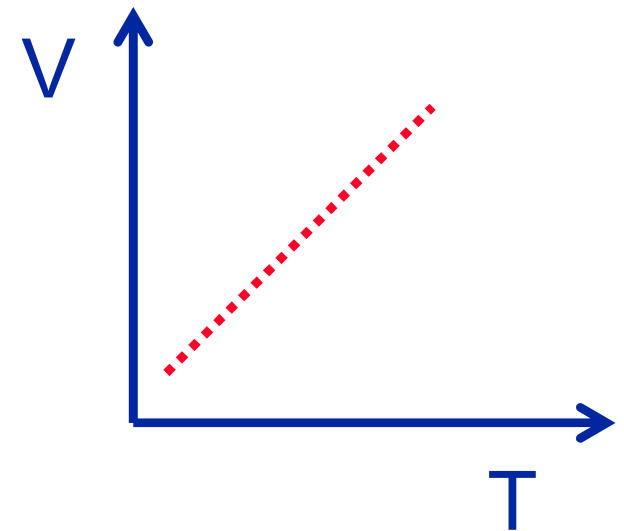


LM35 Precision Centigrade Temperature Sensors

1 Features


- Calibrated Directly in Celsius (Centigrade)
- Linear + 10-mV/°C Scale Factor
- 0.5°C Ensured Accuracy (at 25°C)
- Rated for Full -55°C to 150°C Range
- Suitable for Remote Applications
- Low-Cost Due to Wafer-Level Trimming
- Operates From 4 V to 30 V
- Less Than 60- μ A Current Drain
- Low Self-Heating, 0.08°C in Still Air
- Non-Linearity Only $\pm 1/4^\circ\text{C}$ Typical
- Low-Impedance Output, 0.1 Ω for 1-mA Load

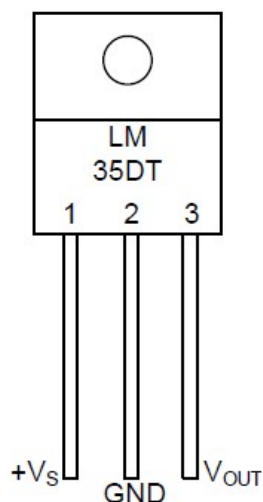

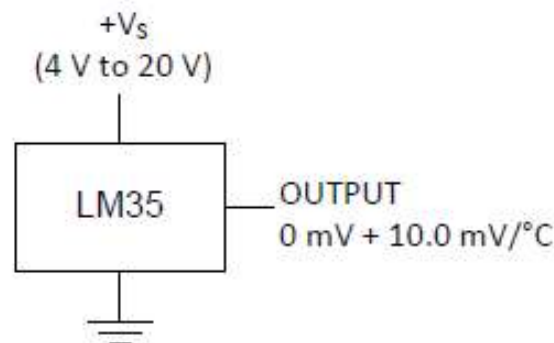
Basic Centigrade Temperature Sensor (2°C to 150°C)



Design Methodology

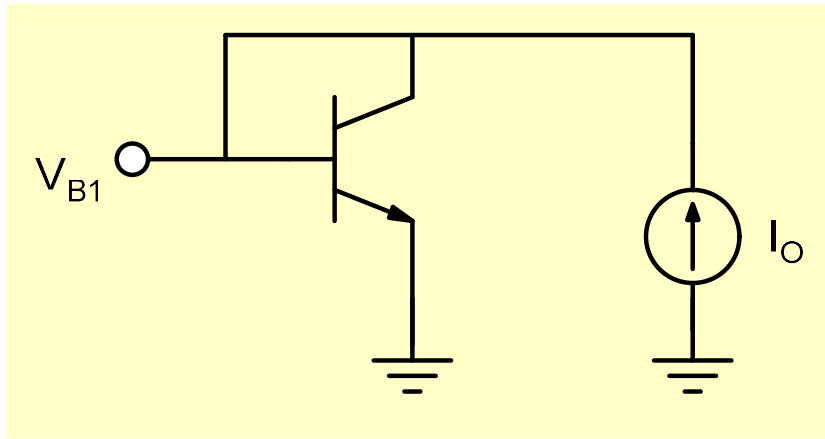
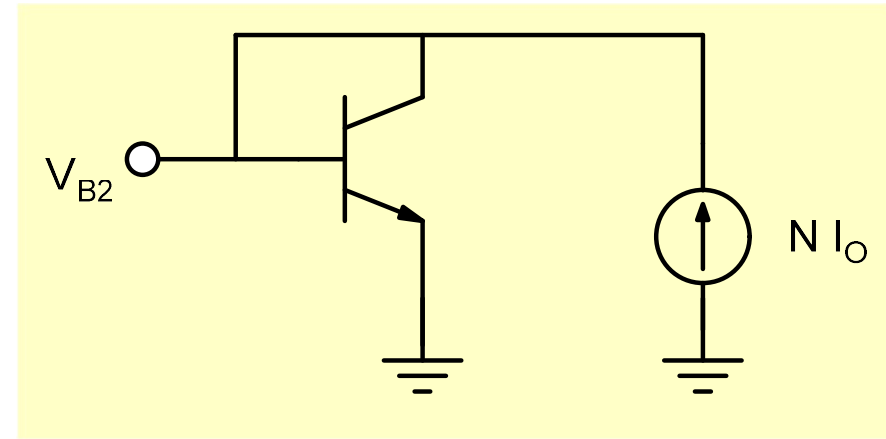
$$V_{B1} = \frac{kT}{q} \times \ln\left(\frac{I_O}{I_S}\right)$$





$$V_{B2} = \frac{kT}{q} \times \ln\left(\frac{N \times I_O}{I_S}\right)$$

$$V_{B2} - V_{B1} = \frac{kT}{q} \times \ln(N)$$

$$T(^{\circ}C) = \left(\frac{V_{B2} - V_{B1}}{\ln(N)}\right) \times \left(\frac{300}{.02588}\right) - 273$$

Example

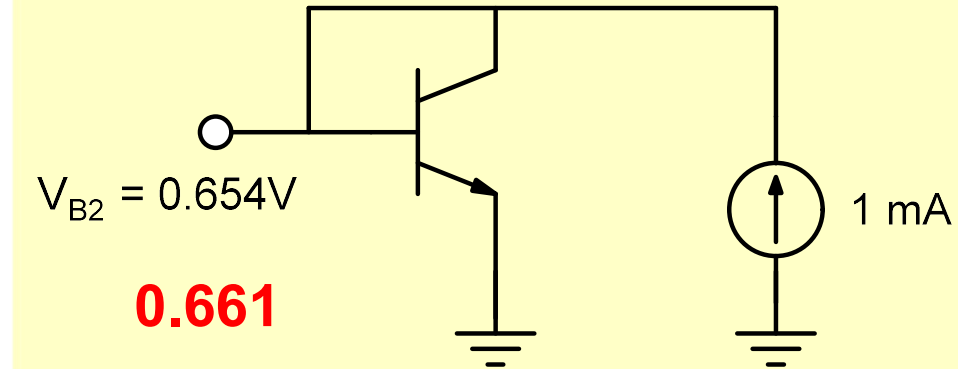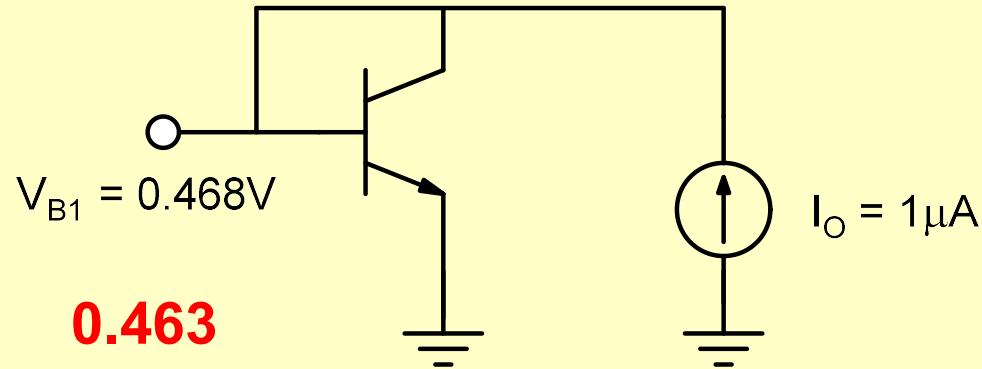

$$V_{B2} - V_{B1} = \frac{kT}{q} \times \ln(N)$$

$$0.187 = \frac{kT}{q} \times 6.908 \Rightarrow T = 313K$$

331.8K

6%

$$T(^{\circ}C) = \left(\frac{V_{B2} - V_{B1}}{\ln(N)} \right) \times \left(\frac{300}{.02588} \right) - 273 = 40^{\circ}C$$

58.8 °C

47%

Impact of 1% error in measurement


$$T(^{\circ}C) = \left(\frac{V_{B2} - V_{B1}}{\ln(N)} \right) \times \left(\frac{300}{.02588} \right) - 273$$

$$T(^{\circ}C) = \left(\frac{\Delta V_B}{\ln(N)} \right) \times \left(\frac{300}{.02588} \right) - 273$$




$$0.187V \rightarrow 40.8^{\circ}C$$

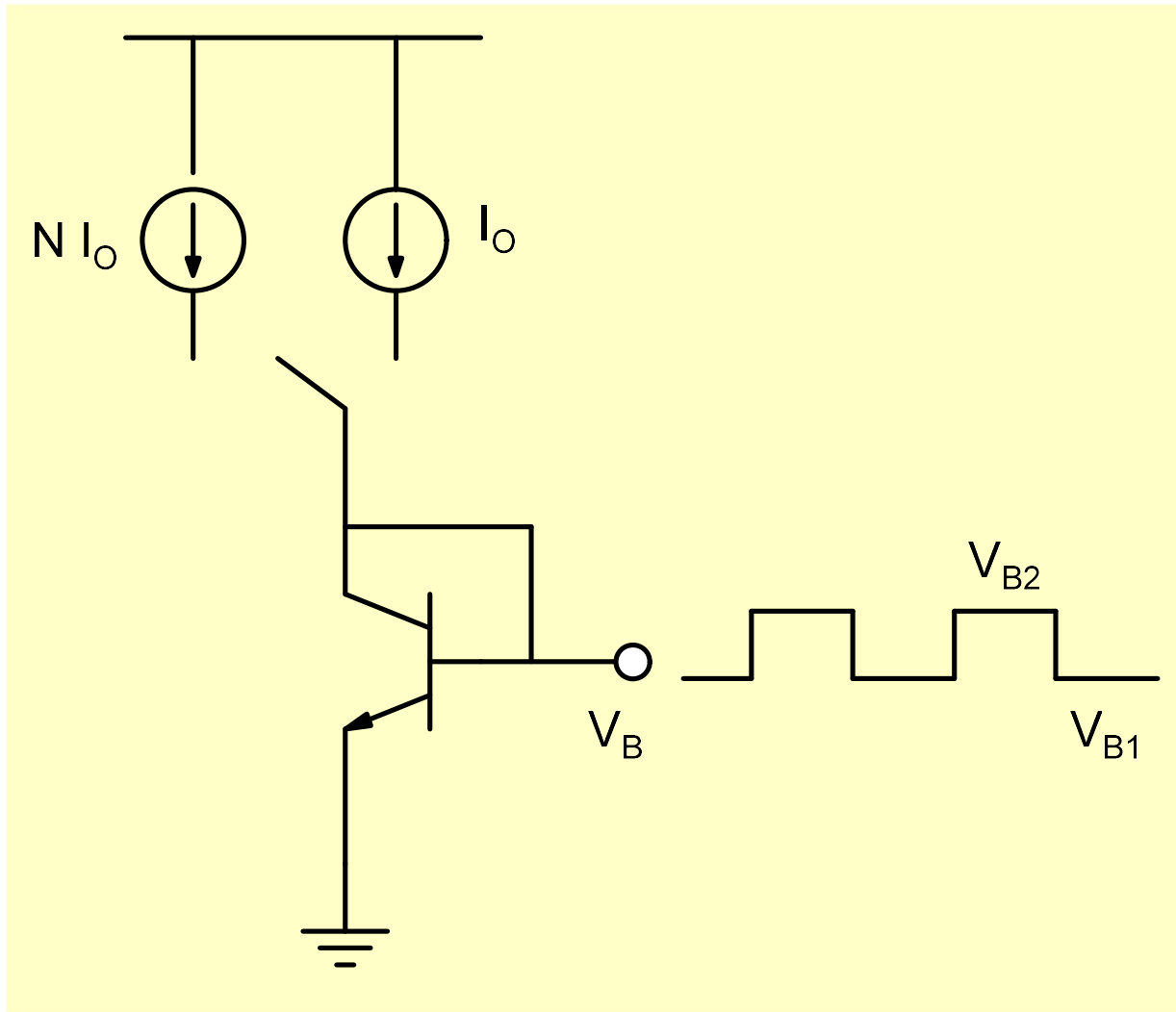
A 1% error in measurement of ΔV_B causes 7.7% error in T




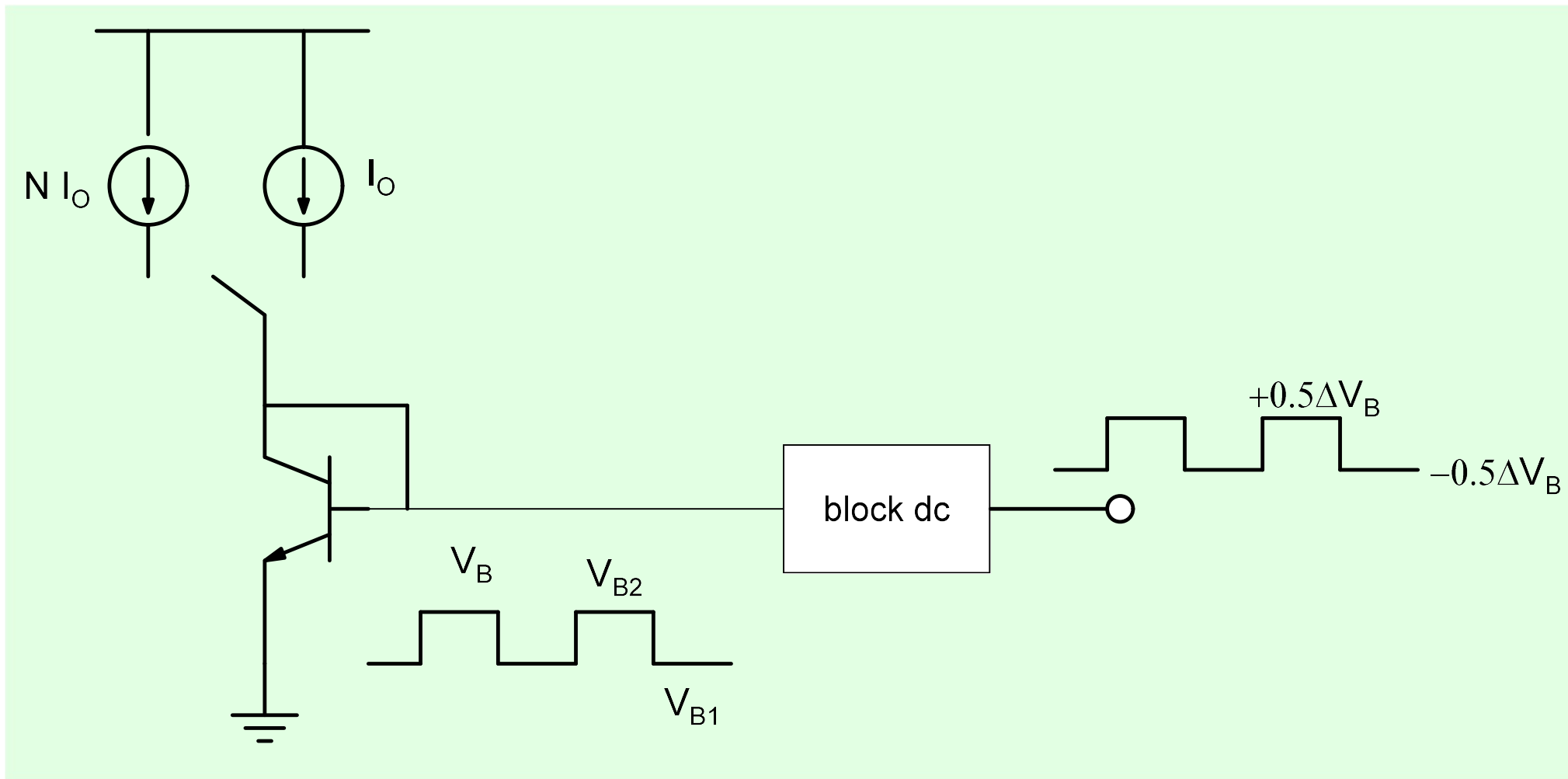
Switching current from I_o to $N \times I_o$ generates base voltage V_B








System Block diagram



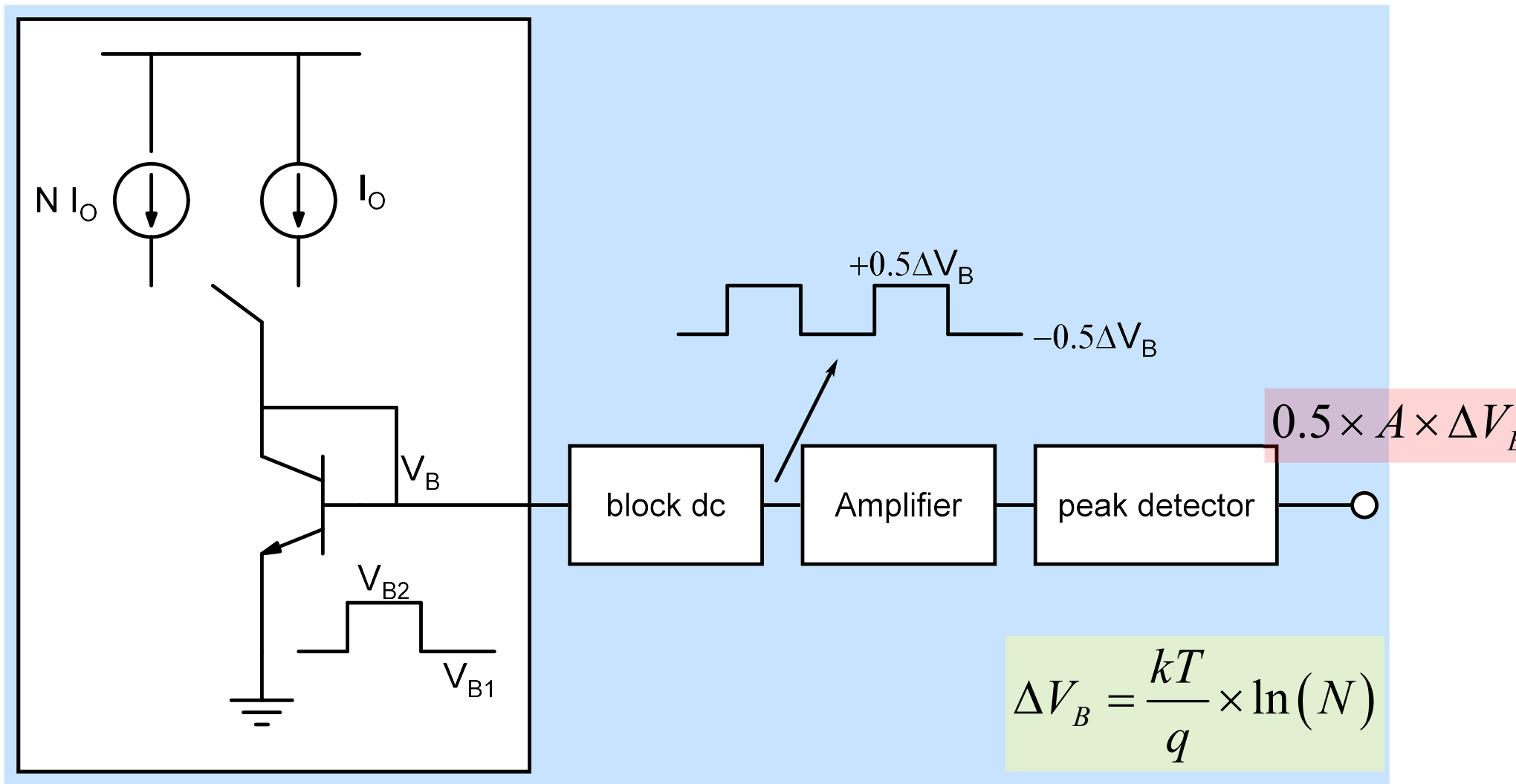


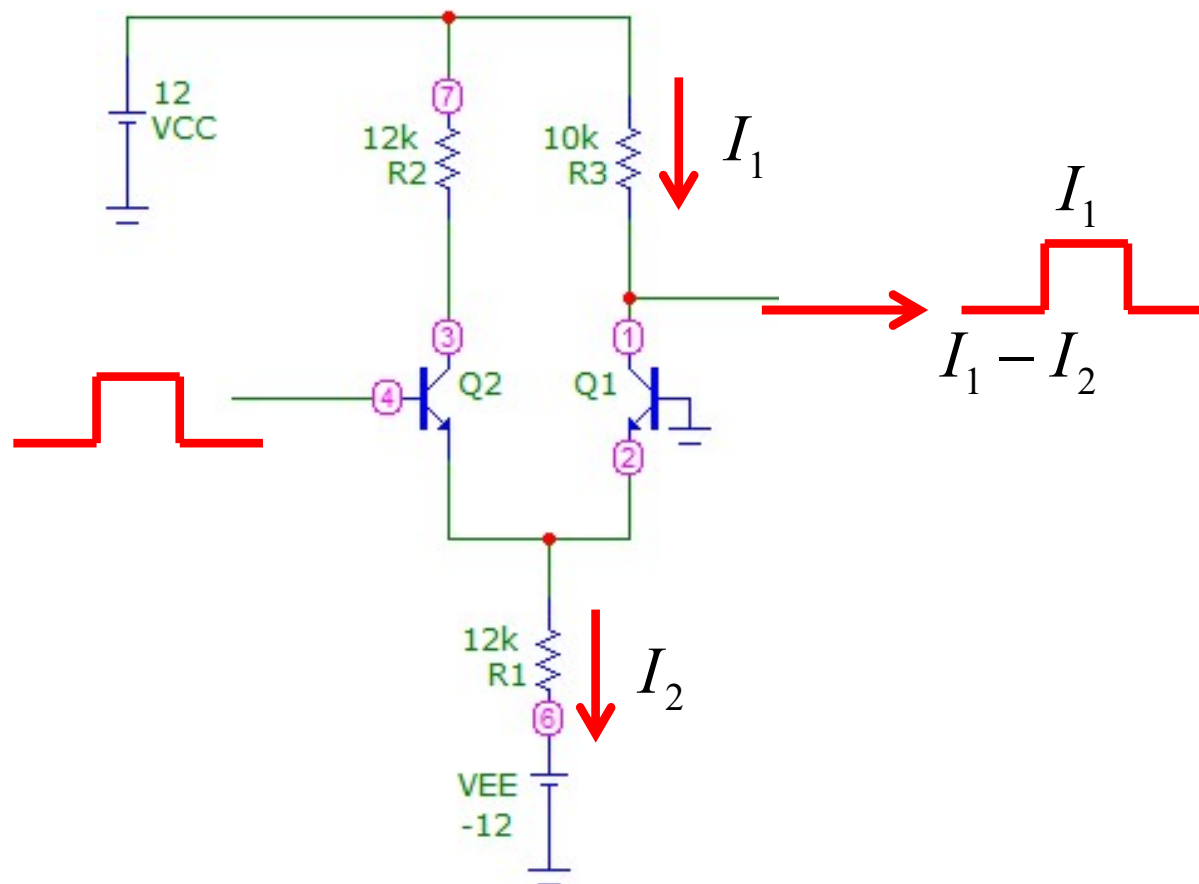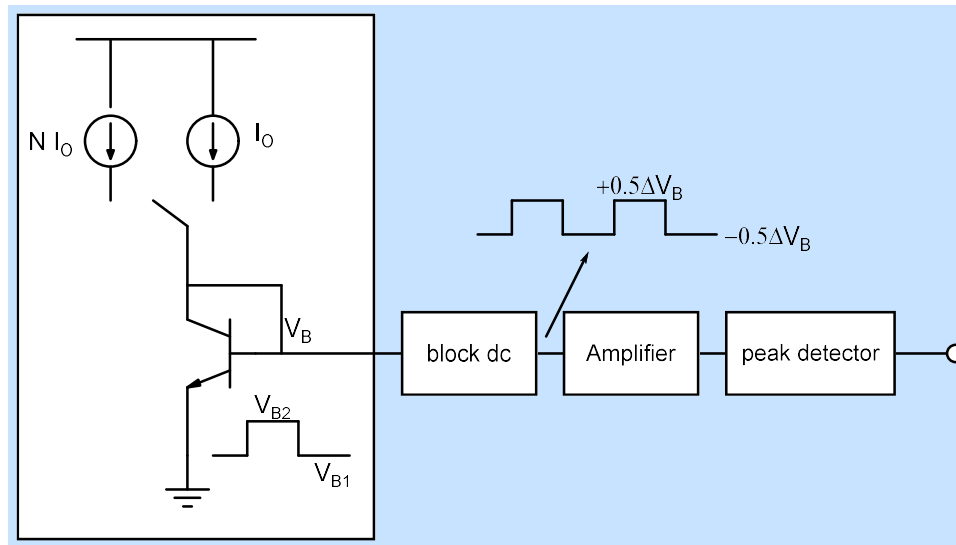The output is proportional to absolute value of temperature



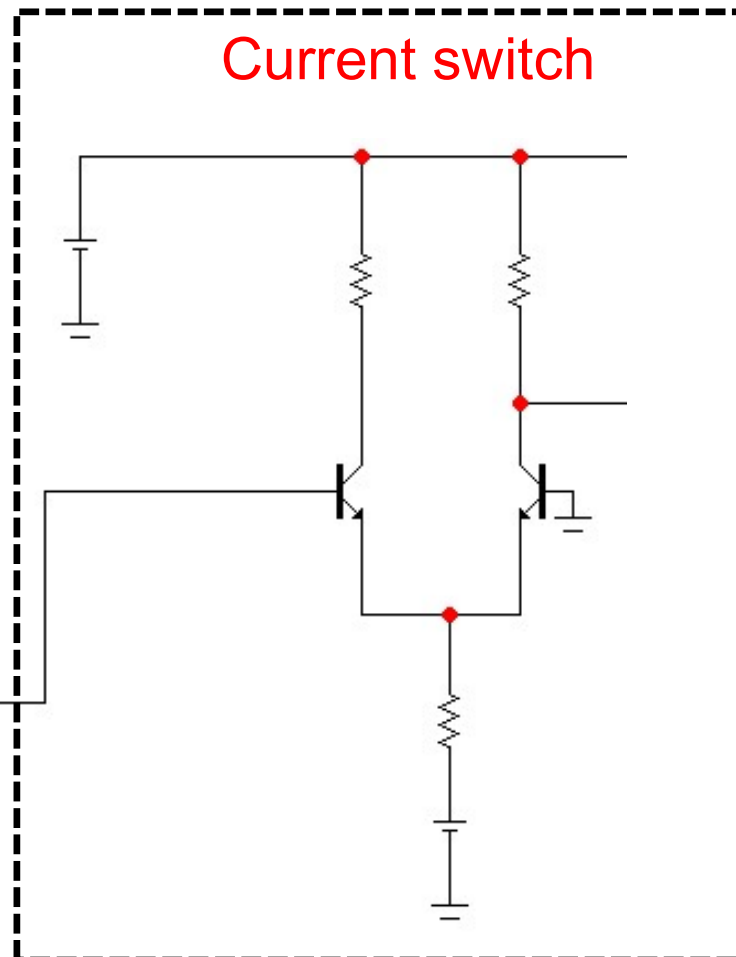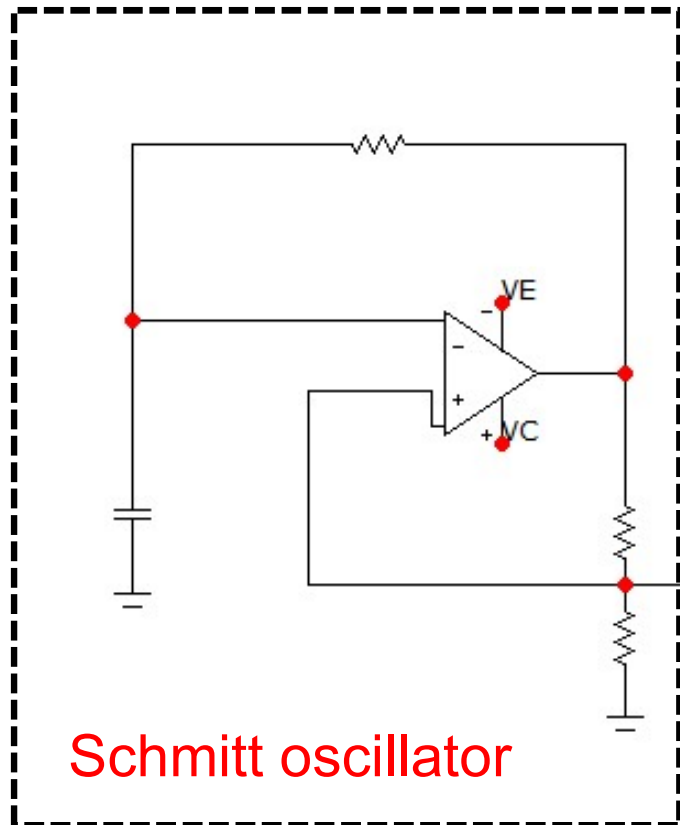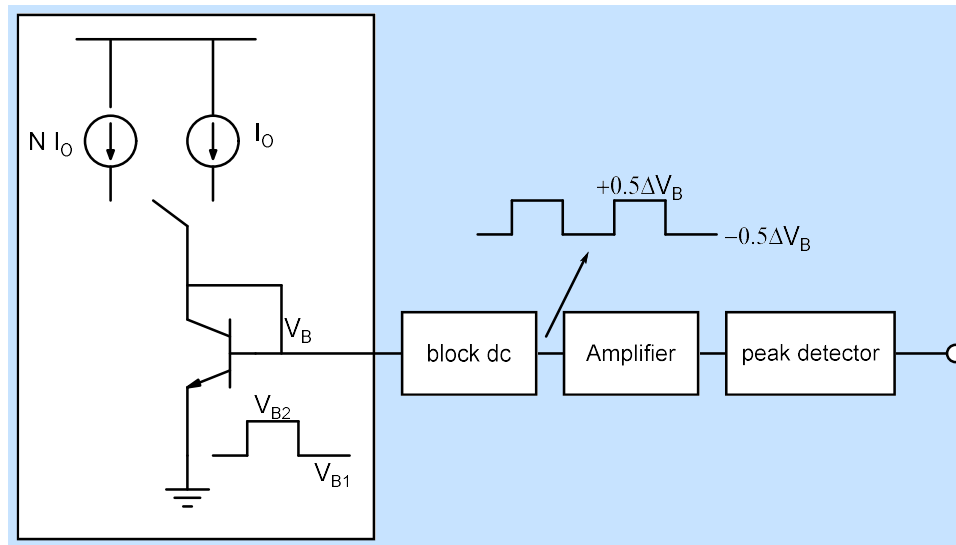

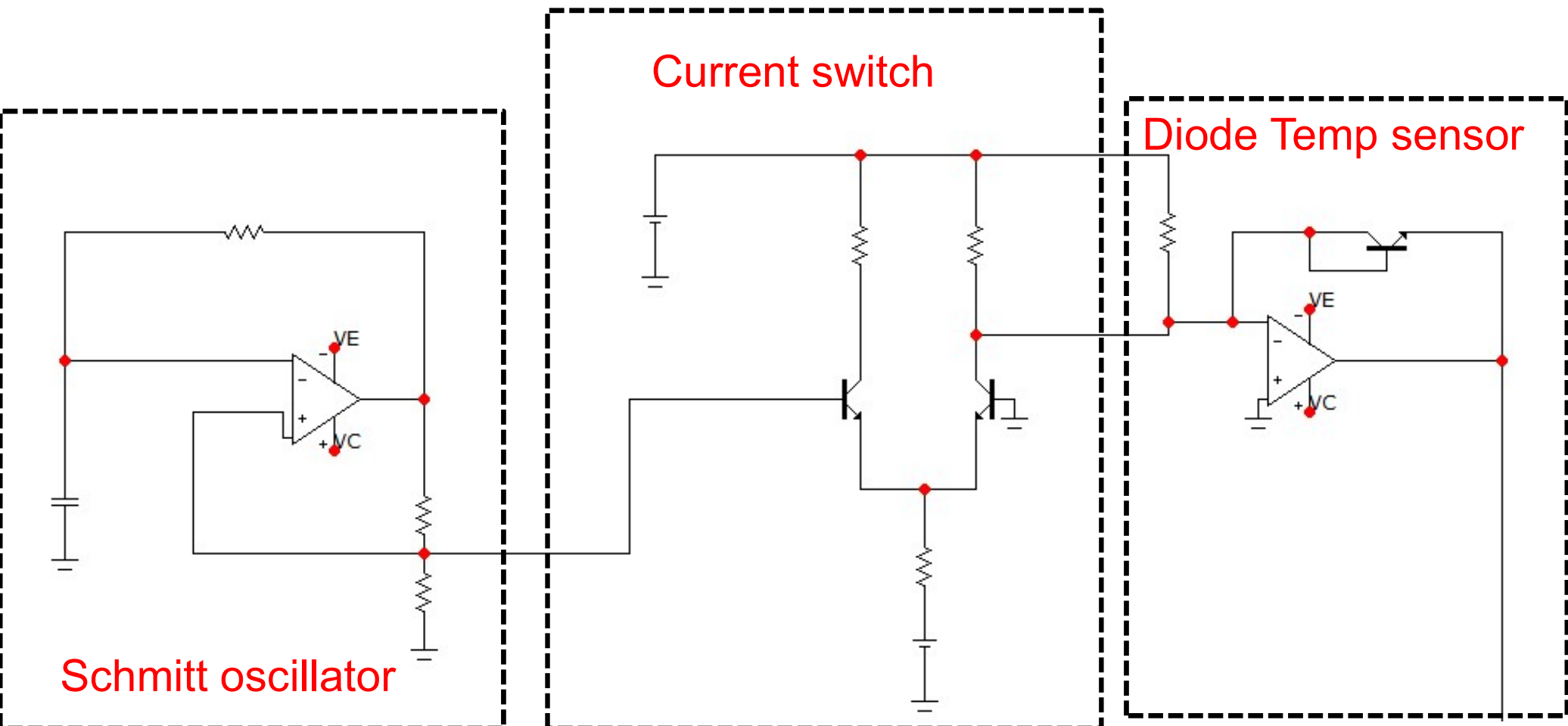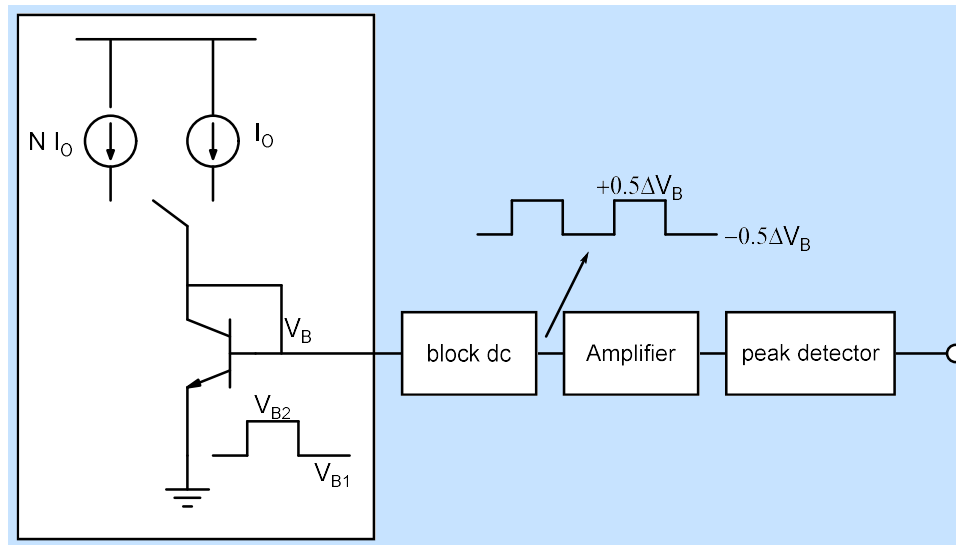

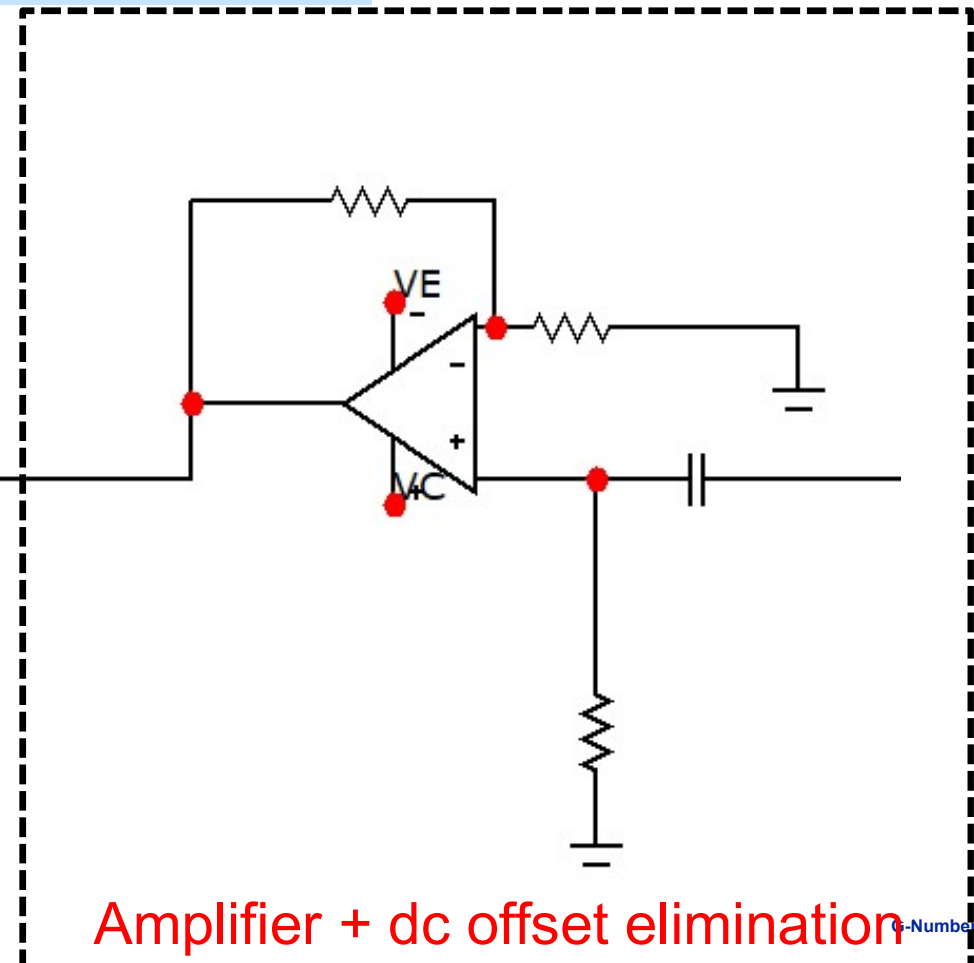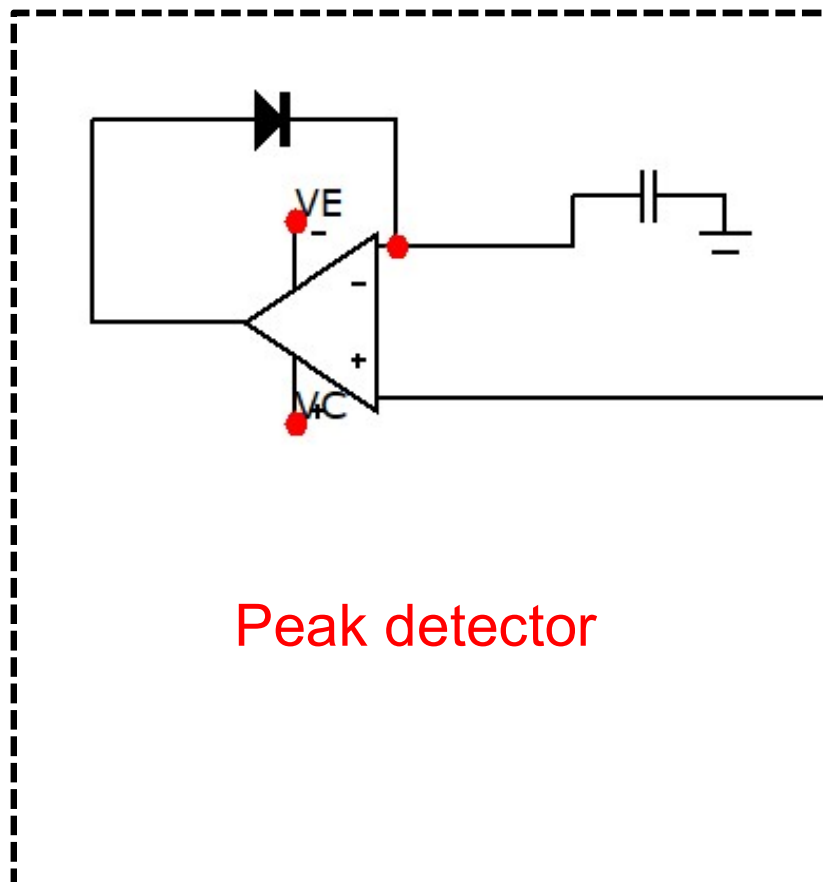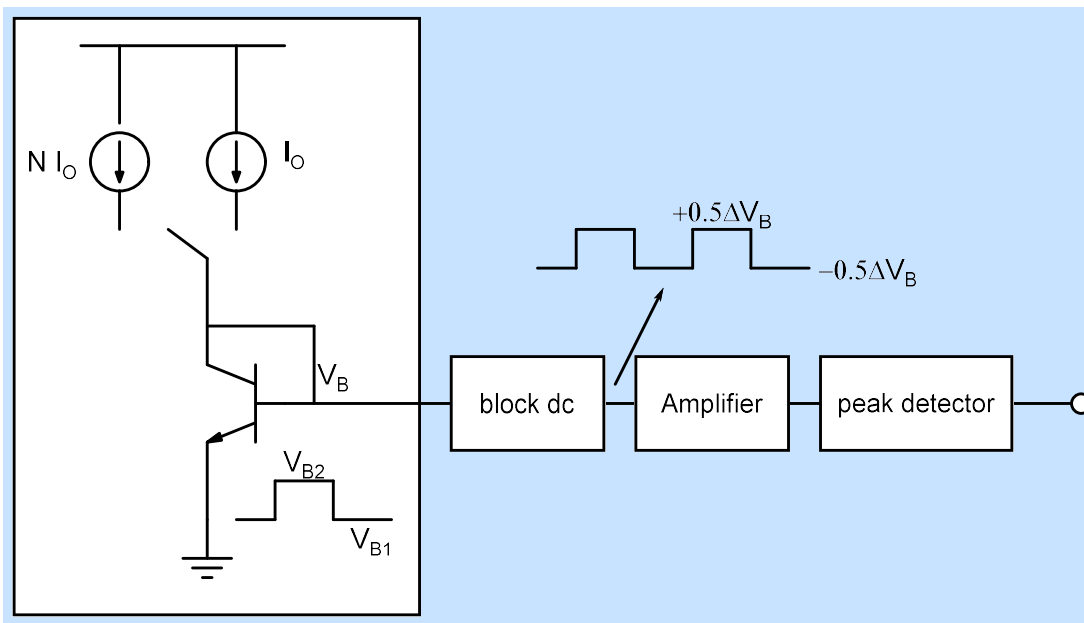

Complete circuit

