


Current Gain

- **Common-Emitter (CE) Current Gain:**
 - $\beta = I_C/I_B$ (*Higher the better!*)
- **Common-Base (CB) Current Gain:**
 - $\alpha = I_C/I_E$ (≤ 1 : *closer to 1, better it is!*)
- Also, $I_E = I_C + I_B$
 - $\alpha = \beta/(\beta + 1)$ and $\beta = \alpha/(1 - \alpha)$
- **Note:** As $\alpha \rightarrow 1$, $\beta \rightarrow \infty$
- **Typical values:** $\beta \sim 100\text{-}5000$, $\alpha \sim 0.99\text{-}0.9998$

Current-Voltage Relation

- ***BE junction*** basically a ***diode***
 - $I_E = I_{ES} \exp(V_{BE}/V_T)$ ($V_{BE} > 4V_T$)
 - I_{ES} : ***Reverse Saturation Current of BE junction***
- A ***fraction*** α of I_E reaches ***collector***
 - $I_C = \alpha I_E = I_S \exp(V_{BE}/V_T)$
 - $I_S (= \alpha I_{ES})$: ***Saturation current of the BJT***
- The ***difference*** between I_E and I_C is I_B
 - $I_B = I_E - I_C$

Output Characteristic

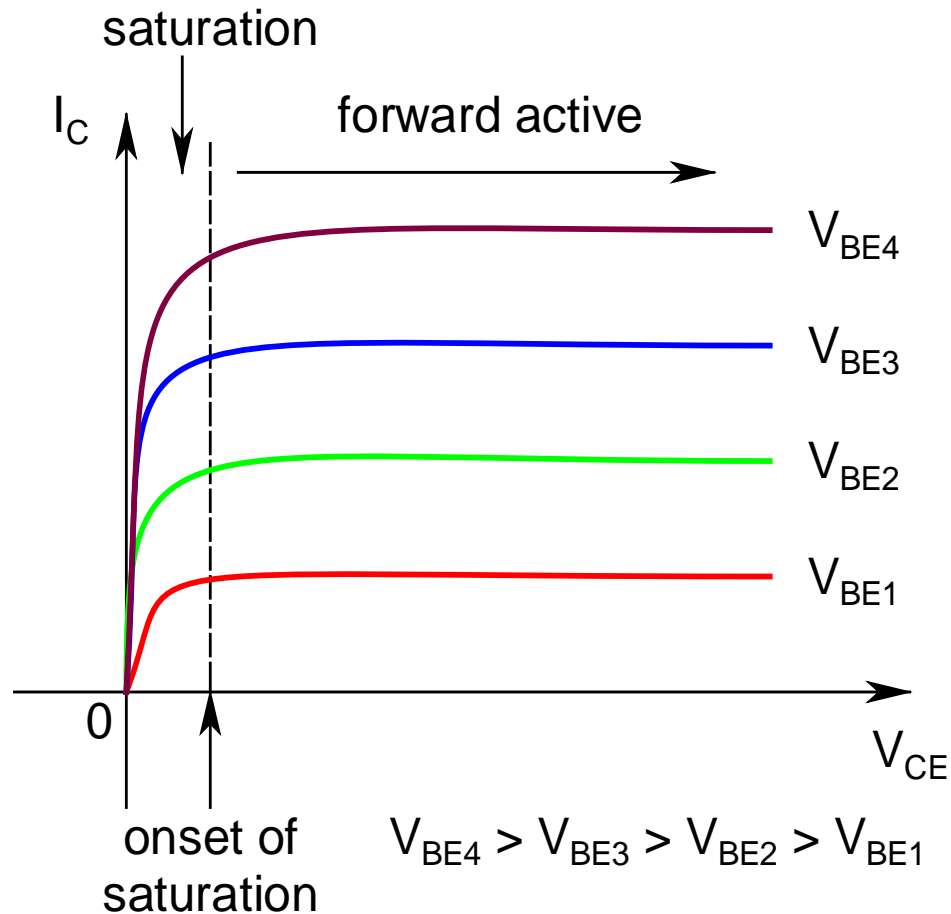

- *Quick Estimate:*

- Under *forward bias*, $V_{BE} \sim 0.7 \text{ V}$

- *Justification:*

- $V_{\gamma} \sim 0.6 \text{ V}$

- 0.7 V is 100 mV above $V_{\gamma} \Rightarrow$ *junction sufficiently forward biased*

- I_C - V_{BE} relation *exponential* \Rightarrow A *little change* in V_{BE} can cause a *large change* in I_C

- *Heuristic estimate: not accurate*, however, *extremely useful* for a *quick hand-calculation*

- $V_{CE} = V_{BE} - V_{BC}$ (*applying chain rule*)

- Thus, for $V_{CE} > 0.7 \text{ V}$, V_{BC} *negative*
 - BC junction *reverse biased* and FA operation is *maintained*
- As $V_{CE} \rightarrow 0.7 \text{ V}$, $V_{BC} \rightarrow 0$
 - BC junction *losing its reverse bias*
- At $V_{CE} = 0.7 \text{ V}$, $V_{BC} = 0$
 - BC junction *under zero bias*
- For $V_{CE} < 0.7 \text{ V}$, V_{BC} turns *positive*
 - Both BE and BC junctions become *forward biased* \Rightarrow *saturation*

- $V_{CE} = 0.7 \text{ V}$ is known as *onset of saturation* (OS)
- *Saturation*:
 - For $V_{CE} < 0.7 \text{ V}$
 - CB junction becomes *forward biased*
 - Collector also starts to *inject* electrons to base
 - *Two effects*:
 - *Net electrons reaching collector* $\downarrow \Rightarrow I_C \downarrow$
 - *Base gets flooded with electrons* \Rightarrow
Recombination increases manyfold $\Rightarrow I_B \uparrow$
 - Thus, $\beta \downarrow \Rightarrow$ Defined as $\beta_{sat} (= I_{C,sat}/I_{B,sat})$

- Noting that $V_\gamma = 0.6 \text{ V}$, for $V_{BC} \leq 0.5 \text{ V}$, *injection* of electrons from *collector to base* will be *negligible*
 - It can be *assumed* that *FA operation* is *maintained* till this point, with β *retaining* its *nominal value*
 - $V_{CE} = 0.2 \text{ V}$ at this point, and is known as the *point of soft saturation* (SS)
- Beyond this point, BJT enters the *operating domain* known as *hard saturation* (HS)


- In *hard saturation*, $V_{BC} \approx 0.7$ V, and collector *injects* electrons *vigorously* into the base
- To *counter* this effect, V_{BE} automatically *increases* to about 0.8 V
- At this point, $V_{CE} = 0.1$ V, and is known as the *point of hard saturation* (HS)
- Note that all these numbers are for *quick estimates*, and *actual values* can be a *little different* from these

- ***Degree of Saturation*** (DoS):
 - $\text{DoS} = \beta/\beta_{\text{sat}} (\geq 1)$
 - Portrays how *deeply* the BJT is driven into *saturation*
- ***Commonly used values*** of *parameters* for *quick estimate*:
 - $V_{\text{BE}}(\text{FA}) = V_{\text{BE}}(\text{SS}) = 0.7 \text{ V}$
 - $V_{\text{BE}}(\text{HS}) = 0.8 \text{ V}$, $V_{\text{CE}}(\text{HS}) = 0.1 \text{ V}$
 - $V_{\text{CE}}(\text{OS}) = 0.7 \text{ V}$, $V_{\text{CE}}(\text{SS}) = 0.2 \text{ V}$
 - $\text{DoS}(\text{FA}, \text{OS}, \text{SS}) = 1$, $\text{DoS}(\text{HS}) > 1$

- BJTs in *analog circuits* are used as *amplifiers*, and should *never* be pushed to *hard saturation* (*β drops significantly*)
 - *Lowest limit* of $V_{CE} = 0.2 \text{ V}$ (*soft saturation*)
- On the other hand, BJTs used in *digital circuits*, while *on*, are always pushed to *hard saturation*, since they act basically as *switches*
 - $V_{CE} = 0.1 \text{ V}$ (*hard saturation*)

Finding the Operating Point: Load Line Analysis

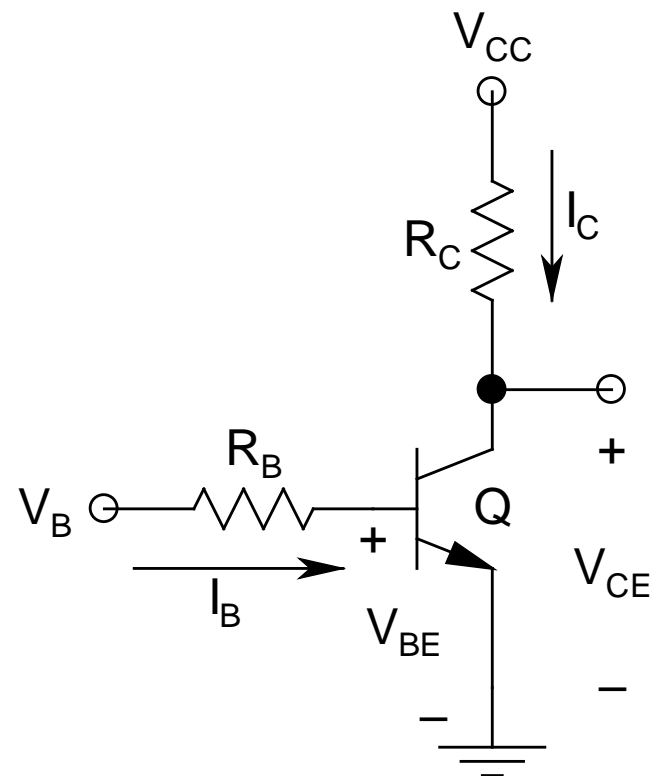- *Quick estimate* in *FA mode*:
 - $I_B = (V_B - V_{BE})/R_B$
 - $V_{BE} = 0.7 \text{ V}$
 - $I_C = \beta I_B$
 - *Independent* of R_C , so long as *FA operation* is *maintained*



- For *continuous variation* of V_B , *continuous variation* of I_C and I_B
 - The *output characteristics* will *fill up* the *entire quadrant*
- The *operating point* (*Q-point*) can *lie anywhere* in this *quadrant*
- To find the *unique* Q-point, need to *draw* the *load line*
- *Load line equation:*
 - $I_C = (V_{CC} - V_{CE})/R_C$