 


p-channel MOSFET (PMOS)

- Before moving to *NMOS stages with active load*, it will be prudent to visit some details regarding *PMOS*
- *Substrate: n-type* (N_D)
 - *Bulk Potential:*
$$\phi_F = V_T \ln(N_D/n_i)$$
- *Source/Drain: p⁺*
- *Channel Carriers: Holes*



- ***Threshold Voltage:***

$$V_{TP} = V_{TP0} - \gamma \left(\sqrt{2\phi_F + V_{BS}} - \sqrt{2\phi_F} \right)$$

V_{TP0} : ***Zero back-bias threshold voltage (negative)***

➤ ***Body effect coefficient:***

$$\gamma = \frac{\sqrt{2q\epsilon_s N_D}}{C'_{ox}}$$

▪ ***$V_{BS} \geq 0$ (to prevent forward biasing of SB junction)***

➤ ***With back bias, V_{TP} becomes more negative***

➤ ***V_{GS} has to be less than V_{TP} to turn device on***

- **Current-Voltage Relation:**

- **Both V_{GS} and V_{DS} negative**

- **I_D flows from source to drain (the *same direction of flow as holes*)**

- **In saturation** [$|V_{DSp}| > (|V_{GSp}| - |V_{TP}|)$]:

$$I_D = \frac{k'_P}{2} \frac{W}{L} \left(|V_{GSp}| - |V_{TP}| \right)^2 \left(1 + \lambda_p |V_{DSp}| \right)$$

- **In non-saturation** [$|V_{DSp}| < (|V_{GSp}| - |V_{TP}|)$]:

$$I_D = k'_P \frac{W}{L} \left[\left(|V_{GSp}| - |V_{TP}| \right) |V_{DSp}| - \frac{|V_{DSp}|^2}{2} \right]$$


$$k'_p = \mu_p C'_{ox}$$

= *Process transconductance parameter*


μ_p = *Channel hole mobility*

- *Based on the value of V_{TN0} and V_{TP0} , there are two classifications:*
 - *Enhancement Mode: Normally Off (with $V_{GS} = 0$)*
 - V_{TN0} *positive* and V_{TP0} *negative*
 - *Depletion Mode: Normally On (with $V_{GS} = 0$)*
 - V_{TN0} *negative* and V_{TP0} *positive*


Symbols

 


Enhancement
Mode NMOS

 

Enhancement
Mode PMOS

 

Depletion
Mode NMOS

 

Depletion
Mode PMOS

- Note the *thick band* in the *channel region* for *depletion mode devices*, which implies that *channel is present* even *with $V_{GS} = 0$*

- *Variants of Actively Loaded CS Stage:*
 - *Saturated Enhancement Load*
 - *Depletion Load*
 - *Complementary PMOS Load*
 - Also known as the *CMOS Gain Stage*
- *The last one is the most popular*

- ***Saturated Enhancement Load:***

- ***Both bodies tied to ground***

- ***For M_1 : $V_{SB1} = 0$***

- ***For M_2 : $V_{SB2} = V_o$***

- ***M_2 is enhancement mode***


- ***V_{TN02} positive***

- ***M_2 is also diode-connected***

- ***Always operates in saturation***

- ***M_2 has a floating body effect***

 problem: V_o is a variable and V_{TN2} will continuously change with a change in V_o




Circuit Schematic

- *For M_2 to remain on*, its V_{GS2} ($= V_{DD} - V_o$) *must be $> V_{TN2}$*
- Thus, there is a *maximum possible V_o* , beyond which *it cannot rise* (*M_2 would cut off*)
- To estimate this *maximum V_o* , for the time being, *neglect that $3V_T$ cushion*
- Then:


$$V_{DD} - V_{o,max} > V_{TN2} \text{ (with } V_{SB2} = V_{o,max} \text{)}$$

$$V_{TN2} = V_{TN02} + \gamma \left(\sqrt{2\phi_F + V_{o,max}} - \sqrt{2\phi_F} \right)$$

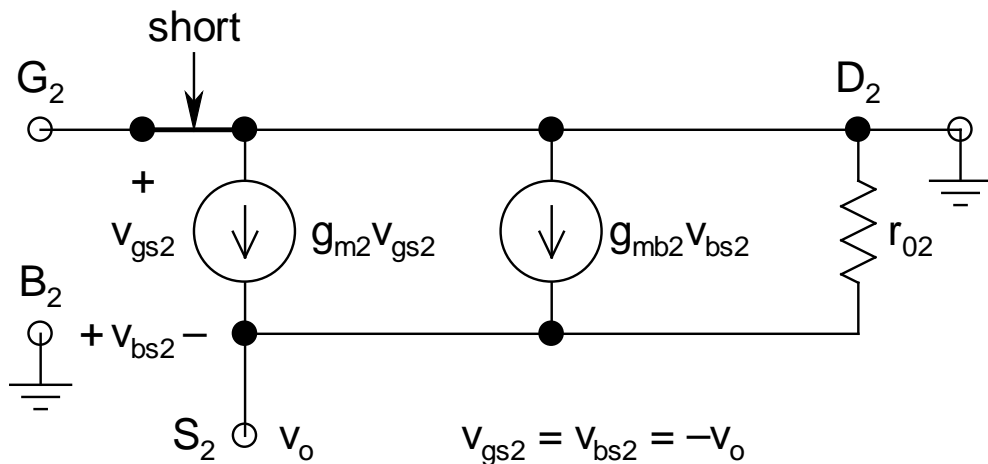- *Solution of this equation would give $V_{o,max}$*
- *Once $V_{o,max}$ is obtained, the best bias point would be at $V_o = V_{o,max}/2$*
- Before doing *ac analysis*, *let's investigate M_2* :



ac Midband Equivalent of M_2

 


Simplified Equivalent

➤ Thus, the *complete equivalent*:

➤ *By inspection*:

$$A_v = \frac{V_o}{V_i} = -g_{m1} (r_{o1} \parallel R_{\text{eff}})$$
 
$$= - \frac{g_{m1}}{g_{m2} + g_{mb2} + g_{o1} + g_{o2}}$$



Complete Equivalent

➤ Now, in general,

$$(g_{m2} + g_{mb2}) \gg (g_{o1} + g_{o2})$$

$$\Rightarrow A_v \approx - \frac{g_{m1}}{g_{m2} + g_{mb2}} = - \frac{g_{m1}}{g_{m2} (1 + \chi_2)}$$

$$\chi_2 = \frac{\gamma}{2\sqrt{2\phi_F + V_{0Q}}}$$

V_{0Q} = *Quiescent DC output voltage*

- Now, if M_2 can be put in its *separate island*, then S_2 and B_2 can be *connected together*

$$\Rightarrow v_{sb2} = 0 \Rightarrow g_{mb2}v_{sb2} = 0$$

$$\Rightarrow A_v \approx -\frac{g_{m1}}{g_{m2}} = -\sqrt{\frac{(W/L)_1}{(W/L)_2}}$$


- $R_0 = (g_{m2} + g_{mb2} + g_{01} + g_{02})^{-1}$

➤ *Insights:*

- *V_o doesn't go all the way to V_{DD}*
⇒ *Full rail-to-rail swing can't be achieved*
- *When V_o falls below ΔV of M_1 , it leaves the saturation region, and enters non-saturation region*
⇒ *Distortion will set in at the output*
- Even for a *moderate voltage gain of 10*, the *ratio of the aspect ratios of M_1 and M_2 has to be 100!*
- *All these problems coupled together make this circuit highly unattractive for practical use*

- **Depletion Load:**

 
- M_2 is *depletion mode*, having *negative* V_{TN0} (*denoted by* V_{TD0})
- *Back bias of* M_2 :
 $V_{SB2} = V_o$
- *With* V_o , V_{TD2} *changes*
- *Maximum* V_o *desired* $= V_{DD}$
- *This is also the maximum back bias of* M_2





Circuit Schematic

- *M_2 has GS short $\Rightarrow V_{GS2} = 0$*
- *Even with $V_o = V_{SB2}(max) = V_{DD}$, V_{TD2} should remain negative with a cushion of at least 100 mV*
 - $\Rightarrow V_{TD2}$ with $V_{SB2} = V_{DD}$ should be -100 mV
 - $\Rightarrow V_{TD0}$ should be chosen based on this
- Now, *$V_{DS2}(min) = V_{DD} - V_o(max) = 0$*
- Under this condition, *$V_{GS2} - V_{TD2} = \Delta V_2 = 100$ mV*
 - $\Rightarrow M_2$ is in the linear region (*since $V_{DS2} < \Delta V_2$*)

 - *This has to be lived with*, and *slight distortion would appear at the output as $V_o \rightarrow V_{DD}$*
- For *best biasing*, $V_{oQ} = V_{DD}/2$
 \Rightarrow *Fixes the DC operating point*
- Before doing *ac analysis*, *let's investigate M_2* :



ac Midband Equivalent of M_2

  


Simplified Equivalent

➤ Thus, the *complete equivalent*:

➤ *By inspection*:

$$A_v = \frac{V_o}{V_i} = -g_{m1} (r_{01} \parallel R_{\text{eff}})$$
 
$$= -\frac{g_{m1}}{g_{mb2} + g_{01} + g_{02}}$$



Complete Equivalent

➤ Now, in general,

$$g_{mb2} \gg (g_{01} + g_{02})$$

$$\Rightarrow A_v \approx -\frac{g_{m1}}{g_{mb2}} = -\frac{g_{m1}}{\chi_2 g_{m2}} = -\frac{1}{\chi_2} \sqrt{\frac{(W/L)_1}{(W/L)_2}}$$