

➤ *The most important property of a DA is to be able to reject common-mode signals (noise), while amplifying the difference between the two signals applied at its two inputs*

➤ Characterized by a parameter known as the *Common-Model Rejection Ratio (CMRR)* (*always expressed in dB*):

$$\text{CMRR} = 20\log_{10}(|A_{\text{dm}}/A_{\text{cm}}|)$$

➤ *Ideal (Desirable) Properties:*

- $|A_{\text{dm}}| \rightarrow \infty (\sim 10^3\text{-}10^5)$
- $|A_{\text{cm}}| \rightarrow 0 (<<< 1)$
- $\text{CMRR} \rightarrow \infty (\sim 40\text{-}120 \text{ dB})$

➤ *The circuit has two inputs and two outputs:*

⇒ *Four possible configurations:*


- *Single-ended i/p, single-ended o/p*
- *Single-ended i/p, double-ended o/p*
- *Double-ended i/p, single-ended o/p*
- *Double-ended i/p, double-ended o/p*

⇒ *Tremendous flexibility*


- *Double-ended o/p eliminates the common-mode signal completely*
- *However, at some point in the circuit, needs to be converted to a single-ended o/p*
 - ⇒ *High CMRR is an absolute must!*

➤ ***Differential-Mode Half Circuit:***

Calculation of A_{dm} :

 

 **nnp DA Under Pure
Differential-Mode Input**



**Differential-Mode
Half-Circuit**


- *Can be shown that $v_e = 0$ in three ways:*
 - ❖ *From the symmetry of the circuit:*
Equal and opposite voltages applied at the bases of Q_1 and Q_2 (perfectly matched)
 \Rightarrow *The emitter potential v_e got to be an average of the inputs, which is zero*
 - ❖ $i_{c1} = g_{m1}(v_{id}/2 - v_e)$ and $i_{c2} = g_{m2}(-v_{id}/2 - v_e)$
Since $g_{m1} = g_{m2}$, i_{c1} must equal $-i_{c2}$ (circulating current)
(this is again from symmetry)
 $\Rightarrow v_e = 0$
 - ❖ *Drawing the complete ac low-frequency hybrid- π model, and summing currents at the common-emitter node:*
Show that $v_e = 0$
- ***Caution: $v_e = 0$ will hold true only for a balanced DA***

- *Thus, the left and right parts of the circuit become absolutely symmetrical*
 - \Rightarrow *Either of the parts can be used*
 - \Rightarrow *Leads to the differential-mode half-circuit*
- $g_{m1} = g_{m2} = g_m = I_{EE}/(2V_T)$, $r_{E1} = r_{E2} = r_E = 2V_T/I_{EE}$,
and $r_{\pi1} = r_{\pi2} = r_{\pi} = \beta r_E$
- *Can be easily identified to be a CE stage*
 - $\Rightarrow A_{dm} = v_{od}/v_{id} = (v_{od}/2)/(v_{id}/2) = -R_C/r_E$
- *Differential-mode input resistance:*


$$R_{id} = v_{id}/i_i = 2(v_{id}/2)/i_i = 2r_{\pi}$$
- *The simplicity of the analysis is simply mind-boggling!*

➤ **Common-Mode Half-Circuit:**

Calculation of A_{cm} :

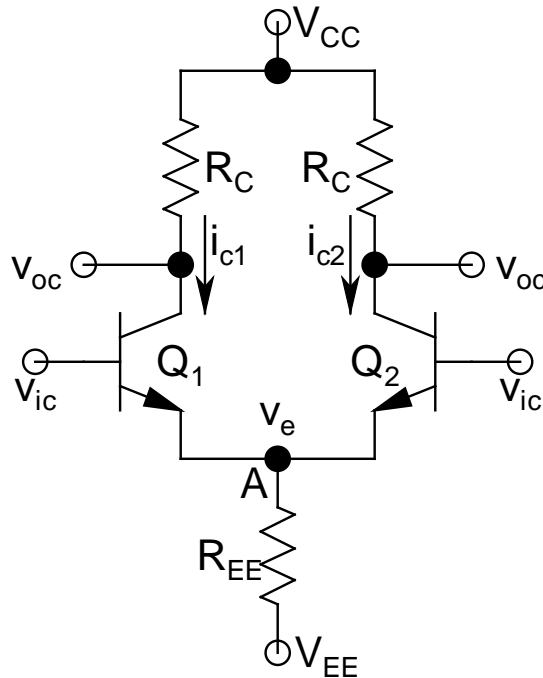

**npn DA Under Pure
Common-Mode Input**

 

**Common-Mode
Half-Circuit**

- $i_{c1} = i_{c2} = i_c = g_m(v_{ic} - v_e)$
- These two currents *sum up at node A* and *flow through R_{EE} , creating a voltage drop of $2i_c R_{EE}$ across it*
- Thus, *R_{EE} can be split into two parts, $2R_{EE}$ each,* and *each part put in the emitter leads of Q_1 and Q_2*
- *The lead connecting the two parts of R_{EE} would not carry any current, and can be removed*
- *Thus, the circuit becomes perfectly symmetric along a vertical cut-line going through the middle of the circuit, and we can consider either of them*
 \Rightarrow *Leads to the common-mode half-circuit*

- *Can be easily identified to be a CE(D) stage*
 $\Rightarrow A_{cm} = v_{oc}/v_{ic} = -R_C/(r_E + 2R_{EE}) \approx -R_C/(2R_{EE})$
 (since, in general, $R_{EE} \gg r_E$)
- *Common-mode input resistance:*
 $R_{ic} = v_{ic}/i_i = r_\pi + (\beta + 1)2R_{EE} \approx 2\beta R_{EE}$
 (since, in general, $R_{EE} \gg r_\pi$)
- *Input resistance of the npn DA:*
 $R_i = R_{id} || R_{ic} \approx R_{id} = 2r_\pi$ (*from superposition*)
 (since, in general, $R_{ic} \gg R_{id}$)
- *CMRR* $= 20\log_{10}(|A_{dm}/A_{cm}|) \approx 20\log_{10}(2R_{EE}/r_E)$

➤ *Some insights:*


- A_{dm} is independent of R_{EE} , however, A_{cm} is a strong function of R_{EE}
- Goal is to make A_{cm} as close to zero as possible
 - ⇒ Make R_{EE} as large as possible
- High value of R_{EE} will automatically ensure high value of CMRR (*highly desirable!*)
- High CMRR can also be achieved by reducing r_E
 - ⇒ Can be obtained by increasing the DC bias current
 - ⇒ DC power dissipation of the circuit goes up
 - ⇒ Also, DC biasing may become suspect!

➤ *Increasing the Linear Range:*

- *Linear Range: $\pm 4V_T$ ($\sim \pm 100 \text{ mV}$ at room temperature)*
- *For some applications, this may not be enough*
- *Linear Range can be increased by attaching two identical resistors (R_E) in the emitter branches of Q_1 and Q_2*
- *Increases Linear Range by $I_{EE}R_E$ (Show!)*
- *This method decreases A_{dm} (differential-mode half-circuit becomes CE(D) topology)*
- *Has minimal effect on A_{cm}*
- *CMRR suffers! \Rightarrow Not a good choice!*

- **NMOS DA (SCP):**

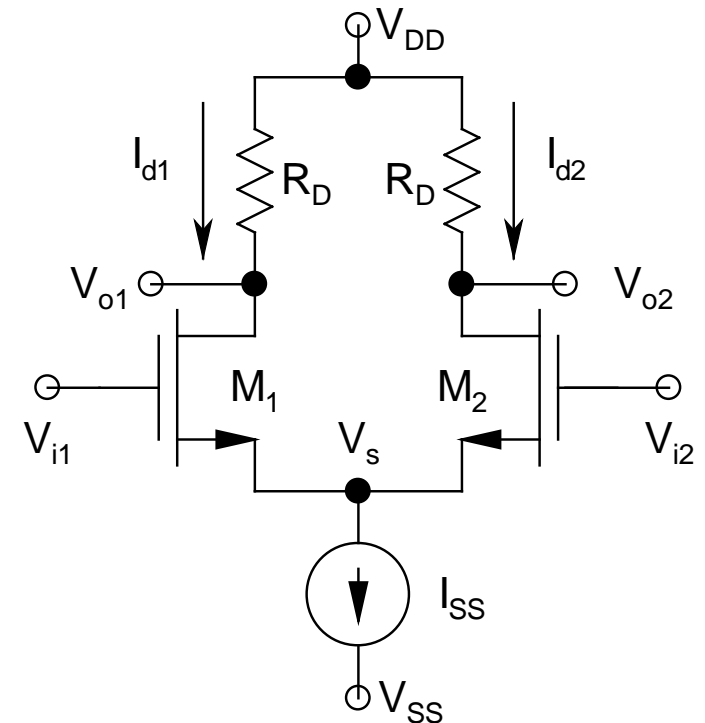- M_1 - M_2 constitute a *perfectly matched pair*, and have their *sources connected together*, hence, the name
- I_{SS} : **DC bias current source**
- *All voltages and currents are instantaneous*



NMOS DA Topology

➤ $V_{gs1} = V_{i1} - V_s$, and $V_{gs2} = V_{i2} - V_s$

➤ ***KVL around M_1 - M_2 GS loop:***

$$V_{i1} - V_{gs1} + V_{gs2} - V_{i2} = 0$$

$$\Rightarrow V_{gs1} - V_{gs2} = V_{i1} - V_{i2} = V_{id}$$

➤ ***Neglecting CLM Effect:***

$$I_{d1} = \frac{k'_N}{2} \left(\frac{W}{L} \right) (V_{gs1} - V_{TN1})^2 \quad \text{and}$$

$$I_{d2} = \frac{k'_N}{2} \left(\frac{W}{L} \right) (V_{gs2} - V_{TN2})^2$$

- Ran into a problem, since *both M_1 and M_2 would have body effect present*
 - *Both bodies connected to V_{SS} , but the common source node is at a floating potential V_s*
 - ⇒ *Analytical evaluation of I_{d1} and I_{d2} becomes pretty tedious*
- *If the CLM effect is also included, then the problem would need numerical solution!*
- To get a *first-order estimate, neglect body effect*
 - ⇒ $V_{TN1} = V_{TN2} = V_{TN0}$

➤ Thus:

$$V_{id} = \frac{\sqrt{I_{d1}} - \sqrt{I_{d2}}}{\sqrt{\frac{k'_N}{2} \left(\frac{W}{L} \right)}} \quad (1)$$

➤ Also:

$$I_{d1} + I_{d2} = I_{SS} \quad (2)$$

➤ ***Solving Eqs.(1) and (2):***

$$I_{d1} = I_{SS}/2 + \xi \quad \text{and}$$

$$I_{d2} = I_{SS}/2 - \xi$$