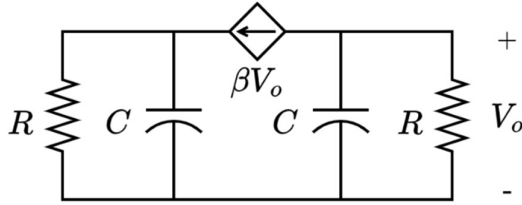



ESO203 Tutorial 5

Question 1:

For what value of β is the circuit in given figure stable?



Solution:

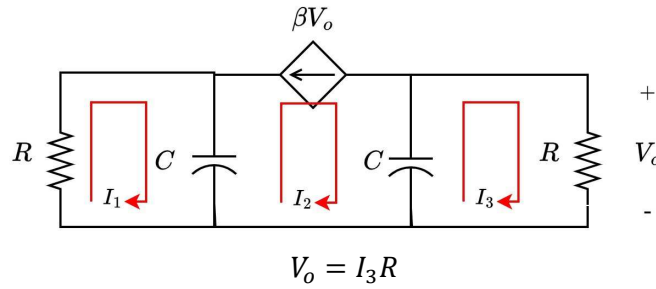

In Laplace transformation,

Applying KVL in mesh 1:

$$I_1 \left(R + \frac{1}{sC} \right) - I_2 \left(\frac{1}{sC} \right) = 0$$

Applying KVL in mesh 2:

$$I_2 = -\beta V_o = -\beta I_3 R$$

Applying KVL in mesh 3:

$$-I_2 \left(\frac{1}{sC} \right) + I_3 \left(R + \frac{1}{sC} \right) = 0$$

Converting to matrix form:

$$\begin{bmatrix} \left(R + \frac{1}{sC} \right) & \left(-\frac{1}{sC} \right) & 0 \\ 0 & 1 & \beta R \\ 0 & \left(-\frac{1}{sC} \right) & \left(R + \frac{1}{sC} \right) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

The determinant of the matrix is given by

$$\Delta = \left(R + \frac{1}{sC} \right) \left[\left(R + \frac{1}{sC} \right) + \frac{\beta R}{sC} \right]$$

Equating the determinant equal to 0, we get

$$\Delta = \left(R + \frac{1}{sC} \right) \left[\left(R + \frac{1}{sC} \right) + \frac{\beta R}{sC} \right] = 0$$

$$\frac{s^2 R^2 C^2 + s(2RC + \beta R^2 C) + (\beta R + 1)}{s^2 C^2} = 0$$

$$s^2 R^2 C^2 + s(2RC + \beta R^2 C) + (\beta R + 1) = 0$$

For system to be stable, all the poles should be left hand side of y-axis of the s-plane.

By solving equation, we get

$$s_1 = -\frac{1}{RC} \quad , \quad s_2 = \frac{-2RC - 2\beta R^2 C}{2R^2 C^2}$$

For poles to be left hand side of s-plane,

$$s_2 = \frac{-2RC - 2\beta R^2 C}{2R^2 C^2} < 0$$

$$(\beta R + 1) < 0$$

$$\beta > -\frac{1}{R}$$

Question 2:

Synthesize the network that has an impedance function as given. Assume the resistance value is 1 ohm.

$$Z_1(s) = \frac{s^2 + 7s + 70}{s(s + 10)}$$

Solution:

For the given transfer function, do the partial fraction expansion, we get,


$$Z_1(s) = \frac{s^2 + 7s + 70}{s(s + 10)} = \frac{7}{s} + \frac{s}{s + 10}$$

The function is realized by a capacitor with a value of $\frac{1}{7}F$ and the second function can be realized by a parallel combination of a resistor and an inductor.

The possible synthesized circuit is given in the figure.

The impedance function can be derived from the circuit, as given below.
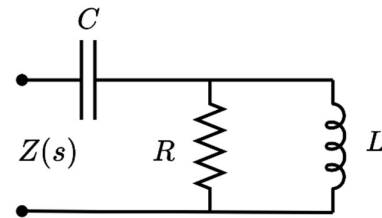
$$Z_2(s) = \frac{1}{sC} + \frac{sRL}{R + sL}$$




Comparing the $Z_1(s)$ and $Z_2(s)$, the obtained parameters with $R = 1\Omega$, are

$$C = \frac{1}{7}F \text{ and } L = \frac{1}{10}H$$

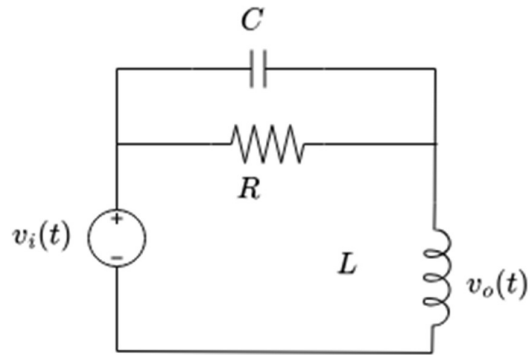Question 3:

Given the transfer function $H(s) = \frac{V_o(s)}{V_i(s)} = \frac{s^2 + 50s}{s^2 + 50s + \dots}$. Realize the function using the

circuit shown below. Find the value of L , for the given $R = 10\Omega$.



Solution:

Let Z_1 is equivalent to parallel combination of R and C .

$$Z_1(s) = \frac{R}{1 + sRC}$$

And similarly,

$$Z_2(s) = sL$$

The transfer function $H(s)$ can be obtained by voltage divide rule.

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{Z_2(s)}{Z_1(s) + Z_2(s)}$$

$$H(s) = \frac{sL}{\frac{R}{1 + sRC} + sL}$$

$$H(s) = \frac{sL(1 + sRC)}{R + sL(1 + sRC)}$$

$$H(s) = \frac{s^2 + \frac{s}{RC}}{s^2 + \frac{s}{RC} + \frac{1}{LC}}$$

Equating with given transfer function, we get

$$\frac{1}{RC} = 50$$

$$C = 2mF$$

$$\frac{1}{LC} = 20$$

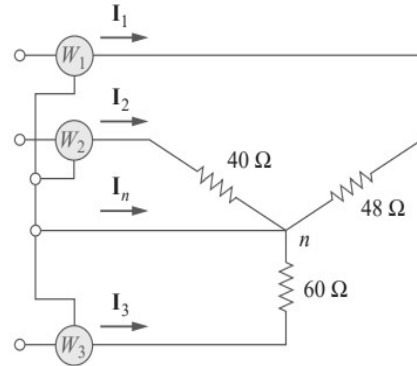
$$L = 25H$$

Question 4:

A three-phase, four-wire system operating with a 208-V line voltage is shown in below figure. The source voltages are balanced. The power absorbed by the resistive wye-connected load is measured by the three-wattmeter method.

Calculate:

- The line to neutral voltage.
- The currents I_1, I_2, I_3 and I_n .
- The readings of the wattmeters.
- The total power absorbed by the load.

**Solution:**

Assume V_{AN}, V_{BN} and V_{CN} are the phase voltage and Z_{AN}, Z_{BN} and Z_{CN} are the per phase impedance of phase a, b and c respectively

(a) The Phase voltage

$$V_{Ph} = \frac{V_{LL}}{\sqrt{3}} = \frac{208}{\sqrt{3}} = 120.08 \text{ V}$$

(b) The currents I_1, I_2, I_3 and I_n

$$I_1 = \frac{V_{AN}}{Z_{AN}} = \frac{120.08 \angle 0^\circ}{48} = 2.50 \angle 0^\circ \text{ A}$$

$$I_2 = \frac{V_{BN}}{Z_{BN}} = \frac{120.08 \angle 120^\circ}{40} = 3.002 \angle 120^\circ \text{ A}$$

$$I_3 = \frac{V_{CN}}{Z_{CN}} = \frac{120.08 \angle -120^\circ}{60} = 2 \angle -120^\circ \text{ A}$$

$$I_n = -(I_1 + I_2 + I_3)$$

$$I_n = -(2.50 \angle 0^\circ + 3.002 \angle 120^\circ + 2 \angle -120^\circ)$$

$$I_n = 0.868 \angle -90^\circ$$

(c) The readings of the wattmeter:

$$P_1 = V_{AN} I_1 \cos(\theta_{v_{AN}} - \theta_{i_1}) = 120.08 \times 2.50 \times \cos(0 - 0) = 300.2 \text{ W}$$

$$P_2 = V_{BN} I_2 \cos(\theta_{v_{BN}} - \theta_{i_2}) = 120.08 \times 3.002 \times \cos(120 - 120) = 360.48 \text{ W}$$

$$P_3 = V_{CN} I_3 \cos(\theta_{v_{CN}} - \theta_{i_3}) = 120.08 \times 2 \times \cos(-120 + 120) = 240.16 \text{ W}$$

(d) The total power absorbed by the load:

$$P_T = P_1 + P_2 + P_3$$

$$P_T = 300.2 + 360.48 + 240.16 = 900.84 \text{ W}$$

Question 5:

The primary current to an ideal transformer rated $\frac{2200}{110} \text{ V}$ is 5 A . Calculate

- (a) the turns ratio,
- (b) the KVA rating,
- (c) the secondary current.

Solution:

This is a step-down transformer since $V_1 = 2200 \text{ V} > V_2 = 110 \text{ V}$

a.

$$n = \frac{V_2}{V_1}$$

$$n = \frac{110}{2200} = \frac{1}{20}$$

b.

$$S = V_1 * I_1 = V_2 * I_2$$

$$S = 2200 \text{ V} * 5 \text{ A} = 11 \text{ kVA}$$

c.

$$n = \frac{I_1}{I_2}$$

$$\frac{1}{20} = \frac{5}{I_2}$$

$$I_2 = 100 \text{ A}$$

Question 6:


For the Y- Δ network shown in the figure, find the following.

- I_{AB} , I_{BC} , and I_{CA}
- I_a and I_β of source v_{an} and v_{bn}

Given the following details of the network:

$$v_{an} = 100 \angle 0^\circ \text{ V}, v_{bn} = 100 \angle -120^\circ \text{ V}, \text{ and } v_{cn} = 100 \angle 120^\circ \text{ V}$$

$$Z_L = 8 + j4 \, \Omega, \text{ and } Z_D = 12 + j6 \, \Omega$$

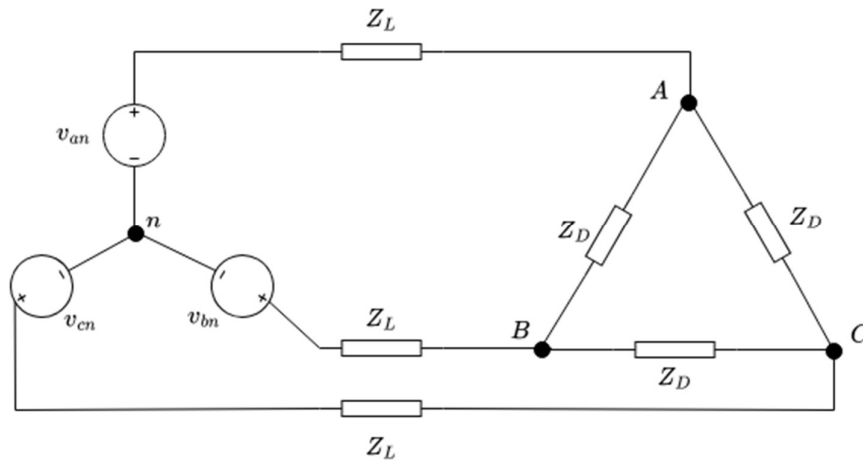**Solution:****Step 1: Convert Δ Load to Y Load**

The Y-equivalent impedance of a Δ load is given by:

$$Z_Y = \frac{Z_D}{3}$$

Substituting $Z_D = 12 + j6$

$$Z_Y = \frac{12 + j6}{3} = 4 + j2$$

Step 2: Total Y Load Impedance

The total impedance in each Y branch is

$$Z_{total} = Z_L + Z_Y$$

$$Z_{total} = (8 + j4) + (4 + j2) = 12 + j6$$

Step 3: Calculate Phase Currents

Using Ohm's law, the phase currents are:

$$I_{\alpha} = \frac{V_{an}}{Z_{total}}, \quad I_{\beta} = \frac{V_{bn}}{Z_{total}}, \quad I_{\gamma} = \frac{V_{cn}}{Z_{total}}$$

Magnitude of Z_{total} :

$$|Z_{total}| = \sqrt{(12^2 + 6^2)} = 13.42$$

Phase angle:

$$\theta_{Z_{total}} = \tan^{-1}\left(\frac{6}{12}\right) = 26.57^{\circ}$$

Now, computing each current:

$$I_{\alpha} = \frac{100}{13.42} \angle(-26.57^{\circ}) = 7.45 \angle(-26.57^{\circ}) \text{ A}$$

$$I_{\beta} = 7.45 \angle(-120^{\circ} - 26.57^{\circ}) = 7.45 \angle(-146.57^{\circ}) \text{ A}$$

$$I_{\gamma} = 7.45 \angle(120^{\circ} - 26.57^{\circ}) = 7.45 \angle 93.43^{\circ} \text{ A}$$

Step 4: Convert Back to Δ Load Currents

To find the delta currents:

$$I_{AB} = I_{\alpha} - I_{\beta}$$

$$I_{BC} = I_{\beta} - I_{\gamma}$$

$$I_{CA} = I_{\gamma} - I_{\alpha}$$

Substituting values:

$$I_{AB} = 7.45 \angle(-26.57^{\circ}) - 7.45 \angle(-146.57^{\circ})$$

$$I_{BC} = 7.45 \angle(-146.57^{\circ}) - 7.45 \angle(93.43^{\circ})$$

$$I_{CA} = 7.45 \angle(93.43^{\circ}) - 7.45 \angle(-26.57^{\circ})$$

These can be computed numerically using phasor subtraction.

Final Answer:

$$I_{\alpha} = 7.45 \angle(-26.57^{\circ}) \text{ A}, \quad I_{\beta} = 7.45 \angle(-146.57^{\circ}) \text{ A}, \quad I_{\gamma} = 7.45 \angle(93.43^{\circ}) \text{ A}$$

$$I_{AB} = 12.9 \angle(-3.43^{\circ}) \text{ A}, \quad I_{BC} = 12.9 \angle(-116.57^{\circ}) \text{ A}, \quad I_{CA} = 12.9 \angle(123.43^{\circ}) \text{ A}$$

Question 7:

A balanced three-phase Y-connected load is supplied by a 415V, 50Hz three-phase supply. The total power consumed by the load is 10 kW, and the power factor is 0.5 lagging. Using the two-wattmeter method, determine:

1. The readings of the two wattmeters (W_1 and W_2).
2. The phase current (I_{ph}).
3. What happens to W_1 and W_2 if the power factor changes to 0.5 leading instead of lagging?

Solution:**Step 1: Given Data**

- Line Voltage: $V_L = 415V$
- Power Factor: $\cos\phi = 0.5$ (Lagging) $\Rightarrow \phi = 60^\circ$
- Total Power: $P = 10 \text{ kW}$

Step 2: Find the Line Current I_L

The total power in a three-phase system is given by:

$$P = \sqrt{3} \times V_L \times I_L \times \cos\phi$$

Substituting the given values:

$$10,000 = \sqrt{3} \times 415 \times I_L \times 0.5$$

$$I_L = \frac{10000}{\sqrt{3} \times 415 \times 0.5} = 27.8 \text{ A}$$

Since the load is Y-connected, the phase current is:

$$I_{ph} = I_L = 27.8 \text{ A}$$

Step 3: Find the Wattmeter Readings W_1 and W_2

The wattmeter readings are given by:

$$W_1 = V_L \times I_L \times \cos(30^\circ + \phi)$$

$$W_2 = V_L \times I_L \times \cos(30^\circ - \phi)$$

Substituting $\phi = 60^\circ$:

$$W_1 = 415 \times 27.8 \times \cos(90^\circ) = 0$$

$$W_2 = 415 \times 27.8 \times \cos(-30^\circ) = 10,000W$$

Thus, $W_1 = 0W$, $W_2 = 10,000W$

This confirms that when $\cos \phi = 0.5$ lagging, one wattmeter reads zero and the other reads the full power.

Step 4: If Power Factor Becomes 0.5 Leading

For $\cos \phi = 0.5$ leading, the only change is the sign of ϕ (i.e., $\phi = -60^\circ$ instead of $+60^\circ$).

New wattmeter readings:

$$W_1 = V_L \times I_L \times \cos(30^\circ - (-60^\circ)) = 0W$$

$$W_2 = V_L \times I_L \times \cos(30^\circ + (-60^\circ)) = 10,000W$$

This means the wattmeter readings remain the same, as the power is unchanged.

Final Answer

1. For $\cos \phi = 0.5$ (lagging or leading):

$$W_1 = 0W, \quad W_2 = 10,000W$$

2. Phase Current: $I_{ph} = 27.8A$

3. If the power factor is leading instead of lagging, the wattmeter readings remain the same.

Key Learning

- At $\phi = 60^\circ$ lagging, one wattmeter reads zero.
- If the power factor is leading instead of lagging, the wattmeter readings remain unchanged.
- For power factor angles closer to 90° , one wattmeter reading becomes negative.