

- ***More on W/L Ratio:***
 - *Generally, in technology, W/L is kept between 0.01 and 100*
 - *The ideal ratio is between 0.02 and 50*
 - ***Minimum Feature Size*** (MFS):
 - *Minimum dimension that can be resolved in an IC chip*
 - ❖ *Has gone down from 10s of μm in 80s to a few nm now!*
 - ***For $W/L > 1$ (or < 1), L (or W) is chosen equal to MFS***
 - *Yields minimum possible device area ($W \times L$)*

- *npn CM With Better β Insensitivity:*

- $I_{REF} = (V_{CC} - 2V_{BE})/R$

- Neglecting I_{B3} :


$$I_{C1} = I_{REF}$$

- *If Q_1 and Q_2 are matched:*

$$I_0 = I_{C2} = I_{C1} = I_{REF}$$

\Rightarrow *Simple CM*

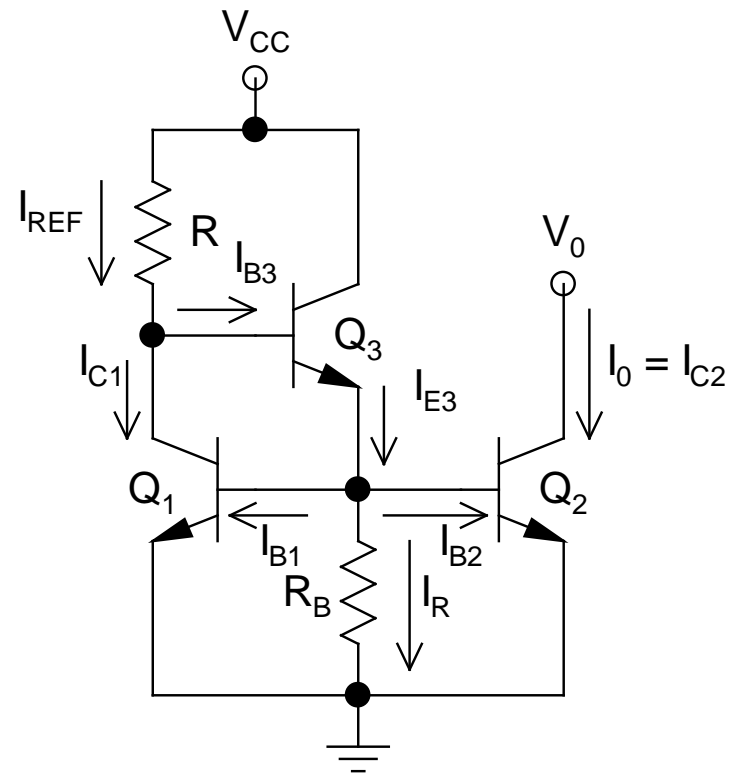- *The actual advantage of the circuit lies elsewhere!*



➤ First, assume *R_B is absent*

$$\Rightarrow I_{E3} = I_{B1} + I_{B2} = I_{C1}/\beta_1 + I_{C2}/\beta_2 = 2I_0/\beta_1$$

(assuming $\beta_1 = \beta_2$)

$$\Rightarrow I_{B3} = \frac{I_{E3}}{\beta_3 + 1} = \frac{2I_0}{\beta_1 (\beta_3 + 1)}$$

$$I_{\text{REF}} = I_{C1} + I_{B3} = I_0 \left[1 + \frac{2}{\beta_1 (\beta_3 + 1)} \right]$$

$$\Rightarrow I_0 = \frac{I_{\text{REF}}}{1 + \frac{2}{\beta_1 (\beta_3 + 1)}}$$

➤ Now, if $\beta_1 = \beta_3 = \beta$, and $\beta \gg 1$:

$$I_0 \approx I_{\text{REF}}(1 - 2/\beta^2)$$

➤ Compare with that of simple CM:

$$I_0 \approx I_{\text{REF}}(1 - 2/\beta)$$

➤ *The advantage is obvious!*

➤ *Further Insights:*

❖ $I_{\text{E3}} (= I_{\text{B1}} + I_{\text{B2}}) \sim \text{few } 10\text{s of } \mu\text{A}$

❖ *At such a low current, β drops significantly from its nominal value*

❖ *Thus, full advantage of the circuit can't be exploited*

- *Here comes the role of R_B :*
- *It drains a constant current ($= V_{BE}/R_B$), which gets added to ($I_{B1} + I_{B2}$), and **boosts** I_{E3} (and, thus, I_{C3})*
 - *Thus, β_3 gets pulled up to its nominal value*
 - *This resistor has a special name: **Keep Alive**, since it keeps Q_3 alive!*
- *However, it creates some issues as well:*
- *Additional power drain due to the additional current flowing through R_B*
 - *If $I_{E3} \uparrow$, so would I_{B3}*
 $\Rightarrow I_{C1}$ may depart from I_{REF}
 - *Design optimization needed*

➤ *Now, for R_0 :*

- *Looking at C_2*
- *E_2 grounded*
- *No connection between C_2 and B_2 (no feedback)*
- *Therefore, by inspection:*

$$R_0 = V_{A2}/I_0$$

➤ *Also, by inspection:*

$$V_{0,\min} = V_{CE2}(\text{SS}) = 0.2 \text{ V}$$

➤ *There is no MOS counterpart for this circuit for obvious reasons!*

- ***npn Ratioed CM:***

- *Q_1 - Q_2 matched pair*

- *Neglecting all I_B , $I_{E1} = I_{C1}$
 $= I_{REF}$, and $I_{E2} = I_{C2} = I_0$*

- $I_{REF} = (V_{CC} - 2V_{BE})/(R + R_1)$


- ***KVL around Q_1 - Q_2 BE loop:***

$$V_{BE1} + I_{REF}R_1 = V_{BE2} + I_0R_2$$

$$\Rightarrow I_0 = (I_{REF}R_1 + \Delta V_{BE})/R_2$$

$$\Delta V_{BE} = V_{BE1} - V_{BE2}$$

$$= V_T \ln(I_{REF}/I_0)$$

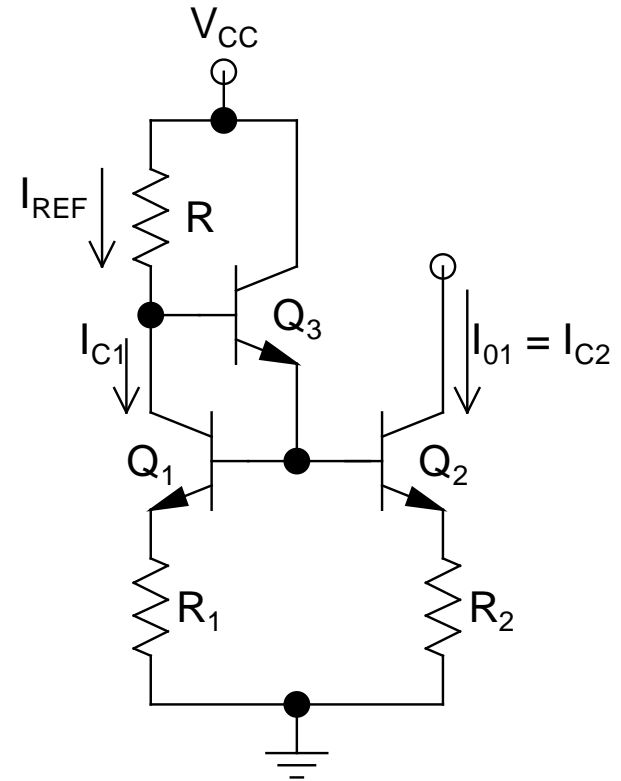

➤ *Note the \ln dependence:*

▪ *For $I_{REF}/I_0 = 2$, $\Delta V_{BE} = 18 \text{ mV}$*

▪ *For $I_{REF}/I_0 = 10$, $\Delta V_{BE} = 60 \text{ mV}$*

$\Rightarrow \Delta V_{BE}$ *can be neglected if $I_{REF}R_1 > 10\Delta V_{BE}$*

$\Rightarrow I_0 = (R_1/R_2)I_{REF}$ (*Ratioed Mirror*)

➤ *Thus, by tinkering R_1 and R_2 , any ratio between I_0 and I_{REF} can be obtained*

▪ *Tremendous advantage*


❖ *Widely used*

➤ *By inspection:*

$$V_{0,\min} = V_{CE2}(\text{SS}) + I_0 R_2 = 0.2 + I_0 R_2$$

➤ *Calculation of R_o :*

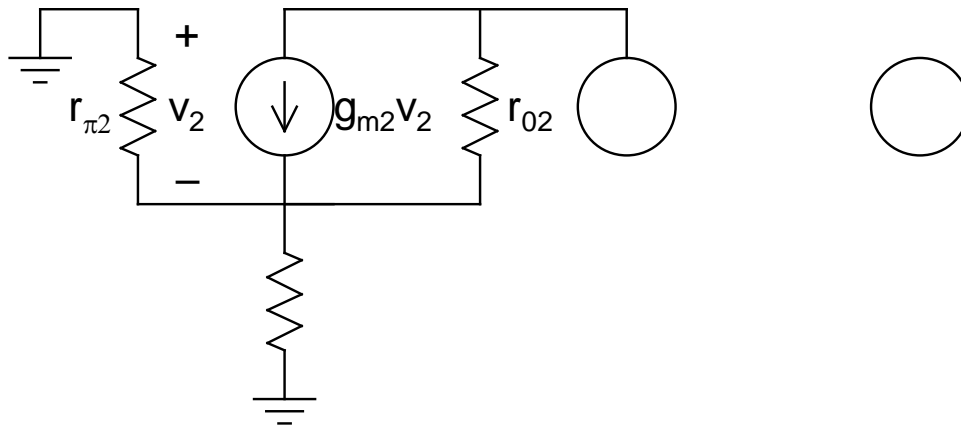- *Golden Rule can't be used since emitter of Q_2 is not grounded (R_2 present there)*
- *Needs analysis*
 - ⇒ *Leads to a module that is frequently encountered*
- *Base of Q_1 - Q_2 at a fixed DC potential ⇒ **ac ground***



$$\begin{aligned}
 i_t &= g_{m2} v_2 + (v_t + v_2)/r_{02} \\
 &= v_t/r_{02} + (g_{m2} + 1/r_{02}) v_2 \quad v_t/r_{02} + g_{m2} v_2
 \end{aligned}$$

$$v_2 = -i_t R_{\text{eff}}$$

$$\Rightarrow i_t = v_t/r_{02} - g_{m2} R_{\text{eff}} i_t$$

$$\Rightarrow R_0 = v_t/i_t = r_{02}(1 + g_{m2} R_{\text{eff}})$$

➤ This is a ***Golden Equation***, which would be *used frequently*

- *Carefully note the topology that produces this result*

➤ ***Exercise***: *Reverse v_2 and show that the expression for R_0 remains invariant*