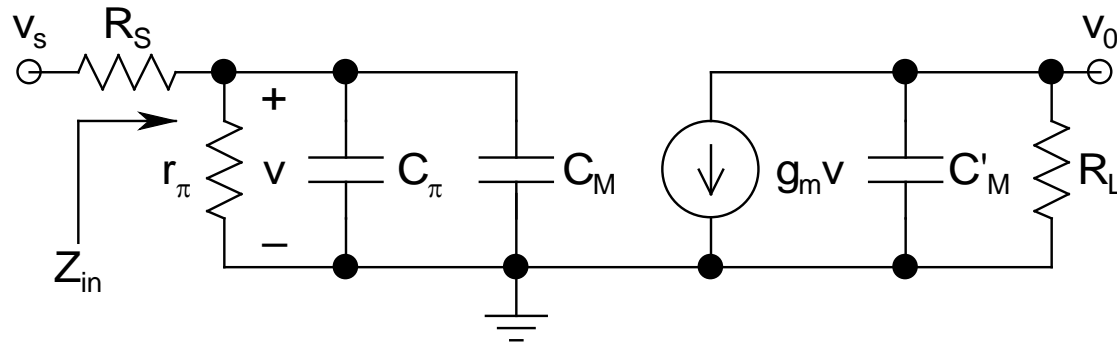


- $C_\mu$  can now be **removed** as the **coupling element**, **split into 2 parts**  $C_M$  and  $C'_M$ , with  $C_M$  appearing in the **input circuit** and  $C'_M$  appearing in the **output circuit**
- Now, **include  $R_S$**  - note that the circuit is **completely decoupled** now



**Complete Circuit Including  $R_S$**

$$\triangleright Z_{\text{in}} = r_{\pi} \parallel [1/(sC_T) = r_{\pi}/(1 + sr_{\pi}C_T)]$$

$$C_T = C_{\pi} + C_M$$

$$\Rightarrow v = \frac{Z_{\text{in}}}{Z_{\text{in}} + R_S} v_s$$

$$= \frac{r_{\pi}}{(R_S + r_{\pi}) \left[ 1 + sr_{\pi}R_S C_T / (R_S + r_{\pi}) \right]} v_s$$

$$v_0 = -g_m \left( R_L \parallel \frac{1}{sC'_M} \right) v = -\frac{g_m R_L}{1 + sR_L C'_M} v$$

➤ Thus:

$$A_v(s) = \frac{V_0}{V_s}$$
$$= -g_m R_L \frac{r_\pi}{R_S + r_\pi} \frac{1}{\left[1 + sR_S r_\pi C_T / (R_S + r_\pi)\right] (1 + sR_L C'_M)}$$

➤ *Comparing* this expression with

$$A_v(s) = \frac{A_{v0}}{(1 - s/p_1)(1 - s/p_2)}$$

we note that the *denominator* is already in a *factorized form*

- $A_{v0} = \text{midband gain} = -g_m R_L r_\pi / (R_S + r_\pi)$
- The *transfer function* shows that the system has *two negative real poles* and *no zero*  
 $\Rightarrow$  *Information regarding the zero is suppressed by this technique*
- Also, the *two poles* obtained by *this technique* are *not identical* to those obtained from the *exact analysis*

➤ Pole  $p_1$  ( $p_2$ ) is referred to as the pole of the *input* (*output*) circuit

➤ Also,  $|p_1| \ll |p_2|$

$\Rightarrow p_1$  ( $p_2$ ) is the *DP* (*NDP*) of the system

➤ *Matching coefficients:*

$$p_1 = -\frac{R_S + r_\pi}{R_S r_\pi} \frac{1}{C_T} = -\frac{1}{(R_S \parallel r_\pi) [C_\pi + (1 + g_m R_L) C_\mu]}$$

$$p_2 = -\frac{1}{R_L C'_M}$$

➤ Obviously,  $|p_1| \ll |p_2|$

- Thus, *using DPA*:  $f_H = |p_1|/(2\pi)$
- Applying *this technique* to the *previous example*,  $f_H = 3.9 \text{ MHz}$  and *NDP frequency = 156 MHz*
  - *Error of only 2.6% in  $f_H$* , but the *ease of solution is much more*
- Thus, *this technique* is *quite popular* in getting a *quick estimate* of  $f_H$ , even though the *solution* may not be *exact*
- *Care*: *The gain in the multiplicative factor is that between the input and output terminals of the capacitor*

- *The Zero-Value Time Constant (ZVTC) Technique:*
  - *Gives information only about the DP of the system*
  - *Suppresses all information regarding other poles and zeros*
  - *The ease of application of this technique is mind-boggling*

- *Slightly less accurate*
- *The maximum error can be as high as 22%  
(under an extremely unusual situation, rarely encountered, if ever)*
- *Underestimates  $f_H$* 
  - *Far better than overestimation and eventually not achieving it*
- *Applicable only for circuits that have a DP*
  - *Fortunately, almost all analog circuits of interest do have a DP*



- *The Algorithm:*

- *Null all independent sources to the circuit*
  - *Short all independent voltage sources*
  - *Open all independent current sources*
  - **DO NOT TOUCH DEPENDENT SOURCES**
- *Name the capacitors  $C_i$  ( $i = 1-n$ )*
- *Consider  $C_1$  and assign zero values to all other capacitors (thus the name!)*
  - Thus, *except  $C_1$ , all other capacitors will open out*
- *Determine the Thevenin Resistance ( $R_1^0$ ) across the two terminals of  $C_1$*

- *Find the time constant  $\tau_1$  associated with  $C_1$*   
 $(\tau_1 = R_1^0 C_1)$
- *Repeat for all other capacitors, taking one at a time, and find all the rest of the time constants  $(\tau_2, \tau_3, \dots, \tau_n)$*
- Determine the *net time constant*  $\tau_{\text{net}}$  by *summing up* all the *individual time constants*  
$$\Rightarrow \tau_{\text{net}} = \sum_{i=1}^n \tau_i$$
- Then the *Upper Cutoff Frequency*  $f_H$  is simply given by:  $f_H = 1/(2\pi\tau_{\text{net}})$

- *Note: The capacitor contributing the largest time constant, in effect, determines  $f_H$*
- *The technique suppresses all information regarding other poles and zeros*
- Will present *several examples* to understand the *application* of this *technique*
- Some *topologies* will be appearing *frequently*, known as *Standard Forms*, which can be treated as *individual modules*, and the *results can be used freely*

- **CE:**

- Refer to the *high-frequency equivalent* given in the *exact analysis*

- **2 capacitors:**  $C_\pi$  and  $C_\mu$

- $\Rightarrow$  *2 time constants:*  $\tau_1$  and  $\tau_2$

- $C_\pi$ :

- **$C_\mu$  opens up**

- *By inspection:*

$$R_\pi^0 = R_S \parallel r_\pi$$

$$\Rightarrow \tau_1 = R_\pi^0 C_\pi$$


➤  $C_\mu$ :

- $C_\pi$  opens up
- This is one *Standard Form*, known as the *Three-Legged Creature*
- Show that:

$$R_\mu^0 = R + R_L + g_m R_L R \quad (R = R_S \parallel r_\pi)$$

$$\Rightarrow \tau_2 = R_\mu^0 C_\mu$$

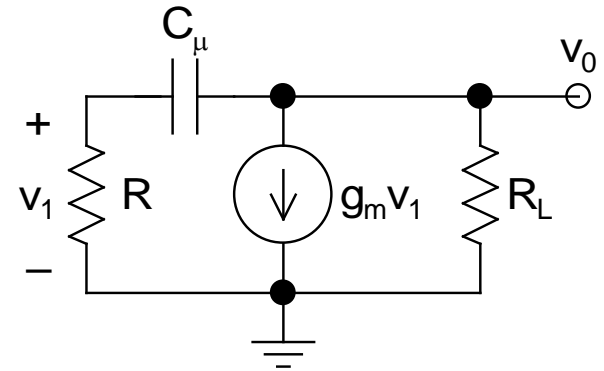- Thus,  $\tau_{\text{net}} = \tau_1 + \tau_2$ , and  $f_H = 1/(2\pi\tau_{\text{net}})$
- Note the *amazing simplicity* of the analysis



- Putting *values* of our previous *example*:

$$R_{\pi}^0 = 838.7 \, \Omega, \, \tau_1 = 8.4 \, \text{ns}$$


$$R_{\mu}^0 = 67.4 \, \text{k}\Omega, \, \tau_2 = 33.7 \, \text{ns}$$

$$\Rightarrow \tau_{\text{net}} = 42.1 \, \text{ns} \quad \text{and} \quad f_H = 3.8 \, \text{MHz}$$


- This is *identical* to the *result* obtained from the *exact analysis*, however, at a *fraction* of the *effort*!

- Also,  *$\tau_2$  is the dominant time constant*  
 $\Rightarrow f_H$  *is primarily dictated by  $C_{\mu}$*

- ***CS*** :

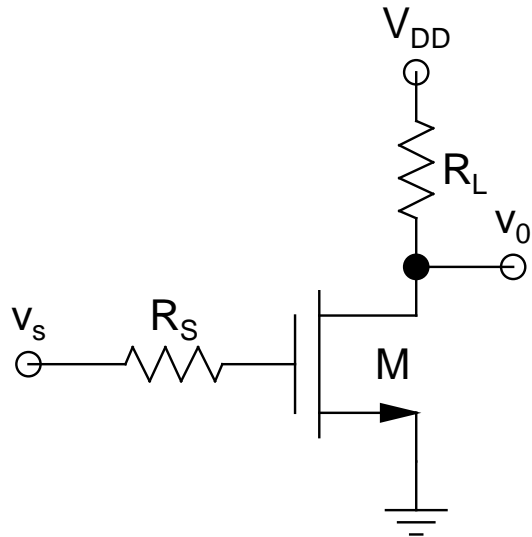

ac Schematic

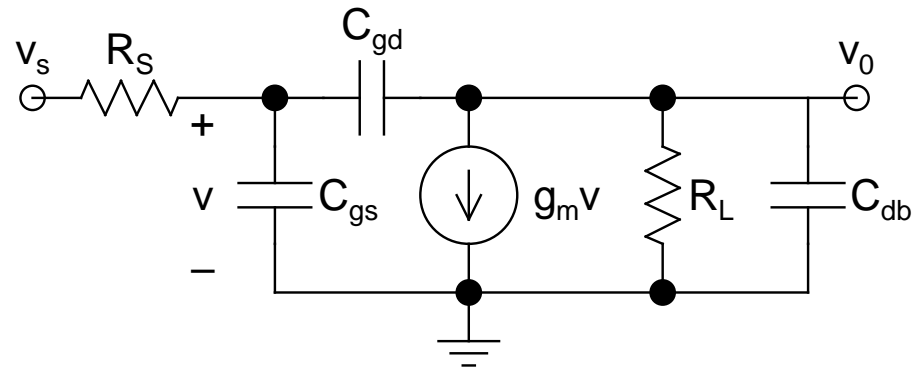

High-Frequency Equivalent

➤ ***C<sub>sb</sub> absent (Why?)***

➤ *3 capacitors*:  $C_{gs}$ ,  $C_{gd}$ , and  $C_{db}$

⇒ *3 time constants*:  $\tau_1$ ,  $\tau_2$ , and  $\tau_3$

➤  $C_{gs}$ :

- *$C_{gd}$  and  $C_{db}$  open up*

- *By inspection*:

$$R_{gs}^0 = R_S$$

$$\Rightarrow \tau_1 = R_{gs}^0 C_{gs}$$

➤  $C_{gd}$ :

- *$C_{gs}$  and  $C_{db}$  open up*

- *By inspection*, it can be *identified* as a *Three-Legged Creature*



- Thus:

$$R_{gd}^0 = R_S + R_L + g_m R_S R_L$$

$$\Rightarrow \tau_2 = R_{gd}^0 C_{gd}$$

➤  *$C_{db}$*  :

- *$C_{gs}$  and  $C_{gd}$  open up*
- *By inspection:*

$$R_{db}^0 = R_L$$


$$\Rightarrow \tau_3 = R_{db}^0 C_{db}$$

➤ Thus:


$$\tau_{\text{net}} = \tau_1 + \tau_2 + \tau_3, \text{ and } f_H = 1/(2\pi\tau_{\text{net}})$$

➤ *Mind-bogglingly simple* - isn't it?

- ***CB*** :

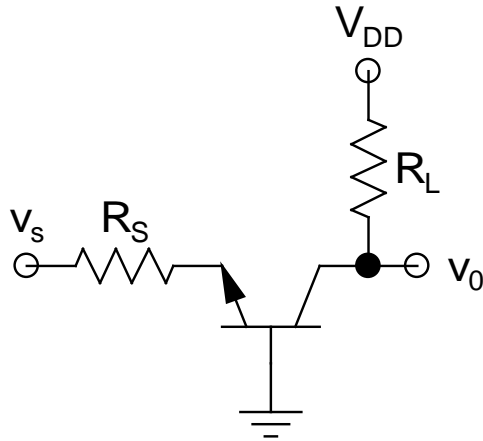

**ac Schematic**

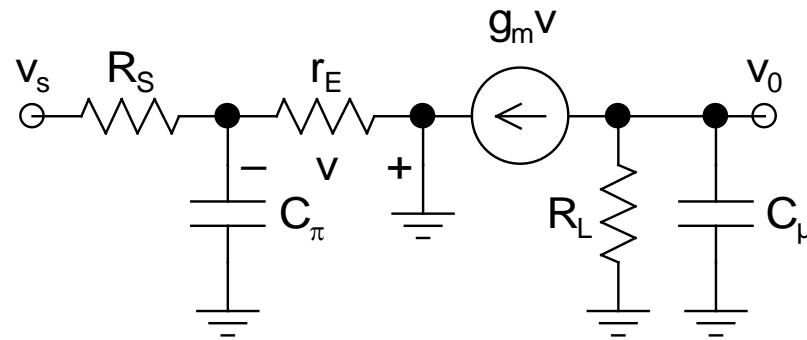

**High-Frequency Equivalent**

➤ ***Note that there is no input-output coupling capacitor present in this circuit***

⇒ ***Miller effect will be absent***, and the ***circuit will have very high  $f_H$***