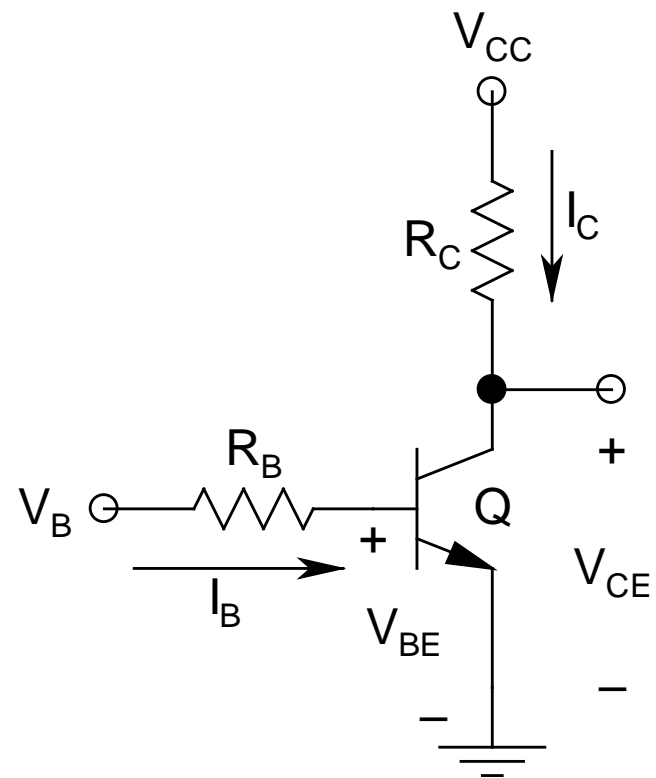


Finding the Operating Point: Load Line Analysis


- *Quick estimate* in *FA mode*:
 - $I_B = (V_B - V_{BE})/R_B$
 - $V_{BE} = 0.7 \text{ V}$
 - $I_C = \beta I_B$
 - *Independent* of R_C , so long as *FA operation* is *maintained*




- For *continuous variation* of V_B , *continuous variation* of I_C and I_B
 - The *output characteristics* will *fill up* the *entire quadrant*
- The *operating point* (*Q-point*) can *lie anywhere* in this *quadrant*
- To find the *unique* Q-point, need to *draw* the *load line*
- *Load line equation*:
 - $I_C = (V_{CC} - V_{CE})/R_C$

- *2 boundary points:*
 - For $I_C = 0$, $V_{CE} = V_{CC}$
 - For $V_{CE} = 0$, $I_C = V_{CC}/R_C$
- *Joining* these *2 points* by a *straight line* gives the *load line*
- The *intersection point* of the *load line* with the *output characteristic* gives the *Q-point*
- Gives *infinite number* of *choices* for *possible Q-point*

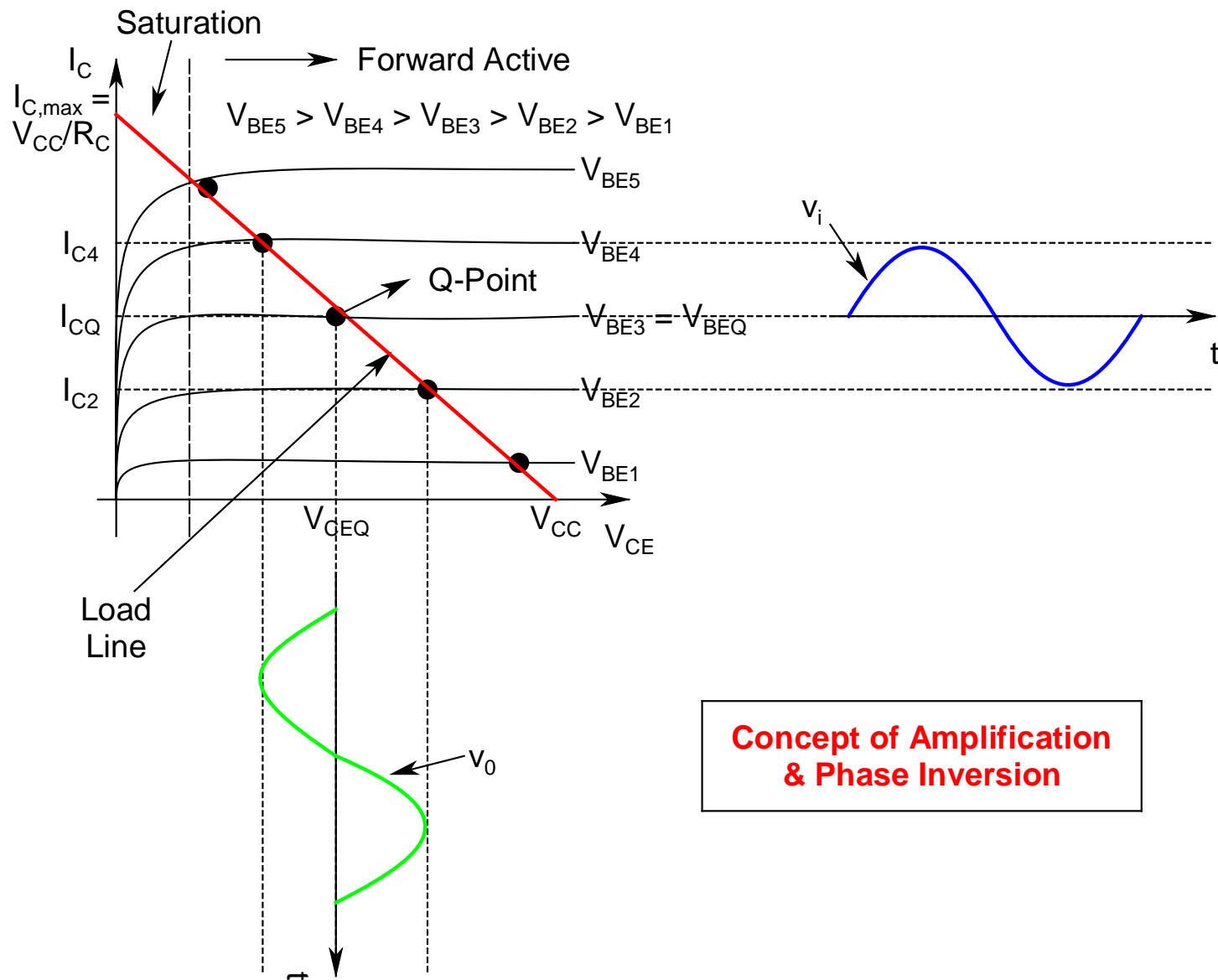
- The *best choice* for the *Q-point* is *right at the center* of the *load line*
 - $V_{CEQ}(\text{best}) = V_{CC}/2$ and $I_{CQ}(\text{best}) = V_{CC}/(2R_C)$
- *Permits the maximum possible signal swing in both directions*
- If $V_{CEQ} > V_{CC}/2$, it's *biased more towards cutoff*
- If $V_{CEQ} < V_{CC}/2$, it's *biased more towards saturation*
- *Either way*, we will get a *distorted output*



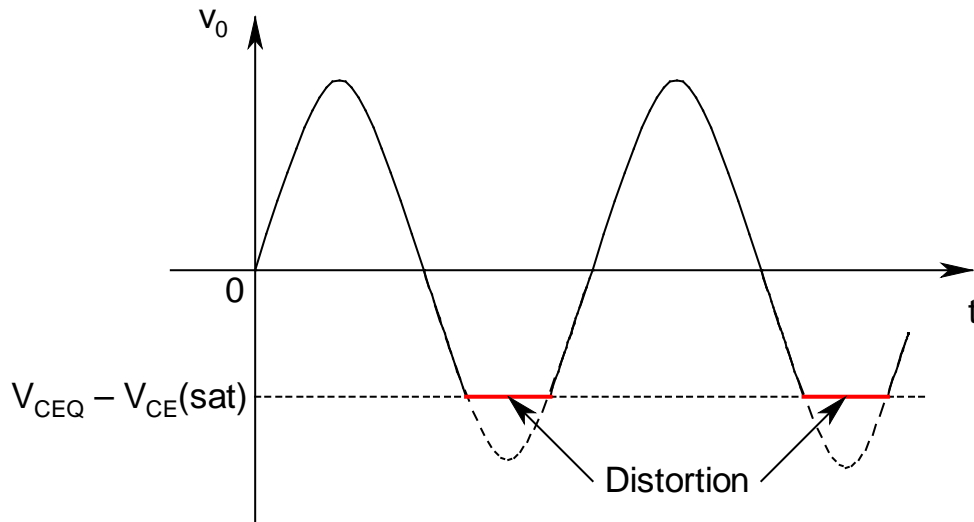**Concept of Amplification
& Phase Inversion**



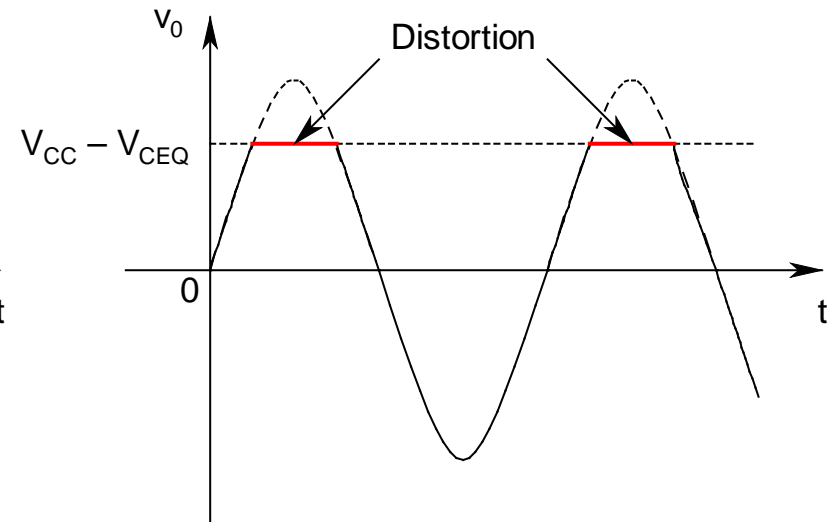(a) Negative Clipping:
Saturation Induced



(b) Positive Clipping:
Cutoff Induced

- Under *application* of an *ac signal* (v_i), the *dynamic operating point* (DOP) will *move along the load line*
- For *positive* v_i , the DOP *will move* Q *towards saturation* ($V_{CE} \rightarrow 0, I_C \rightarrow I_{C,max}$)
 - The *output signal* (v_o) will be in its *negative excursion*
 - If Q enters *saturation*, *negative peak* of v_o will get *clipped*
 - *Distorted output*

- For *negative* v_i , the DOP *will move* Q *towards cutoff* ($V_{CE} \rightarrow V_{CC}$, $I_C \rightarrow 0$)
 - The *output signal* (v_o) will be in its *positive excursion*
 - If Q *cuts off*, *positive peak* of v_o will get *clipped*
 - *Distorted output*
- *Golden rule of thumb for BJT biasing:*
 - *To get maximum undistorted peak-to-peak swing of v_o , Q-point must be chosen to be at the middle of the load line*

- ***Role of R_C :***

- Under ***FA mode***, R_C ***does not control I_C*** ,
however, it ***changes V_{CE}*** ($= V_{CC} - I_C R_C$)
- If $R_C \uparrow$, $V_{CE} \downarrow \Rightarrow Q$ moves ***towards saturation***
- If $R_C \downarrow$, $V_{CE} \uparrow \Rightarrow Q$ moves ***towards cutoff***
- Thus, ***different values of R_C*** can produce
different Q -points (in terms of V_{CE})

- ***DC Power Dissipation:***

- $P_D = V_{BEQ} \times I_{BQ} + V_{CEQ} \times I_{CQ}$
 $\approx V_{CEQ} \times I_{CQ}$ (***under FA mode***)

Some Observations

- Q should be *biased* such that it is in the *FA* mode of operation
 - Behaves like a *constant and ideal current source with infinite output resistance*, since I_C is *independent* of V_{CE}
 - *Ideal region to bias a BJT*
- For *very high* R_C , $I_{C,max}$ *very small*
 - *Load line may not have any intersection point in the FA region at all*

- *Q-point moves to saturation region*
- *Ceases to become a constant current source*, since in *saturation*, I_C becomes a *strong function* of V_{CE}
- *Disastrous way of biasing a BJT*
- *Similar situation* will arise if R_C is *very small*
 - $I_{C,max}$ will become *very large* and *Q-point will move towards cutoff*
 - *Another disastrous way of biasing a BJT*

- **Example:** Let $V_{CC} = V_B = 5 \text{ V}$, $R_B = 430 \text{ k}\Omega$, and $\beta = 100$
 - $I_B = (V_B - V_{BE})/R_B = (5 - 0.7)/(430 \text{ k}\Omega) = 10 \text{ }\mu\text{A}$ (assuming **FA** mode of operation with $V_{BE} = 0.7 \text{ V}$)
 - $I_C = \beta I_B = 1 \text{ mA}$
 - V_{CE} will **depend** on our **choice** of R_C
 - R_C for **best biasing** (BB) ($V_{CE}(\text{BB}) = V_{CC}/2$):
 - $R_C(\text{BB}) = V_{CC}/(2I_C) = 2.5 \text{ k}\Omega$
 - R_C that puts Q at OS ($V_{CE}(\text{OS}) = 0.7 \text{ V}$):
 - $R_C(\text{OS}) = [V_{CC} - V_{CE}(\text{OS})]/I_C = 4.3 \text{ k}\Omega$

➤ *Any value of R_C higher than $4.3\text{ k}\Omega$ would push Q in saturation*

➤ Choose $R_C = 20\text{ k}\Omega$:

- Assuming *FA* operation is maintained, V_{CE} comes out to be -15 V !

- *Golden rule:*

 - ❖ *Potential at any point in a circuit can never go beyond the positive and negative extremes of the power supply voltages, unless there is a power source within the circuit*

- Thus, $V_{CE} = -15\text{ V}$ is *absurd*


- Hence, Q is *no more* in the *FA* mode of operation, rather it has been pushed into *saturation*

- Whether it is in *soft saturation* (SS) or *hard saturation* (HS), would *depend* on the *degree of saturation* (DoS)
- *For HS, DoS must be ≥ 2* ($\beta_{\text{sat}} \leq \beta$)
- Assume *HS*: $V_{\text{BE}}(\text{HS}) = 0.8 \text{ V}$, $V_{\text{CE}}(\text{HS}) = 0.1 \text{ V}$
 - ❖ $I_{\text{B,sat}} = [V_{\text{CC}} - V_{\text{BE}}(\text{HS})]/R_{\text{B}} = (5 - 0.8)/(430 \text{ k}\Omega) = 9.77 \text{ }\mu\text{A}$
 - ❖ $I_{\text{C,sat}} = [V_{\text{CC}} - V_{\text{CE}}(\text{HS})]/R_{\text{C}} = (5 - 0.1)/(20 \text{ k}\Omega) = 245 \text{ }\mu\text{A}$
 - ❖ $\beta_{\text{sat}} = I_{\text{C,sat}}/I_{\text{B,sat}} = 245/9.77 = 25$
 - ❖ $\text{DoS} = \beta/\beta_{\text{sat}} = 4 (> 2)$
 - ❖ *Assumption verified, and analysis is correct!*
- *Ex.*: Find the values of R_{C} that would put Q at the edge of: i) HS, and ii) SS

Base Width Modulation Effect

- In **FA** mode, as $|V_{BC}| \uparrow$, BC *depletion region width* $\uparrow \Rightarrow$ *neutral base width* \downarrow
 - *Electrons spend less time in base* \Rightarrow *chance of recombination* \downarrow
 - *More electrons make it to the collector* $\Rightarrow I_C \uparrow$
as $V_{CE} \uparrow$
 - Known as the **Base Width Modulation Effect**
(or *Early Effect*, after inventor **J.M. Early**)

- The *current-voltage characteristic*, including *Early Effect*, is modeled as:
 - $I_C = I_S[\exp(V_{BE}/V_T)](1 + V_{CE}/V_A)$
 - V_A : *Early Voltage* (~ 130 V for *npn*, and ~ 52 V for *pn*p)
 - V_A is a *negative number*, but taken to be a *positive quantity*
- Imparts a *positive slope* in the *output characteristics* in the *FA region*
 - Introduces an *output resistance*, and makes the current source *non-ideal*!

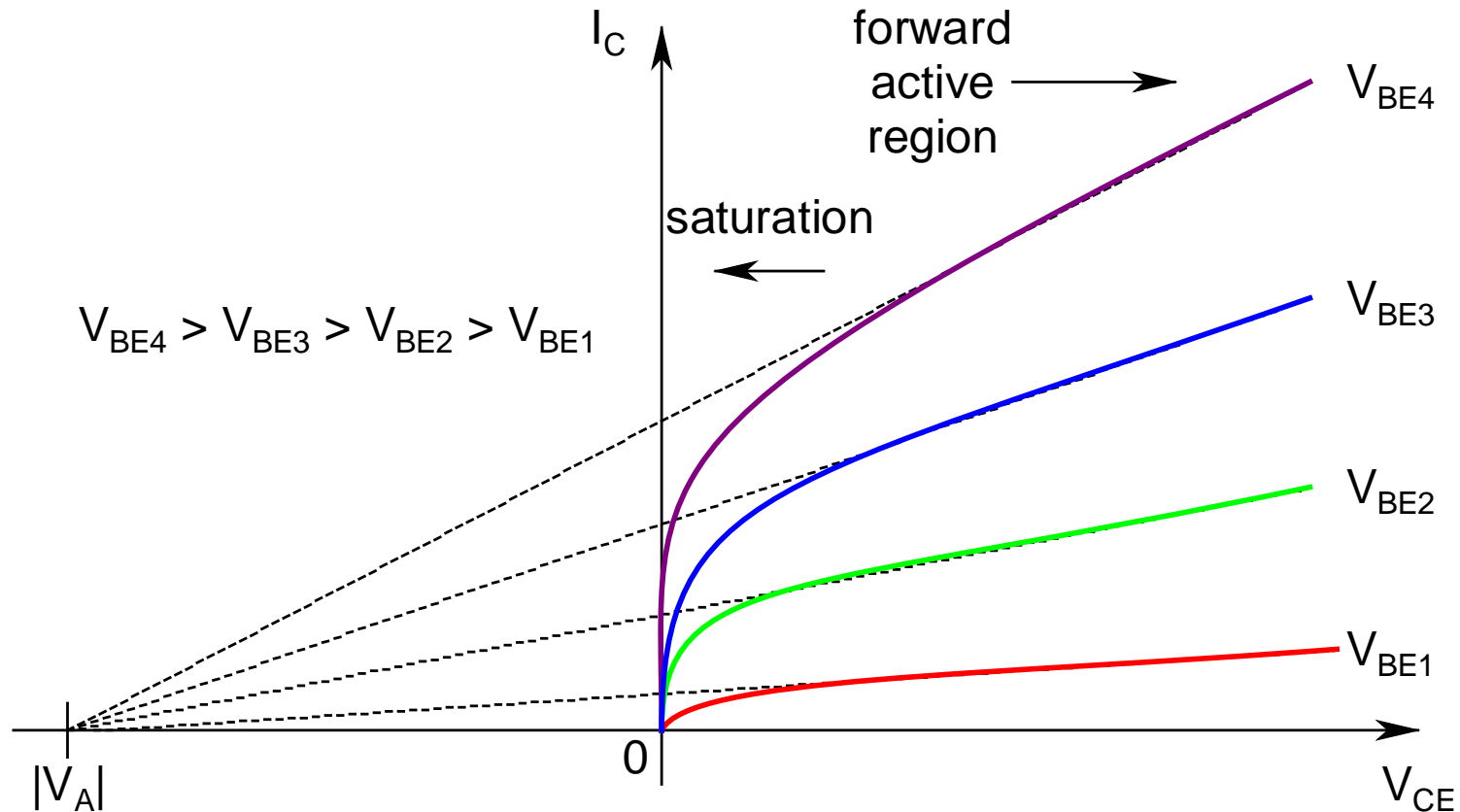

All characteristics merge at $|V_A|$ in the negative V_{CE} axis

Note: If $V_A \rightarrow \infty$, all characteristics become horizontal in the FA region