
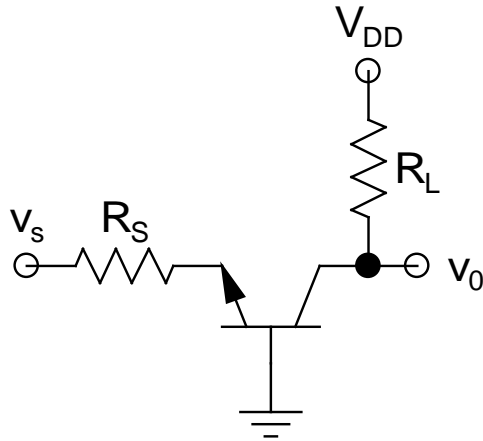


- ***CB*** :

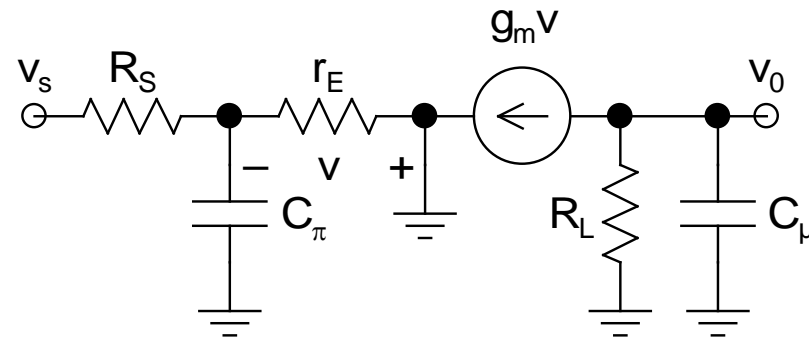

**ac Schematic**



**High-Frequency Equivalent**

➤ ***Note that there is no input-output coupling capacitor present in this circuit***

⇒ ***Miller effect will be absent***, and the ***circuit will have very high  $f_H$***

➤  $C_\pi$ :

$$R_\pi^0 = R_S \parallel r_E \quad \text{and} \quad \tau_1 = R_\pi^0 C_\pi$$

➤  $C_\mu$ :

$$R_\mu^0 = R_L \quad \text{and} \quad \tau_2 = R_\mu^0 C_\mu$$

➤ Taking the *values* of our previous *example*:


$$R_\pi^0 = 25.34 \, \Omega, \quad \tau_1 = 0.253 \, \text{ns}$$

$$R_\mu^0 = 2 \, \text{k}\Omega, \quad \tau_2 = 1 \, \text{ns}$$


$$\Rightarrow \tau_{\text{net}} = 1.25 \, \text{ns} \quad \text{and} \quad f_H = 127.3 \, \text{MHz}$$

➤ *Note the enormous increase of  $f_H$  from about 4 MHz for a CE amplifier*

- **CG :**

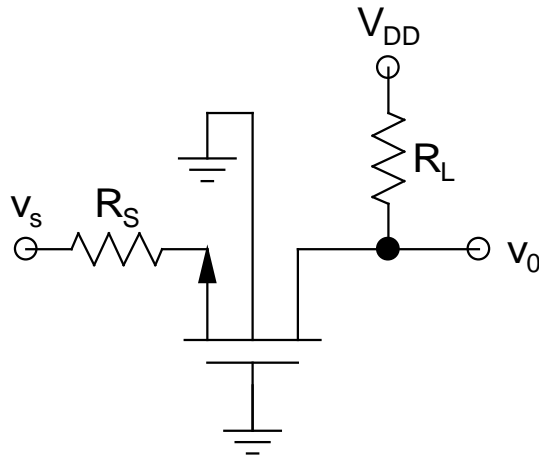

ac Schematic

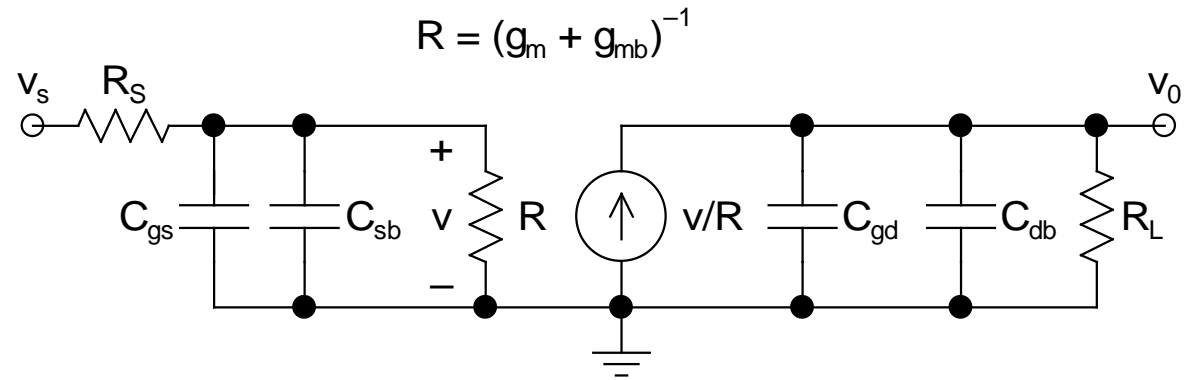


High-Frequency Equivalent


➤ *Note that all 4 capacitors would be present and none could be eliminated*

- *$C_{gs}$  and  $C_{sb}$  are in parallel*
  - ⇒ *Can be clubbed to a single capacitor  $C_1 = C_{gs} + C_{sb}$ , with time constant  $\tau_1$*
- Also,  *$C_{gd}$  and  $C_{db}$  can be clubbed to another single capacitor  $C_2 = C_{gd} + C_{db}$ , with time constant  $\tau_2$*
- *Again note the absence of any input-output coupling capacitor*
  - ⇒ *This circuit should also have very high  $f_H$*
- *$C_1$ :  $R_1^0 = R_s \parallel R$  and  $\tau_1 = R_1^0 C_1$*
- *$C_2$ :  $R_2^0 = R_L$  and  $\tau_2 = R_2^0 C_2$*

- **CC :**

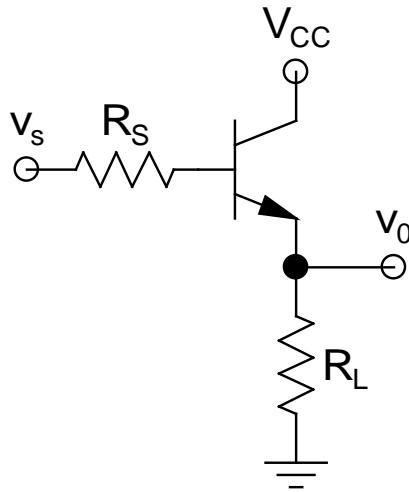

ac Schematic

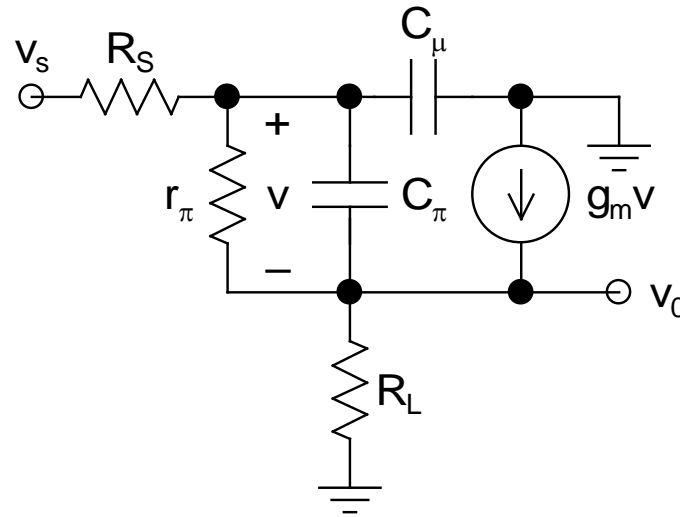

High-Frequency Equivalent

- *This circuit is slightly more involved - can't be done by inspection*
- *But we will have some other Standard Forms*

➤ This circuit has a *peculiar frequency response*

- *At midband:*

$$A_v = v_o/v_s = [R_L/(R_L + r_E)] \times [R_i/(R_i + R_S)]$$

$$R_i = r_\pi + (\beta + 1)R_L$$

- *Beyond  $f_H$ , as  $f \uparrow$ , reactance of  $C_\pi \downarrow$  earlier than that of  $C_\mu$  (since, in general,  $C_\pi \gg C_\mu$ )*
- *Eventually, reactance of  $C_\pi$  would approach zero, thus shorting out  $r_\pi$*
- *Under this condition, circuit behaves like a simple voltage divider with a gain of  $R_L/(R_L + R_S)$*
- *If  $f \uparrow$  further, then eventually  $C_\mu$  also will short out, and  $v_o$  would go to zero*

- Thus, the *frequency response* of this circuit looks like a *staircase*, having *two steps*


➤  $C_\pi$ :

- $R_\pi^0$  *can't be obtained by inspection*
- *Analyze the circuit and show that:*

$$R_\pi^0 = r_\pi \parallel \left( \frac{R_s + R_L}{1 + g_m R_L} \right)$$

$$\Rightarrow \tau_1 = R_\pi^0 C_\pi$$

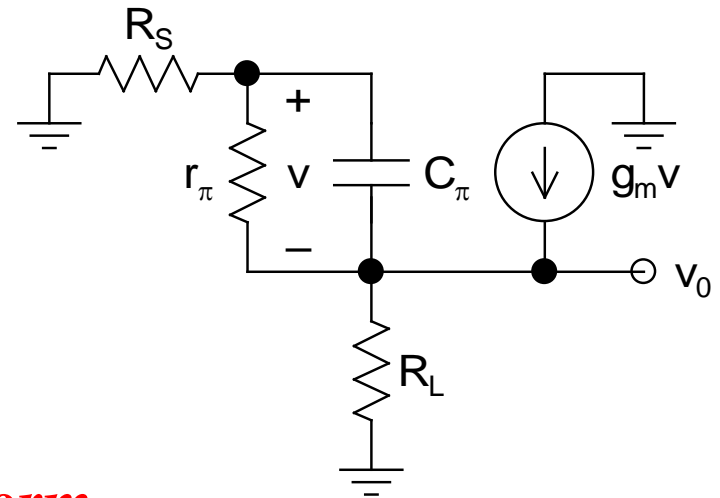- This is another *Standard Form* and the *topology should be carefully noted*




➤  $C_\mu$ :

- This is *relatively straightforward*
- *By inspection*:

$$R_{eq} = r_\pi + (\beta + 1) R_L$$

$$R_\mu^0 = R_S \parallel R_{eq}$$


$$\Rightarrow \tau_2 = R_\mu^0 C_\mu$$

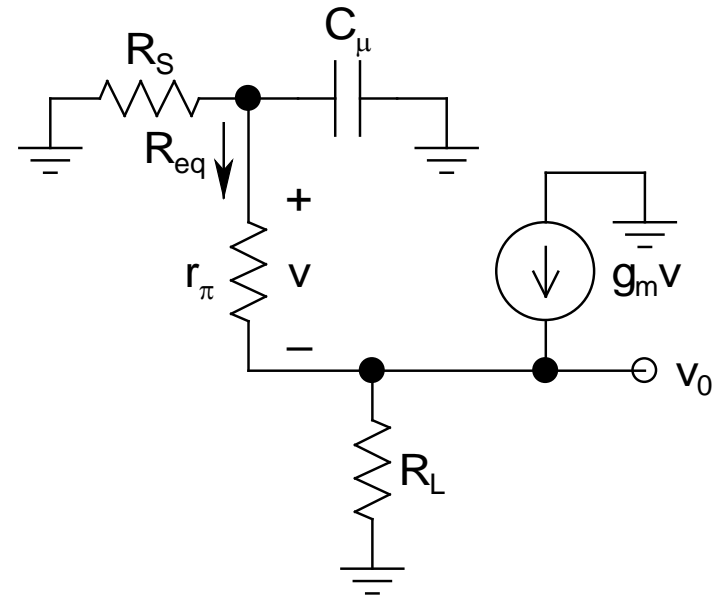


➤ *This circuit also has reasonably good frequency response*



- ***CD*** :

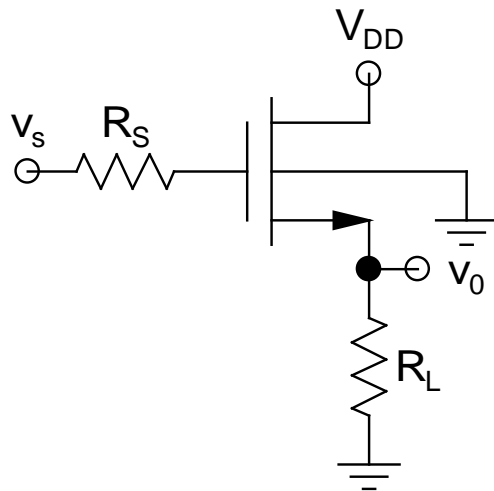

**ac Schematic**

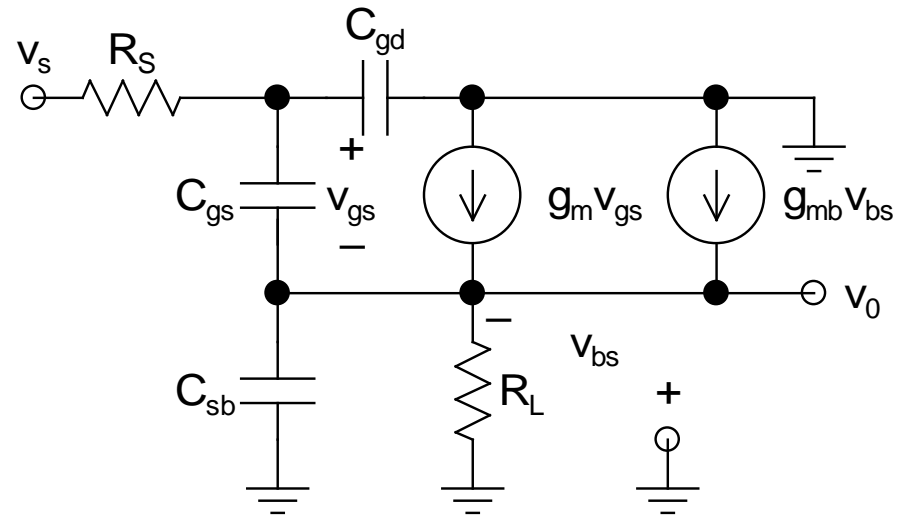

**High-Frequency Equivalent**

➤  ***$C_{db}$  absent due to obvious reason***

➤  $V_{bs} = -V_0$

$\Rightarrow g_{mb}v_{bs}$  is simple a conductance  $g_{mb}$ , in parallel with  $R_L$

$\Rightarrow$  Club them to  $R$  [ $= R_L || (1/g_{mb})$ ]

➤  $C_{gs}$  :

▪ Standard Form sans  $r_\pi$  (CC)

$$\Rightarrow R_{gs}^0 = \frac{R_s + R}{1 + g_m R}$$

$$\Rightarrow \tau_1 = R_{gs}^0 C_{gs}$$

➤  $C_{gd}$  :

■ *By inspection:*

$$R_{gd}^0 = R_S$$

$$\Rightarrow \tau_2 = R_{gd}^0 C_{gd}$$

➤  $C_{sb}$  :


■ *By inspection:*

$$R_{sb}^0 = R \parallel (1/g_m)$$


$$\Rightarrow \tau_3 = R_{sb}^0 C_{sb}$$

➤ *Loving it ? :)*

- ***CE(D)*** :

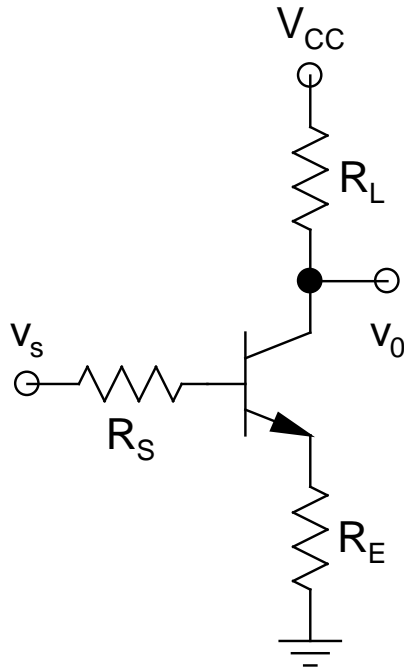

ac Schematic

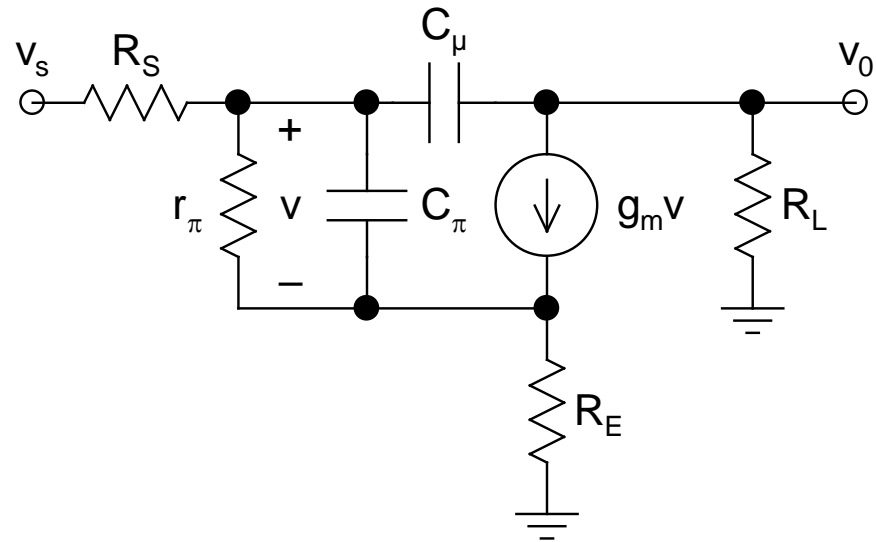

High-Frequency Equivalent

➤  $C_\pi$ :

- *Standard Form* (similar to CC, with  $R_L$  replaced by  $R_E$ )

$$\Rightarrow R_\pi^0 = r_\pi \parallel \left( \frac{R_S + R_E}{1 + g_m R_E} \right)$$

$$\Rightarrow \tau_1 = R_\pi^0 C_\pi$$

➤  $C_\mu$ :

- *Slightly more complicated*
- *Remove  $C_\pi$  and look across 2 terminals of  $C_\mu$*
- *Can be represented by a 2-port network*

- *Show that:*

$$R_{eq} = R_S || R_{\pi}$$


$$\text{with } R_{\pi} = r_{\pi}(1 + g_m R_E)$$

$$G_m = g_m / (1 + g_m R_E)$$

- This can be *easily identified* as a *Three-Legged Creature*


$$\Rightarrow R_{\mu}^0 = R_{eq} + R_L + G_m R_{eq} R_L$$
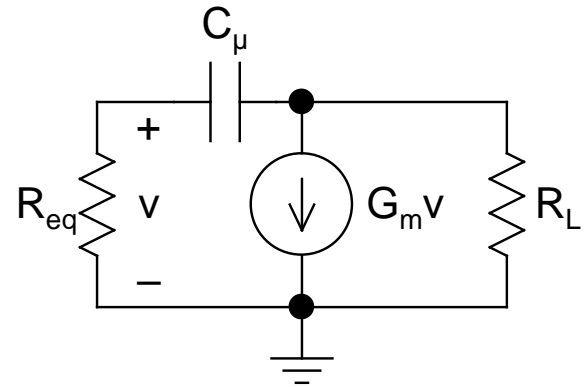
$$\Rightarrow \tau_2 = R_{\mu}^0 C_{\mu}$$




**2-Port Representation  
of a CE(D) Stage**

- ***CS(D)***:

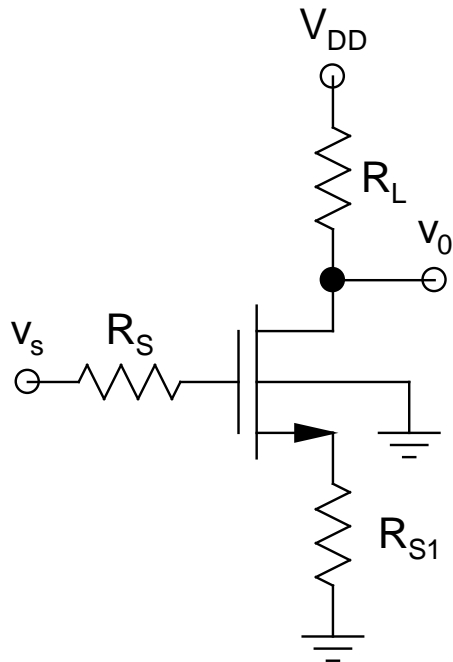


ac Schematic

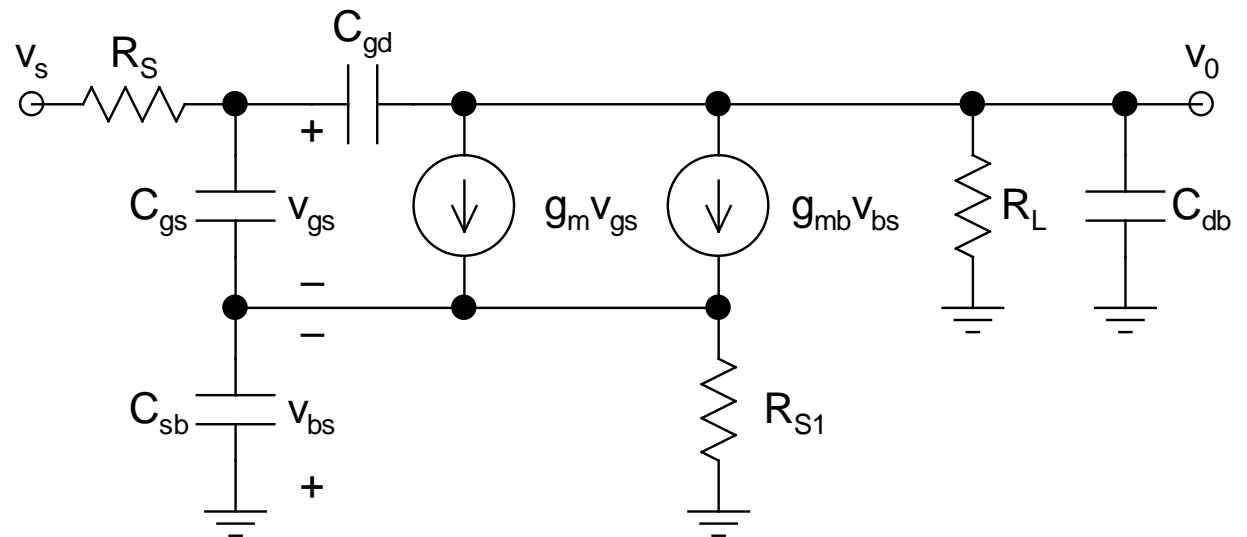

High-Frequency Equivalent

- *Inarguably, the most complex module*
  - *All the capacitors will be present*
  - *Except  $C_{db}$ , none else will have **Standard Form***
  - *Detailed analysis needed for each of them*

➤  $C_{gs}$ :

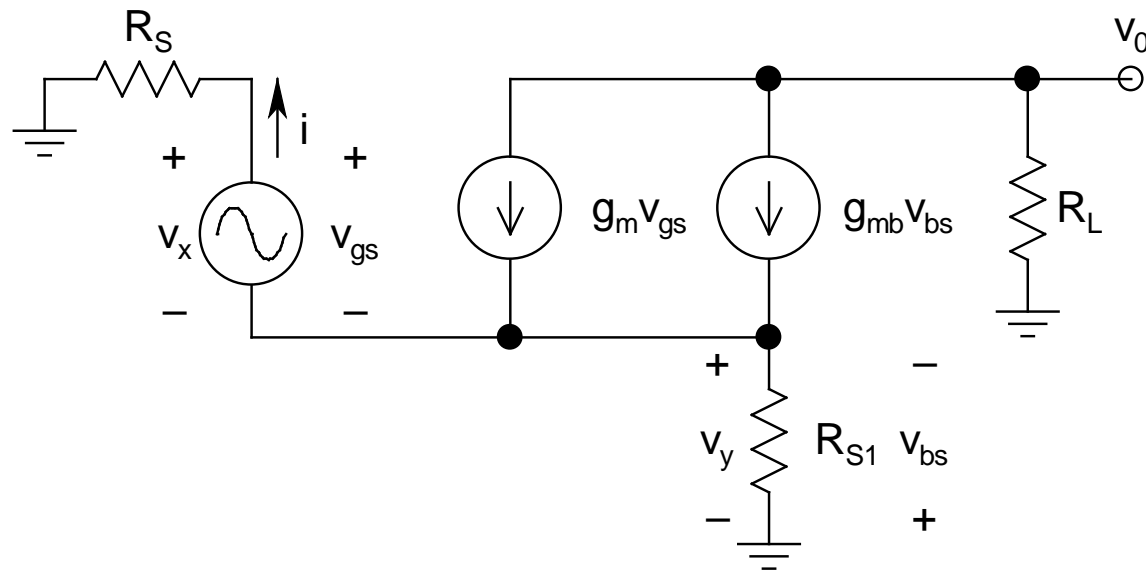



- *Open all other capacitors*
- *Replace  $C_{gs}$  by a voltage source  $v_x$*
- $v_{gs} = v_x$  and  $v_{bs} = -v_y$
- $i = (v_x + v_y)/R_S$ 

$$= g_m v_{gs} + g_{mb} v_{bs} - v_y/R_{S1}$$


$$= g_m v_x - g_{mb} v_y - v_y/R_{S1}$$

$$\Rightarrow v_y = [R_{S1}(g_m R_S - 1)]v_x / (R_{S1} + R_S + g_{mb} R_S R_{S1})$$

$$\Rightarrow R_{gs}^0 = \frac{v_x}{i} = \frac{R_S + R_{S1} + g_{mb} R_S R_{S1}}{1 + (g_m + g_{mb}) R_{S1}}$$

$$\Rightarrow \tau_1 = R_{gs}^0 C_{gs}$$
- Note that *if body effect is neglected ( $g_{mb}$  ignored)*, then it becomes *identical to that of a CD stage*

➤  $C_{gd}$ :

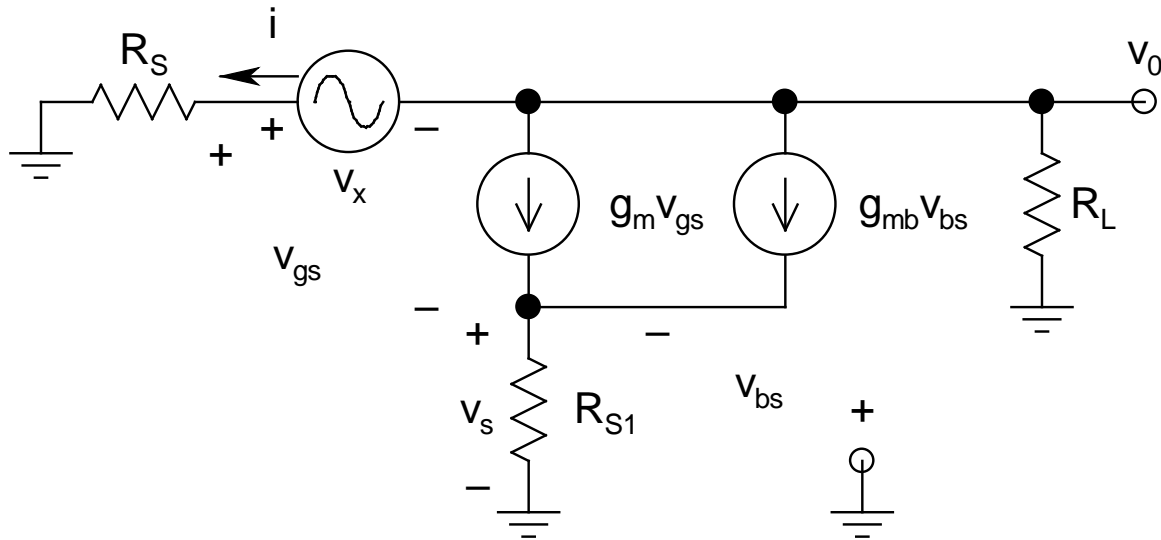

- *Open all other capacitors*
- *Replace  $C_{gd}$  by  $v_x$*
- $v_{gs} = (v_0 + v_x - v_s)$  and  $v_{bs} = -v_s$

- $i = (v_0 + v_x)/R_S$
- $v_s = (g_m v_{gs} + g_{mb} v_{bs})R_{S1}$   
 $\Rightarrow v_s = g_m R_{S1} (v_0 + v_x) / [1 + (g_m + g_{mb})R_{S1}]$
- ***KCL at output node:***  
 $i + g_m v_{gs} + g_{mb} v_{bs} + v_0/R_L = 0$
- ***The rest of the process involves huge amount of algebra!***
- ***Finally, if done right (check!)***

$$R_{gd}^0 = \frac{v_x}{i} = R_L \left[ 1 + g_m R_S + \frac{R_S}{R_L} - \frac{(g_m + g_{mb}) g_m R_S R_{S1}}{1 + (g_m + g_{mb}) R_{S1}} \right]$$

$$\Rightarrow \tau_2 = R_{gd}^0 C_{gd}$$

- *This is by far the most complicated calculation/expression*
- However, an *exact analysis* would have yielded a *4<sup>th</sup>-order transfer function* in  $\omega$ , which had to be *solved* to get the *individual poles*
- *This is still simpler than that :)*


➤ *C<sub>db</sub>*:

- *The easiest of the lot*
- *By inspection:*

$$R_{db}^0 = R_L$$

$$\Rightarrow \tau_3 = R_{db}^0 C_{db}$$


➤  $C_{sb}$ :

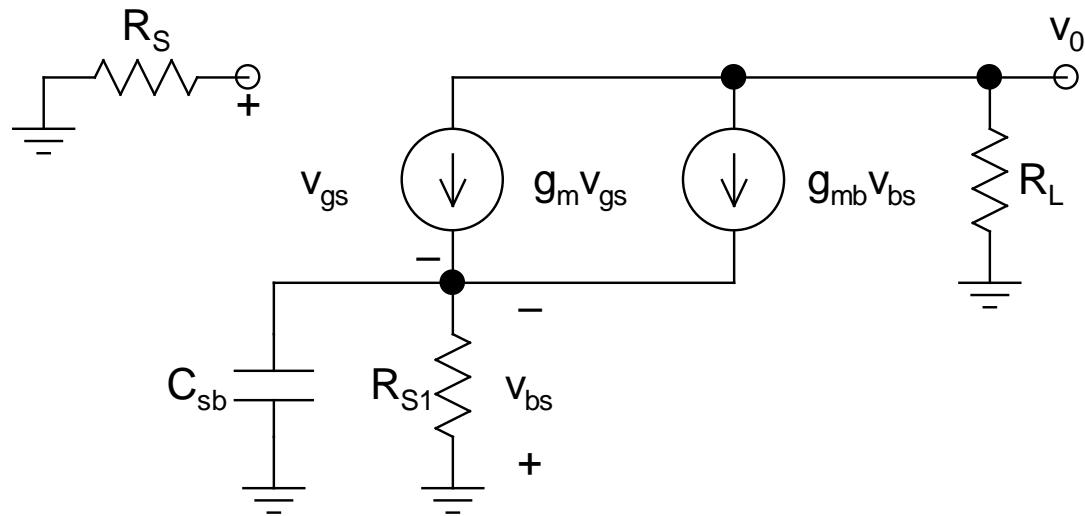


- *Analysis of this circuit is pretty straightforward*

$$R_{sb}^0 = \frac{R_{S1}}{1 + (g_m + g_{mb}) R_{S1}} \Rightarrow \tau_4 = R_{sb}^0 C_{sb}$$

- *npn Cascode:*

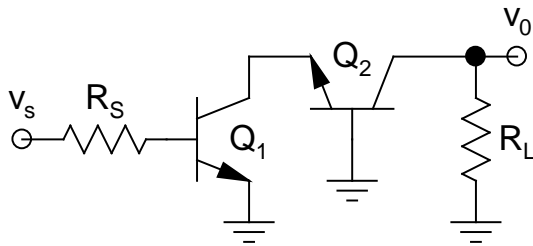

ac Schematic

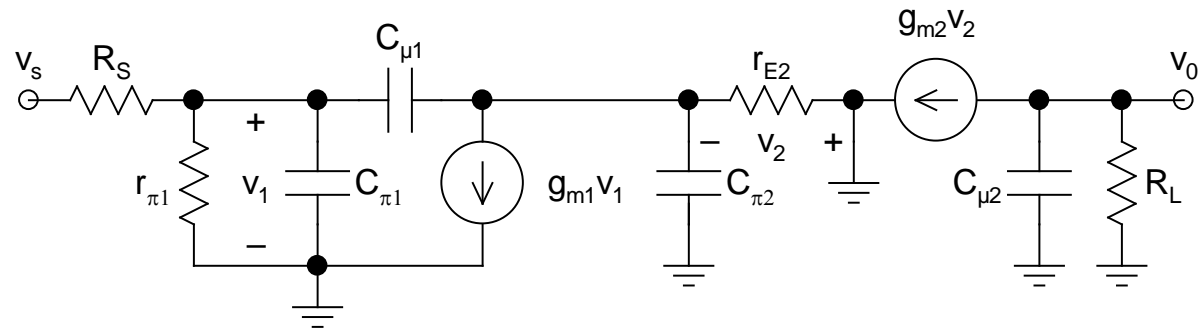

High-Frequency Equivalent

- *Looks intimidating*, but *extremely easy to solve* (just by inspection)
- Also known as *Wideband* (or *Broadband*) *Amplifier* due to its *superb frequency response*