

Lecture-15

On


INTRODUCTION TO ELECTRICAL ENGINEERING (ESO203)

- Step Response of an RC Circuit.
- Step Response of an RL Circuit.

Step Response of an RC Circuit (Cont..)

□ EXAMPLE:

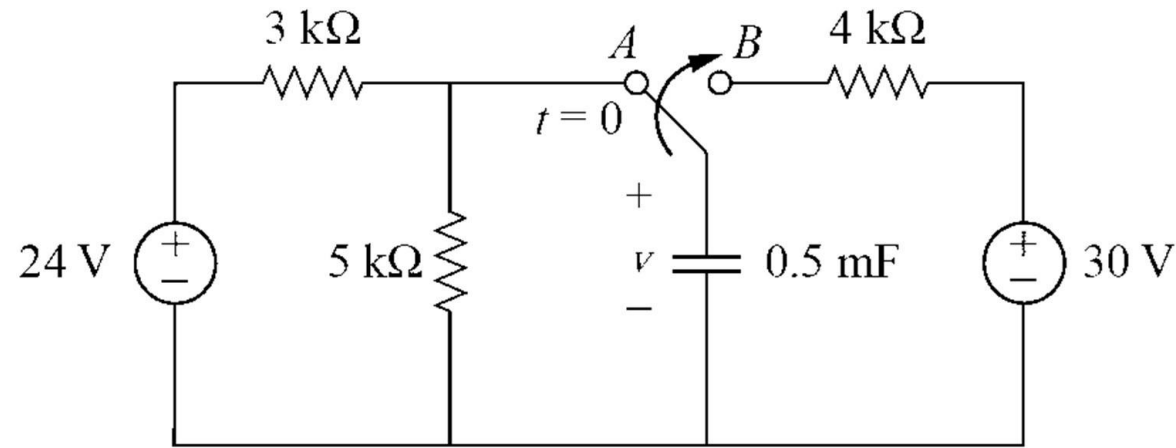
- The switch in Fig. below has been in position *A* for a long time. At $t=0$, the switch moves to *B*. Determine $v(t)$ for $t > 0$ and calculate its value at $t=1\text{s}$ and 4s .



Step Response of an RC Circuit (Cont..)

- For $t < 0$, the switch is at position A . Since v is the same as the voltage across the $5\text{ k}\Omega$ resistor, the voltage across the capacitor just before $t=0$ is obtained by voltage division as
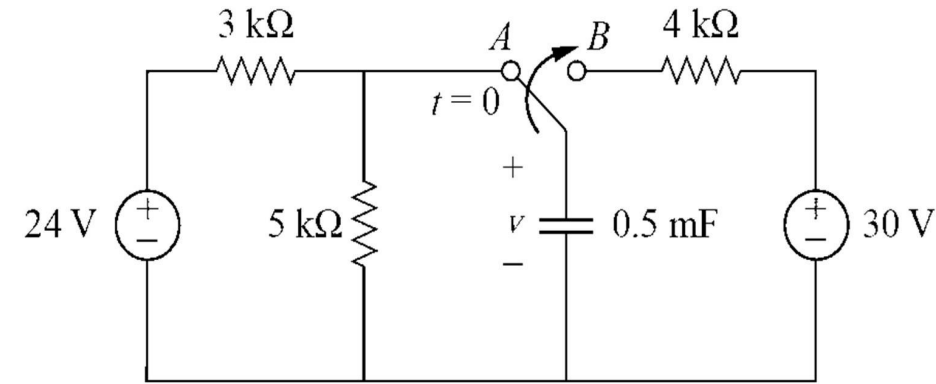
$$v = \frac{5}{5 + 3}(24) = 15\text{ V}$$



- As the capacitor voltage cannot change instantaneously, so,

$$v(0^-) = v(0^+) = v(0) = 15\text{ V}$$

- For $t > 0$, the switch is in position B . The thevenin resistance connected to the capacitor is $R_{Th} = 4\text{ k}\Omega$, and the time constant can be calculated as,

$$\tau = R t_h C = 4 \times 10^3 \times 5 \times 10^{-4} = 2\text{ s}$$

Step Response of an RC Circuit (Cont..)

- The capacitor acts like an open circuit to DC at steady state, therefore, $v(\infty) = 30V$.
- So,


$$\begin{aligned}v(t) &= v(\infty) + [v(0) - v(\infty)]e^{-\frac{t}{\tau}} \\&= 30 + (15 - 30)e^{-\frac{t}{\tau}}\end{aligned}$$

At $t=1$,

$$v(1) = 30 - 15 e^{-0.5} = 20.902 \text{ V}$$



At $t=4$,
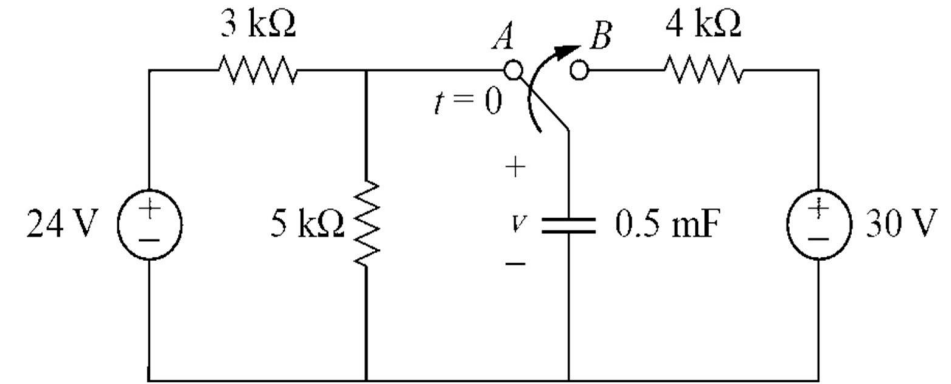
$$v(4) = 30 - 15 e^{-2} = 27.97 \text{ V}$$



Step Response of an RL Circuit

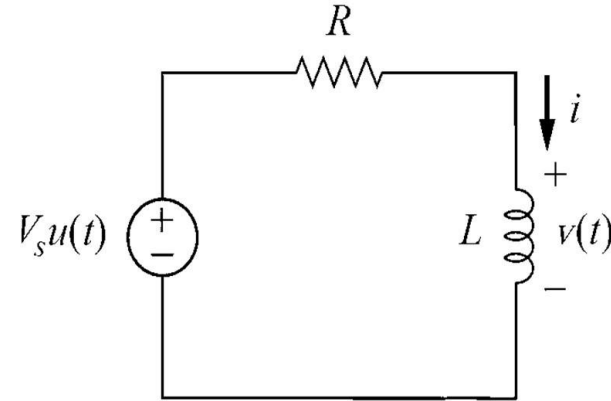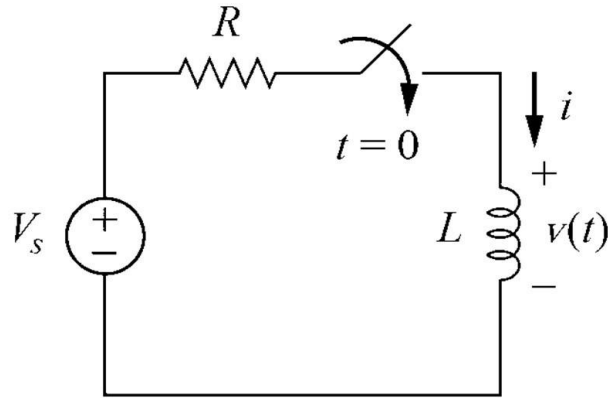- Consider the R - L circuit in left Figure below, which is replaced by the circuit in right Figure.
- We need to find the inductor current i as the circuit response.



Step Response of an RL Circuit (Cont..)

- There are two Methods to find the **R-L** response of the circuit:
 - Apply Kirchhoff's laws,
 - Apply alternate technique as explained earlier

Let the response be the sum of the natural current and the forced current,

$$i = i_f + i_n$$

As the natural response is always a decaying exponential, that is,

$$i_n = Ae^{-\frac{t}{\tau}}, \quad \tau = L/R$$

where A is a constant to be determined.


Step Response of an RL Circuit (Cont..)

- The forced response is the value of the current a long time after the switch is closed as shown in the Figure.
 - The natural response essentially dies out after five time constants.
 - At that time, the inductor becomes a short circuit, and the voltage across it will be zero.
 - The entire source voltage V_s appears across R .

Thus, the forced response is -

$$i_f = \frac{V_s}{R}$$
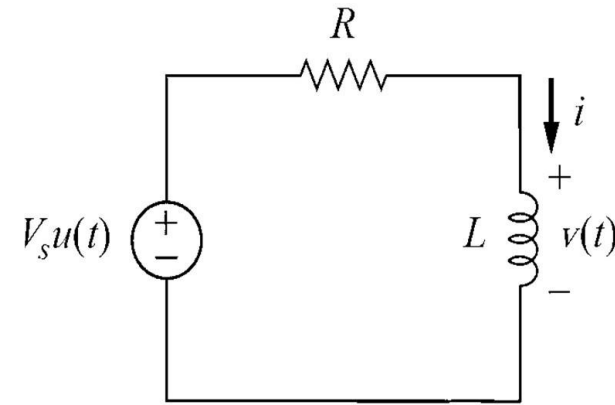
$$i = \frac{V_s}{R} + Ae^{-\frac{t}{\tau}}$$



Step Response of an RL Circuit (Cont..)

- **Next, determine the constant A from the initial value of i .**
- Let I_0 be the initial current through the inductor, which may come from a source other than V_s . **Since the current through the inductor cannot change instantaneously,**

$$i(0^-) = i(0^+) = I_0$$

Thus, at $t = 0$, Equation $i = \frac{V_s}{R} + Ae^{-\frac{t}{\tau}}$ becomes

$$I_0 = \frac{V_s}{R} + A$$

From this, we obtain A as

$$A = I_0 - \frac{V_s}{R}$$

Step Response of an RL Circuit (Cont..)


- Substituting for A , we get

$$i = \frac{V_s}{R} + (I_0 - \frac{V_s}{R}) e^{-\frac{t}{\tau}}$$

- This is the complete response of the R - L circuit as shown in the Figure
- The response in above equation may be written as

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-\frac{t}{\tau}}$$

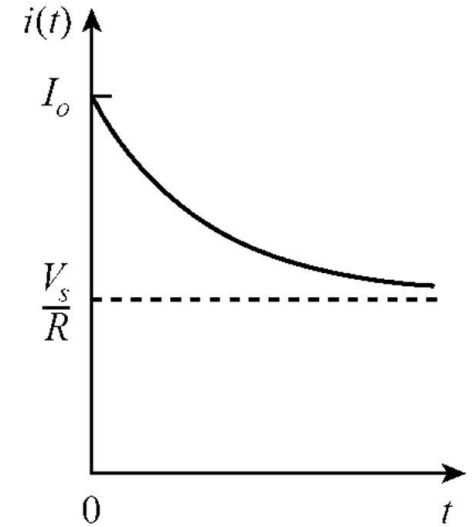where $i(0)$ and $i(\infty)$ are the initial and final values of i



Step Response of an RL Circuit (Cont..)

If $I_0 = 0$, then

$$i(t) = \begin{cases} 0, & t < 0 \\ \frac{V_s}{R} (1 - e^{-\frac{t}{\tau}}), & t > 0 \end{cases}$$

or

$$i(t) = \frac{V_s}{R} (1 - e^{-\frac{t}{\tau}}) u(t)$$

This equation is called the step response of the *R-L* circuit.


Step Response of an RL Circuit (Cont..)

The voltage across the inductor is, $v = L \frac{di}{dt}$



$$i(t) = \frac{V_s}{R} (1 - e^{-\frac{t}{\tau}}) u(t)$$

$$v(t) = L \frac{di}{dt} = \frac{L}{\tau R} V_s e^{-\frac{t}{\tau}} \quad , \quad t > 0 \quad \text{or}$$

$$v(t) = V_s e^{-\frac{t}{\tau}} u(t)$$

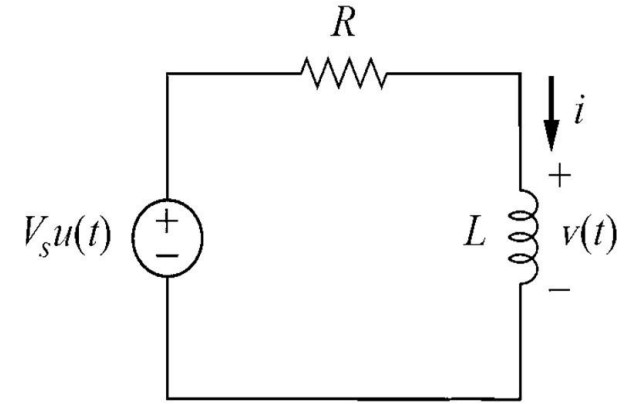

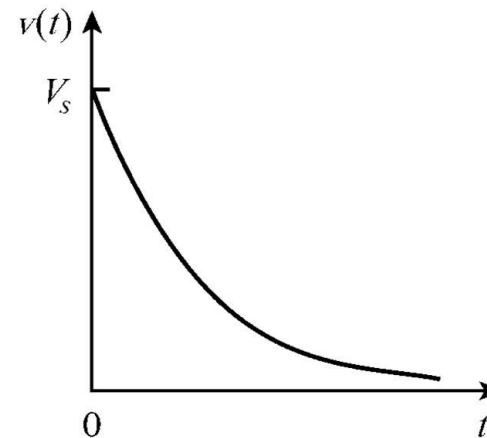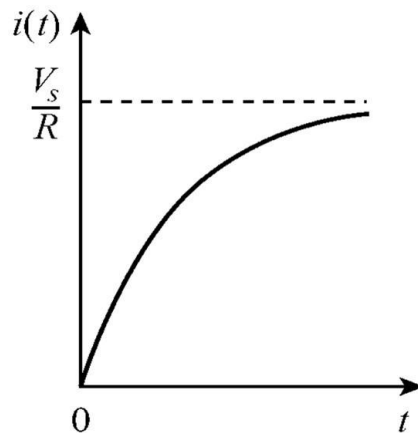
Figure, below, shows the step responses of inductor current and voltage



Step Response of an RL Circuit (Cont..)

□ EXAMPLE:

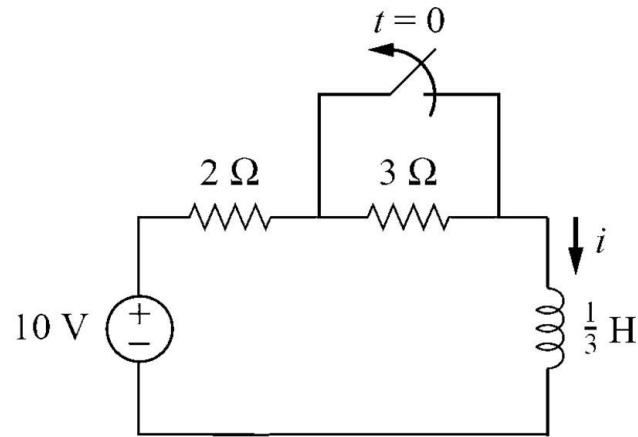- Find $i(t)$ in the circuit in Fig. below for $t > 0$. Assume that the switch has been closed for a long time.



Step Response of an RL Circuit (Cont..)

□ Solution:

- When $t < 0$, the 3Ω resistor is short-circuited, and the inductor also acts like a short circuit. The current through the inductor at $t = 0^-$ is

$$i(0^-) = \frac{10}{2} = 5 \text{ A}$$

- Since the inductor current cannot change instantaneously, so,


$$i(0) = i(0^-) = i(0^+) = 5 \text{ A}$$

- When $t > 0$, the switch is open. Therefore, 2Ω and 3Ω resistors are now in series, so,

$$i(\infty) = \frac{10}{2 + 3} = 2 \text{ A}$$

- The Thevenin resistance across the inductor terminals is

$$R_{Th} = 2 + 3 = 5 \Omega$$

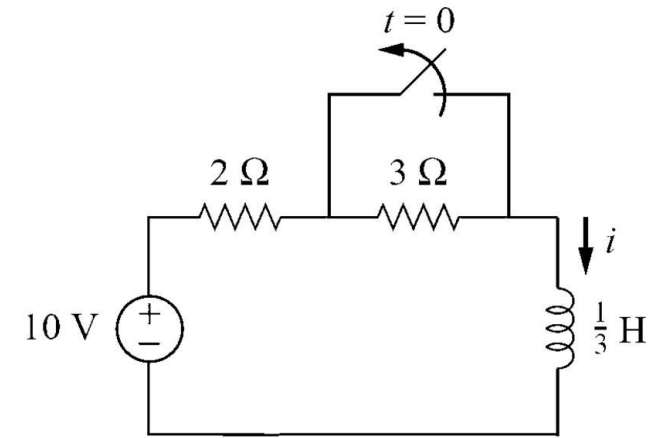

Step Response of an RL Circuit (Cont..)

The value of time constant,

$$\tau = \frac{L}{R_{Th}} = \frac{\frac{1}{3}}{5} = \frac{1}{15} \text{ s}$$

Thus,

$$\begin{aligned} i(t) &= i(\infty) + [i(0) - i(\infty)]e^{-\frac{t}{\tau}} \\ &= 2 + (5 - 2)e^{-15t} \\ &= 2 + 3e^{-15t} \text{ A, } t > 0 \end{aligned}$$

