 


➤ Thus, the **complete equivalent**:

➤ **By inspection**:

$$A_v = \frac{V_o}{V_i} = -g_{m1} (r_{01} \parallel R_{\text{eff}})$$

$$= -\frac{g_{m1}}{g_{mb2} + g_{01} + g_{02}}$$



Complete Equivalent

➤ Now, in general,

$$g_{mb2} \gg (g_{01} + g_{02})$$

$$\Rightarrow A_v \approx -\frac{g_{m1}}{g_{mb2}} = -\frac{g_{m1}}{\chi_2 g_{m2}} = -\frac{1}{\chi_2} \sqrt{\frac{(W/L)_1}{(W/L)_2}}$$

$$\chi_2 = \frac{\gamma}{2\sqrt{2\phi_F + V_{DD}/2}} < 1$$

\Rightarrow **Improvement** as compared to previous stage

➤ Now, if M_2 can be put in its *separate island*, then *S_2 and B_2 can be connected together*


$$\Rightarrow v_{sb2} = 0 \Rightarrow g_{mb2}v_{sb2} = 0$$

$$\Rightarrow A_v = -\frac{g_{m1}}{g_{01} + g_{02}}$$


- Can be *very large* (*a magnitude greater than 100 is possible*)

- $R_0 = (g_{mb2} + g_{01} + g_{02})^{-1}$ (*with body effect*)
- $R_0 = (g_{01} + g_{02})^{-1}$ (*without body effect*)
- The latter case produces *very high* R_0
- Thus, this circuit produces *much superior performance* as compared to the *saturated enhancement load*, in terms of:
 - *Rail-to-rail swing*
 - *With island technology:*
 - ❖ *Very large A_v and R_0*
 - *Without island technology:*
 - ❖ *Moderate A_v and R_0*

- ***Complementary PMOS Load:***
 - Also known as ***CMOS Gain Stage***
 - ***CMOS*** (***Complementary MOS***: ***Having both NMOS and PMOS*** in the circuit)
 - ***The Ultimate: Much superior performance*** and ***outclasses all other gain stages***
 - ***Widely used***
 - ***High A_v and R_o***
 - ***Easy to bias and easy to operate***
 - ***Design also extremely simple***
 - ***Doesn't produce any anomalies***

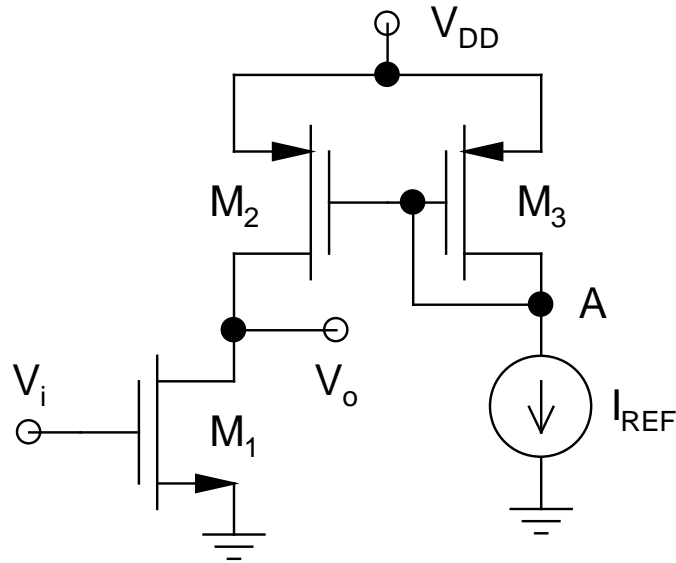

Circuit Schematic

 

ac Midband Equivalent

- *M_1 body connected to ground, M_2 - M_3 bodies connected to V_{DD}*
 - *No body effect problem for any of the devices (biggest advantage of this circuit)*

- Identify M_2 - M_3 as a *PMOS current mirror* (*perfectly matched*)
 - $\Rightarrow I_{D1} = I_{D2} = I_{D3} = I_{REF}$
- This gives the *required value* of V_I
 - \Rightarrow *DC biasing* of the circuit is *pretty straightforward*
- For *ac analysis*, we note that *node A* is *both open and short* at the same time (similar to *npn gain stage* with *pnp active load*)
 - $\Rightarrow A_v = v_o/v_i = -g_{m1}R_0$
 - $R_0 (= r_{o1}||r_{o2})$: *Output resistance* of the circuit

- **Caution:** $r_{o1} \neq r_{o2}$, even though M_1 and M_2 carry the same *DC bias current*, since $\lambda_n \neq \lambda_p$ (in general)
- This circuit is *immensely useful* since it gives *extremely large voltage gain and output resistance*
- Only **problem** is that it needs a *PMOS current mirror*, thus necessitating use of an *extra PMOS*
- An **even better design** exists, which *eliminates* the need for this *extra PMOS*


- ***A Better CMOS Gain Stage:***

- *No body effect issue*
- However, there are *some design issues*
- M_1 - M_2 have *same magnitude* of the *threshold voltage*:

$$V_{TN0} = |V_{TP0}|$$

- *Process transconductance parameters:*
 
$$k'_N = \mu_n C'_{ox} \quad \text{and} \quad k'_P = \mu_p C'_{ox}$$




Circuit Schematic

- *Oxide capacitance per unit area* ($C'_{ox} = \epsilon_{ox} / t_{ox}$) *same for both devices*, since they have *same* t_{ox}
- However, $\mu_n \sim 2\mu_p$ (for Si)
- Thus, $k'_N = 2k'_P$
- *Ideal DC bias point* of the circuit is $V_I = V_O = V_{DD}/2$ (yields $V_{GSn} = |V_{GSp}|$ and $V_{DSn} = |V_{DSp}|$)
- Can be achieved only if the stage is *completely balanced* (*same threshold voltage magnitude* and *same device transconductance parameter*)
- Thus, k_N and k_P need to be matched


- *Can be achieved by making $(W/L)_p = 2(W/L)_n$*
- If *CLM effect* is *not that important*, or if $\lambda_n = \lambda_p$, then this procedure works out *just fine*
- However, if $\lambda_n \neq \lambda_p$, then for *balancing the circuit*, the following relation *must hold* (*show!*):

$$(W/L)_p(1 + \lambda_p V_{DD}/2) = 2(W/L)_n(1 + \lambda_n V_{DD}/2)$$
- Under this condition, $k_N \neq k_P$, but the circuit will be *perfectly matched and balanced*
- Known as: *Stage unmatched by nature, but matched by performance*

➤ *ac Analysis:*

 

ac Midband Equivalent

 

Simplified Equivalent

➤ *By inspection:*

$$\begin{aligned} A_v &= - (g_{mn} + g_{mp}) R_0 \\ &= - (g_{mn} + g_{mp}) / (g_{0n} + g_{0p}) \end{aligned}$$

$$R_0 = r_{0n} || r_{0p} = (g_{0n} + g_{0p})^{-1}$$

➤ *Very high A_v and R_0*

➤ *Extremely popular* and *widely used circuit*

➤ Sometimes, *level shifters* are used at the *input* for *better ease* of application