

Lecture-21


On

INTRODUCTION TO ELECTRICAL ENGINEERING (ESO203)

- Three phase system.
- Y-Y system.
- Y- Δ system.



Three Phase Circuits

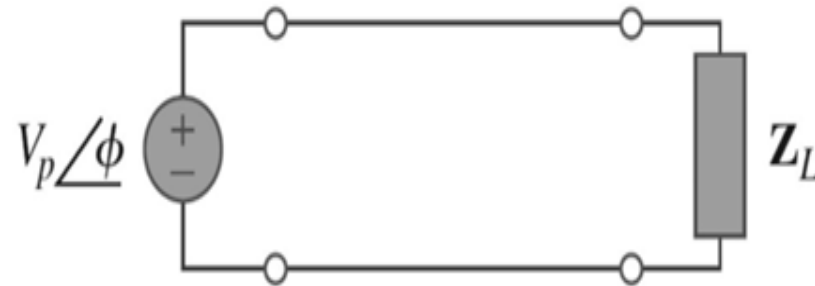- So far in this course, we have been dealing with single-phase circuits.
- A single-phase **AC** power system consists of a generator connected through a pair of wires (a transmission line) to a load.
- This is illustrated in the below figure, where a single-phase two wire system is used.
- Here V_p is the rms magnitude of the source voltage and ϕ is the phase.



Three Phase Circuits (Cont...)

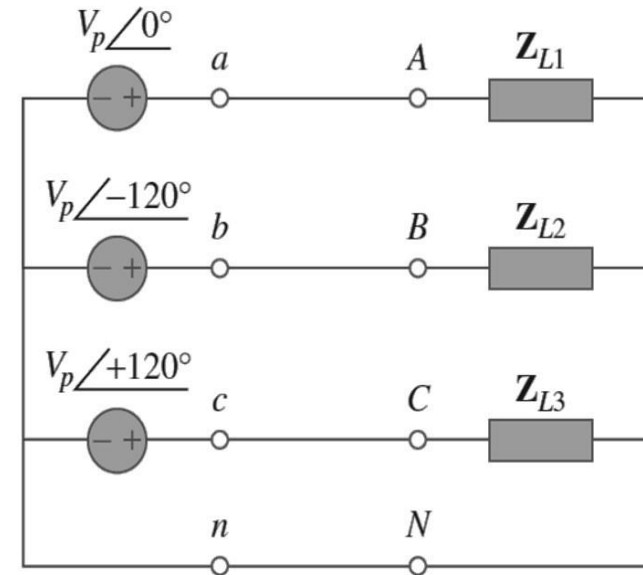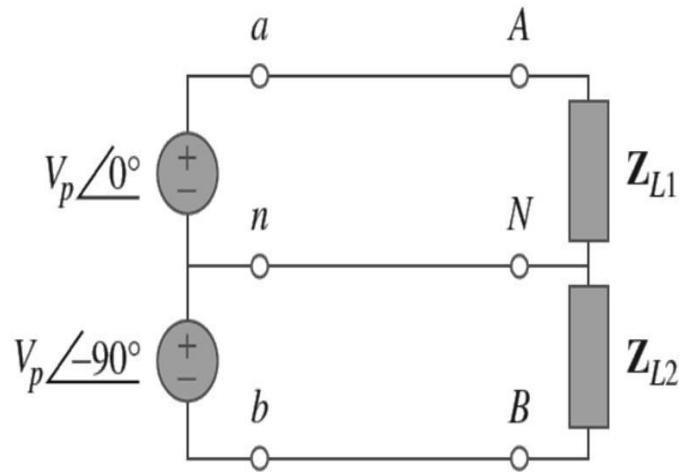- Circuits or systems in which the ac sources operate at the same frequency but different phases are known as **polyphase**.
- The figure on the left below shows a two-phase three-wire system, and the figure on the right shows a three-phase four wire system.




Three Phase Circuits (Cont...)

- As distinct from a single-phase system, a two-phase system is produced by a generator consisting of two coils placed perpendicular to each other so that the voltage generated by one lags the other by 90° .
- In the same way, a three-phase system is produced by a generator consisting of three sources having the same amplitude and frequency but out of phase with each other by 120° .
- Since the three-phase system is by far the most prevalent and most economical polyphase system, our discussion will mainly be on three-phase systems.
- Three-phase systems are important for at least three reasons.
 1. Nearly all electric power is generated and distributed in three-phase, at the operating frequency of 50 or 60 Hz.
 2. The instantaneous power in a three-phase system can be constant (not pulsating), as will be discussed later.
 3. The three-phase system is more economical than single phase system as the amount of wire required for a three-phase system is lesser than the amount of wire needed for an equivalent single-phase system.



Balanced Three-Phase Voltages

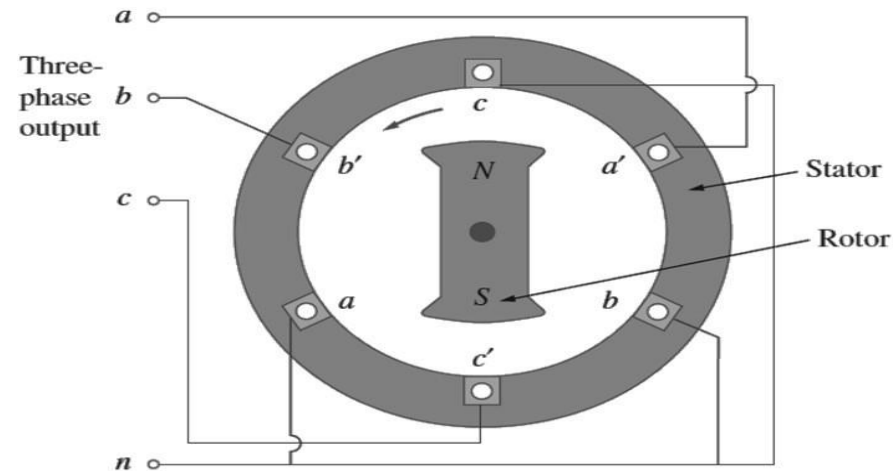- Three-phase voltages are often produced with a three-phase ac generator (or alternator) whose cross-sectional view is shown below.
- The generator basically consists of a rotating magnet (called the *rotor*) surrounded by a stationary winding (called the *stator*).





Balanced Three-Phase Voltages (Cont..)

- Three separate windings or coils with terminals $a - a'$, $b - b'$, and $c - c'$ and are physically placed 120° apart around the stator.
- Terminals a and a' for example, stand for one of the ends of coils going into and the other end coming out of the page.
- As the rotor rotates, its magnetic field “cuts” the flux from the three coils and induces voltages in the coils.
- Because the coils are placed 120° apart, the induced voltages in the coils are equal in magnitude but out of phase by 120° as shown below.

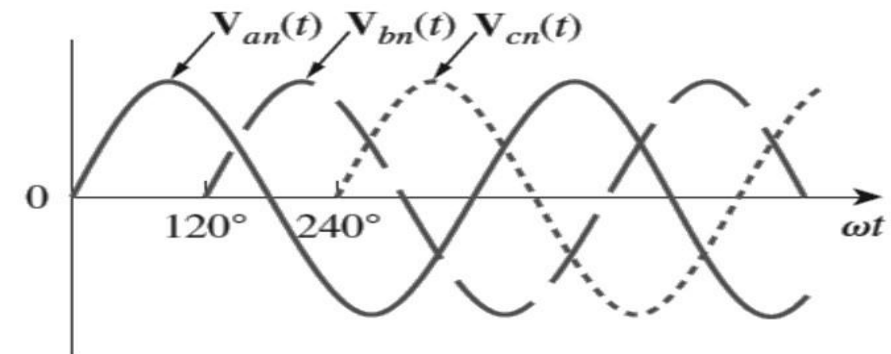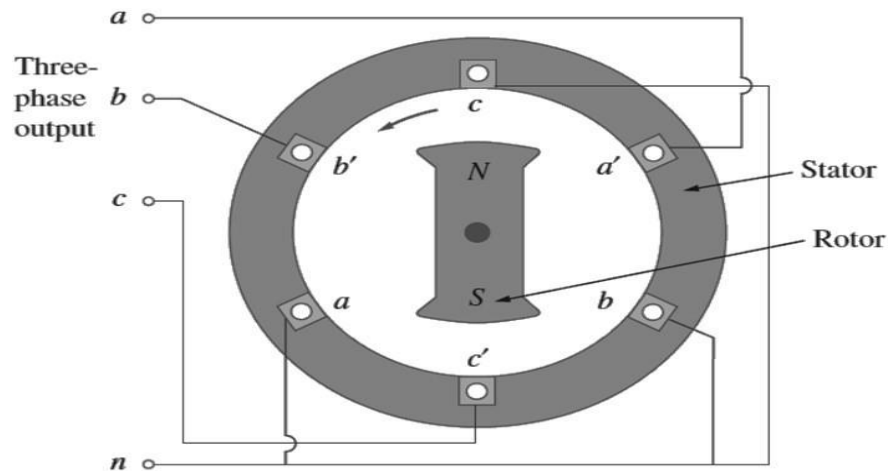

Balanced Three-Phase Voltages (Cont..)

- Since each coil can be regarded as a single-phase generator by itself, the three-phase generator can supply power to both single-phase and three-phase loads.
- A typical three-phase system consists of three voltage sources connected to loads by three or four wires (or transmission lines)
- A three-phase system is equivalent to three single-phase circuits.
- The voltage sources can be either wye (Y)-connected or delta (Δ)-connected as shown below.

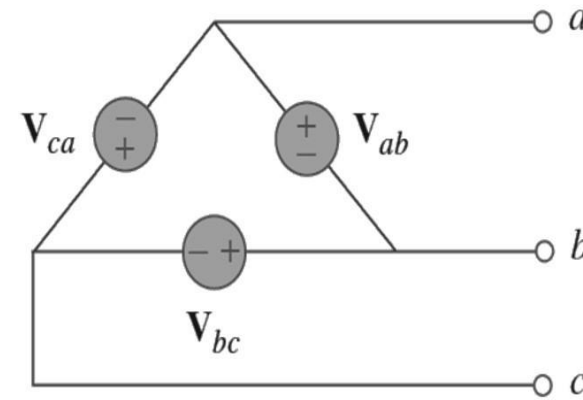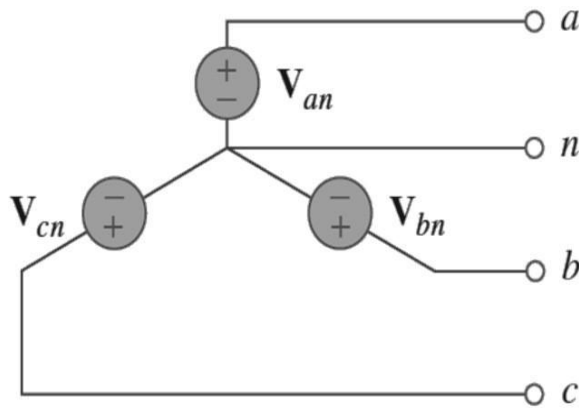



Balanced Three-Phase Voltages (Cont..)

- Let us consider the wye-connected voltages for now.
- The voltages V_{an} , V_{bn} , and V_{cn} are respectively between lines a , b , and c , and the neutral line n .
- These voltages are called *phase voltages*.
- If the voltage sources have the same amplitude and frequency ω and are out of phase with each other by 120° the voltages are said to be *balanced*.

- This implies that

$$V_{an} + V_{bn} + V_{cn} = 0$$


$$|V_{an}| = |V_{bn}| = |V_{cn}|$$

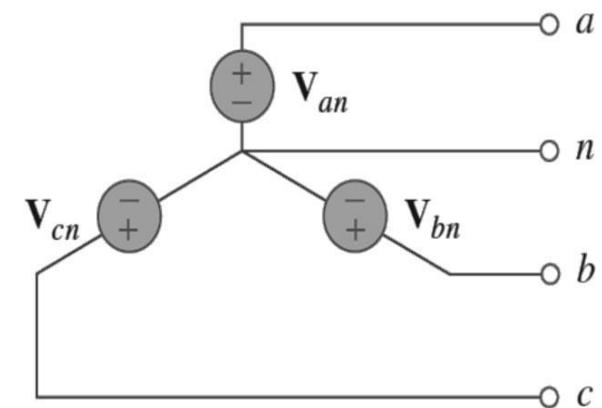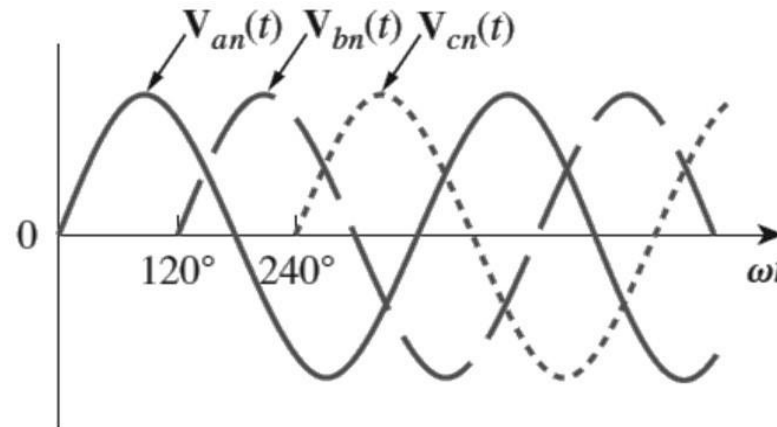

- Thus, balanced phase voltages are equal in magnitude and are out of phase with each other by 120° .

Balanced Three-Phase Voltages (Cont..)

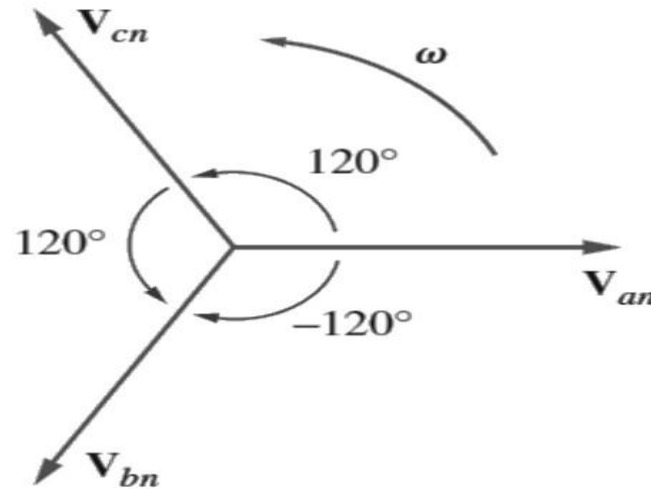- Since the three-phase voltages are 120° out of phase with each other, there are two possible combinations.



- One possibility is as shown above and expressed mathematically as.


$$V_{an} = V_p \angle 0^\circ$$

$$V_{bn} = V_p \angle -120^\circ$$

$$V_{cn} = V_p \angle -240^\circ = V_p \angle 120^\circ$$


Balanced Three-Phase Voltages (Cont..)

- Here V_p is the effective or **RMS** value of the phase voltage.
- Please note, as a common tradition in power systems, in this module voltage and current are considered in rms values unless otherwise stated.
- This is known as the *abc sequence* or *positive sequence*.
- In this phase sequence, V_{an} leads V_{bn} which in turn leads V_{cn} .
- This sequence is produced when the rotor in the figure, discussed earlier in this lecture, rotates counterclockwise.
- The phase sequence may also be regarded as the order in which the phase voltages reach their peak (or maximum) values with respect to time.

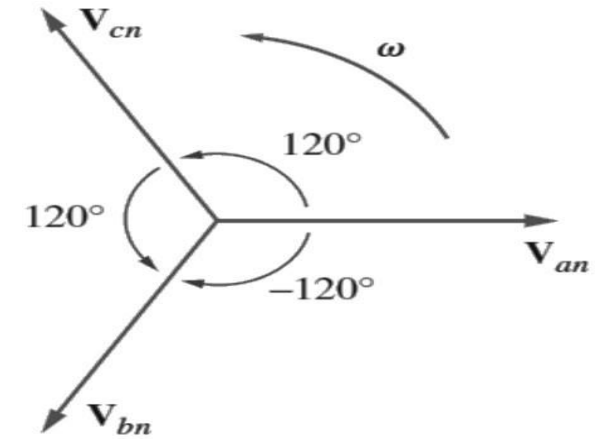


Balanced Three-Phase Voltages (Cont..)

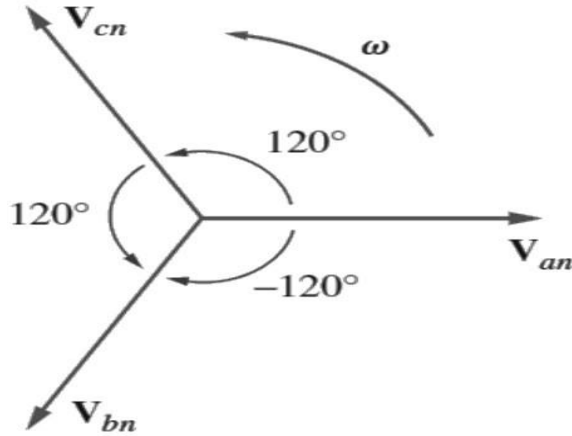- The second possible phase combination is as shown in the figure below.



(i) abc sequence or positive sequence.

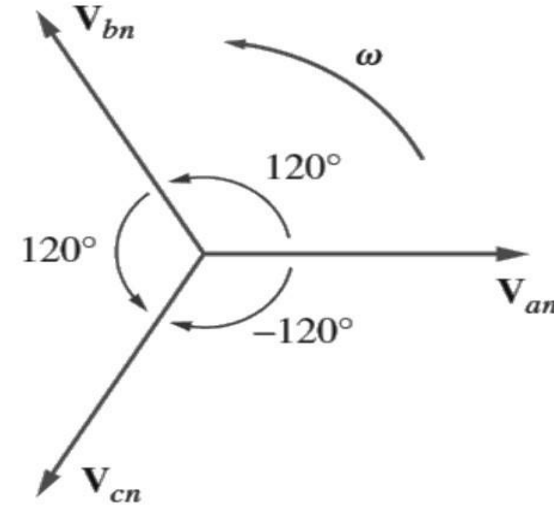

(ii) acb sequence or negative sequence.

- This is expressed mathematically as.

$$V_{an} = V_p \angle 0^\circ$$

$$V_{cn} = V_p \angle -120^\circ$$

$$V_{bn} = V_p \angle -240^\circ = V_p \angle 120^\circ$$

Balanced Three-Phase Voltages (Cont..)


- This is known as the *acb sequence* or *negative sequence*.
- In this phase sequence, V_{an} leads V_{cn} which in turn leads V_{bn} .
- This sequence is produced when the rotor in previous figure rotates clockwise.

$$\begin{aligned} V_{an} + V_{bn} + V_{cn} &= V_p \angle 0^\circ + V_p \angle -120^\circ + V_p \angle 120^\circ \\ &= V_p (1 - 0.5 - j0.866 - 0.5 + j0.866) \\ &= 0 \end{aligned}$$

- The phase sequence is determined by the order in which the phasors pass through a fixed point in the phase diagram.

Balanced Three-Phase Voltages (Cont..)

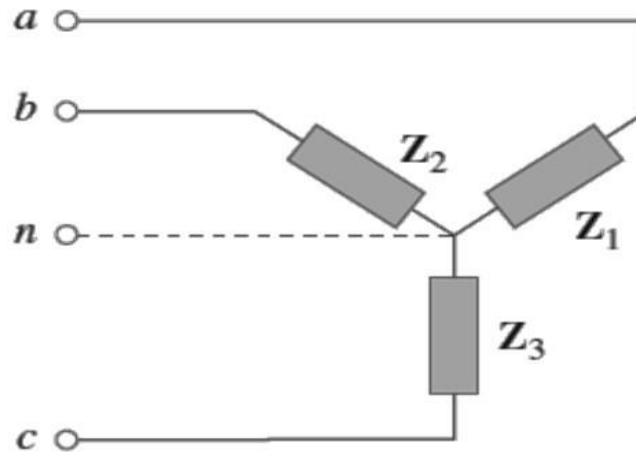
- Like the generator connections, a three-phase load can be either **wye-connected** or **delta-connected**, depending on the end application.
- Figure below shows a **wye (Y)-connected** load.



- The neutral line in the above figure may or may not be there, depending on whether the system is **four-** or **three-** **wire**.

Balanced Three-Phase Voltages (Cont..)

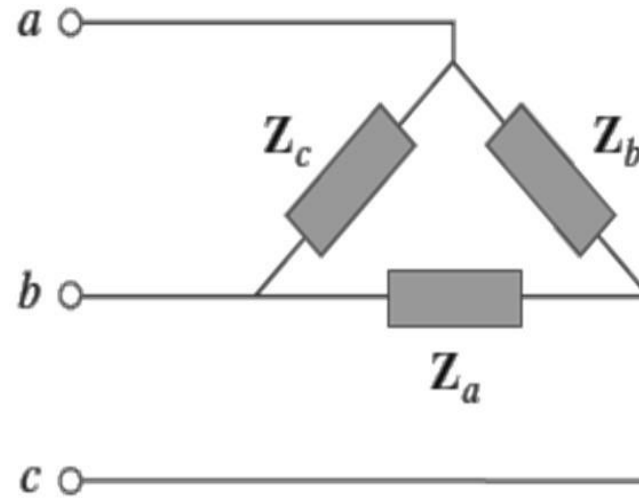- Figure below shows a **delta (Δ)-connected** load.



- A neutral line is topologically impossible for a delta connection.

Balanced Three-Phase Voltages (Cont..)

- A wye- or delta-connected load is said to be *unbalanced* if the phase impedances are not equal in magnitude or out of phase.
- A balanced load is one in which the phase impedances are equal in magnitude and in phase.
- For a balanced wye (Y)-connected load,

$$\mathbf{Z}_1 = \mathbf{Z}_2 = \mathbf{Z}_3 = \mathbf{Z}_Y$$

- For a balanced delta (Δ)-connected load,

$$\mathbf{Z}_a = \mathbf{Z}_b = \mathbf{Z}_c = \mathbf{Z}_\Delta$$

- We recall from our previous discussions that,

$$\mathbf{Z}_\Delta = 3\mathbf{Z}_Y \text{ or } \mathbf{Z}_Y = \mathbf{Z}_\Delta/3$$

- So we can say that a wye (Y)-connected load can be transformed into a delta connected load, or vice versa using Y- Δ transformation discussed earlier.

Balanced Three-Phase Voltages (Cont..)

- Since both the three-phase source and the three-phase load can be either **wye (Y)**- or **delta (Δ)**-connected, we have four possible connections:
 1. Y-Y connection (i.e., Y-connected source with a Y-connected load)
 2. Y- Δ connection
 3. Δ - Δ connection
 4. Δ -Y connection.
- It is important to note that a balanced **delta-connected** load is more common than a balanced **wye- connected load**.
- This is due to the ease with which loads may be added or removed from each phase of a delta- connected load.
- It is very difficult with a wye-connected load because the neutral may not be accessible.
- On the other hand, **delta-connected sources** are not common in **practice** because of the circulating current that will result in the delta-mesh if the three-phase voltages are slightly unbalanced.

Balanced Three-Phase Voltages (Cont..)

Example:

- Determine the phase sequence of the set of voltages $v_{an} = 200 \cos(\omega t + 10)$, $v_{bn} = 200 \cos(\omega t - 230)$, $v_{cn} = 200 \cos(\omega t - 110)$?

Solution: We first convert the voltages to phasors as,

$$\mathbf{V}_{an} = 200\angle 10^\circ, \mathbf{V}_{bn} = 200\angle -230^\circ, \mathbf{V}_{cn} = 200\angle -110^\circ$$


We notice that \mathbf{V}_{an} leads \mathbf{V}_{cn} by 120° and \mathbf{V}_{cn} in turn leads \mathbf{V}_{bn} by 120° . Hence, we have an *acb* sequence.

Balanced Wye Wye Connection

- We begin with the **Y-Y system**, because any balanced three-phase system can be reduced to an equivalent **Y-Y system**.
- Therefore, analysis of this system is considered as the key to solve all balanced three-phase systems.
- A balanced **Y-Y system** is a three-phase system with a balanced **Y-connected source** and a balanced **Y-connected load**.
- Consider a balanced four-wire **Y-Y system**, where a **Y-connected load** is connected to a **Y-connected source**.

Balanced Wye Wye Connection (cont...)

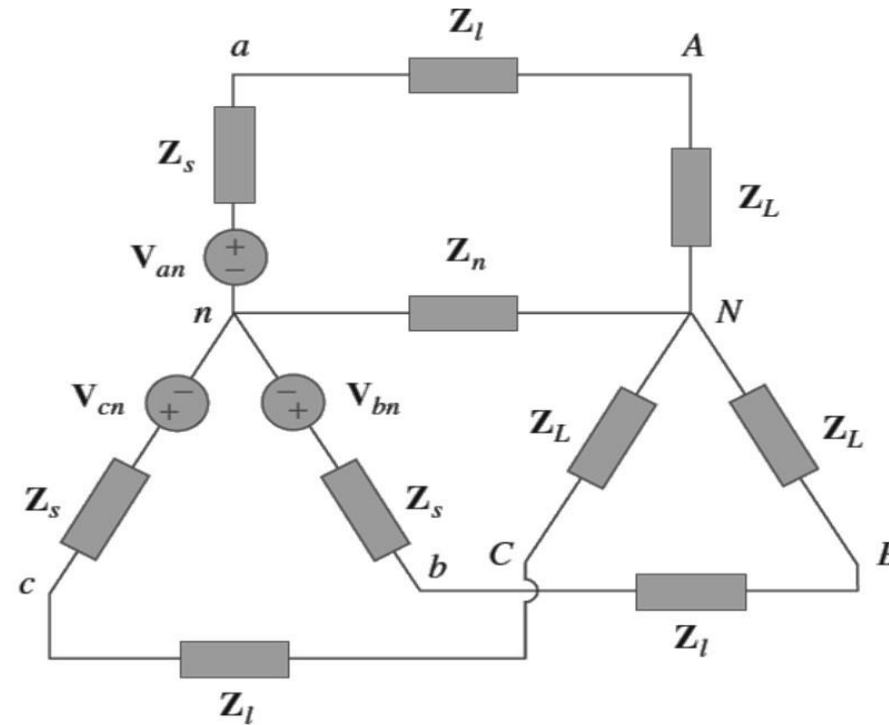
- We assume a balanced load so that load impedances are equal.
- Although the impedance $\mathbf{Z_Y}$ is the total load impedance per phase, it may also be regarded as the sum of the source impedance $\mathbf{Z_s}$, line impedance $\mathbf{Z_l}$, and load impedance $\mathbf{Z_L}$ for each phase, since these impedances are in series.



Balanced Wye Wye Connection (cont...)




- As illustrated in the previous figure,
 - $\mathbf{Z_s}$ denotes the internal impedance of the phase winding of the generator;
 - $\mathbf{Z_l}$ is the impedance of the line joining **a-phase** of the source with **a-phase** of the load;
 - $\mathbf{Z_L}$ is the impedance of each phase of the load;
 - $\mathbf{Z_n}$ is the impedance of the neutral line.
- Thus, in general,

$$\mathbf{Z_Y = Z_s + Z_l + Z_L}$$

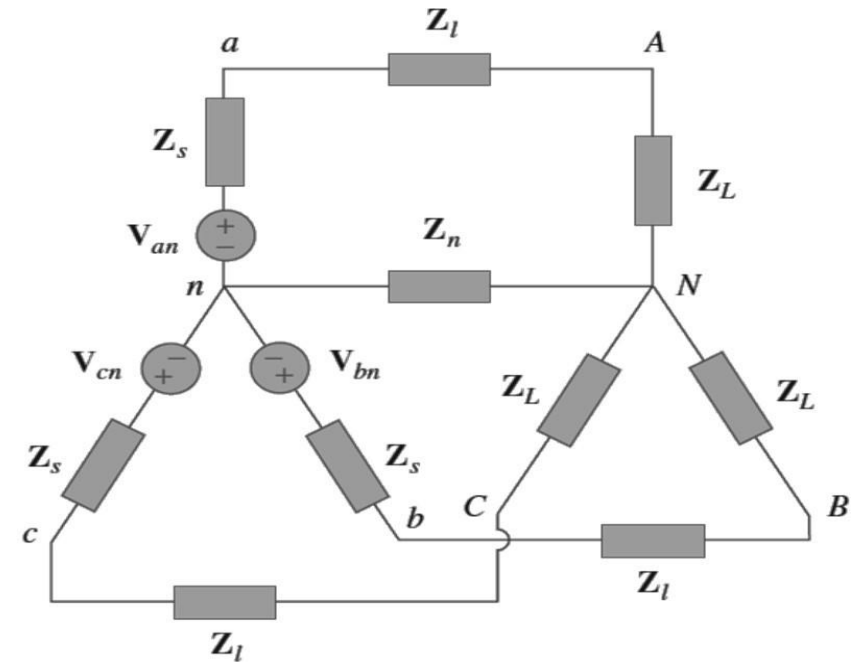

- $\mathbf{Z_s}$ and $\mathbf{Z_l}$ are often very small compared with $\mathbf{Z_L}$, so we can assume $\mathbf{Z_Y = Z_L}$, if no source or line impedance is given.
- In any event, by lumping the impedances together, the **Y-Y system** can be simplified to that shown in the next slide.

Balanced Wye Wye Connection (cont...)

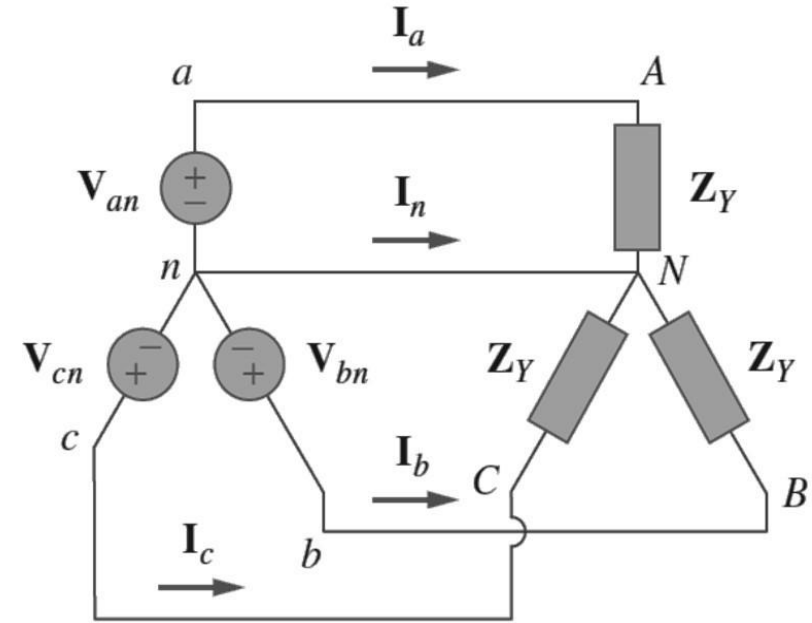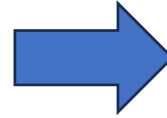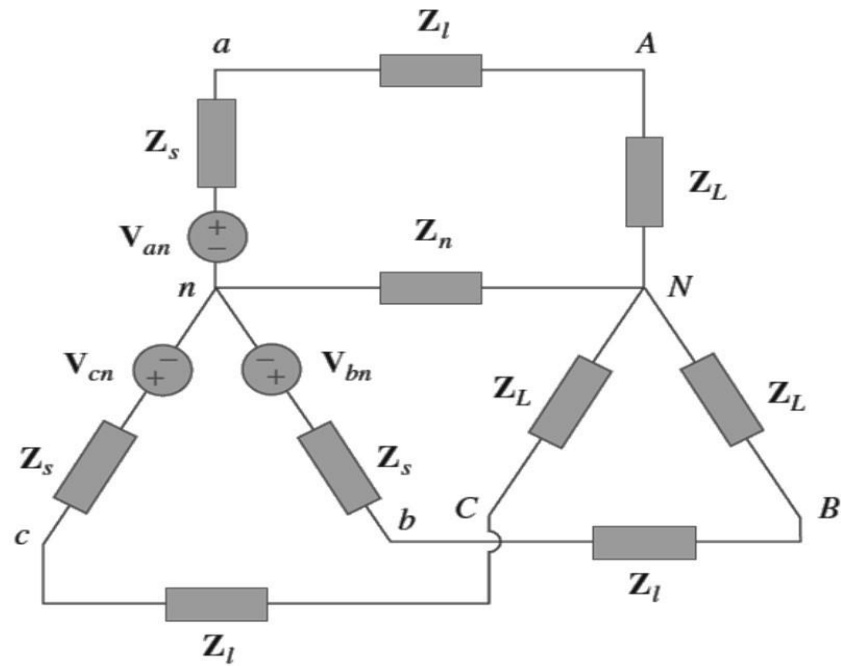

- Assuming the positive sequence, the **phase voltage** or **line to neutral voltage** are,

$$V_{an} = V_p \angle 0^\circ$$

$$V_{bn} = V_p \angle -120^\circ$$

$$V_{cn} = V_p \angle 120^\circ$$

Balanced Wye Wye Connection (cont...)

- The line to line voltages or simply the line voltages \mathbf{V}_{ab} , \mathbf{V}_{bc} , and \mathbf{V}_{ca} are related to the phase voltages as,


$$\mathbf{V}_{ab} = \mathbf{V}_{an} + \mathbf{V}_{nb} = \mathbf{V}_{an} - \mathbf{V}_{bn} = V_p \angle 0^\circ - V_p \angle -120^\circ$$

$$= V_p \left(1 + \frac{1}{2} + \frac{j\sqrt{3}}{2} \right) = \sqrt{3}V_p \angle 30^\circ$$

- Similarly,

$$\mathbf{V}_{bc} = \mathbf{V}_{bn} + \mathbf{V}_{nc} = \mathbf{V}_{bn} - \mathbf{V}_{cn} = \sqrt{3}V_p \angle -90^\circ$$
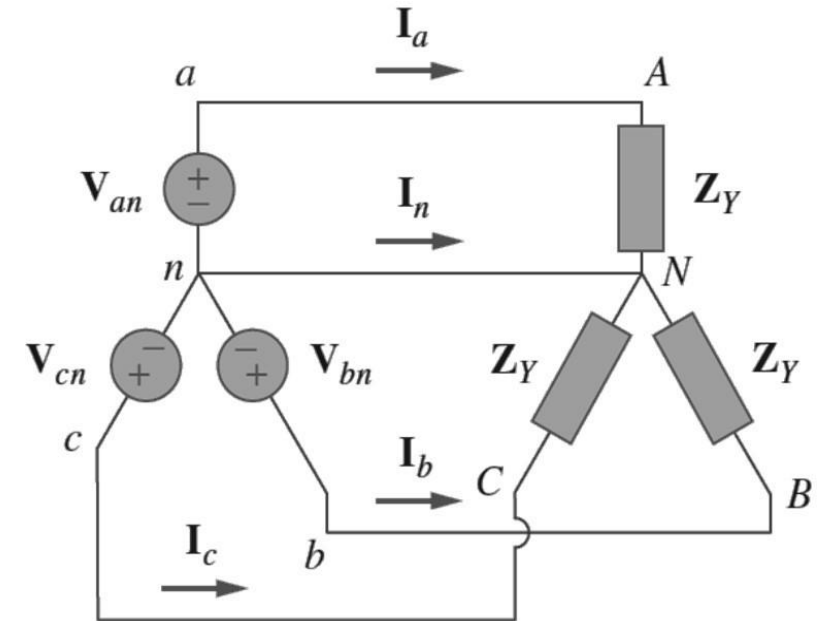
$$\mathbf{V}_{ca} = \mathbf{V}_{cn} + \mathbf{V}_{na} = \mathbf{V}_{cn} - \mathbf{V}_{an} = \sqrt{3}V_p \angle -210^\circ$$





- Thus, the magnitude of the line voltages V_L is $\sqrt{3}$ times the magnitude of the phase voltages V_p or

$$V_L = \sqrt{3}V_p$$

Balanced Wye Wye Connection (cont...)

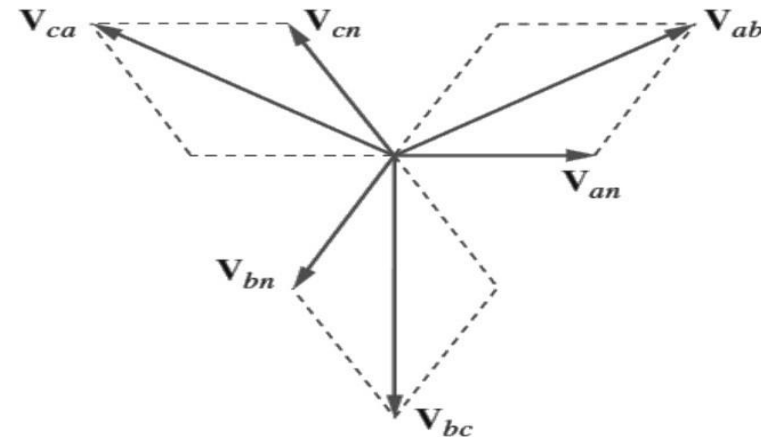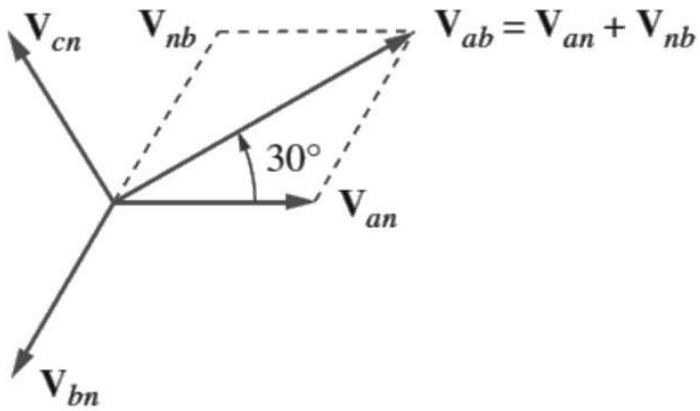- Also the line voltages lead their corresponding phase voltages by 30° as illustrated in the figure below.
- The figure also shows how to determine V_{ab} from the phase voltages.
- Notice that V_{ab} leads V_{bc} by 120° and V_{bc} leads V_{ca} by 120° so that the line voltages sum up to zero as do the phase voltages.




Balanced Wye Wye Connection (cont...)

- Applying KVL to each phase in the following figure,

$$I_a = \frac{V_{an}}{Z_Y}$$

$$I_b = \frac{V_{bn}}{Z_Y} = \frac{V_{an} \angle -120^\circ}{Z_Y} = I_a \angle -120^\circ$$
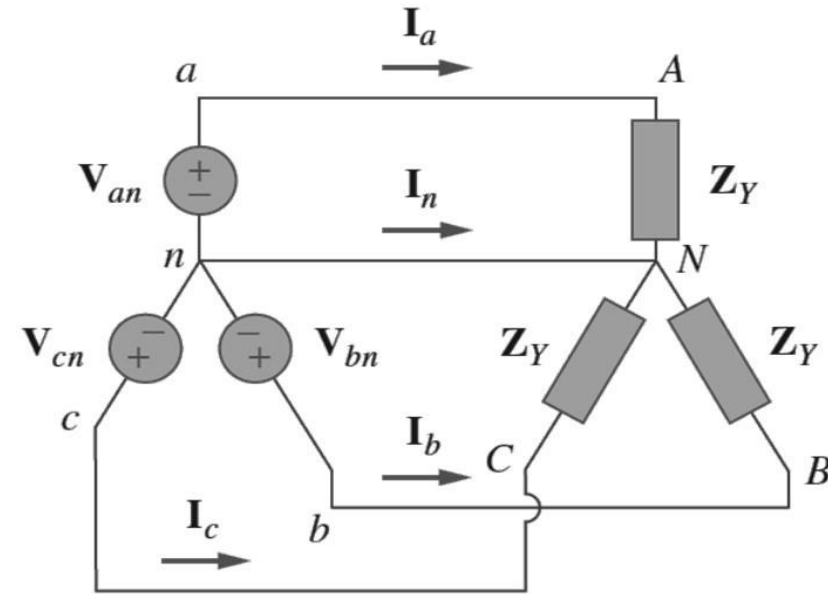
$$I_c = \frac{V_{cn}}{Z_Y} = \frac{V_{an} \angle -240^\circ}{Z_Y} = I_a \angle -240^\circ$$



Balanced Wye Wye Connection (cont...)

- It can be readily inferred that,

$$\mathbf{I}_a + \mathbf{I}_b + \mathbf{I}_c = 0$$


- So that,

$$\mathbf{I}_n = -(\mathbf{I}_a + \mathbf{I}_b + \mathbf{I}_c) = 0$$

or


$$\mathbf{V}_{nN} = \mathbf{Z}_n \mathbf{I}_n = 0$$

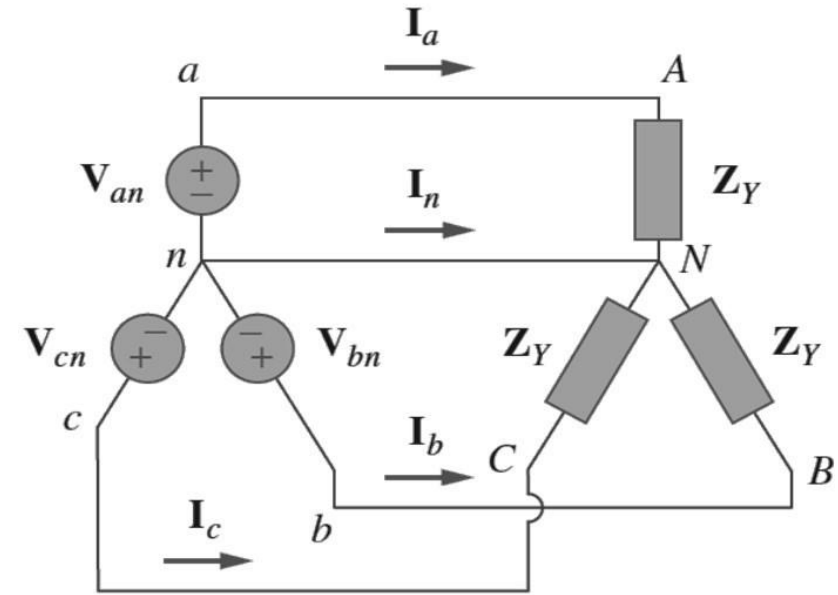- Therefore, the voltage across the neutral wire is **zero**.
- The neutral line can thus be removed without affecting the system.
- In long distance power transmission, conductors are used in multiples of three with the earth itself acting as the neutral conductor.
- Power systems designed in this way are well grounded at all critical points to ensure safety.



Balanced Wye Wye Connection (cont...)

- While the *line* current is the current in each line, the *phase* current is the current in each phase of the source or load.
- In the **Y-Y system**, the **line current** is the same as the **phase current**.
- We will use single subscripts for line currents because it is natural and conventional to assume that line currents flow from the source to the load.
- An alternative way of analyzing a balanced **Y-Y system** is to do so on a “per phase” basis.
- We look at one phase, say **phase a** , and analyze the single-phase equivalent circuit in the below figure.

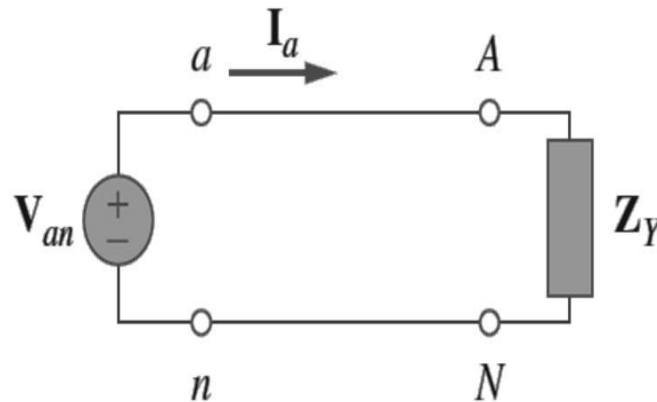

Balanced Wye Wye Connection (cont...)

- The single-phase analysis yields the line current \mathbf{I}_a as


$$\mathbf{I}_a = \frac{\mathbf{V}_{an}}{\mathbf{Z}_Y}$$

- We use the phase sequence to obtain other line currents.
- So, as long as the system is balanced, we need only analyze one phase.
- We may do this even if the neutral line is absent, as in the three-wire system.

Balanced Wye Wye Connection (cont...)

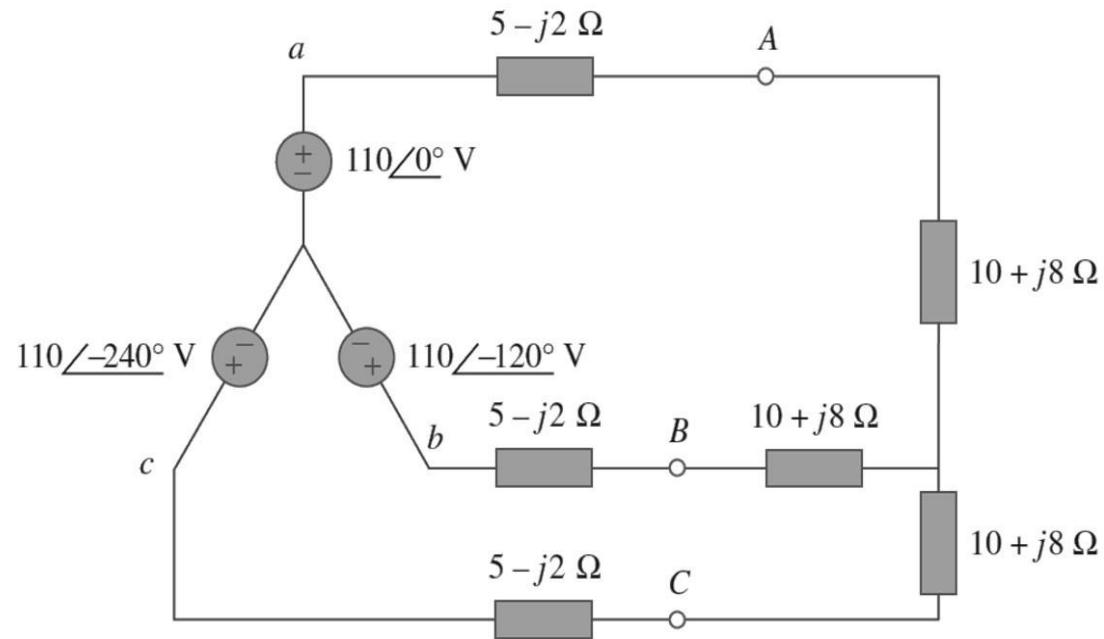Example:

- Calculate the line currents in the three-wire Y-Y system given in the following figure?



Solution: The three-phase circuit is balanced; we may replace it with its single-phase equivalent circuit as discussed previously.

Balanced Wye Wye Connection (cont...)

- The single-phase analysis yields the line current \mathbf{I}_a as

$$\mathbf{I}_a = \frac{\mathbf{V}_{an}}{\mathbf{Z}_Y}$$

- Here,


$$\mathbf{Z}_Y = (5 - j2) + (10 + j8) = 15 + j6 = 16.155\angle 21.8^\circ.$$

$$\mathbf{I}_a = \frac{\mathbf{V}_{an}}{\mathbf{Z}_Y} = \frac{110\angle 0^\circ}{16.155\angle 21.8^\circ} = 6.81\angle -21.8^\circ \text{ A}$$

- Since the source voltages are in positive sequence, the line currents are also in positive sequence:


$$\mathbf{I}_b = \mathbf{I}_a\angle -120^\circ = 6.81\angle -141.8^\circ \text{ A}$$
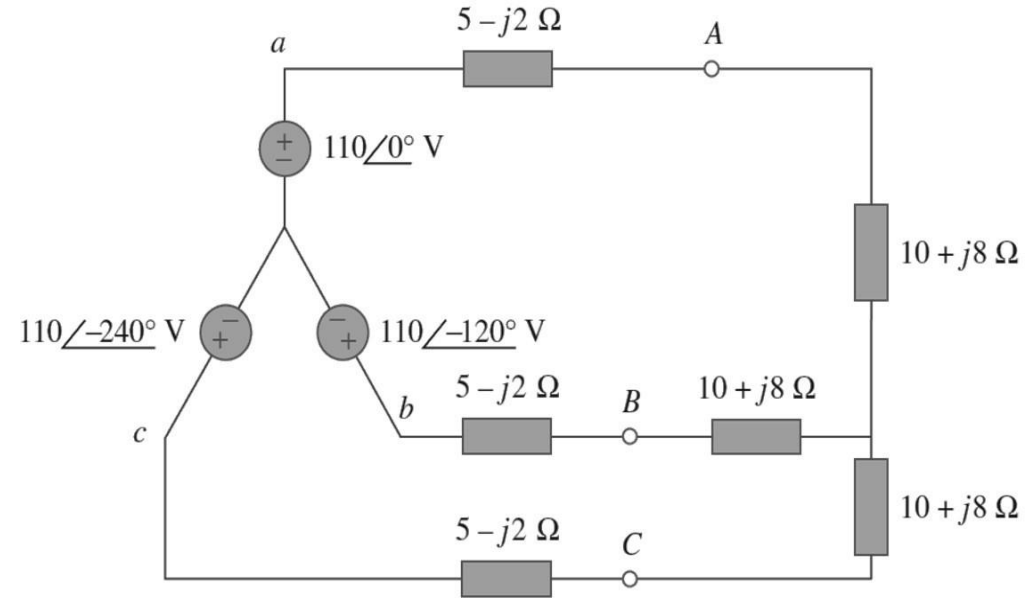
$$\mathbf{I}_c = \mathbf{I}_a\angle -240^\circ = 6.81\angle -261.8^\circ = 6.81\angle 98.2^\circ \text{ A}$$



Balanced Wye-Delta Connection

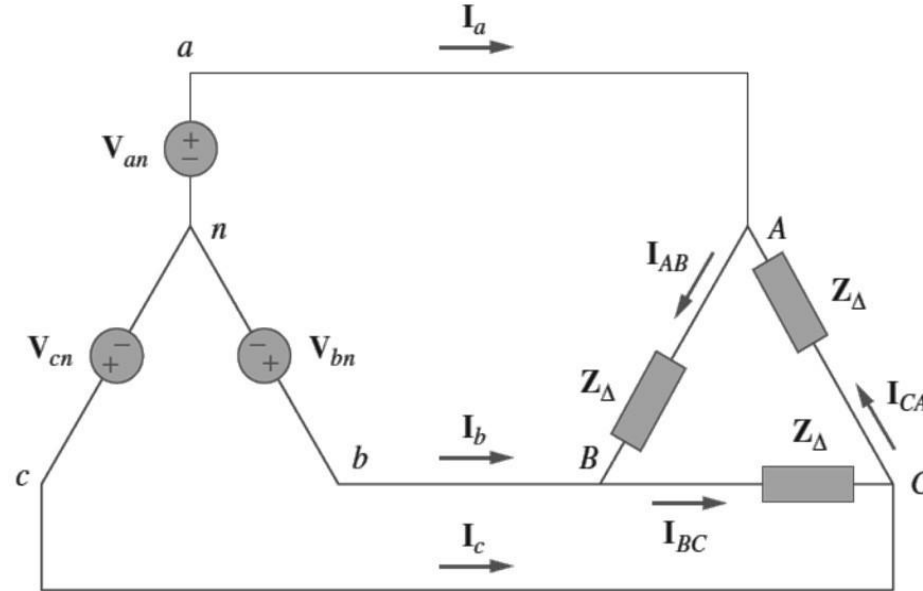- A balanced **Y- Δ system** consists of a balanced **Y-connected** source feeding a balanced **Δ -connected** load.
- The balanced **Y-delta** system is shown in the below figure, where the source is **Y-connected** and the load is **Δ -connected**.
- There is, of course, no neutral connection from source to load for this case.



Balanced Wye-Delta Connection (Cont...)

- Assuming the positive sequence, the phase voltage or line to neutral voltage are,

$$\mathbf{V}_{an} = V_p \angle 0^\circ$$

$$\mathbf{V}_{bn} = V_p \angle -120^\circ$$

$$\mathbf{V}_{cn} = V_p \angle 120^\circ$$


- As discussed previously the line voltages are,

$$\mathbf{V}_{ab} = \sqrt{3} V_p \angle 30^\circ = \mathbf{V}_{AB}$$

$$\mathbf{V}_{bc} = \sqrt{3} V_p \angle -90^\circ = \mathbf{V}_{BC}$$

$$\mathbf{V}_{ca} = \sqrt{3} V_p \angle -210^\circ = \mathbf{V}_{CA}$$

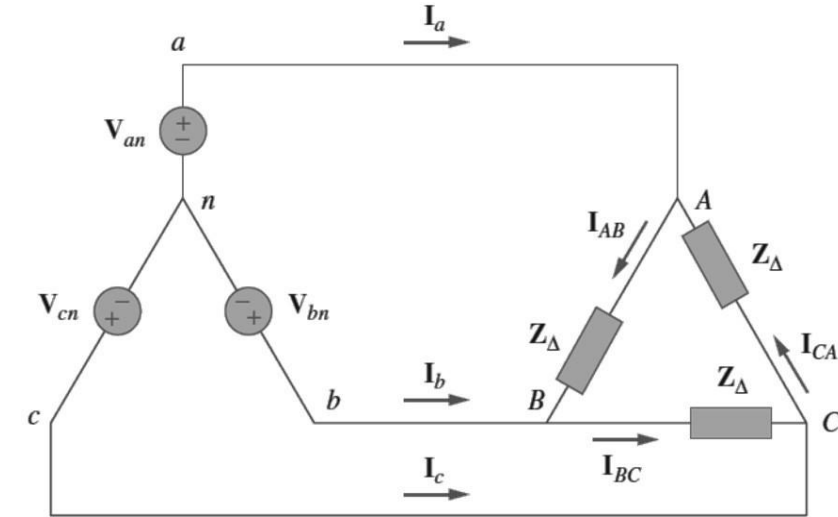- This shows that the line voltages are equal to the voltages across the load impedances for this system configuration.




Balanced Wye-Delta Connection (Cont...)

- From these voltages, we can obtain the phase currents as,

$$I_{AB} = \frac{V_{AB}}{Z_{\Delta}}$$

$$I_{BC} = \frac{V_{BC}}{Z_{\Delta}}$$

$$I_{CA} = \frac{V_{CA}}{Z_{\Delta}}$$

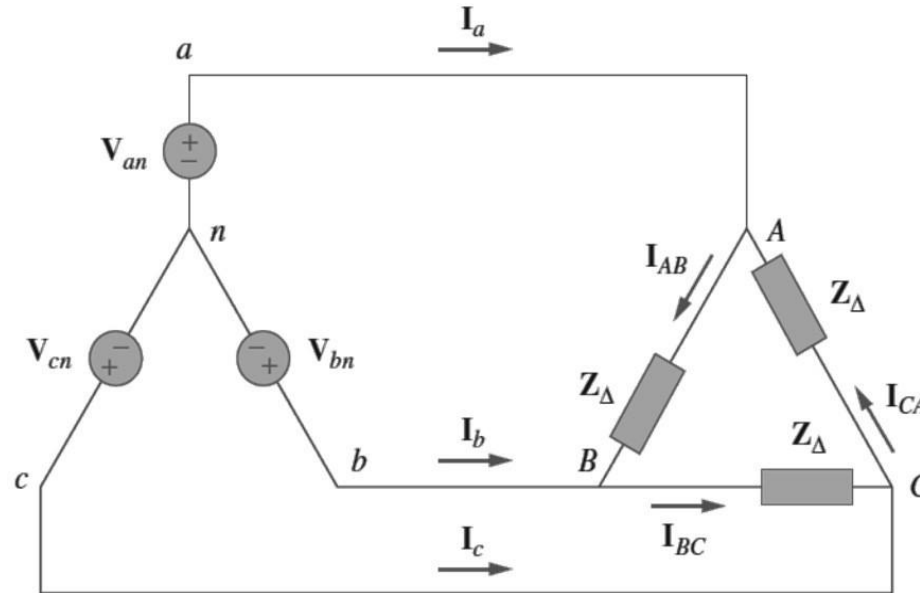

- These currents have the same magnitude but are out of phase with each other by 120° .
- Another way to obtain these phase currents is by applying KVL to the balanced wye-delta connection.


Balanced Wye-Delta Connection (Cont...)

- Applying KVL around the loop $aABbna$ gives,

$$-V_{an} + Z_{\Delta} I_{AB} + V_{bn} = 0$$

or
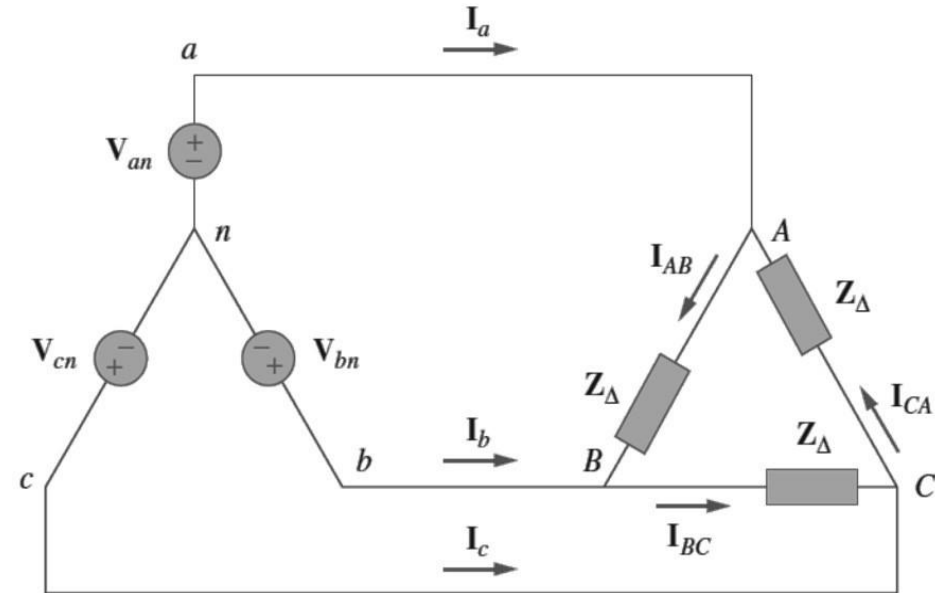
$$I_{AB} = \frac{V_{an} - V_{bn}}{Z_{\Delta}} = \frac{V_{ab}}{Z_{\Delta}} = \frac{V_{AB}}{Z_{\Delta}}$$



- The **line currents** are obtained from the phase currents by applying KCL at nodes A, B, and C.

Balanced Wye-Delta Connection (Cont...)

- Thus,

$$\mathbf{I}_a = \mathbf{I}_{AB} - \mathbf{I}_{CA}$$

- Since,


$$\mathbf{I}_{CA} = \mathbf{I}_{AB} \angle -240^\circ$$

$$\begin{aligned}\mathbf{I}_a &= \mathbf{I}_{AB} - \mathbf{I}_{CA} = \mathbf{I}_{AB}(1 - 1 \angle -240^\circ) \\ &= \mathbf{I}_{AB}(1 + 0.5 - j0.866) = \mathbf{I}_{AB}\sqrt{3} \angle -30^\circ\end{aligned}$$

- Similarly,

$$\mathbf{I}_b = \mathbf{I}_{BC} - \mathbf{I}_{AB} = \mathbf{I}_{BC}\sqrt{3} \angle -30^\circ$$
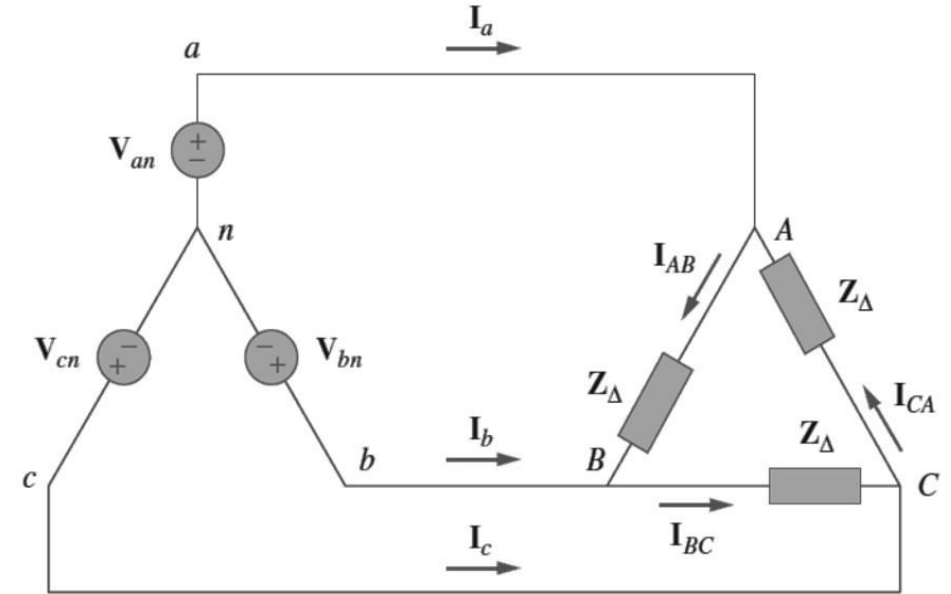
$$\mathbf{I}_c = \mathbf{I}_{CA} - \mathbf{I}_{BC} = \mathbf{I}_{CA}\sqrt{3} \angle -30^\circ$$



- This shows that the magnitude of the line current is $\sqrt{3}$ times the magnitude of the phase current, i.e.,

$$\mathbf{I}_L = \sqrt{3} \mathbf{I}_p$$

Balanced Wye-Delta Connection (Cont...)



- Here,

line current, $\mathbf{I}_L = |\mathbf{I}_a| = |\mathbf{I}_b| = |\mathbf{I}_c|$

and

phase current, $\mathbf{I}_p = |\mathbf{I}_{AB}| = |\mathbf{I}_{BC}| = |\mathbf{I}_{CA}|$

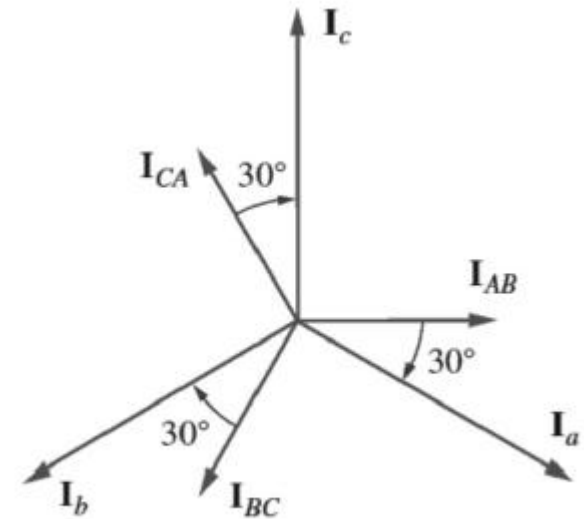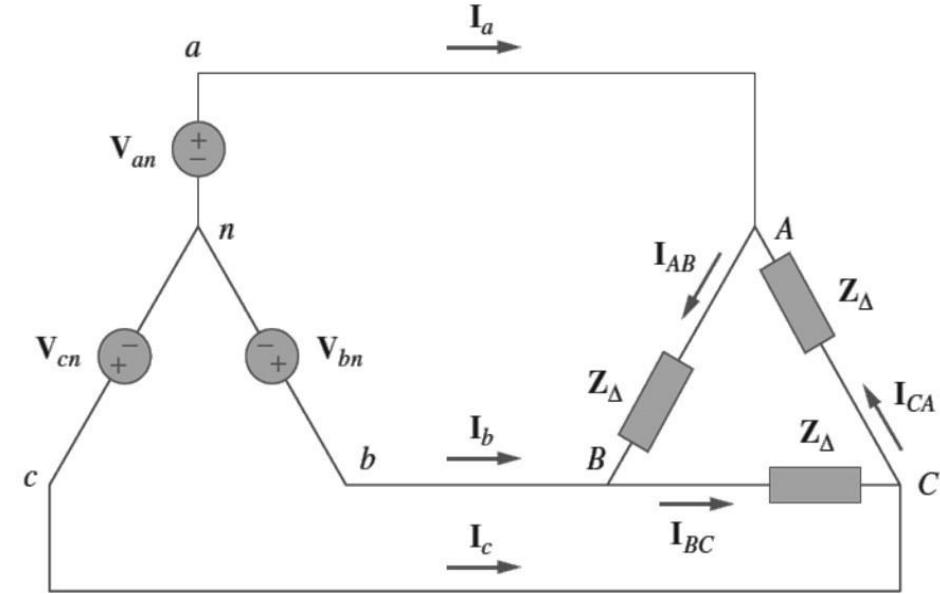- Also, the line currents lag the corresponding phase currents by 30° assuming the positive sequence.
- This is illustrated in the phasor diagram shown below.



Balanced Wye-Delta Connection (Cont...)

- An alternative way of analyzing the circuit is to transform the **Y- Δ connected** load to an equivalent **Y-Y connected** load.
- Using the transformation formula

$$\mathbf{z}_Y = \frac{\mathbf{z}_\Delta}{3}$$

- After this transformation, we now have a **Y-Y system**.
- The three-phase system can then be replaced by the single phase equivalent circuit as discussed in the balanced **Y-Y case**.
- This allows us to calculate only the line currents.
- The phase currents are obtained using $\mathbf{I}_L = \sqrt{3} \mathbf{I}_p$ and utilizing the fact that each of the phase currents leads the corresponding line current by **30°** .

Balanced Wye-Delta Connection (Cont...)

Example:

- A balanced abc sequence Y-connected source with $V_{an} = 100\angle 10^\circ$ V is connected to a delta connected balanced load $(8 + j4)\Omega$ per phase. Calculate the phase and line currents?

Solution: The load impedance is,

$$\mathbf{Z}_{\Delta} = (8 + j4) \Omega = 8.944\angle 26.57^\circ \Omega$$

If the phase voltage $V_{an} = 100\angle 10^\circ$ V, then the line voltage is

$$\mathbf{V}_{ab} = \mathbf{V}_{an}\sqrt{3}\angle 30^\circ = 100\sqrt{3}\angle (10^\circ + 30^\circ)\mathbf{V} = 173.2\angle 40^\circ\mathbf{V} = \mathbf{V}_{AB}$$

Balanced Wye-Delta Connection (Cont...)

- The phase currents are

$$\mathbf{I}_{AB} = \frac{\mathbf{V}_{AB}}{\mathbf{Z}_{\Delta}} = \frac{173.2\angle 40^{\circ}}{8.944\angle 26.57^{\circ}} = 19.36\angle 13.43^{\circ} \text{ A}$$

$$\mathbf{I}_{BC} = \mathbf{I}_{AB}\angle -120^{\circ} = 19.36\angle -106.57^{\circ} \text{ A}$$

$$\mathbf{I}_{CA} = \mathbf{I}_{AB}\angle 120^{\circ} = 19.36\angle 133.43^{\circ} \text{ A}$$

- The line currents are

$$\mathbf{I}_a = \mathbf{I}_{AB}\sqrt{3}\angle -30^{\circ} = \sqrt{3}(19.36)\angle (13.43^{\circ} - 30^{\circ}) = 33.53\angle -16.57^{\circ} \text{ A}$$

$$\mathbf{I}_b = \mathbf{I}_a\angle -120^{\circ} = 33.53\angle -136.57^{\circ} \text{ A}$$

$$\mathbf{I}_c = \mathbf{I}_a\angle 120^{\circ} = 33.53\angle 103.43^{\circ} \text{ A}$$

