

# Transmission Lines - II

**Prof. M. Jaleel Akhtar**

[mjakhtar@iitk.ac.in](mailto:mjakhtar@iitk.ac.in)

<https://home.iitk.ac.in/~mjakhtar/>

**Department of Electrical Engineering  
Indian Institute of Technology Kanpur  
Kanpur – 208016 (U.P.)**



$$Z_0 = \frac{V(z)}{I(z)} = \frac{V_0^+}{I_0^+} = -\frac{V_0^-}{I_0^-} = \sqrt{\frac{R + j\omega L}{G + j\omega C}} \quad (\Omega)$$



Characteristic Impedance

□ The ratio of the voltage and the current at any  $z$  for an infinitely long line is independent of  $z$  and it is called the **Characteristic Impedance**.


$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$\gamma$ : Propagation Constant

$\alpha$ : Attenuation Constant (Np/m)

$\beta$ : Phase Constant (rad/m)

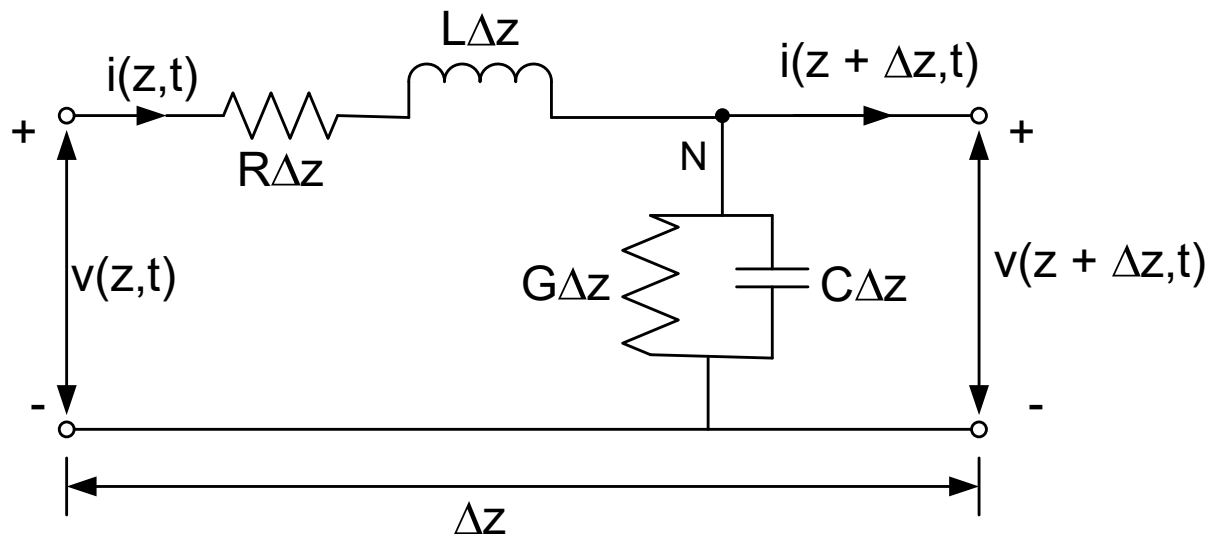**$\gamma$  and  $Z_0$  are the characteristics of a transmission line.**




$$\overline{E} = \overline{a}_y E_y = \overline{a}_y E_0 e^{-\gamma z}$$

$$\overline{H} = \overline{a}_x H_x = -\overline{a}_x \frac{E_0}{\eta} e^{-\gamma z}$$

$$\gamma = j\beta = j\omega\sqrt{\mu\epsilon}$$

$$\eta = \sqrt{\frac{\mu}{\epsilon}}$$

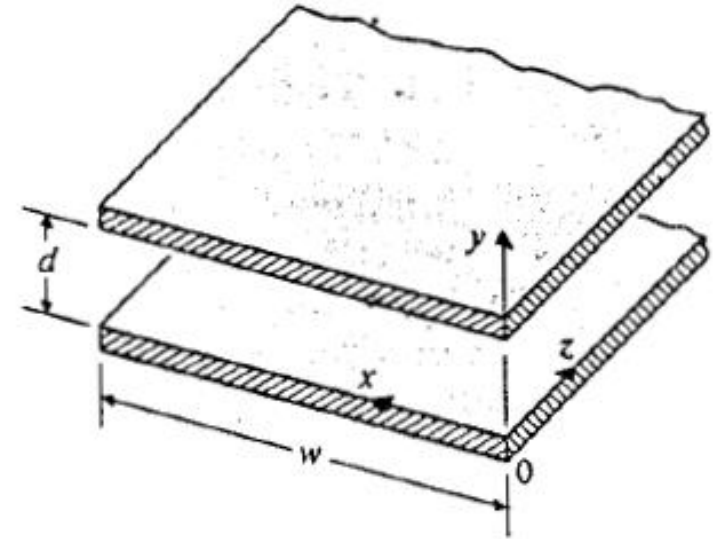

Capacitance per unit length of the parallel plate transmission line



$$C \equiv \epsilon \frac{w}{d} \quad (\text{F/m})$$

Inductance per unit length of the parallel plate transmission line



$$L \equiv \mu \frac{d}{w} \quad (\text{H/m})$$

$$Z_0 = \sqrt{\frac{L}{C}} \quad (\Omega)$$



## Lossless Line ( $R = 0, G = 0$ )

$$\alpha = 0$$

$$\beta = \omega\sqrt{LC}$$

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$



$$\gamma = \alpha + j\beta = j\omega\sqrt{LC}$$

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} \equiv \sqrt{\frac{L}{C}} \text{ } (\Omega)$$

$$R_0 = \sqrt{\frac{L}{C}}$$

➡ Characteristic Impedance

❑ The characteristic impedance becomes purely real and constant.

$$u_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}$$

➡ Phase velocity

❑ Phase velocity is independent of the frequency, which basically means that all the frequency components travel with same velocity.

## Low Loss Line ( $R \ll \omega L, G \ll \omega C$ )

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\equiv \sqrt{j\omega L \left(1 + \frac{R}{j\omega L}\right) \times j\omega C \left(1 + \frac{G}{j\omega C}\right)}$$

$$\equiv j\omega\sqrt{LC} \left(1 + \frac{R}{j\omega L}\right)^{1/2} \times \left(1 + \frac{G}{j\omega C}\right)^{1/2}$$

$$\cong j\omega\sqrt{LC} \left[1 + \frac{R}{2j\omega L}\right] \times \left[1 + \frac{G}{2j\omega C}\right]$$

$$\cong j\omega\sqrt{LC} \left[1 + \frac{R}{2j\omega L} + \frac{G}{2j\omega C} + \dots\right]$$

$$\cong j\omega\sqrt{LC} + j\omega\sqrt{LC} \left[\frac{R}{2j\omega L} + \frac{G}{2j\omega C}\right]$$

$$\cong j\omega\sqrt{LC} + \frac{1}{2} \left[R\sqrt{\frac{C}{L}} + G\sqrt{\frac{L}{C}}\right]$$

$$\alpha \cong \frac{1}{2} \left[R\sqrt{\frac{C}{L}} + G\sqrt{\frac{L}{C}}\right]$$

$$\beta \cong \omega\sqrt{LC}$$

$$u_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}$$



Phase velocity



## Low Loss Line ( $R \ll \omega L, G \ll \omega C$ )

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} = R_0 + jX_0 \quad \text{☞ Characteristic Impedance}$$

$$\equiv \sqrt{\frac{L}{C}} \frac{\left(1 + \frac{R}{j\omega L}\right)^{1/2}}{\left(1 + \frac{G}{j\omega C}\right)^{1/2}}$$

$$\cong \sqrt{\frac{L}{C}} \left[1 + \frac{R}{2j\omega L}\right] \times \left[1 - \frac{G}{2j\omega C}\right]$$

$$\cong \sqrt{\frac{L}{C}} \left[1 + \frac{R}{2j\omega L} - \frac{G}{2j\omega C} \dots\right]$$

$$\cong \sqrt{\frac{L}{C}} + \frac{1}{2j\omega} \sqrt{\frac{L}{C}} \left[\frac{R}{L} - \frac{G}{C}\right]$$

$$R_0 \cong \sqrt{\frac{L}{C}}$$

$$X_0 \cong -\frac{1}{2\omega} \sqrt{\frac{L}{C}} \left[\frac{R}{L} - \frac{G}{C}\right]$$

☐ The characteristic impedance becomes purely real and constant.



## Distortion-less Line ( $R / L = G / C$ )

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L) \left( \frac{RC}{L} + j\omega C \right)}$$

$$\equiv \sqrt{(R + j\omega L) \frac{C}{L} (R + j\omega L)}$$

$$\equiv (R + j\omega L) \sqrt{\frac{C}{L}}$$

$$\alpha = R \sqrt{\frac{C}{L}}$$

$$\beta = \omega \sqrt{LC}$$

$$u_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}$$

❑ All the frequency components travel with same velocity and get attenuated with the same factor, therefore shape of wave remains the same for the distortion-less transmission line.

✓ The distortion would result for a lossy line when different frequency components of a signal attenuate by different amount even when they travel at the same speed.



## Distortion-less Line ( $R / L = G / C$ )

$$Z_0 = \sqrt{\frac{R + j\omega L}{RC/L + j\omega C}}$$

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$= \sqrt{\frac{(R + j\omega L)L}{RC + j\omega LC}}$$

$$\equiv \sqrt{\frac{L}{C}}$$

$$\alpha = R \sqrt{\frac{C}{L}}$$

$$R_0 = \sqrt{\frac{L}{C}}; \quad X_0 = 0$$

$$\beta = \omega \sqrt{LC}$$

$$u_p = \frac{1}{\sqrt{LC}}$$

✓ The characteristic impedance becomes purely real.

- ❑ If different frequency components travel with different velocity, it would lead to **dispersion**.
- ❑ A general lossy line may be dispersive as the phase constant may not be a linear function of the radial frequency.





## Attenuation Constant from Power Relations

$$\alpha = \Re[\gamma] = \Re\left[\sqrt{(R + j\omega L)(G + j\omega C)}\right]$$

- For an infinitely long transmission line, there would not be any reflection, and hence only forward traveling waves would be present.

$$V(z) = V_0^+ e^{-\gamma z} = V_0^+ e^{-(\alpha + j\beta)z}$$

No reflections

$$I(z) = I_0^+ e^{-\gamma z} = I_0^+ e^{-(\alpha + j\beta)z} = \frac{V_0^+}{Z_0} e^{-(\alpha + j\beta)z}$$

$$P(z) = \frac{1}{2} \Re[V(z)I^*(z)] \qquad P(z) = \frac{1}{2} \frac{V_0^2}{|Z_0|^2} R_0 e^{-2\alpha z}$$

- ☞ The power flow along a lossy transmission line, in the absence of the reflection, may be written using the following expression:

$$P(z) = P_0 e^{-2\alpha z}$$

$$P_0 = \frac{1}{2} \frac{V_0^2}{R_0}$$

- ☞ where  $P_0$  is the power at the  $z=0$  plane and  $\alpha$  is the attenuation constant we wish to determine.



☞ Let us define the power loss per unit length along the line as:

$$\mathcal{P}_l(z) \equiv -\frac{\partial P}{\partial z} = 2\alpha P_0 e^{-2\alpha z}$$

$$P(z) = P_0 e^{-2\alpha z}$$

$$= 2\alpha P(z)$$

✓ The negative sign on the derivative was introduced so that  $P_l$  would be a positive quantity.

☞ From the above expression, the attenuation constant may be derived as:

$$\alpha = \frac{\mathcal{P}_l(z)}{2P(z)} = \frac{\mathcal{P}_l(z=0)}{2P_0} \quad (\text{Np/m})$$

