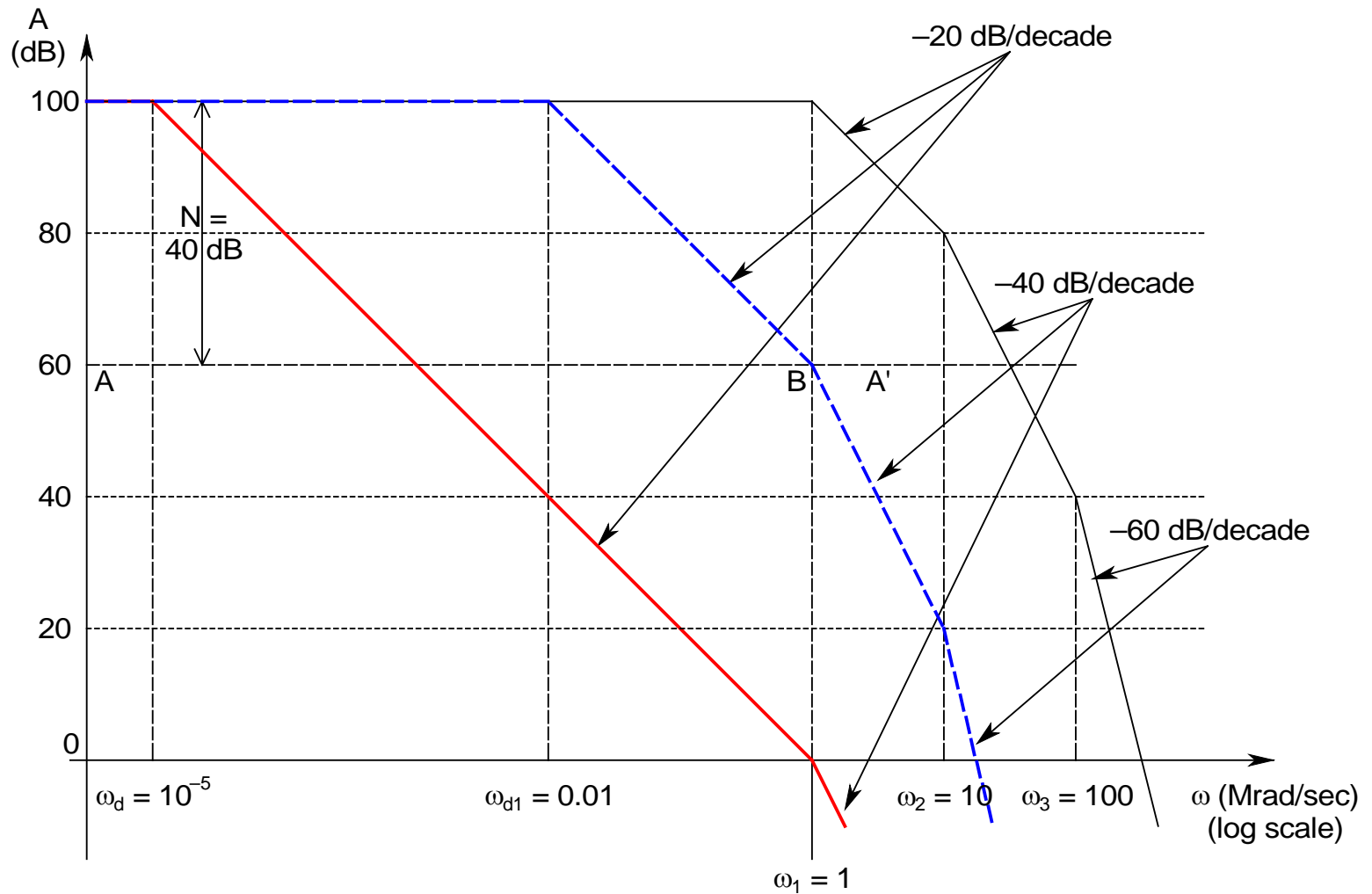


Compensation

- **Basic Idea:**
 - To *tailor* the *gain characteristic* of a system, having *three or more poles*, such that it would be *stable* for *any value* of the *feedback factor* f , all the way *up to unity* (referred to as the *unity feedback system*, where the *entire output* is *fed back* to the *input*)
 - *After compensation*, the system will become *either conditionally or unconditionally stable*

- *Two widely used methods:*
 - *Dominant Pole Compensation (DPC)*
 - *Pole Zero Compensation (PZC)*
- *Dominant Pole Compensation (DPC):*
 - This technique introduces a *dominant pole (DP)* into the system
 - Also known as *Miller Compensation Scheme*
 - This *DP* is chosen such that the *compensated gain characteristic* meets the *first pole* of the *uncompensated system* at *0 dB*, with a *slope* of *-20 dB/decade*

- This will make the system *unconditionally stable*, i.e., the *stability* of the system will be *independent* of the *amount of feedback*
- *Example:*
- Assume $A = 10^5$ (100 dB), $\omega_1 = 1$ Mrad/sec, $\omega_2 = 10$ Mrad/sec, $\omega_3 = 100$ Mrad/sec
 - Refer to the slide on the next page
 - For *unconditional stability*:
 - ❖ Refer to the *red line*
 - ❖ The *compensated transfer function* should meet the *first pole* (ω_1) of the *uncompensated system* at $A = 0$ dB with a *slope* of *-20 dB/decade*



Normal Line: Open-loop system
Red Line: Compensated system for unconditional stability
Blue Line: Compensated system with conditional stability
 (till a feedback of 40 dB)


- ❖ To construct the *compensation characteristic*, *start at ω_1* and *go back 5 decades* ($= 100/20$)
- ❖ *Ends up at the DP frequency (ω_d) of 10 rad/sec*
- ❖ *Note that in between ω_d and ω_1 , the system behaves as if it has a single-pole transfer function*
- ❖ The *total phase* of the system at ω_1 will be -135° [-90° *due to the pole at ω_d* , and -45° *due to the pole at ω_1* (*since ω_2 is ten times away from ω_1 , the phase due to ω_2 is yet to start at this point*)
- ❖ Thus, the *PM of the compensated system will be 45°*
- ❖ This implies a *stable system*, since the *PM is positive*
- ❖ Note that *if ω_2 and ω_1 were closer than 10 times*, the *PM would have been less than 45°* , but *still positive*, and thus, *would have retained the stable nature of the system*

- ❖ Note that in order to achieve *unconditional stability* of the system, the *bandwidth* has *reduced drastically* from *1 Mrad/sec* to only *10 rad/sec*!
- ❖ *This is the most severe limitation of the DPC technique*
- *For conditional stability:*
 - ❖ The *previous compensation scheme* ensured *system stability* for f all the way *up to unity* (corresponding to the *amount of feedback* of *100 dB*, i.e., the *entire output is fed back to the input*)
 - ❖ In some cases, it may be an *overkill*, if it is known *a priori* that the *entire output* will *NOT* be *fed back* to the *input*, *rather only a part of it*
 - ❖ This is what is known as *conditional stability*
 - ❖ Suppose that the *maximum amount of feedback* that the system would have is *40 dB*


- ❖ For this system to be *stable*, the *DP frequency need not be at ω_d , but at a higher value*
- ❖ To construct the *compensation characteristic* of this system, draw a *horizontal line* AA', corresponding to the *amount of feedback* (*40 dB in our example $\Rightarrow A_f = 60$ dB*)
- ❖ From the *intersection point* (B) of this *line* with the *first pole* (ω_1), *go back 2 decades* (40/20), to get the *new dominant pole* ω_{d1} at *10 krad/sec* (shown by the *blue line*)
- ❖ This *compensation scheme protects the system from any stability issues only till a maximum feedback of 40 dB, by ensuring* that *from 0 to 40 dB of feedback, no other pole will be encountered, apart from ω_{d1}*
- ❖ Note the *tremendous bandwidth improvement* of *1000 times* (*from 10 rad/sec for unconditional stability to 10 krad/sec for conditional stability till a feedback of 40 dB*)

➤ **Technique:**

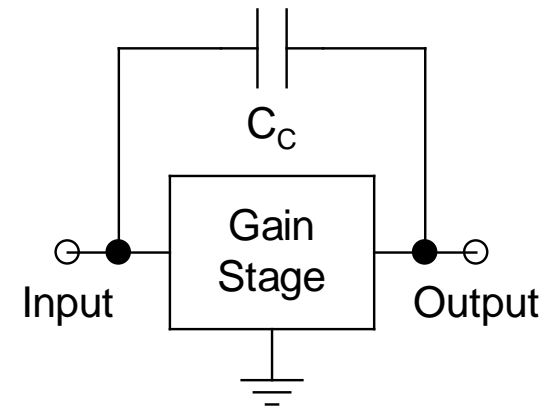- **Simplest way:** Attach a capacitor between the input and output of the gain stage (similar to Miller Capacitor)
- This capacitor is labeled as the **Compensation Capacitor** (C_C)



Schematic

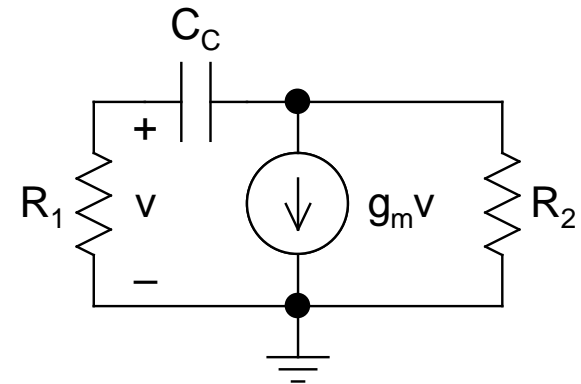

Equivalent Circuit

- *By inspection*, the equivalent circuit can be identified as a *Three-Legged Creature*:

$$\Rightarrow R_C^0 = R_1 + R_2 + g_m R_1 R_2$$

$R_1 =$ *Thevenin resistance to the left of C_C*

$R_2 =$ *Thevenin resistance to the right of C_C*

$g_m =$ *Transconductance of the gain stage*

- Thus:

$$\omega_d = 1 / (R_C^0 C_C)$$

- *From a knowledge of ω_d , we can find C_C*

- *Pole Zero Compensation (PZC):*

- In the *DPC technique*, we observed a *drastic reduction* in *bandwidth* after *compensation*
- *PZC technique alleviates this problem to some extent*
- *Novelty of this technique:*
 - *It adds both a pole and a zero to the open-loop transfer function, with the added zero canceling the first pole of the uncompensated system*

- Consider a *three-pole uncompensated transfer function*:

$$A(s)\big|_{\text{uncompensated}} = \frac{A_0}{(1 + s/\omega_1)(1 + s/\omega_2)(1 + s/\omega_3)}$$

A_0 : *Low-Frequency Gain*

$\omega_1, \omega_2, \omega_3$: *Pole Frequencies* ($\omega_3 > \omega_2 > \omega_1$)

- *After adding the network for PZC*, the *compensated transfer function* will be:

$$A(s)\big|_{\text{compensated}} = \frac{A_0 (1 + s/\omega_z)}{(1 + s/\omega_p)(1 + s/\omega_1)(1 + s/\omega_2)(1 + s/\omega_3)}$$

ω_z : *added zero*, and ω_p : *added pole*

➤ *By design*, ω_z is made equal to ω_1


⇒ *They cancel each other*

➤ Thus, the *compensated transfer function* still has *three poles*, but the *first pole gets shifted from ω_1 to ω_p*

➤ *The procedure for finding ω_p is the same as that for the DPC technique*

➤ We take the *same example* as that considered for the *DPC technique*

➤ Refer to the next slide

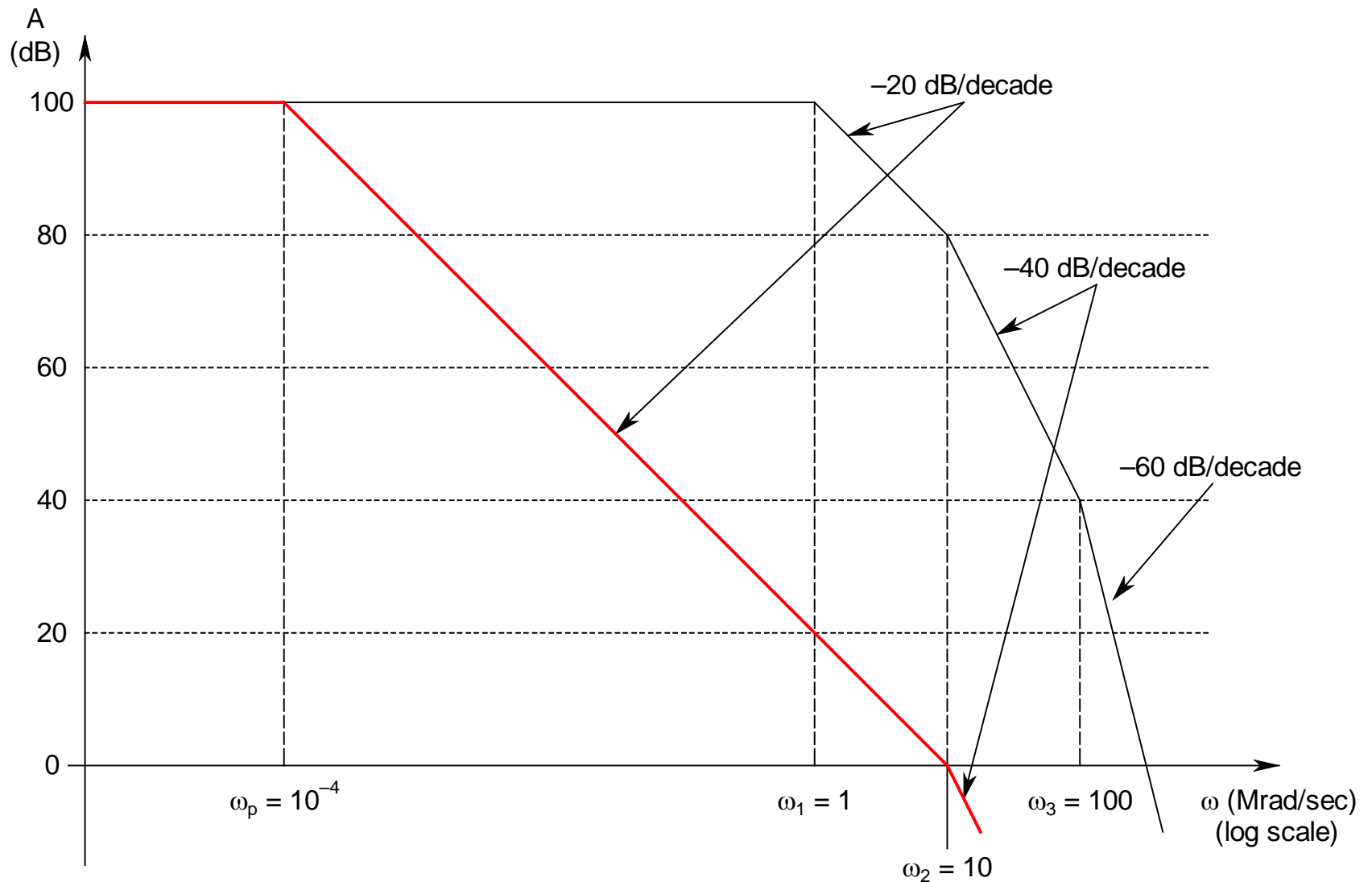


Normal Line: Open-loop system
Red Line: Compensated system for unconditional stability

- Here, the *added zero* (ω_z) *cancels* the *first pole* (ω_1)
- Thus, we now *start from* ω_2 and *go back 5 decades* to find ω_p , which comes out to be *100 rad/sec* (refer to the *red line*)
- The *compensated system* will be *unconditionally stable* with *PM of 45°* (*since ω_3 is ten times away from ω_2*)
- The *increase in bandwidth*, *as compared to DPC*, is *10 times* (*from 10 rad/sec to 100 rad/sec: equal to the ratio of ω_2 and ω_1*)


➤ **Technique:**

- *Just attach a resistor R_C with the compensation capacitor C_C*
- *Put this R_C - C_C network between the input and output of the gain stage*
- Show that the **transfer function** of the **compensated system** is of the form:

$$A(s) \Big|_{\text{compensated}} \propto \frac{1 + s(R_C - 1/g_m)C_C}{1 + s(R_C + R_2)C_C}$$

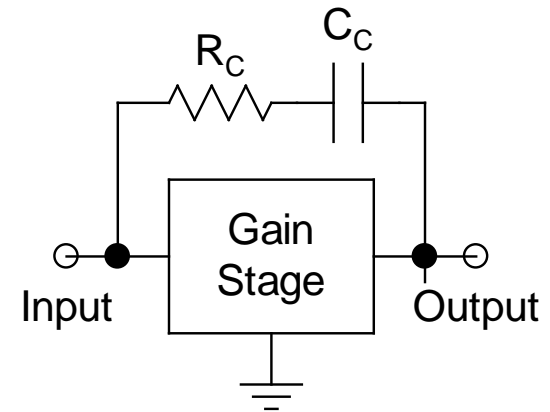

Schematic

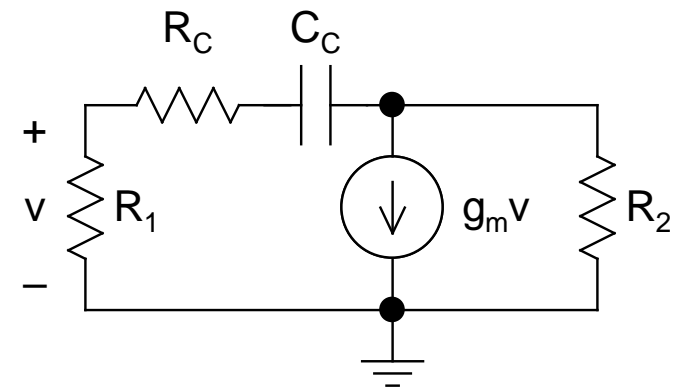

Equivalent Circuit

- Here

$$\omega_z = 1/[(R_C - 1/g_m)C_C]$$

$$\omega_p = 1/[(R_C + R_2)C_C]$$

- *Choose R_C and C_C such that*
 - ❖ ω_z is equal to ω_1 (the first pole of the uncompensated system)
 - ❖ ω_p is as found from the example given

THE OPERATIONAL AMPLIFIER (OP-AMP)

- ***The Ultimate***: A *phenomenal application* of everything that we have learnt so far in this course
- ***Op-Amp***: ***Operational Amplifier***
- *Hugely powerful block*
- *Capable of performing various circuit functions*
- ***Original inventor***: *George Philbrick* of *Bell Labs* in *1952* using *vacuum tube technology*

- *Remarkable innovations* in *design* in the form of an *IC* by *Bob Widlar* of *Fairchild Semiconductors* in *1963*
- After that, *several improvements* took place, and the *most versatile design*, widely came to be known as the *741 op-amp*, originated
- Basically a *three-stage architecture*:
 - *The Input Stage*
 - *The Gain Stage*
 - *The Output Stage*

- *The Input Stage:*
 - *Should be capable of double-ended to single-ended conversion*
 - *Should have moderate to high gain*
 - *Must definitely have extremely large CMRR (this is the main requirement)*
 - *Almost invariably a Differential Amplifier (DA)*

- *The Gain Stage:*

- *Can be any one of the many that we have studied in the chapter on Amplifiers*
- *CC-CE Darlington configuration preferred*
- *Should have moderate to large gain*

- *The Output Stage:*

- *Needed when the op-amp is expected to either source or sink large amount of current to or from the load*