
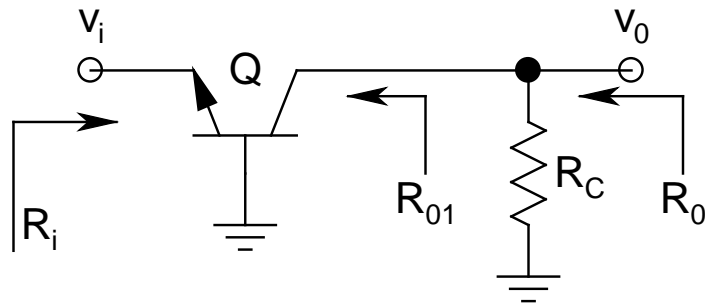


- **Common-Base (CB):**

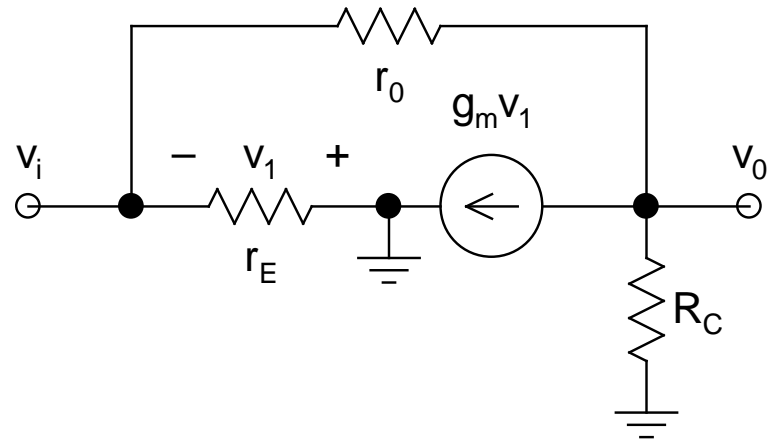

ac Schematic



ac Low-Frequency Equivalent

- Note that the **alternate hybrid- π model** appropriate for **CB circuit** has been used
- **r_o appears between input and output**

- For now, *neglect r_o*
- Noting that $v_1 = -v_i$:

$$A_v = \frac{v_o}{v_i} = \frac{-g_m v_1 R_C}{v_i} = +g_m R_C \simeq \frac{R_C}{r_E}$$

- Note that the *expression* for A_v is *identical* to that for the *CE stage*, *without the negative sign in front*
- For this circuit, *input and output are in phase*
- $A_i = i_c/i_e = \alpha$
- $R_i = r_E$

➤ $R_0 = R_{01} || R_C$

$R_{01} \rightarrow \infty$ (Why?)


$\Rightarrow R_0 = R_C$

➤ *Ex.: Find A_v and R_i with r_o included*


➤ *With r_o included*, the circuit shows *two different values* of R_{01} :

- *When excited by a voltage source*, $R_{01} = r_o$
- *When excited by a current source*, $R_{01} = \beta r_o$ (*Show*)
[*Hint: For this derivation, need to use $g_m r_E = \alpha$*]
- *Thus, possibility of huge R_0 under the second case, but R_C ruins it!*


- **Common-Gate (CG):**

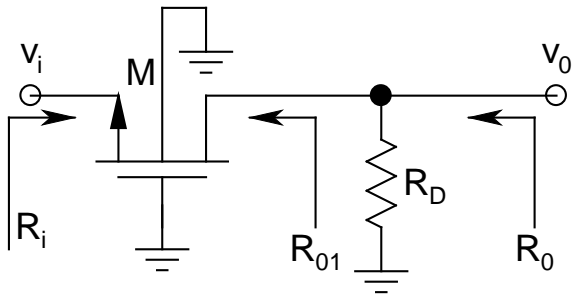


ac Schematic

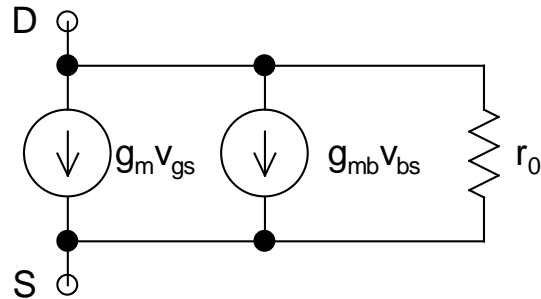


ac Low-Frequency Model for M

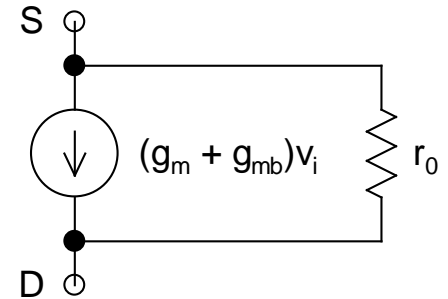

Simplified ac Low-Frequency Model for M

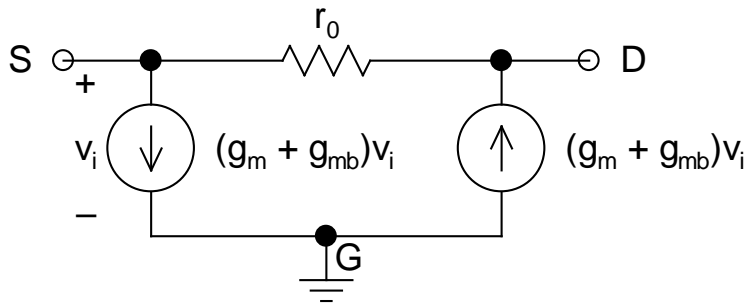

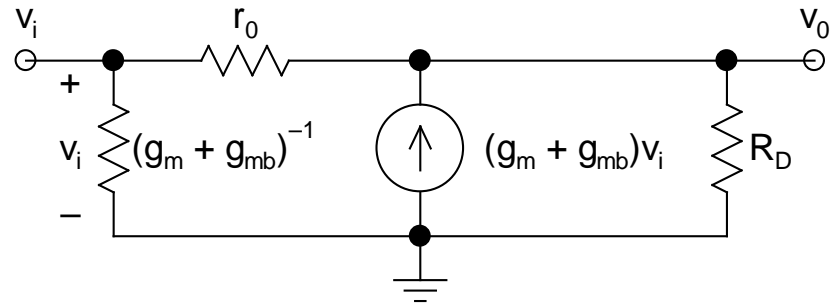Rerouting the current source between S and D to S to G and then from G to D



Final ac Low-Frequency Equivalent for CG Stage

➤ *G and B both ground:*

$$\Rightarrow V_{gs} = V_{bs} = -V_i$$

$\Rightarrow g_m V_{gs}$ and $g_{mb} V_{bs}$ can be *combined to a single current source* $(g_m + g_{mb})V_i$, *flowing from S to D*

➤ *Reroute this current source from S to G and then from G to D (the circuit remains invariant)*

\Rightarrow Leads to the *final ac low-frequency equivalent* of the CG stage

➤ *Note again that r_o appears between input and output (similar to CB stage)*

➤ *Neglect r_o for now*

➤ Noting that $v_1 = v_i$:

$$A_v = \frac{v_o}{v_i} = \frac{(g_m + g_{mb}) v_1 R_D}{v_i} = + (g_m + g_{mb}) R_D$$

➤ *Identical result to a CB stage, if **body effect** is neglected*

➤ $R_i = (g_m + g_{mb})^{-1}$

➤ $R_o = R_{o1} || R_D$

$R_{o1} \rightarrow \infty$ (**Why?**)


$\Rightarrow R_o = R_D$

- *Ex.: Find A_v and R_i with r_o included*
- *With r_o included*, the circuit shows *three different values* of R_{o1} :
 - *When excited by a voltage source*, $R_{o1} = r_o$
 - *When excited by an ideal current source*, $R_{o1} \rightarrow \infty$ (*Show*)
 - *If the current source is non-ideal with shunt resistance R_S* :
$$R_{o1} = r_o[1 + (g_m + g_{mb})R_S] \text{ (*Show*)}$$


Quick Reckoner for BJT Stages

Topology	A_v	A_i	PG	R_i	R_o
CE	Moderate to Large	Large	Large	Moderate	Moderate
CC	≤ 1	Large	Moderate	Large	Small
CB	Moderate to Large	≤ 1	Moderate	Small	Moderate
CE(D)	Low to Moderate	Large	Moderate	Large	Moderate

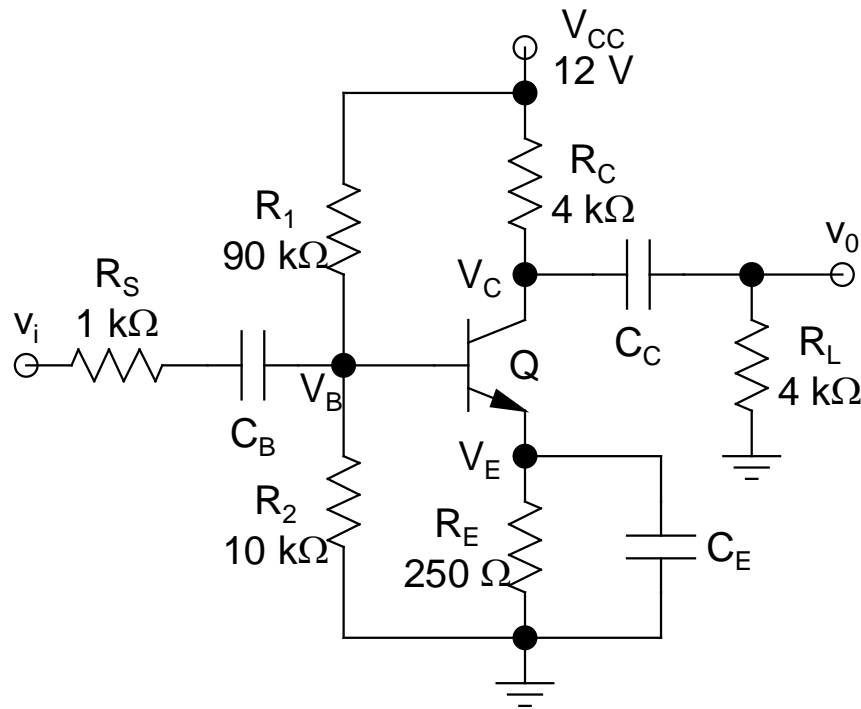- *The RC-Coupled Amplifier:*
 - *Immensely popular*, particularly for *audio circuits*
 - Can be designed to produce *significant power gain*
 - Several such stages can be *cascaded* to produce *very large gain*
 - Can be used either with *single-supply* or *dual-supply*
 - Used primarily in *discrete designs* (*PCB*)



Complete Circuit

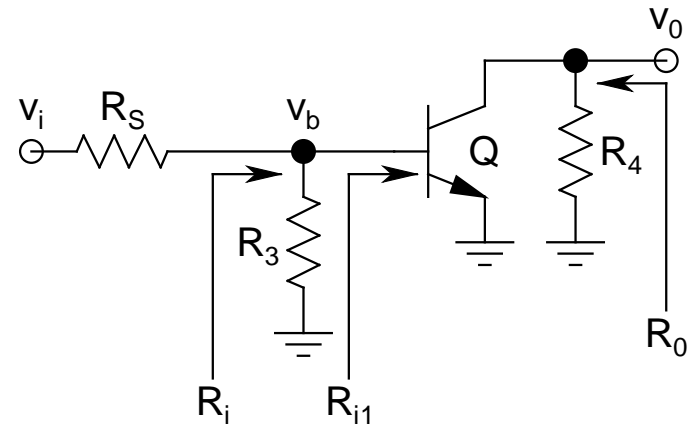

ac Schematic

C_B : Base Blocking Capacitor, C_C : Collector Coupling Capacitor
 C_E : Emitter Bypass Capacitor, R_S : Source Resistance, R_L : Load Resistance

- C_B, C_C : Used for *DC isolation* of the *bias circuit* from *the source and the load*
 - *DC biasing becomes independent of source and load*
- C_E : *Plays no role in DC (opens up)*, but *shorts out R_E in ac* (will see its effects later)
- These 3 capacitors dictate the *lower cutoff frequency* (f_L) of the circuit
- Typically have values in the order of *μF to 100s of μF* in order to give *f_L as close to 0 (DC)* as possible

- First need to do the *DC analysis* to find the *operating point*
- *All capacitors open up for DC analysis*
 - *R_S and R_L play no role*
- *Neglecting base current:*
$$V_B = V_{CC}R_2/(R_1 + R_2) = 1.2 \text{ V}$$
$$\Rightarrow V_E = V_B - V_{BE} = 0.5 \text{ V}$$
$$\Rightarrow I_E \approx I_C = V_E/R_E = 2 \text{ mA}$$
$$V_C = V_{CC} - I_C R_C = 4 \text{ V}$$
$$V_{CE} = 3.5 \text{ V (quite close to } V_{CC}/3)$$
- *DC bias point analysis done!*

- Now we can move on to the *ac analysis*
- *All capacitors get shorted* due to their *high values*, assuming *frequency of operation* is *beyond f_L* and *less than f_H* , i.e., *midband range*
- *C_E bypasses R_E*
 - ⇒ *Emitter of Q goes to ground*
 - ⇒ *R_E plays no role in ac analysis*
- *Refer to the ac schematic*
 - $R_3 = R_1 || R_2 = 9 \text{ k}\Omega$
 - $R_4 = R_C || R_L = 2 \text{ k}\Omega$
- *Need β for ac analysis (choose 100)*