

Lecture-20

On

INTRODUCTION TO ELECTRICAL ENGINEERING (ESO203)


- Interconnection of Networks.
- Network Theorems in AC circuits.

Interconnection of Networks

- A large, complex network may be divided into sub-networks for the purposes of analysis and design.
- The sub-networks can be modeled as two-port networks, interconnected to form the original network.
- The two-port networks may therefore be considered as building blocks that can be interconnected to form a complex network.
- The interconnection can be in series, in parallel, or in cascade.
- Although the interconnected network can be described by any of the six parameter sets, a certain set of parameters may have a definite advantage.
- For example, when the networks are in series, their individual z parameters add up to give the z parameters of the larger network.

Interconnection of Networks (Cont...)

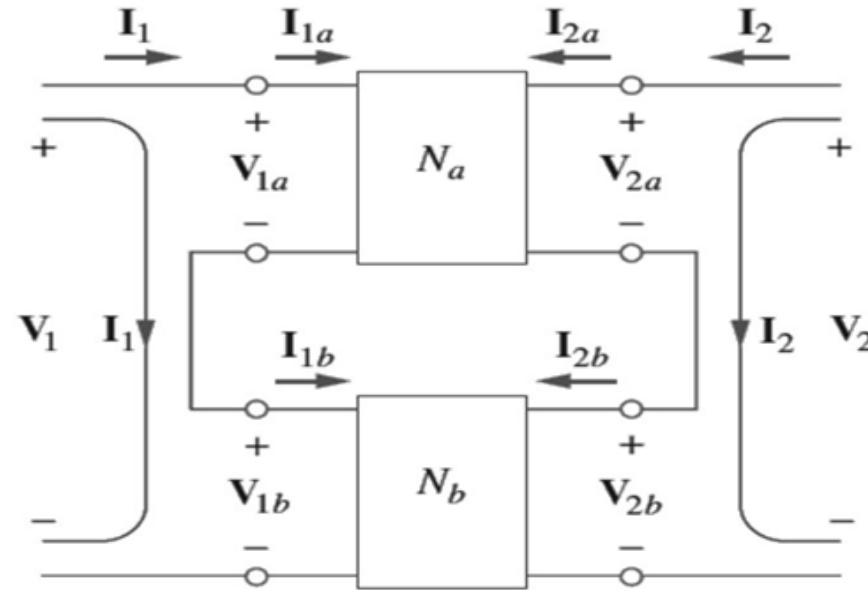- When they are in parallel, their individual y parameters add up to give the y parameters of the larger network.
- When they are cascaded, their individual transmission parameters can be multiplied together to get the transmission parameters of the larger network.
- Consider the series connected network shown in the figure below.



Interconnection of Networks (Cont...)

- The networks are regarded to be in series as their input currents are the same and their voltages add.

- For network N_a ,


$$V_{1a} = z_{11a} I_{1a} + z_{12a} I_{2a}$$

$$V_{2a} = z_{21a} I_{1a} + z_{22a} I_{2a}$$

- and for network N_b ,

$$V_{1b} = z_{11b} I_{1b} + z_{12b} I_{2b}$$
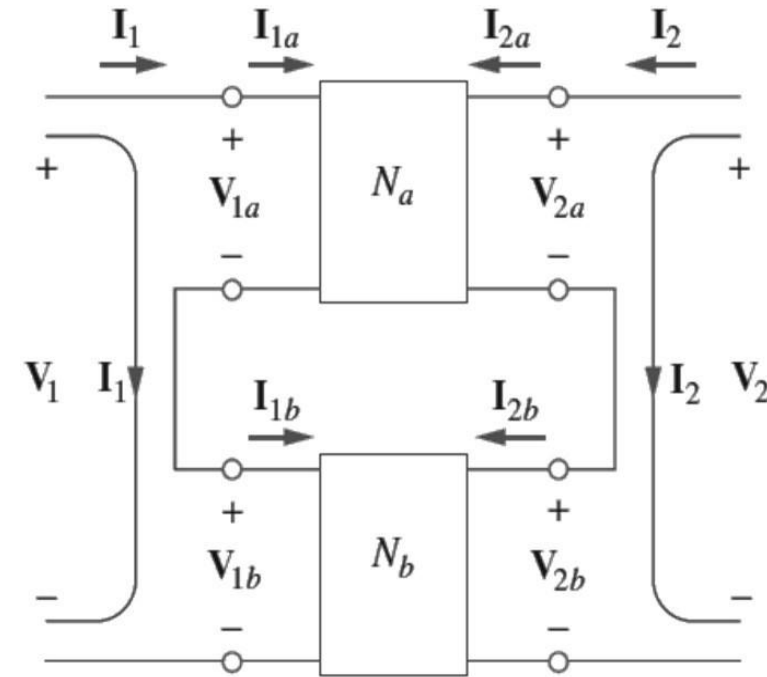
$$V_{2b} = z_{21b} I_{1b} + z_{22b} I_{2b}$$



Interconnection of Networks (Cont...)

- From the figure it can be observed that, when circuits are in series,

$$\mathbf{I}_1 = \mathbf{I}_{1a} = \mathbf{I}_{1b}, \mathbf{I}_2 = \mathbf{I}_{2a} = \mathbf{I}_{2b}$$

- and that

$$\mathbf{V}_1 = \mathbf{V}_{1a} + \mathbf{V}_{1b} = (\mathbf{z}_{11a} + \mathbf{z}_{11b})\mathbf{I}_1 + (\mathbf{z}_{12a} + \mathbf{z}_{12b})\mathbf{I}_2$$


$$\mathbf{V}_2 = \mathbf{V}_{2a} + \mathbf{V}_{2b} = (\mathbf{z}_{21a} + \mathbf{z}_{21b})\mathbf{I}_1 + (\mathbf{z}_{22a} + \mathbf{z}_{22b})\mathbf{I}_2$$

- The \mathbf{z} parameters of the overall network are,

$$\begin{bmatrix} \mathbf{z}_{11} & \mathbf{z}_{12} \\ \mathbf{z}_{21} & \mathbf{z}_{22} \end{bmatrix} = \begin{bmatrix} \mathbf{z}_{11a} + \mathbf{z}_{11b} & \mathbf{z}_{12a} + \mathbf{z}_{12b} \\ \mathbf{z}_{21a} + \mathbf{z}_{21b} & \mathbf{z}_{22a} + \mathbf{z}_{22b} \end{bmatrix}$$

or
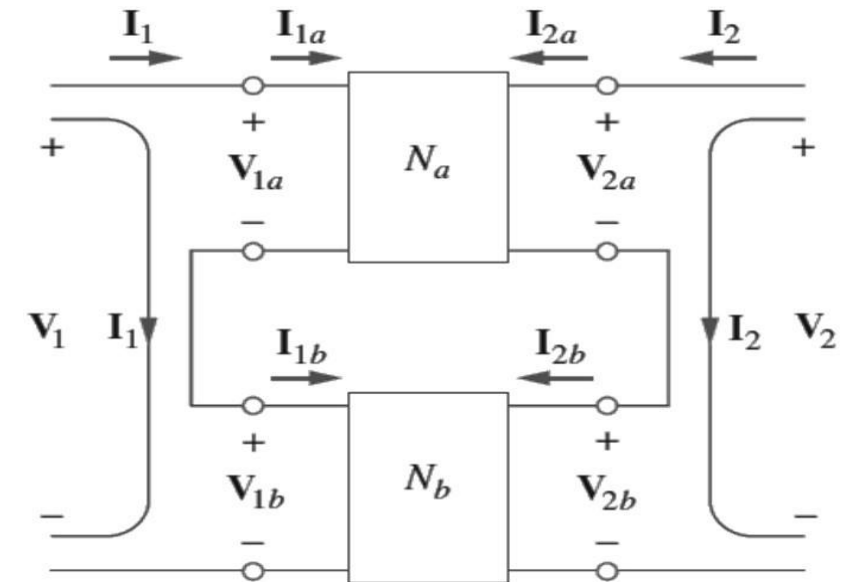
$$[\mathbf{z}] = [\mathbf{z}_a] + [\mathbf{z}_b]$$




Interconnection of Networks (Cont...)

- Thus, the above derivation proves that the z parameters for the overall network are the sum of the z parameters for the individual networks.
- This can be extended to n networks in series.
- If two networks represented using the $[h]$ parameters are connected in series, its equivalent can be computed by first converting the $[h]$ parameters to $[z]$ by comparing the equivalent circuit of both the models.
- Once the overall parameters of the circuit for the series network has been evaluated the $[z]$ parameter of the equivalent circuit can then be converted back to the $[h]$ parameters.
- This is applicable for all interconnections.

Interconnection of Networks (Cont...)

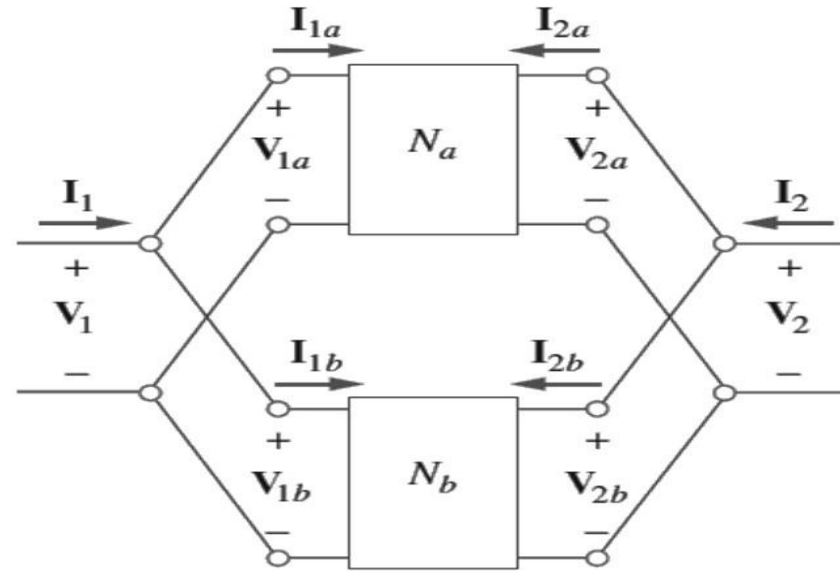- Consider the parallel connected network shown in the figure below.



- Two two-port networks are in parallel when their port voltages are equal and the port currents of the larger network are the sums of the individual port currents.
- Here, each circuit must have a common reference and when the networks are connected together, they must all have their common references tied together.

Interconnection of Networks (Cont...)

- For network N_a ,

$$\mathbf{I}_{1a} = \mathbf{y}_{11a} \mathbf{V}_{1a} + \mathbf{y}_{12a} \mathbf{V}_{2a}$$

$$\mathbf{I}_{2a} = \mathbf{y}_{21a} \mathbf{V}_{1a} + \mathbf{y}_{22a} \mathbf{V}_{2a}$$

- and for network N_b ,

$$\mathbf{I}_{1b} = \mathbf{y}_{11b} \mathbf{V}_{1b} + \mathbf{y}_{12b} \mathbf{V}_{2b}$$

$$\mathbf{I}_{2b} = \mathbf{y}_{21b} \mathbf{V}_{1b} + \mathbf{y}_{22b} \mathbf{V}_{2b}$$

- From the figure it can be observed that,

$$\mathbf{V}_1 = \mathbf{V}_{1a} = \mathbf{V}_{1b},$$

$$\mathbf{V}_2 = \mathbf{V}_{2a} = \mathbf{V}_{2b}$$

$$\mathbf{I}_1 = \mathbf{I}_{1a} + \mathbf{I}_{1b},$$

$$\mathbf{I}_2 = \mathbf{I}_{2a} + \mathbf{I}_{2b}$$

Interconnection of Networks (Cont...)

- Using the above relations we get,

$$\mathbf{I}_1 = \mathbf{I}_{1a} + \mathbf{I}_{1b} = (\mathbf{y}_{11a} + \mathbf{y}_{11b})\mathbf{V}_1 + (\mathbf{y}_{12a} + \mathbf{y}_{12b})\mathbf{V}_2$$

$$\mathbf{I}_2 = \mathbf{I}_{2a} + \mathbf{I}_{2b} = (\mathbf{y}_{21a} + \mathbf{y}_{21b})\mathbf{V}_1 + (\mathbf{y}_{22a} + \mathbf{y}_{22b})\mathbf{V}_2$$

- The \mathbf{y} parameters of the overall network are,

$$\begin{bmatrix} \mathbf{y}_{11} & \mathbf{y}_{12} \\ \mathbf{y}_{21} & \mathbf{y}_{22} \end{bmatrix} = \begin{bmatrix} \mathbf{y}_{11a} + \mathbf{y}_{11b} & \mathbf{y}_{12a} + \mathbf{y}_{12b} \\ \mathbf{y}_{21a} + \mathbf{y}_{21b} & \mathbf{y}_{22a} + \mathbf{y}_{22b} \end{bmatrix}$$


or

$$[\mathbf{y}] = [\mathbf{y}_a] + [\mathbf{y}_b]$$

- Thus, \mathbf{y} parameters of the overall network are the sum of the \mathbf{y} parameters of the individual networks.
- The result can be extended to n two-port networks in parallel.

Interconnection of Networks (Cont...)

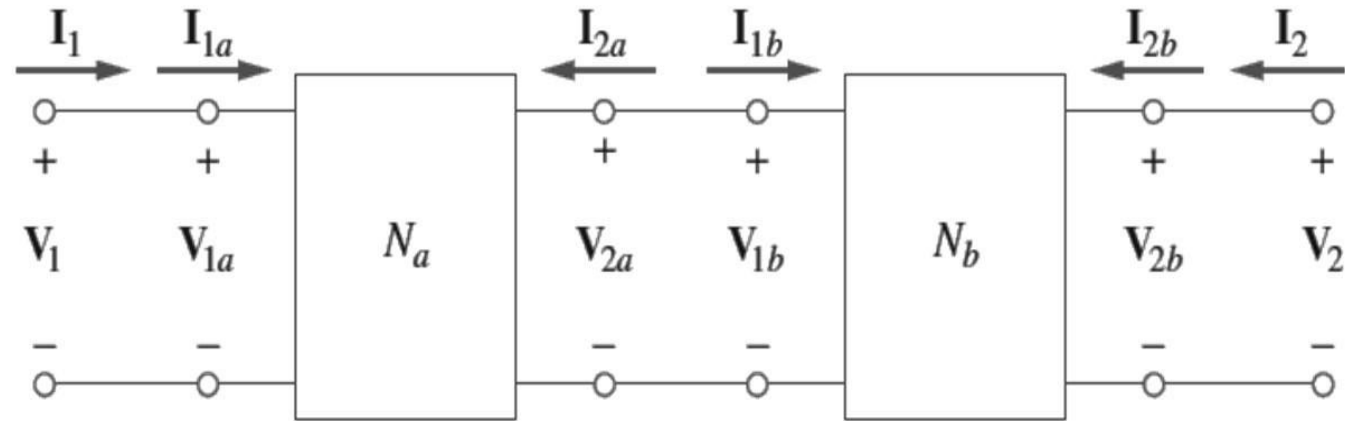- Consider the cascaded network shown in the figure below.



- Two networks are said to be *cascaded* when the output of one is the input of the other.


Interconnection of Networks (Cont...)

- For network N_a ,

$$\begin{bmatrix} \mathbf{V}_{1a} \\ \mathbf{I}_{1a} \end{bmatrix} = \begin{bmatrix} \mathbf{A}_a & \mathbf{B}_a \\ \mathbf{C}_a & \mathbf{D}_a \end{bmatrix} \begin{bmatrix} \mathbf{V}_{2a} \\ -\mathbf{I}_{2a} \end{bmatrix}$$

- and for network N_b ,
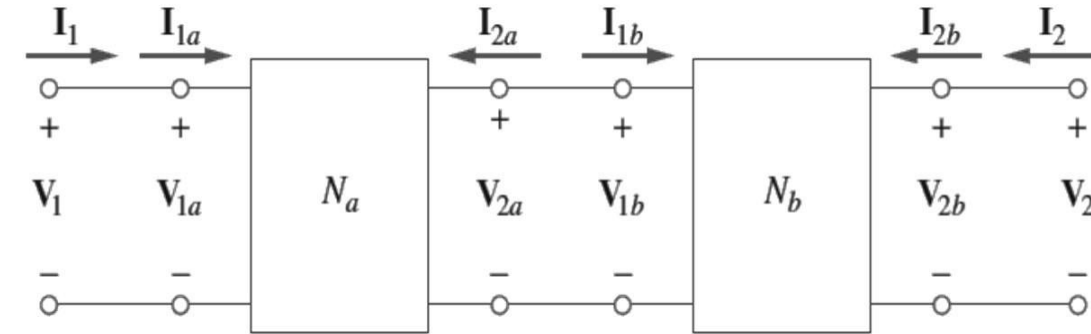
$$\begin{bmatrix} \mathbf{V}_{1b} \\ \mathbf{I}_{1b} \end{bmatrix} = \begin{bmatrix} \mathbf{A}_b & \mathbf{B}_b \\ \mathbf{C}_b & \mathbf{D}_b \end{bmatrix} \begin{bmatrix} \mathbf{V}_{2b} \\ -\mathbf{I}_{2b} \end{bmatrix}$$



- From the figure it can be observed that,

$$\begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I}_1 \end{bmatrix} = \begin{bmatrix} \mathbf{V}_{1a} \\ \mathbf{I}_{1a} \end{bmatrix}, \quad \begin{bmatrix} \mathbf{V}_{2a} \\ -\mathbf{I}_{2a} \end{bmatrix} = \begin{bmatrix} \mathbf{V}_{1b} \\ \mathbf{I}_{1b} \end{bmatrix}, \quad \begin{bmatrix} \mathbf{V}_{2b} \\ -\mathbf{I}_{2b} \end{bmatrix} = \begin{bmatrix} \mathbf{V}_2 \\ -\mathbf{I}_2 \end{bmatrix}$$

Introduction

- The concept of phasors, we discussed in the first module, finds application in AC circuit analysis.
- From the previous discussions we know that Ohm's law and Kirchhoff's laws can be applied to AC circuits as well.
- In this module, we will discuss how the theorems, discussed for DC circuits, can be used to analyze AC circuits.
- The techniques discussed previously are equally valid for AC circuits as well.
- This will be illustrated through various examples in the upcoming lectures.

□ Steps to Analyze AC Circuits:


1. Transform the circuit to the phasor or frequency domain.
 2. Solve the problem using circuit theorems.
 3. Transform the resulting phasor to the time domain.
- **Step 1** is not necessary if the problem is already specified in frequency domain.
 - **Step 2** is performed in a similar manner to the **DC** circuits except that complex numbers are involved.
 - Complex numbers can be easily handled using the techniques discussed previously.

□ Nodal and Mesh Analysis:

- The basis of nodal analysis is Kirchhoff's current law (KCL) and the basis for mesh analysis is the Kirchhoff's voltage law (KVL).
- Since both KCL and KVL are valid for complex numbers also, nodal and mesh analysis can be used to analyze AC circuits.
- The following examples illustrate circuit analysis using nodal and mesh analysis.

□ Example:

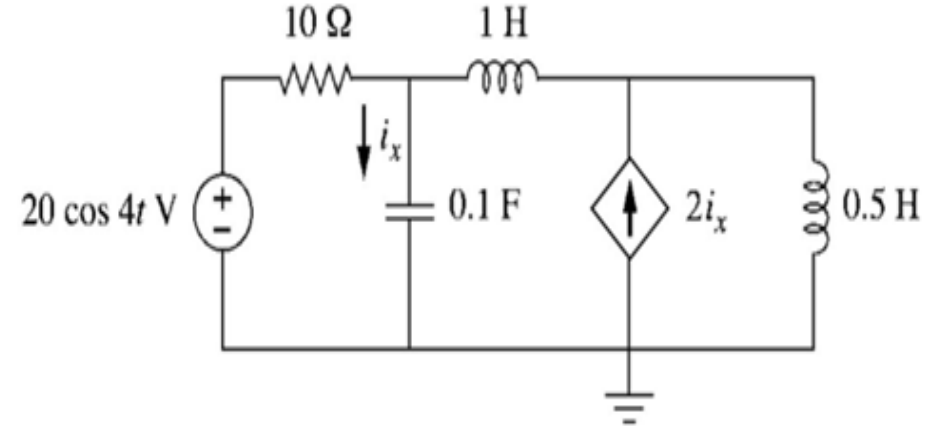- Find i_x in the circuit using nodal analysis?



Solution: We first convert the circuit to frequency domain,


$$20 \cos 4t \Rightarrow 20 \angle 0^\circ, \quad \omega = 4 \text{ rad/s}$$

$$1 \text{ H} \Rightarrow j\omega L = j4$$

$$0.5 \text{ H} \Rightarrow j\omega L = j2$$

$$0.1 \text{ F} \Rightarrow \frac{1}{j\omega C} = -j2.5$$

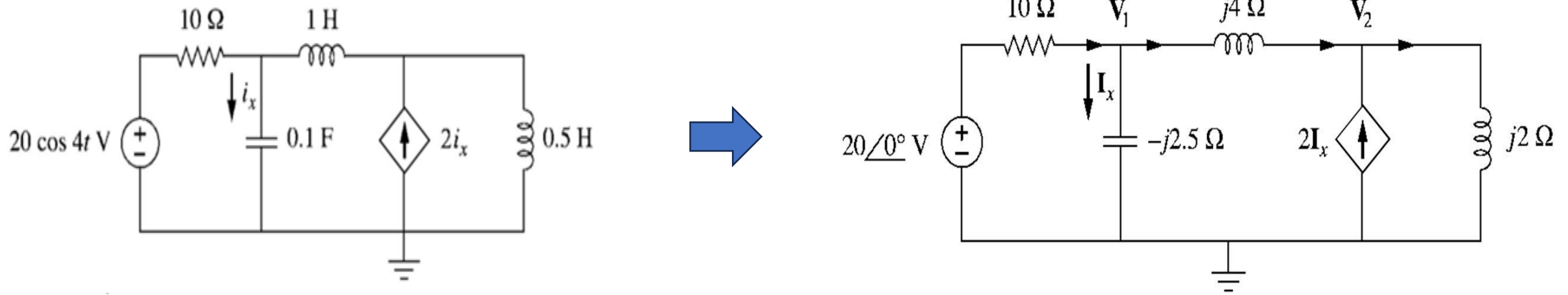Thus, the frequency domain equivalent circuit is as shown below.



Applying KCL at node 1,

$$\frac{20 - V_1}{10} = \frac{V_1}{-j2.5} + \frac{V_1 - V_2}{j4}$$

or

$$V_1(1 + j1.5) + j2.5V_2 = 20$$

Applying KCL at node 2,

$$\frac{\mathbf{V}_2}{j2} = 2\mathbf{I}_x + \frac{\mathbf{V}_1 - \mathbf{V}_2}{j4}$$

But $\mathbf{I}_x = \mathbf{V}_1 / -j2.5$. Substituting this gives,


$$\frac{\mathbf{V}_2}{j2} = \frac{2\mathbf{V}_1}{-j2.5} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{j4}$$

By simplifying, we get,

$$11\mathbf{V}_1 + 15\mathbf{V}_2 = 0$$

The nodal equations can be expressed in matrix form as,
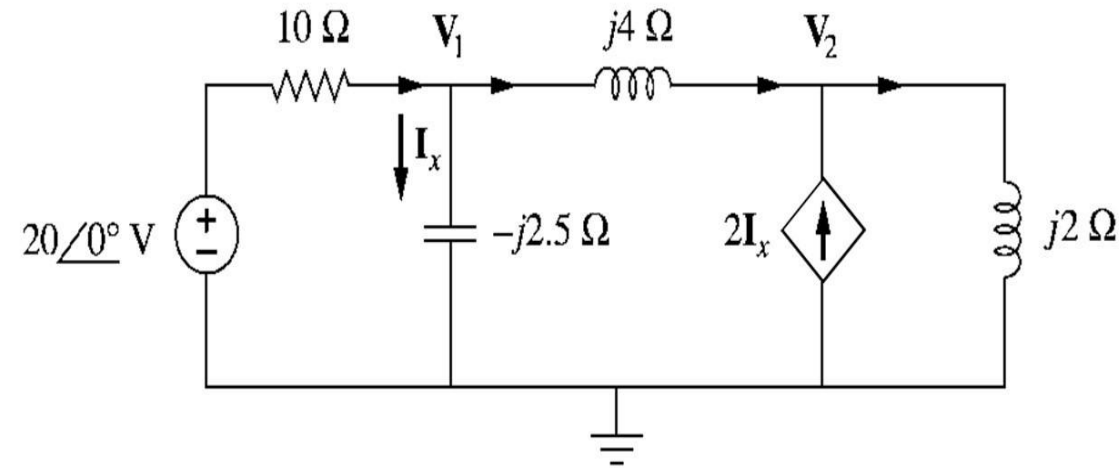
$$\begin{bmatrix} 20 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 + j1.5 & j2.5 \\ 11 & 15 \end{bmatrix} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix}$$



We obtain the determinants as,

$$\Delta = \begin{vmatrix} 1 + j1.5 & j2.5 \\ 11 & 15 \end{vmatrix} = 15 - j5$$

$$\Delta_1 = \begin{vmatrix} 20 & j2.5 \\ 0 & 15 \end{vmatrix} = 300, \quad \Delta_2 = \begin{vmatrix} 1 + j1.5 & 20 \\ 11 & 0 \end{vmatrix} = -220$$

$$\begin{aligned} \mathbf{V}_1 &= \frac{\Delta_1}{\Delta} = \frac{300}{15 - j5} \\ &= 18.97 \angle 18.43^\circ \text{V} \end{aligned}$$

$$\begin{aligned} \mathbf{V}_2 &= \frac{\Delta_2}{\Delta} = \frac{-220}{15 - j5} \\ &= 13.91 \angle 198.3^\circ \text{V} \end{aligned}$$

The current \mathbf{I}_x is given by,


$$\begin{aligned} \mathbf{I}_x &= \frac{\mathbf{V}_1}{-j2.5} = \frac{18.97 \angle 18.43^\circ}{2.5 \angle -90^\circ} = 7.59 \angle 108.4^\circ \Rightarrow i_x \\ &= 7.59 \cos(4t + 108.4^\circ) \text{A} \end{aligned}$$

❑ Superposition Theorem:

- Since ac circuits are linear, the superposition theorem applies to ac circuits the same way it applies to dc circuits.
- The problem becomes interesting if the circuit has sources operating at different frequencies.
- Since the impedances are dependent on frequency there will be separate circuits corresponding to each frequency domain.
- The total response is then obtained by adding the individual responses in time domain.
- Please note it is incorrect to add the responses in the phasor form or frequency domain

□ Example:

- Find v_0 using superposition theorem?

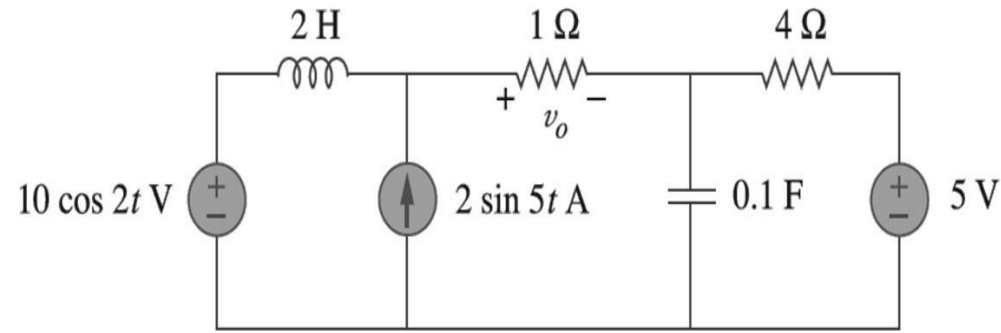


Solution: Since the circuit operates at 3 different frequencies, we can use superposition theorem to break the problem into 3 single frequency problems and express v_0 as,

$$v_0 = v_1 + v_2 + v_3$$

Here, v_1 is due to the 5 V dc source, v_2 is due to the $10 \cos 2t$ voltage source, and v_3 is due to the $2 \sin 5t$ current source.

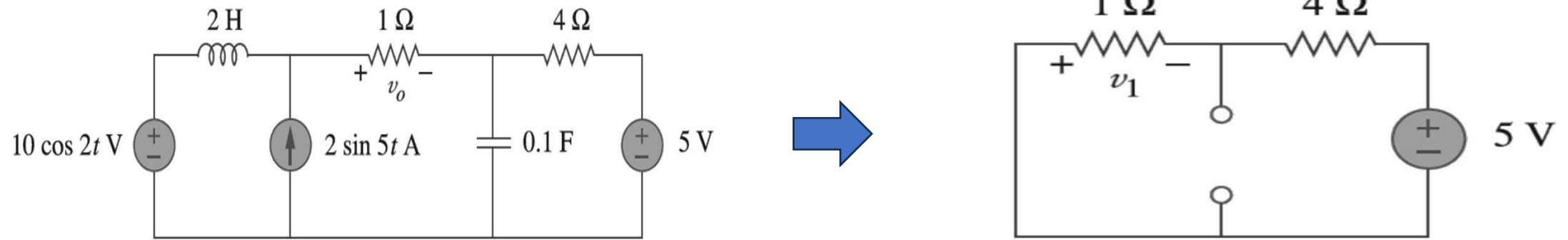- To find v_1 , we set all sources except the 5 V DC source to zero.
- Please recall that for DC sources a capacitor acts as an open circuit and an inductor acts as a short circuit.
- The circuit can therefore, be represented as,



- Hence, by voltage division,

$$-v_1 = \frac{1}{1 + 4} (5) = 1\text{ V}$$


- To find v_2 , we set both the 5 V DC source and $2 \sin 5t$ current source to zero.
- The circuit is then transformed to frequency domain, as,

$$10 \cos 2t \Rightarrow 10\angle 0^\circ, \omega = 2 \text{ rad/s}$$

$$2\text{H} \Rightarrow j\omega L = j4$$

$$0.1\text{F} \Rightarrow \frac{1}{j\omega C} = -j5$$

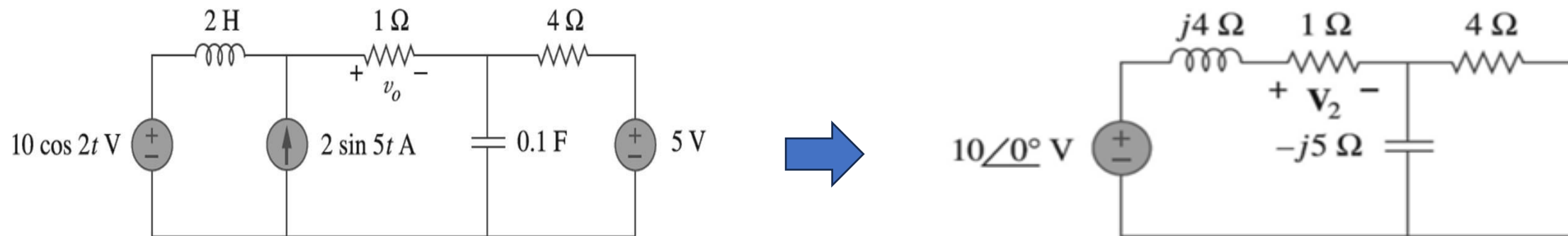- The equivalent circuit is as shown in the figure below.



- The effective impedance is

$$\mathbf{Z} = -j5 \parallel 4 = 2.439 - j1.951$$

- Hence, by voltage division,

$$\begin{aligned}\mathbf{V}_2 &= \frac{1}{1 + j4 + \mathbf{Z}} (10 \angle 0) \\ &= 2.498 \angle -30.79^\circ \text{ V}\end{aligned}$$

- The voltage in time domain is represented as,

$$v_2 = 2.498 \cos(2t - 30.79^\circ) \text{ V}$$



- To find v_3 , we set both the 5 V DC source and $10 \cos 2t$ voltage source to zero.
- The circuit is then transformed to frequency domain, as,

$$2 \sin 5t \Rightarrow 2 \angle -90^\circ, \omega = 5 \text{ rad/s}$$

$$2\text{H} \Rightarrow j\omega L = j10$$

$$0.1\text{F} \Rightarrow \frac{1}{j\omega C} = -j2$$

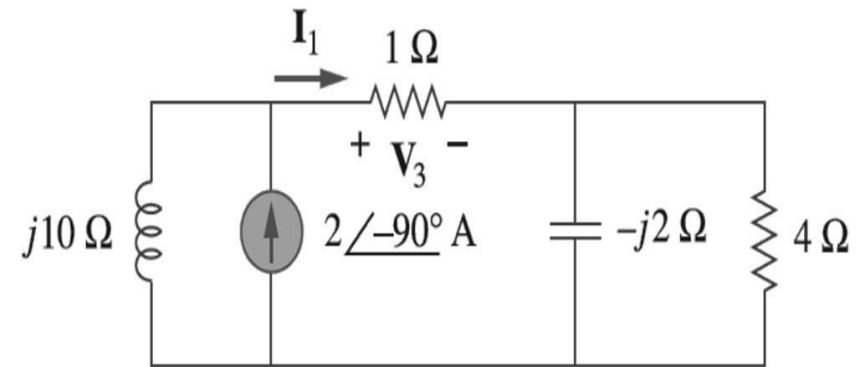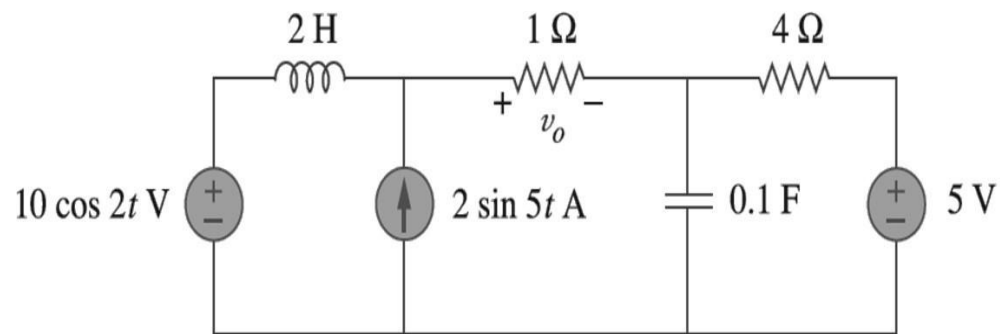- The equivalent circuit is as shown in the adjacent figure.



- The effective impedance is

$$\mathbf{Z}_1 = -j2 || 4 = 0.8 - j1.6$$

- Hence, by current division,

$$\mathbf{I}_1 = \frac{j10}{1 + j10 + \mathbf{Z}_1} (2\angle -90)$$

$$\mathbf{V}_3 = \mathbf{I}_1 * 1 = 2.328\angle -80 \text{ V}$$

- The voltage in time domain is represented as,

$$v_3 = 2.328 \cos(5t - 80^\circ) \text{ V} = 2.328 \sin(5t + 10^\circ) \text{ V}$$


- Therefore,

$$v_0 = -1 + 2.498\cos(2t - 30.79^\circ) + 2.328\sin(5t + 10^\circ)\text{V}$$

□ Source Transformation:


- Source transformation in the frequency domain involves transforming a voltage source in series with an impedance to a current source in parallel with an impedance, or vice versa.
- This is expressed as,
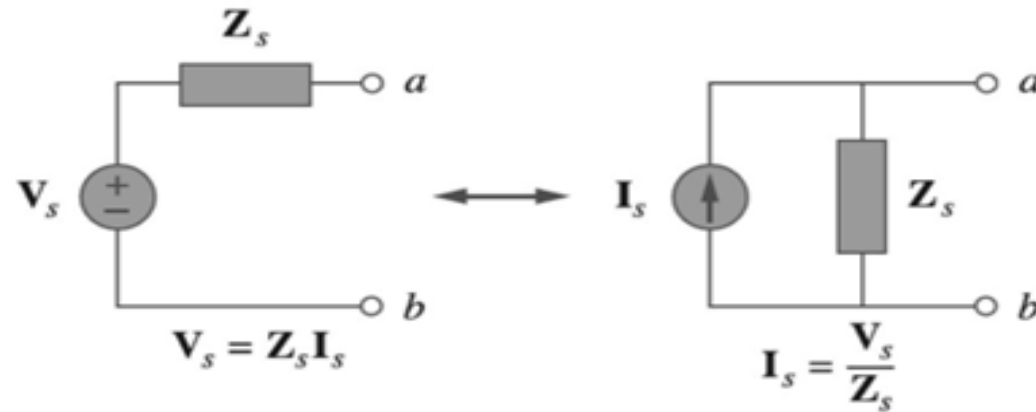
$$\mathbf{V}_s = \mathbf{I}_s \mathbf{Z}_s \Leftrightarrow \mathbf{I}_s = \frac{\mathbf{V}_s}{\mathbf{Z}_s}$$




□ Example:

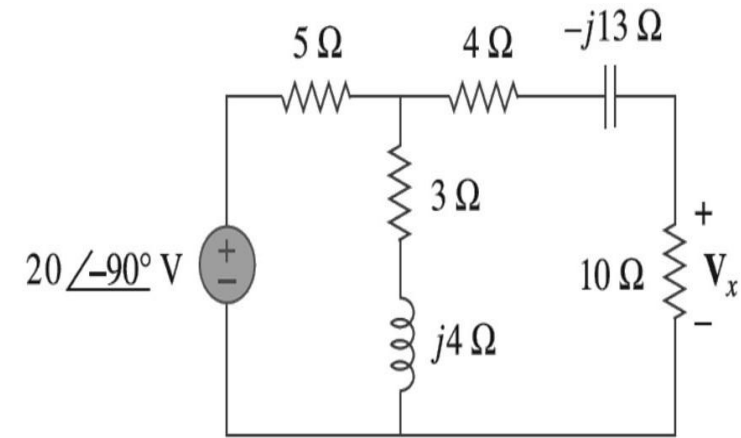- Find $\mathbf{V_x}$ using source transformation?



Solution: We transform the voltage source to a current source to obtain the circuit shown below.
Here,
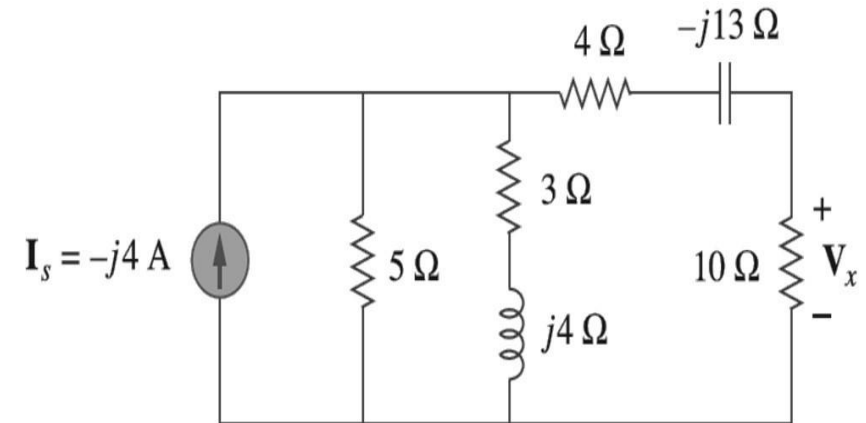
$$\mathbf{I_s} = \frac{20 \angle -90^\circ}{5} = 4 \angle -90^\circ$$




- The parallel combination 5 and $(3 + j4)$ impedances give

$$\mathbf{Z}_1 = 5 \parallel (3 + j4) = 2.5 + j1.25$$

- Converting the current source to voltage source, we get the following circuit.
- Here,
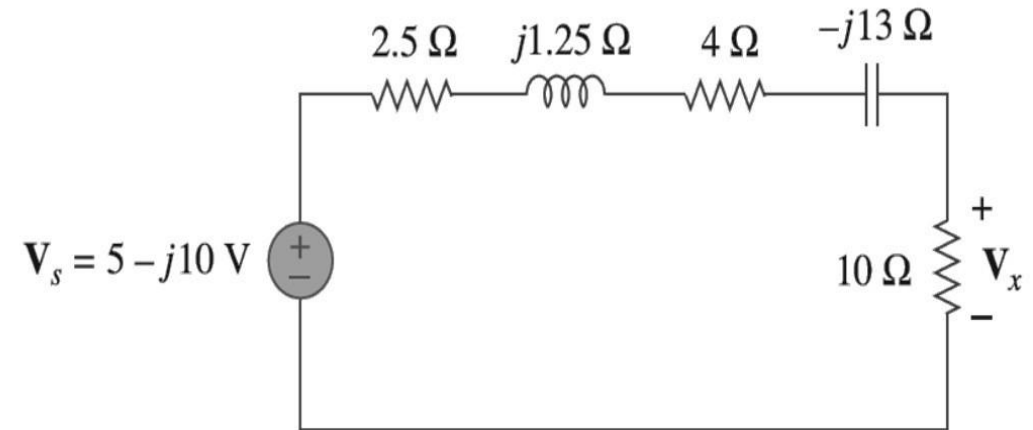
$$\begin{aligned}\mathbf{V}_s &= \mathbf{I}_s \mathbf{Z}_s = -j4(2.5 + j1.25) \\ &= 5 - j10\text{V}\end{aligned}$$





- By voltage division,

$$\mathbf{V}_x = \frac{10}{10 + 2.5 + j1.25 + 4 - j13} (5 - j10) = 5.519 \angle -28^\circ \text{V}$$

Thevenin and Norton Equivalent Circuit


- Thevenin's and Norton's theorems are applied to **AC** circuits in the same way as **DC** circuits.
- As in the case of superposition theorem, if there are sources operating at different frequencies there will be separate circuits corresponding to each frequency domain.
- The frequency domain equivalent circuits for Thevenin and Norton equivalent are expressed as,
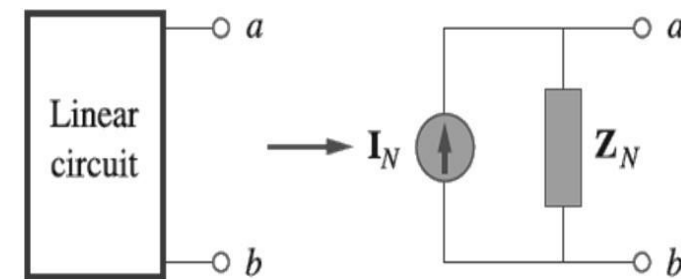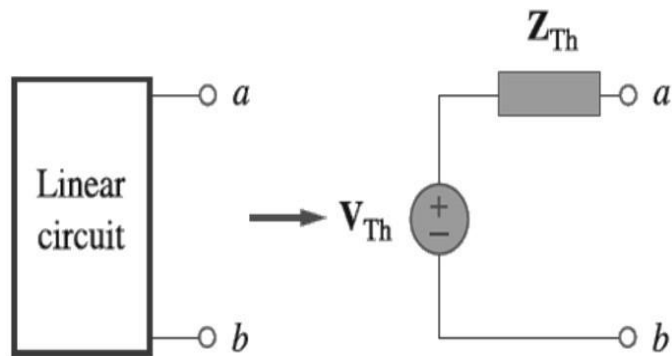
$$\mathbf{V}_{Th} = \mathbf{Z}_N \mathbf{I}_N, \quad \mathbf{Z}_{Th} = \mathbf{Z}_N$$



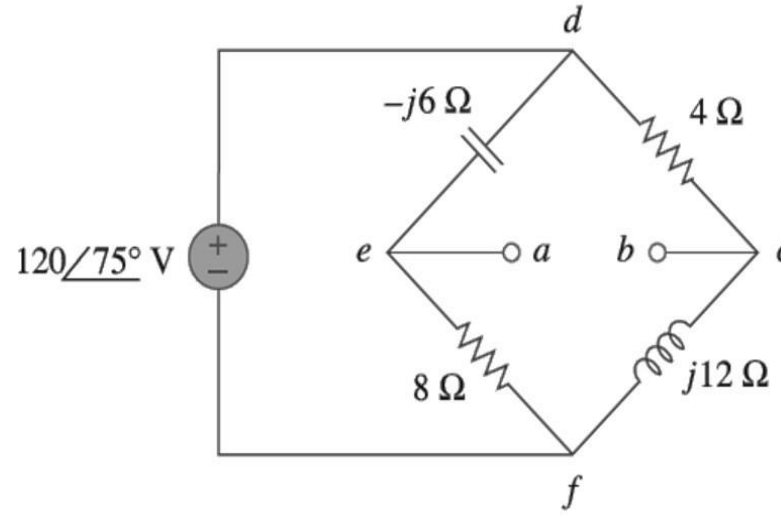
Example:

- Obtain Thevenin equivalent circuit across terminal **a-b** for the circuit given below?



Solution: $\mathbf{Z_{Th}}$ is found by setting voltage source to 0.

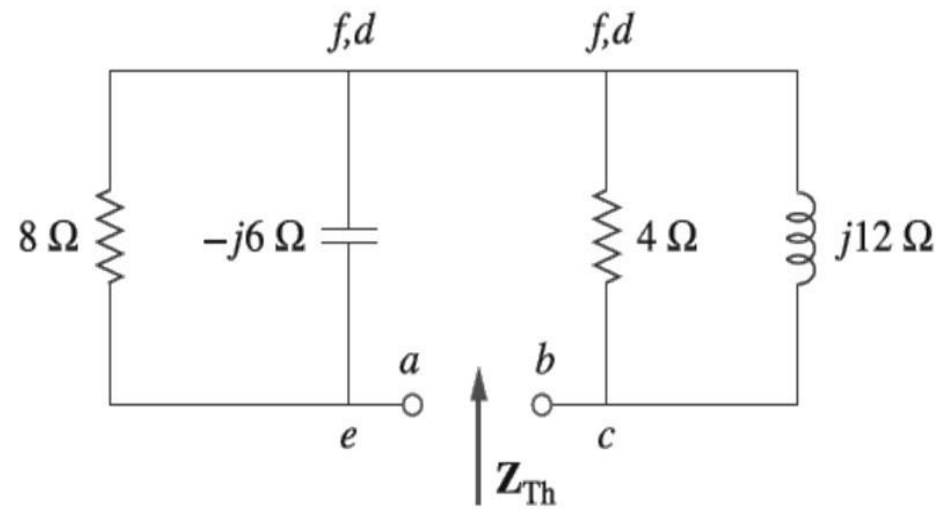The circuit then contains two parallel combinations of $8\ \Omega$ and $-j6\ \Omega$ impedances in the first branch and $4\ \Omega$ and $j12\ \Omega$ impedances in the second branch.



Then we have,

$$\mathbf{Z}_1 = -j6 || 8 = \frac{-j6(8)}{-j6 + 8} = 2.88 - j3.84\Omega$$


and

$$= j12 || 4 = \frac{j12(4)}{j12 + 4} = 3.6 + j1.2\Omega$$

Thevenin equivalent impedances is then given by,

$$\mathbf{Z}_{Th} = \mathbf{Z}_1 + \mathbf{Z}_2 = 6.48 - j2.64\Omega$$

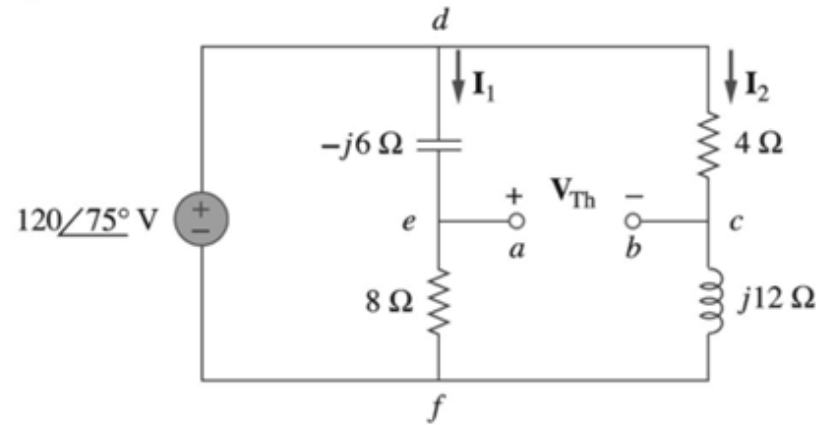To find $\mathbf{V_{Th}}$ consider the below circuit.



Currents $\mathbf{I_1}$ and $\mathbf{I_2}$ are obtained as follows,

$$\mathbf{I_1} = \frac{120\angle 75}{8 - j6} \text{ A}, \quad \mathbf{I_2} = \frac{120\angle 75}{4 + j12} \text{ A}$$

Applying KVL around loop **bcdeab**,

$$\mathbf{V_{Th}} - 4\mathbf{I_2} + (-j6)\mathbf{I_1} = 0$$

Therefore,

$$\mathbf{V}_{Th} = 4\mathbf{I}_2 + j6\mathbf{I}_1$$


$$= \frac{480\angle 75}{4 + j12} + \frac{720\angle (75 + 90)}{8 - j6}$$

$$= 37.95\angle 3.43 + 72\angle 201.87$$


$$= 37.95\angle 220.31\text{V}$$

□ Example:

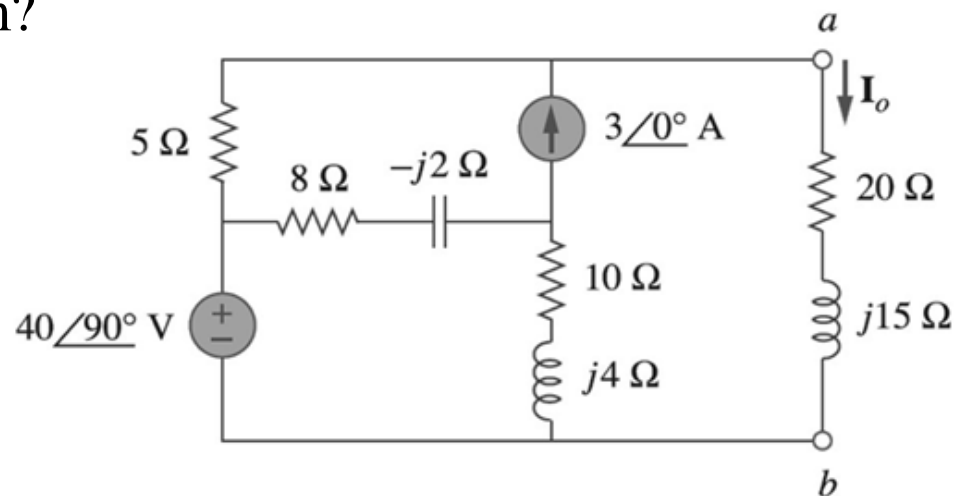- Find \mathbf{I}_0 using Norton theorem?



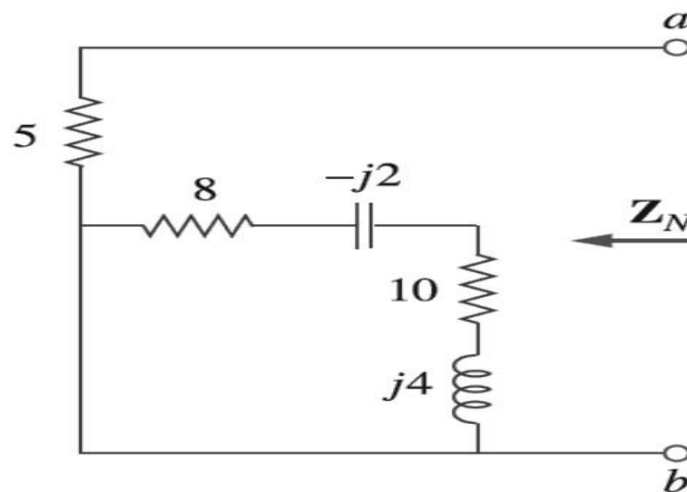
Solution: To find \mathbf{Z}_N we set the sources to 0 as shown in the below figure,



- As evident from the figure $(8 - j2)$ and $(10 + j4)$ impedances are short circuited
- Therefore,

$$\mathbf{Z_N = 5 \, \Omega}$$

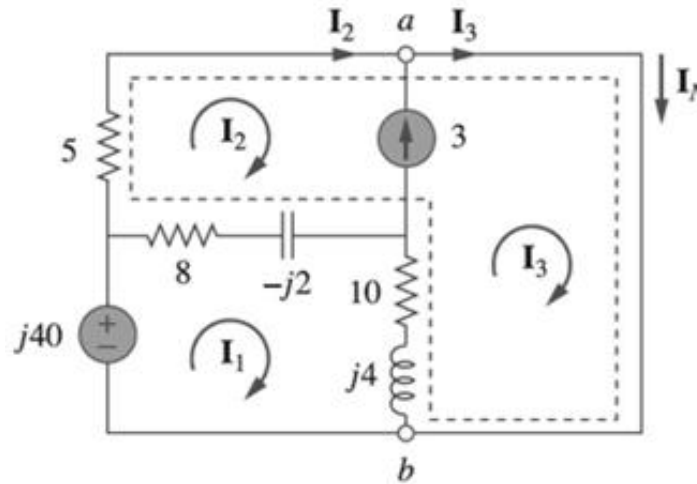- To get $\mathbf{I_N}$ we short-circuit terminals **a-b** as shown below and apply mesh analysis,



- It can be observed that meshes **2** and **3** form a supermesh because of the current source linking them.

- From mesh-1,

$$-j40 + \mathbf{I}_1(18 + j2) - \mathbf{I}_2(8 - j2) - \mathbf{I}_3(10 + j4) = 0$$

- From the supermesh,

$$-\mathbf{I}_1(18 + j2) + \mathbf{I}_2(13 - j2) + \mathbf{I}_3(10 + j4) = 0$$

- At node *a* due to current source between meshes 2 and 3,


$$\mathbf{I}_3 = \mathbf{I}_2 + 3$$

- Adding the first two equations we get,

$$-j40 + 5\mathbf{I}_2 = 0$$

- Therefore,

$$\mathbf{I}_2 = j8$$

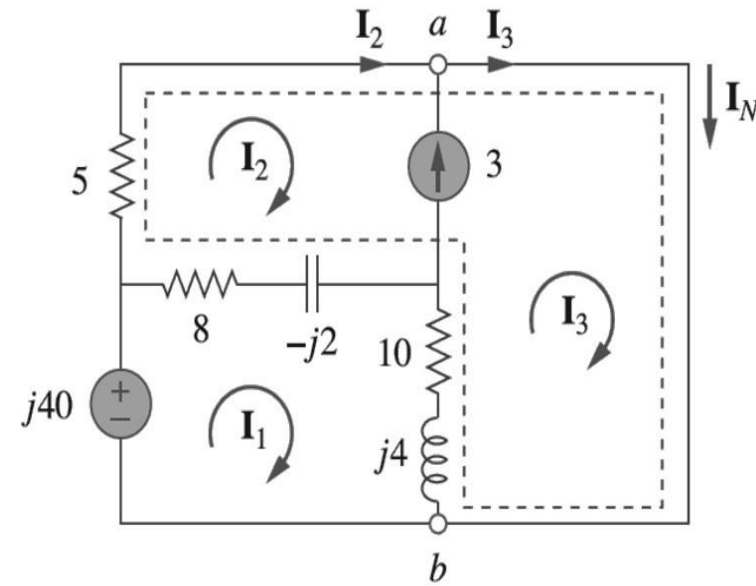


- But,

$$\mathbf{I}_3 = \mathbf{I}_2 + 3 = 3 + j8$$

- The Norton current is ,

$$\mathbf{I}_N = \mathbf{I}_3 = 3 + j8$$

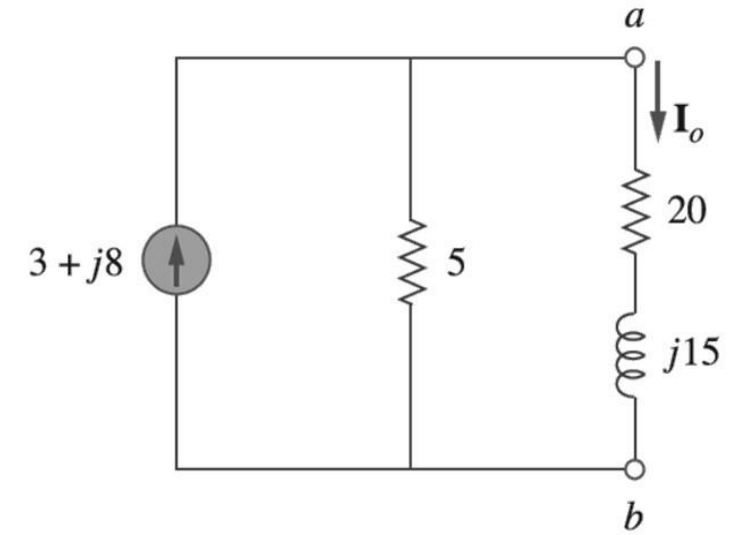


- The Norton equivalent circuit is as shown and by current division,

$$\mathbf{I}_0 = \frac{5}{5 + 20 + j15} \mathbf{I}_N = \frac{3 + j8}{5 + j3} = 1.465 \angle 38.48^\circ \text{A}$$

Maximum Power Transfer Theorem

- Earlier, in **DC** circuit, we solved the problem of maximizing the power delivered by a power-supplying resistive network to a load R_L .
- Representing the circuit by its Thevenin equivalent, we proved that the maximum power would be delivered to the load if the load resistance is equal to the Thevenin resistance, i.e. $R_L = R_{Th}$
- We now extend that result to **AC** circuits.

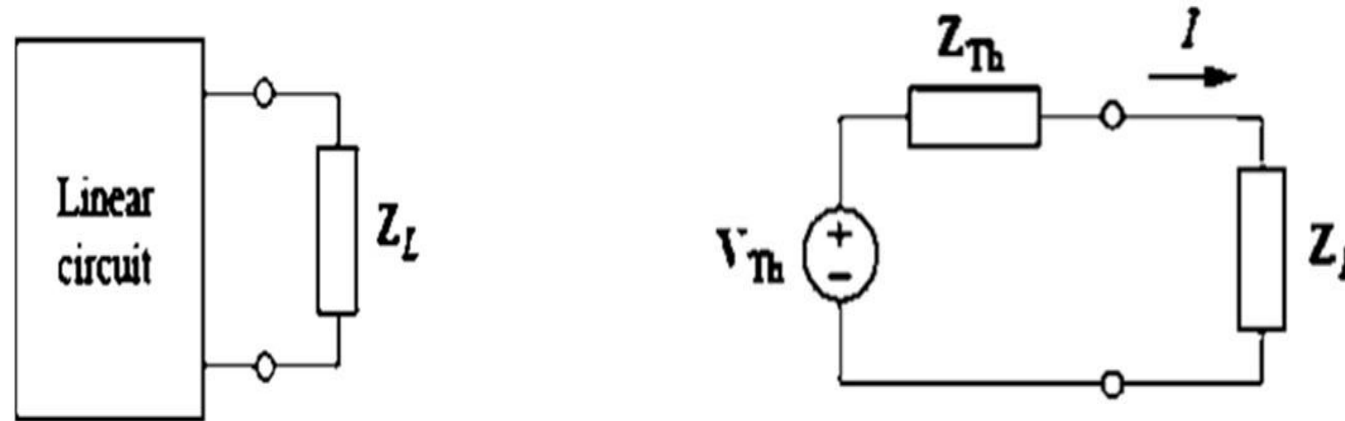- Consider the circuit shown in figure below where an ac circuit is connected to a load Z_L and is represented by its Thevenin equivalent



- The load is usually represented by an impedance.
- In rectangular form, the Thevenin impedance Z_{Th} and the load impedance Z_L are –

$$Z_{Th} = R_{Th} + jX_{Th}$$

$$Z_L = R_L + jX_L$$

- The current through the load is –

$$I = \frac{V_{Th}}{Z_{Th} + Z_L} = \frac{V_{Th}}{(R_{Th} + jX_{Th}) + (R_L + jX_L)}$$

- The average power delivered to the load is given as –

$$P = \left(\frac{1}{2}\right) I^2 R_L = \frac{V_{Th}^2 \times \frac{R_L}{2}}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2}$$

- Our objective is to adjust the load parameters R_L and X_L so that P is maximum.
- To do this, we set $\partial P / \partial R_L$ and $\partial P / \partial X_L$ equal to zero.
- Using above Equation of P , we can obtain the values of $\partial P / \partial R_L$ and $\partial P / \partial X_L$

- Therefore,

$$\frac{\partial P}{\partial X_L} = \frac{V_{Th}^2 R_L (X_{Th} + X_L)}{[(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2]^2}$$

$$\frac{\partial P}{\partial R_L} = \frac{V_{Th}^2 [(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2 - 2R_L(R_{Th} + R_L)]}{2[(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2]^2}$$

- Setting $\partial P/\partial X_L$ equal to zero gives –

$$X_L = -X_{Th}$$

- Setting $\partial P/\partial R_L$ equal to zero gives –

$$R_L = \sqrt{R_{Th}^2 + (X_{Th} + X_L)^2} = R_{Th}$$

- Therefore, we can conclude that, for maximum average power transfer, Z_L must be selected so that $X_L = -X_{Th}$ and $R_L = R_{Th}$ i.e.,

$$Z_L = R_L + jX_L = R_{Th} - jX_{Th} = Z_{Th}^*$$

- So, for maximum average power transfer, the load impedance Z_L must be equal to the complex conjugate of the Thevenin impedance Z_{Th}
- The maximum average power is given as –

$$P_{max} = \frac{V_{Th}^2}{8R_{Th}}$$

(Note: If V_{Th} is the RMS Value, then $P_{max} = \frac{V_{Th}^2}{4R_{Th}}$)


- If the load is purely real, the condition for maximum power transfer is obtained by setting $X_L = 0$; that is –

$$R_L = \sqrt{R_{Th}^2 + X_{Th}^2}$$



- This means that for maximum average power transfer to a purely resistive load, the load impedance (or resistance) is equal to the magnitude of the Thevenin impedance.

□ Example:

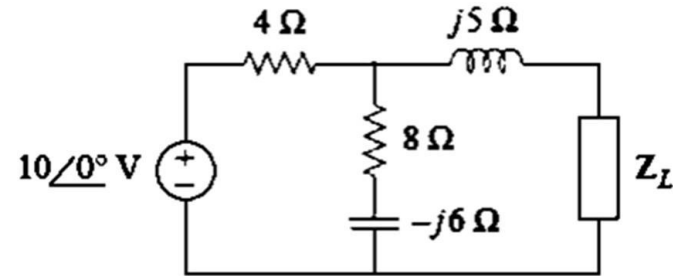- Determine the load impedance Z_L that maximizes the average power drawn from the circuit?



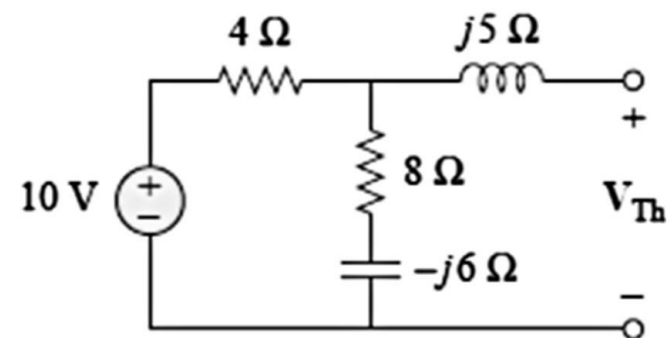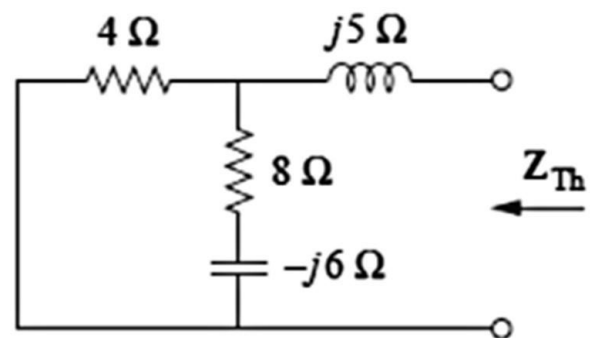Solution: First we obtain the Thevenin equivalent at the load terminals,



$$Z_{Th} = 2.933 + j4.467\ \Omega$$


$$V_{Th} = 7.454 \angle -10.3^\circ\text{ V}$$

So,

$$Z_L = Z_{Th}^* = 2.933 - j4.467\ \Omega$$



Three Phase Circuits

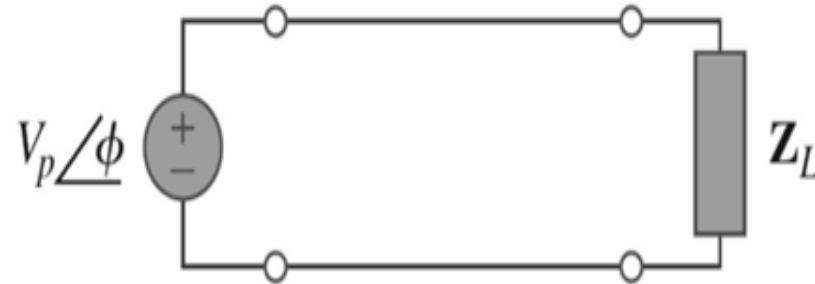- So far in this course, we have been dealing with single-phase circuits.
- A single-phase **AC** power system consists of a generator connected through a pair of wires (a transmission line) to a load.
- This is illustrated in the below figure, where a single-phase two wire system is used.
- Here V_p is the rms magnitude of the source voltage and ϕ is the phase.



Three Phase Circuits (Cont...)

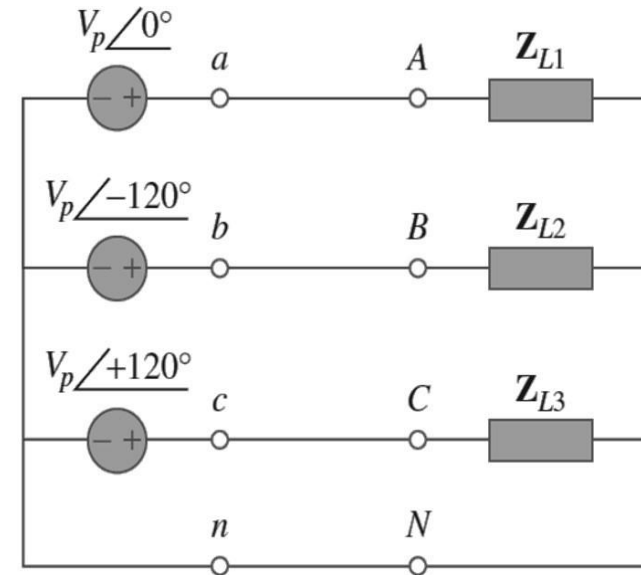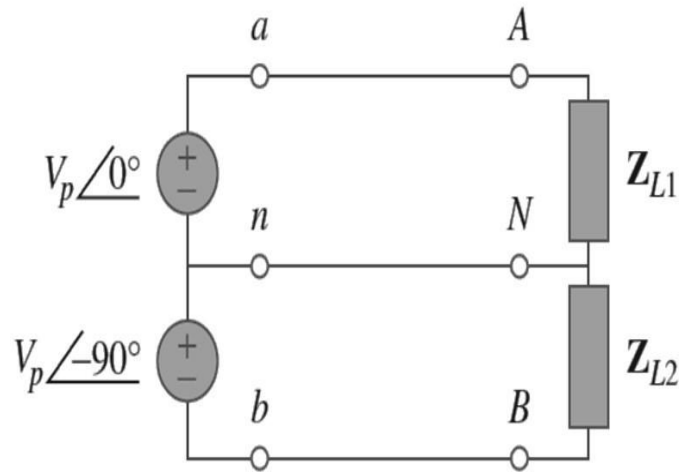- Circuits or systems in which the ac sources operate at the same frequency but different phases are known as polyphase.
- The figure on the left below shows a two-phase three-wire system, and the figure on the right shows a three-phase four wire system.




Three Phase Circuits (Cont...)


- As distinct from a single-phase system, a two-phase system is produced by a generator consisting of two coils placed perpendicular to each other so that the voltage generated by one lags the other by 90° .
- In the same way, a three-phase system is produced by a generator consisting of three sources having the same amplitude and frequency but out of phase with each other by 120° .
- Since the three-phase system is by far the most prevalent and most economical polyphase system, our discussion will mainly be on three-phase systems.
- Three-phase systems are important for at least three reasons.
 1. Nearly all electric power is generated and distributed in three-phase, at the operating frequency of 50 or 60 Hz.
 2. The instantaneous power in a three-phase system can be constant (not pulsating), as will be discussed later.
 3. The three-phase system is more economical than single phase system as the amount of wire required for a three-phase system is lesser than the amount of wire needed for an equivalent single-phase system.

Balanced Three-Phase Voltages

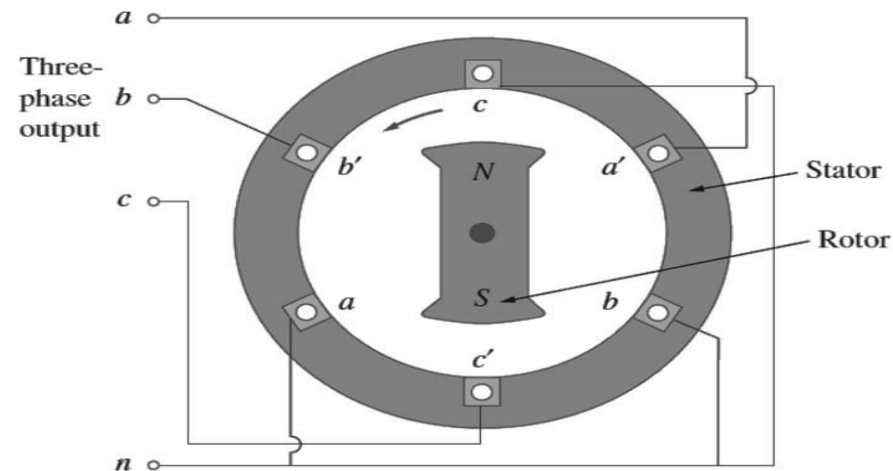- Three-phase voltages are often produced with a three-phase ac generator (or alternator) whose cross-sectional view is shown below.
- The generator basically consists of a rotating magnet (called the *rotor*) surrounded by a stationary winding (called the *stator*).



- Three separate windings or coils with terminals $a - a'$, $b - b'$, and $c - c'$ and are physically placed 120° apart around the stator.
- Terminals a and a' for example, stand for one of the ends of coils going into and the other end coming out of the page.
- As the rotor rotates, its magnetic field “cuts” the flux from the three coils and induces voltages in the coils.
- Because the coils are placed 120° apart, the induced voltages in the coils are equal in magnitude but out of phase by 120° as shown below.

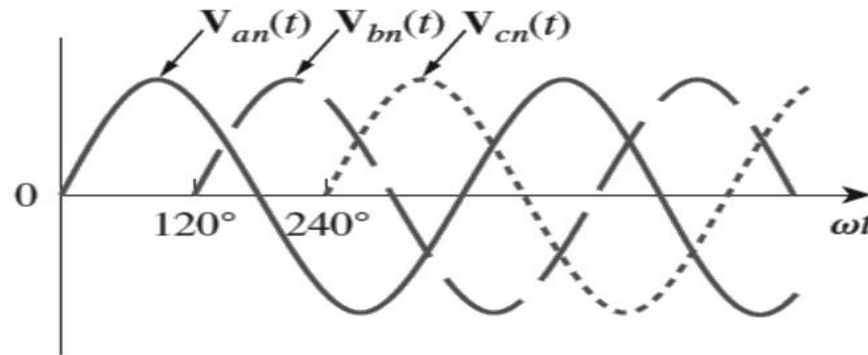

- Since each coil can be regarded as a single-phase generator by itself, the three-phase generator can supply power to both single-phase and three-phase loads.
- A typical three-phase system consists of three voltage sources connected to loads by three or four wires (or transmission lines)
- A three-phase system is equivalent to three single-phase circuits.
- The voltage sources can be either **wye (Y)**-connected or **delta (Δ)**-connected as shown below.

