

## Tutorial 1 Solution

- 1) Three light bulbs are connected to a 200 V battery in series. The bulbs are consuming 60 W, 80 W, and 100 W power as shown below. Find the current 'I' through it.

**Solution:**

Let, the resistance of Bulb B<sub>1</sub>, B<sub>2</sub>, and B<sub>3</sub> are R<sub>1</sub>, R<sub>2</sub>, and R<sub>3</sub> respectively

The bulbs are in series. So, the current  $I$  is the same for all the bulbs.

$$R_1 = \frac{P_1}{I^2} \quad R_2 = \frac{P_2}{I^2} \quad R_3 = \frac{P_3}{I^2}$$


We know that,

$$V = IR$$

$$200 = I(R_1 + R_2 + R_3) = I \left( \frac{60}{I^2} + \frac{80}{I^2} + \frac{100}{I^2} \right)$$

$$200 = I \left( \frac{240}{I^2} \right)$$

$$I = 1.2 \text{ A}$$

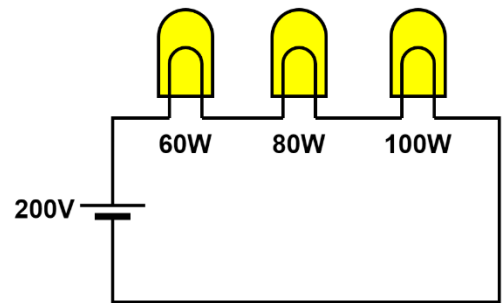

- 2) The current through a 0.2 Henry inductor is  $i = 5te^{-2t}$  A. Find the voltage across it and the energy stored in the inductor?

**Solution:**

Given,

$$L = 0.2 \text{ H}$$

$$i(t) = 5te^{-2t} \text{ A}$$

We know that, voltage across the inductor is given by

$$v(t) = L \frac{di}{dt} = 0.2 \frac{d}{dt} (5te^{-2t})$$

$$v(t) = 0.2 \{ 5t(-2)e^{-2t} + e^{-2t}(5) \}$$

$$v(t) = (1 - 2t)e^{-2t}$$

- 3) A certain circuit element has the current  $i = 10e^{-5000t}$  A and voltage  $v = 50(1 - e^{-5000t})$  V. Find the total energy transferred during  $t \geq 0$ .

**Solution:**

The instantaneous power is

$$p(t) = v(t) * i(t)$$

$$p(t) = 500(e^{-5000t} - e^{-10000t})$$

The total energy is given by

$$E = \int_0^{\infty} p(t) dt$$

$$E = \int_0^{\infty} 500(e^{-5000t} - e^{-10000t}) dt = 500 \left[ \frac{e^{-5000t}}{-5000} - \frac{e^{-10000t}}{-10000} \right]_0^{\infty} = 500 \left[ \frac{1}{5000} - \frac{1}{10000} \right]$$

$$E = 0.05 \text{ Joules}$$

**4) Find the number of node, branch, mesh, and loop in the given figures 4(a) and 4(b).**

**Solution:**

**4(a):** The nodes are A, B, C, D, E, F, G, and H.

The number of nodes 'n' = 8


The number of branches 'b' = 11

The number of mesh 'm' is given by

$$m = b - n + 1$$

$$m = 4$$

The number of loops 'l' is 10.

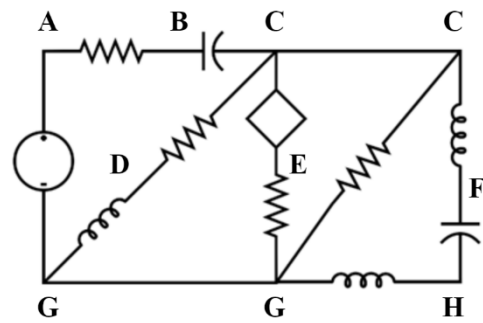

**4(a)**

**4(b):** The nodes are A, B, C, D, E, F, G, and H.


The number of nodes 'n' = 8

The number of branches 'b' = 10

The number of mesh 'm' is given by

$$m = b - n + 1$$

$$m = 3$$

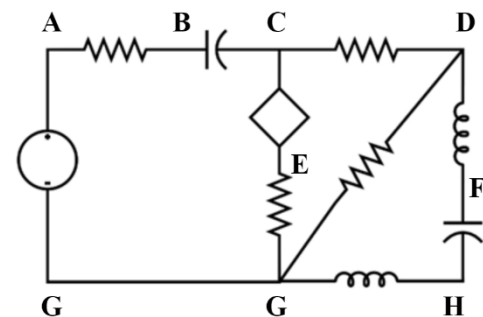

**4(b)**

The number of loops 'l' is 6.

**5) Calculate the power supplied or absorbed by each element in the figure and**

**show**  $\sum P_{absorbed} = \sum P_{supplied}$

**Solution:**

The current goes out from the positive terminal of the battery. So, power is supplied by the voltage source.

$$P_1 = VI$$

$$P_1 = 25 \times 10 = 250W$$

The current goes in the positive terminal of the voltage of the resistor. So, the power is absorbed by the component 2 and 3.

The voltage appeared across the dependent source is positive with respect to current direction. So, power is supplied by the dependent source.

$$P_2 = VI$$

$$P_2 = 10 \times 10 = 100W$$

$$P_3 = VI$$


$$P_3 = 15 \times 15 = 225W$$

$$P_4 = VI$$

$$P_4 = 15 \times 0.5 \times 10 = 75W$$

$$P_{absorbed} = P_2 + P_3 = 325W$$

$$P_{supplied} = P_1 + P_4 = 325W$$

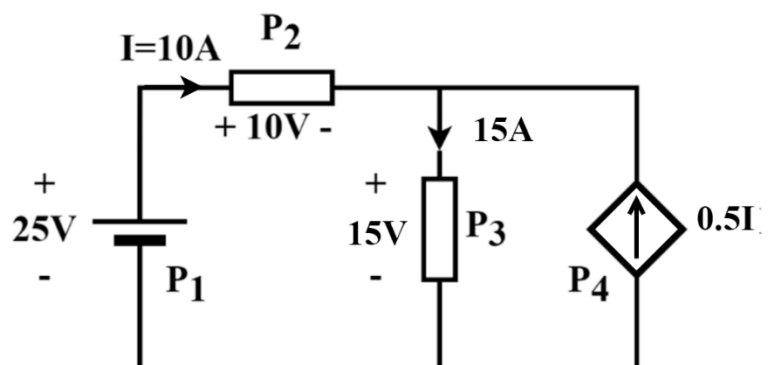

- 6) In the interval  $0 < t < 5\pi \text{ ms}$ , a  $20 \mu\text{F}$  capacitor has a voltage  $V = 100 \sin 200t \text{ (V)}$ . Find the charge, power, and energy.

**Solution:**

$$\text{Charge, } Q = CV = 20 \times 100 \sin 200t \mu\text{C} = 2 \sin 200t \text{ mC}$$

$$\text{Current, } i = C \frac{dV}{dt} = 20 \times 100 \times 200 \cos 200t \mu\text{C} = 400 \cos 200t \text{ mA}$$

$$\text{Power, } p = Vi = 400 \times 100 \sin 200t \times \cos 200t \text{ mW} = 20 \sin 400t \text{ W}$$

$$\text{Energy, } E = \frac{1}{2} CV^2 = \frac{1}{2} \times 20 \mu \times (100 \sin 200t)^2 = 100 \sin^2 200t \text{ mJ}$$

For the interval  $0 < t < 5\pi \text{ ms}$ ,

$$E(5\pi) - E(0) = 0$$

- 7) The two electrical network  $N_1$  and  $N_2$  are connected through three resistors as shown in figure. Find the voltage across  $3\Omega$  resistor.

**Solution:**

Current flows in closed path.


Current flows from  $N_1$  to  $N_2$  = Current flows from  $N_1$  to  $N_2$

The net current flows from  $N_1$  to  $N_2$  is given by

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V}{R_3} = 0$$

$$\frac{6}{2} + \frac{16}{4} + \frac{V}{3} = 0$$

$$V = -21 \text{ V}$$

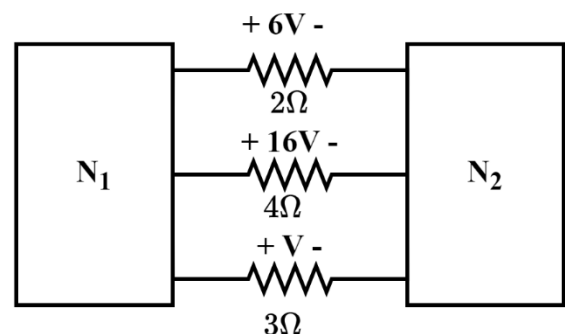

- 8) Find the current going out from the positive terminal of the 2V battery using mesh analysis.

**Solution:**

For mesh 1,


$$-2 + 225I_1 + 50I_1 + 100(I_1 - I_2) + 4 + 75I_1 = 0$$

$$450I_1 - 100I_2 = -2 \quad \dots \dots \dots (i)$$

For mesh 2,

$$-4 + 100(I_2 - I_1) + 150I_2 + 200I_2 + 8 + 50I_2 = 0$$
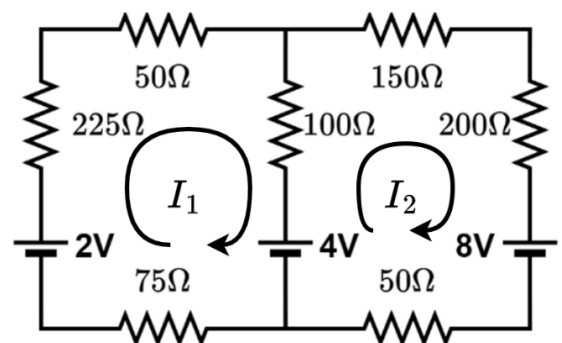
$$-100I_1 + 500I_2 = -4 \quad \dots \dots \dots (ii)$$



From equation (i) and (ii), The current going out from the positive terminal of 2V battery is

$$I_1 = -6.51 \text{ mA}$$


9) Find the equivalent capacitance between A and B.

**Solution:**

$C_2$  and  $C_4$  are in parallel.

Similarly,  $C_3$  and  $C_6$  are in parallel.

Equivalent is  $C_2 + C_4 = 2\text{ F}$

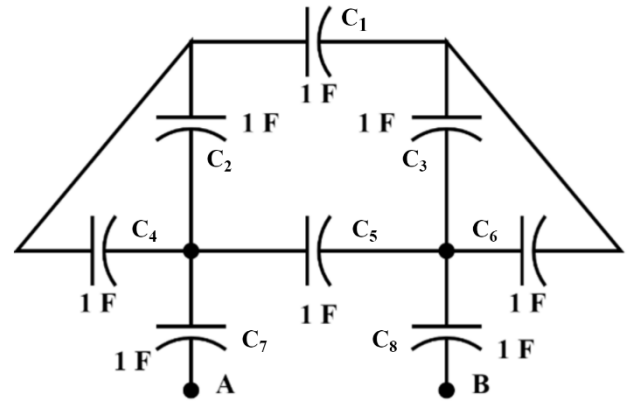


Now, equivalent circuit is

The equivalent capacitance between X and Y is given by

$$C_{XY} = \left( \frac{1}{\frac{1}{C_1} + \frac{1}{2} + \frac{1}{2}} \right) + C_5$$


$$C_{XY} = 1.5\text{ F}$$

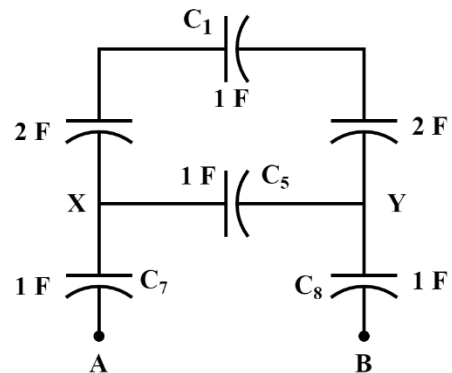

The equivalent capacitance between A and B is given by


$$C_{AB} = \left( \frac{1}{\frac{1}{C_7} + \frac{1}{C_8} + \frac{1}{1.5}} \right)$$

$$C_{AB} = 0.375\text{ F}$$

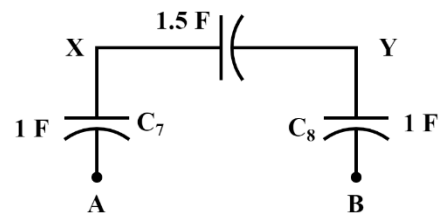

10) Find the equivalent resistance between A and B.

**Solution:**

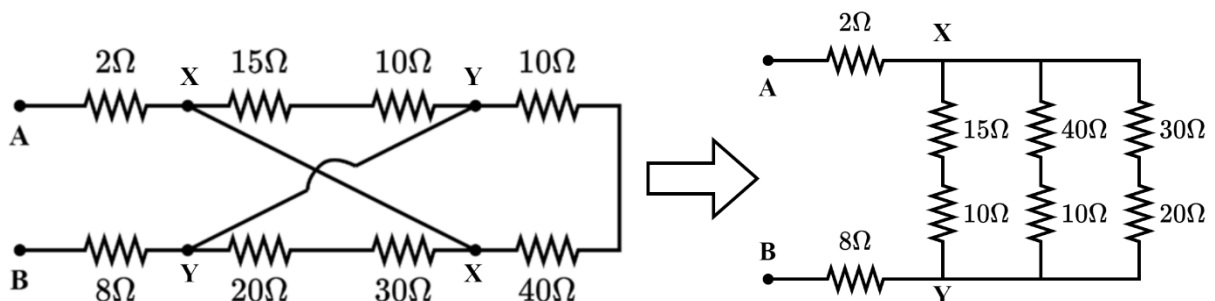

The equivalent resistance across terminal A and B is given by

$$R_{AB} = 2 + 8 + (50 || 50 || 25)$$

$$R_{AB} = 2 + 8 + (12.5)$$

$$R_{AB} = 22.5\ \Omega$$