

Transmission Lines - I

Prof. M. Jaleel Akhtar

mjakhtar@iitk.ac.in

<https://home.iitk.ac.in/~mjakhtar/>

**Department of Electrical Engineering
Indian Institute of Technology Kanpur
Kanpur – 208016 (U.P.)**



Free Space ↔ **Wireless Communication**

Transmission of Electromagnetic energy through unguided media

Transmission Lines ↔ **Wired Communication**

Transmission of Electromagnetic energy through guided media




RF Cables


Commonly used Transmission Lines

Distributed effects are important


Parallel Plate lines

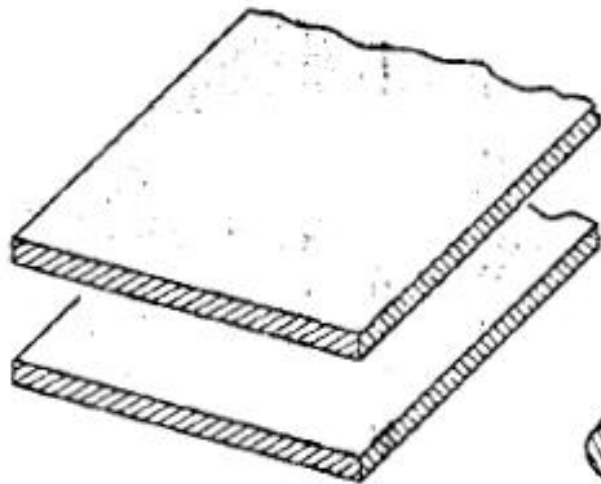

Two wire lines

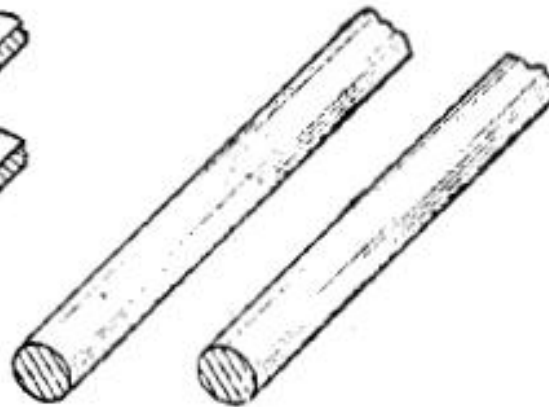


Coaxial lines

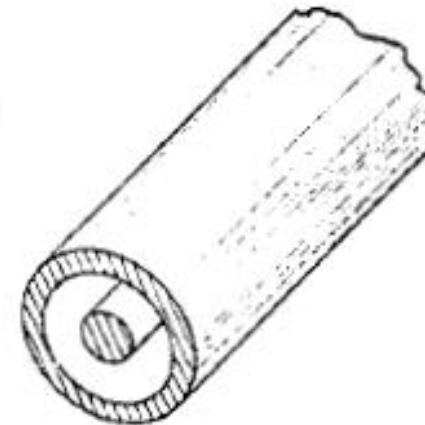

The elements are distributed along the length of conductors.




General Transmission Line Equations

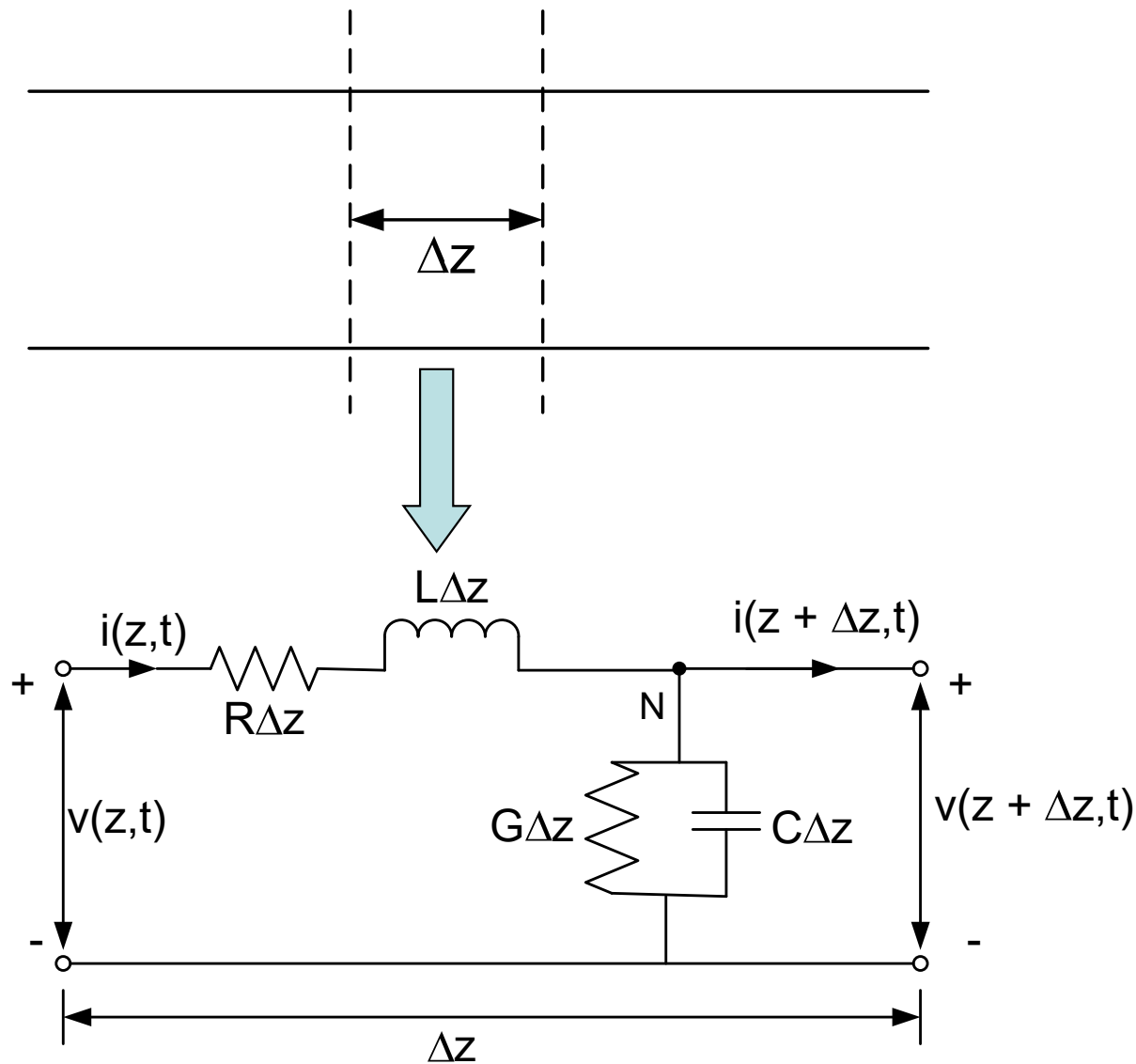
 $R: (\Omega/\text{m})$
 $G: (\text{S}/\text{m})$
 $L: (\text{H}/\text{m})$
 $C: (\text{F}/\text{m})$

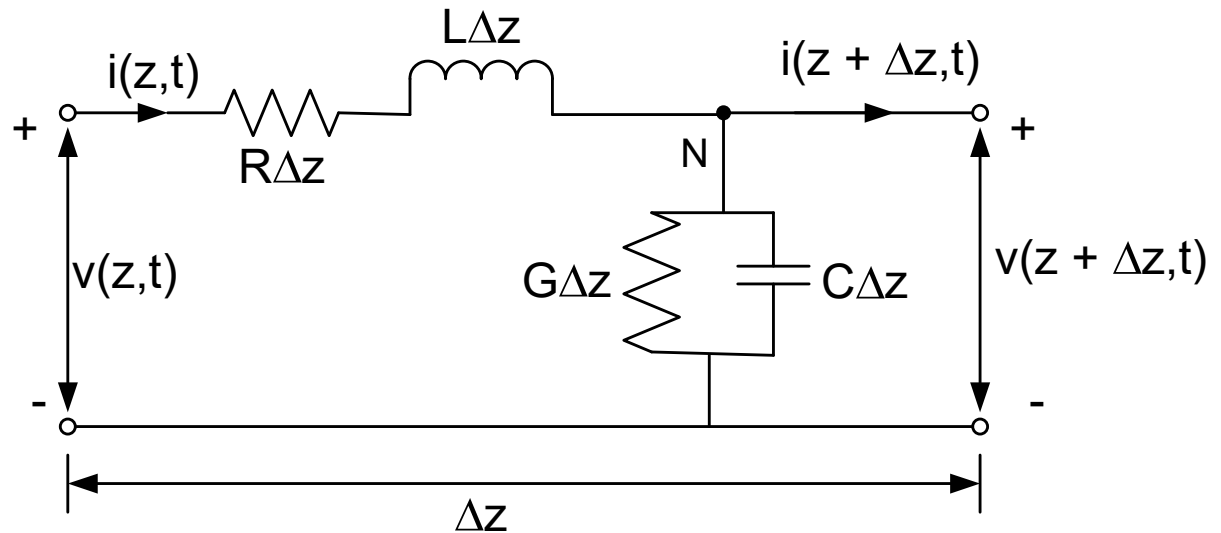Equivalent Circuit of a small length z of two wire transmission line





Applying KVL


$$v(z,t) - R\Delta z i(z,t) - L\Delta z \frac{\partial i(z,t)}{\partial t} - v(z + \Delta z,t) = 0$$

$$-\frac{v(z + \Delta z,t) - v(z,t)}{\Delta z} = R i(z,t) + L \frac{\partial i(z,t)}{\partial t}$$

$$\Delta z \rightarrow 0$$
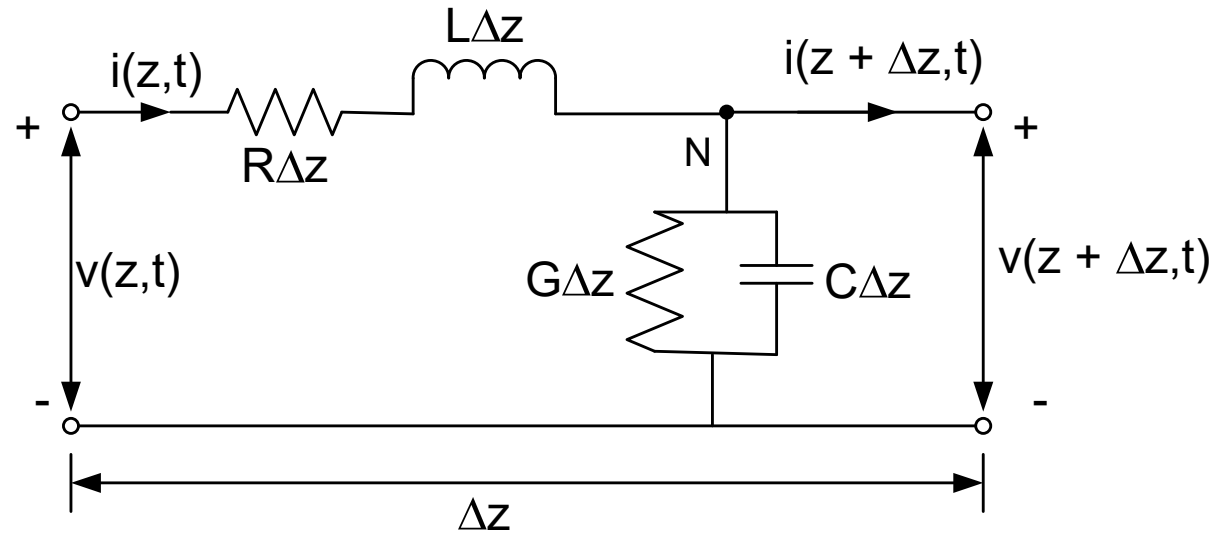
$$-\frac{\partial v(z,t)}{\partial z} = R i(z,t) + L \frac{\partial i(z,t)}{\partial t}$$





Applying KCL at node N

$$i(z, t) - G\Delta z v(z + \Delta z, t) - C\Delta z \frac{\partial v(z + \Delta z, t)}{\partial t} - i(z + \Delta z, t) = 0$$

$$-\frac{i(z + \Delta z, t) - i(z, t)}{\Delta z} = G v(z + \Delta z, t) + C \frac{\partial v(z + \Delta z, t)}{\partial t}$$

$$\Delta z \rightarrow 0$$

$$-\frac{\partial i(z, t)}{\partial z} = G v(z, t) + C \frac{\partial v(z, t)}{\partial t}$$



$$-\frac{\partial v(z, t)}{\partial z} = R i(z, t) + L \frac{\partial i(z, t)}{\partial t}$$

$$-\frac{\partial i(z, t)}{\partial z} = G v(z, t) + C \frac{\partial v(z, t)}{\partial t}$$

General transmission line equations

$$v(z, t) = \mathcal{R}e[V(z)e^{j\omega t}]$$
$$i(z, t) = \mathcal{R}e[I(z)e^{j\omega t}]$$

➡ Phasor form


$$-\frac{dV(z)}{dz} = (R + j\omega L)I(z)$$
$$-\frac{dI(z)}{dz} = (G + j\omega C)V(z)$$

➡ Time harmonic transmission line equations



$$-\frac{dV(z)}{dz} = (R + j\omega L)I(z)$$

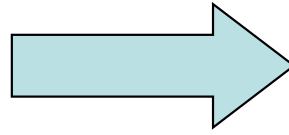
$$-\frac{dI(z)}{dz} = (G + j\omega C)V(z)$$



$$-\frac{d^2V(z)}{dz^2} = (R + j\omega L) \frac{dI(z)}{dz}$$


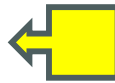
$$\frac{d^2V(z)}{dz^2} = (R + j\omega L)(G + j\omega C)V(z)$$



$$\frac{d^2V(z)}{dz^2} = \gamma^2 V(z)$$

$$\frac{d^2I(z)}{dz^2} = \gamma^2 I(z)$$

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)} \equiv \alpha + j\beta$$




Wave characteristic on Transmission Lines


γ : Propagation Constant

α : Attenuation Constant (Np/m)

β : Phase Constant (rad/m)

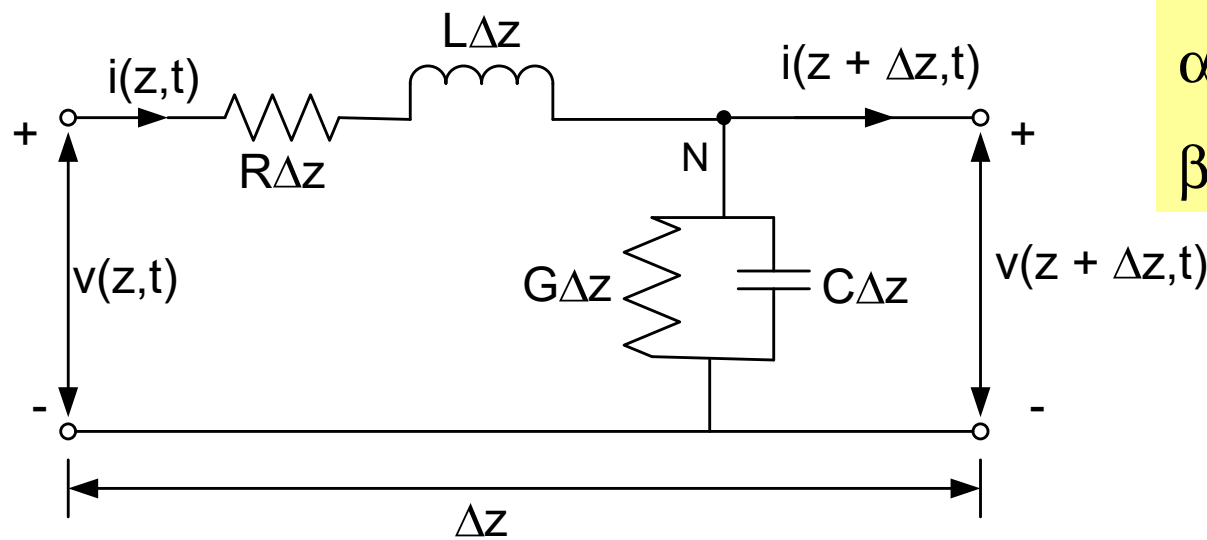
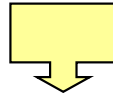
$$\frac{d^2 V(z)}{dz^2} = \gamma^2 V(z)$$



$$\frac{d^2 I(z)}{dz^2} = \gamma^2 I(z)$$



General Solution

$$V(z) = V^+(z) + V^-(z)$$

$$\equiv V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}$$

$$I(z) = I^+(z) + I^-(z)$$

$$\equiv I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z}$$

V^+ and I^+ waves propagating in + z-direction

V^- and I^- waves propagating in - z-direction

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$-\frac{dV(z)}{dz} = (R + j\omega L)I(z)$$



$$-\frac{d[V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}]}{dz} = (R + j\omega L)[I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z}]$$



$$\gamma V_0^+ e^{-\gamma z} - \gamma V_0^- e^{\gamma z}$$

$$\equiv (R + j\omega L)I_0^+ e^{-\gamma z} + (R + j\omega L)I_0^- e^{\gamma z}$$


$$\gamma V_0^+ = (R + j\omega L)I_0^+$$

$$\gamma V_0^- = -(R + j\omega L)I_0^-$$



$$\gamma V_0^+ = (R + j\omega L)I_0^+$$

$$\gamma V_0^- = -(R + j\omega L)I_0^-$$

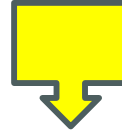

$$\frac{V_0^+}{I_0^+} = -\frac{V_0^-}{I_0^-} = \frac{R + j\omega L}{\gamma}$$

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$



For an infinite long line transmission line with source at the left end, the term $e^{\gamma z}$ term disappears (because of **no reflection**)



$$V(z) = V^+(z) = V_0^+ e^{-\gamma z}$$

$$I(z) = I^+(z) = I_0^+ e^{-\gamma z}$$



$$Z_0 = \frac{V(z)}{I(z)} = \frac{V_0^+}{I_0^+} = \frac{R + j\omega L}{\gamma}$$



$$Z_0 = \frac{V(z)}{I(z)} = \frac{V^+}{I^+} = \frac{R + j\omega L}{\gamma}$$

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$Z_0 = \frac{R + j\omega L}{\gamma} = \frac{\gamma}{G + j\omega C} = \sqrt{\frac{R + j\omega L}{G + j\omega C}} \quad (\Omega)$$



Characteristic Impedance

□ The ratio of the voltage and the current at any z for an infinitely long line is independent of z and it is called the **Characteristic Impedance**.

γ and Z_0 are the characteristics of a transmission line.



These parameters depend on R , L , G and C , but are independent of the length of transmission line.



The **Characteristic Impedance** of a line primarily depends upon the material properties and the line geometry.